



**ENEE2313**

## **Tank Water Level Indicator**



### **Student's Name:**

Huda AbuZayed 1192495

Mohammad Zidan 1191630

Alaa Mahanyah 1182754

### **Instructor:**

Dr. Mohammad Jehad Al Ju'Beh.


**Date:** 28-8-2021

### Abstract:


The aim of this project is to design a simple tank water that can indicate to the water level in the tank by using sensors connected with **LEDS\_ LIGHTS** which glowing when the water level increased. That's mean when the water level increases in the tank, then the number of glowing **LEDS\_ LIGHTS** will increase. At this time, the resistor become small and the height of water and the voltage around one 1K ohm will increase.
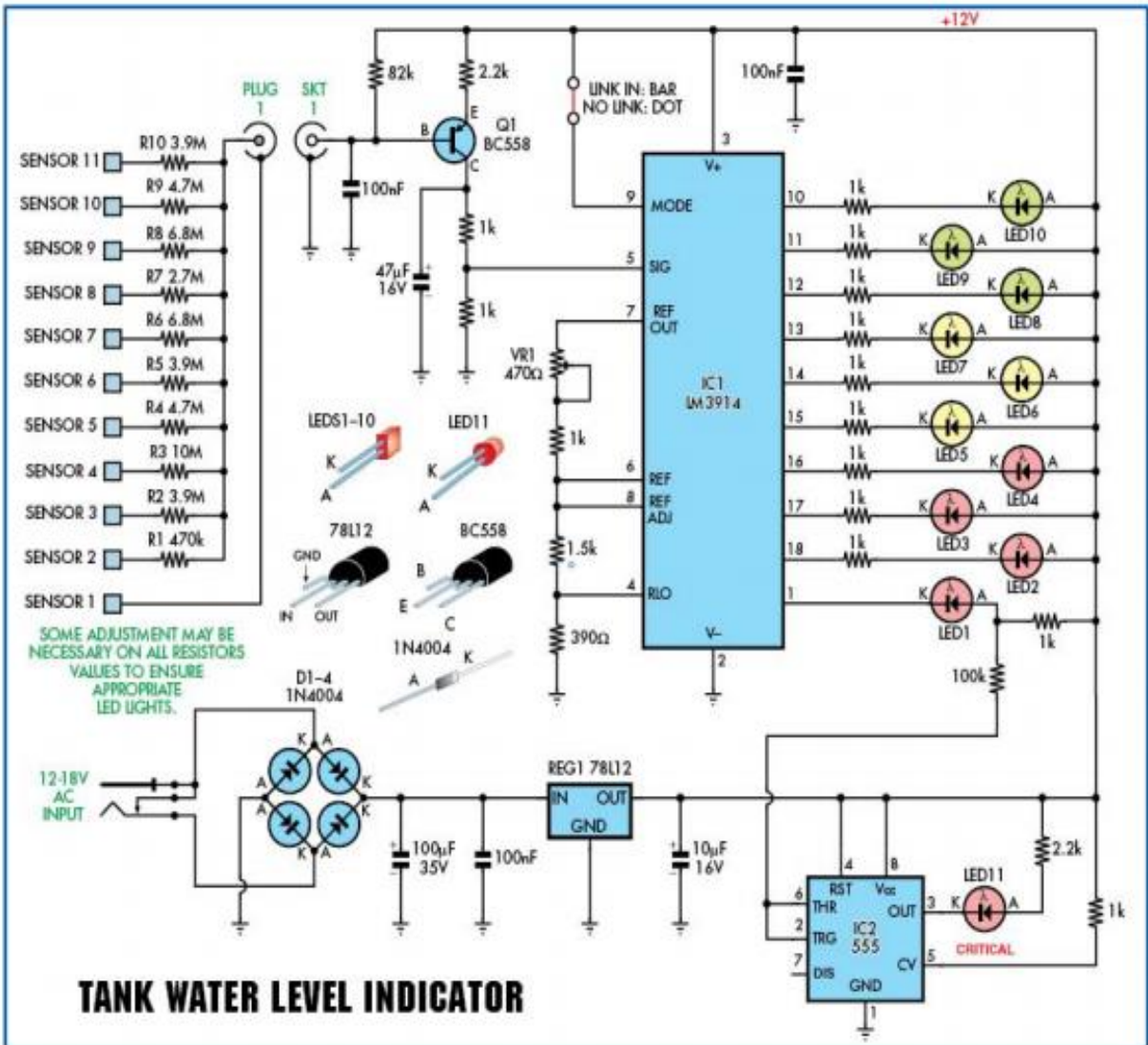
### The Components of the circuit which used to build this project:

Resistor, Regulator, Ac source, BJT Transistor, Capacitors and Diodes.




**TANK WATER LEVEL INDICATOR**

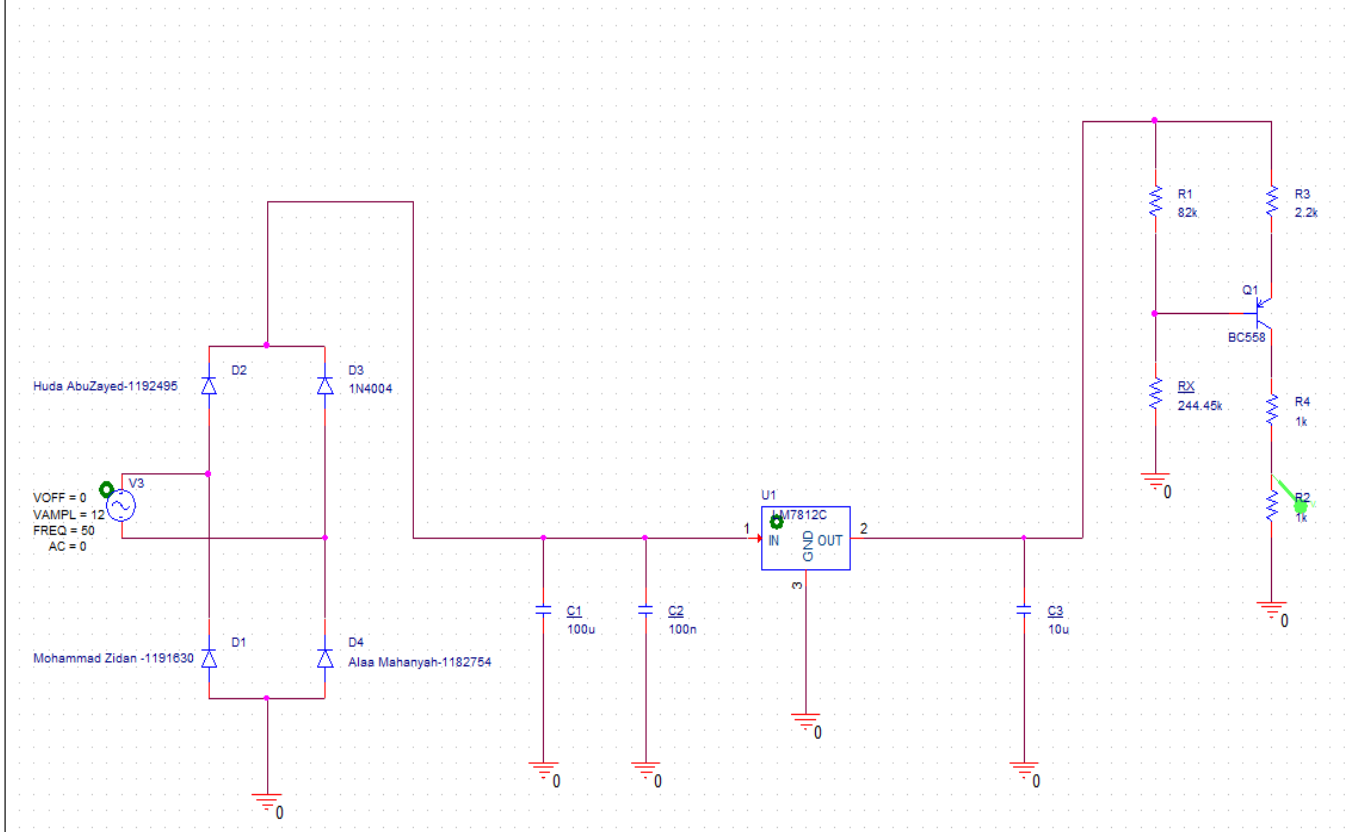


**Simulations:**


**When Rx=470k:**

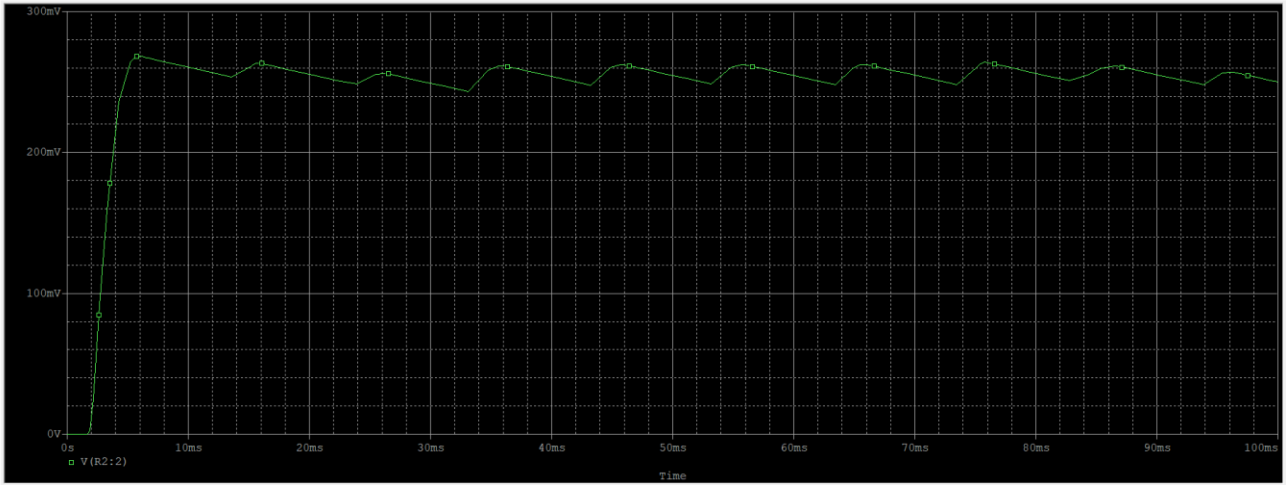

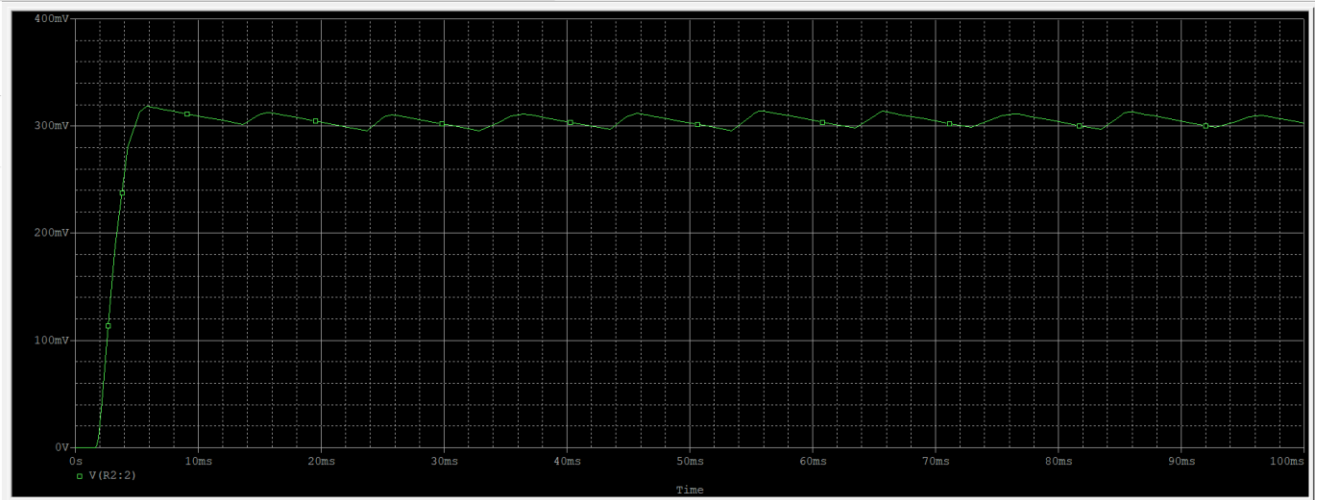
**When  $R_x=419.45k$  (3.9M parallel with 470k):**



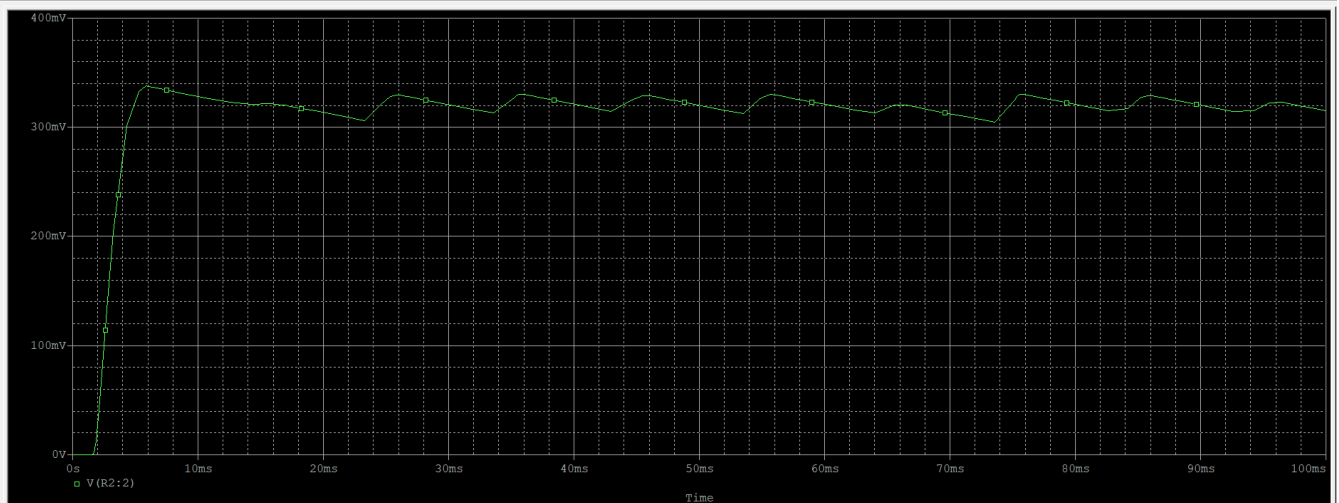
**When  $R_x=402.56k$  (419.45k parallel with 10M):**



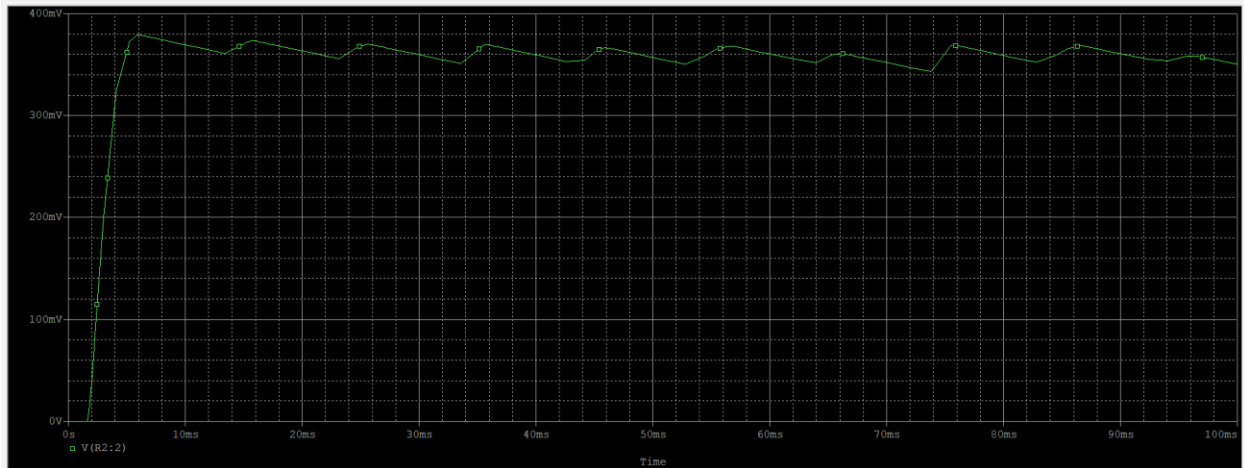
**When  $R_x = 370.80\text{K}$  ( $402.56\text{K}$  parallel with  $4.7\text{M}$ ):**



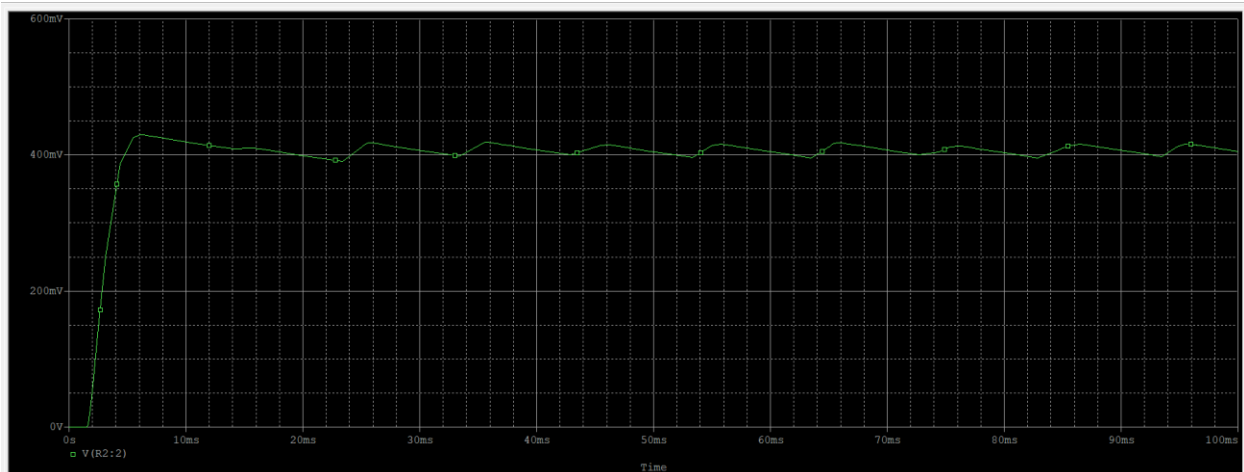
**When  $R_x = 338.6\text{k}$  ( $370.80\text{k}$  parallel  $3.9\text{M}$ ):**



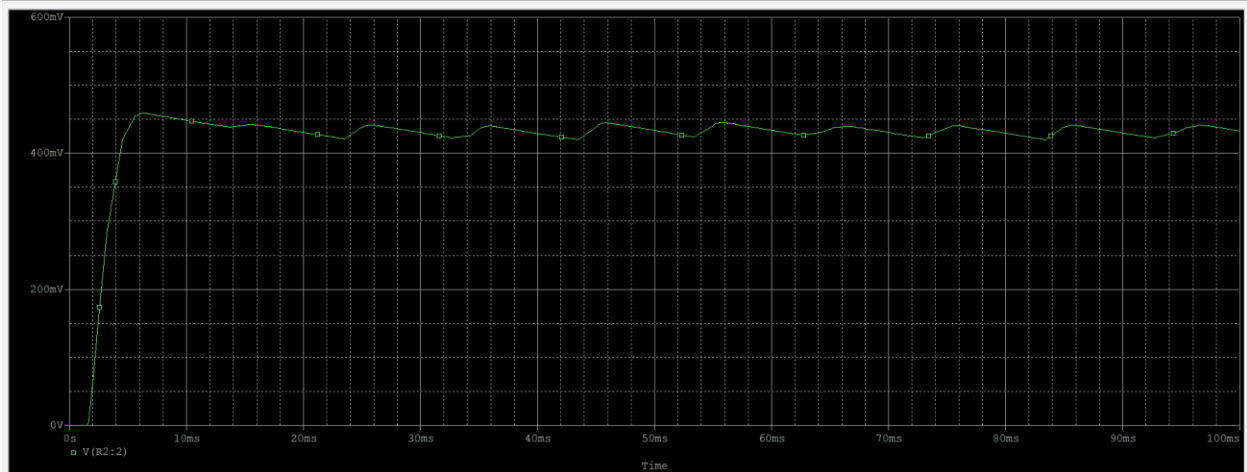
**When  $R_x=322.5K$  (338.60K Parallel with 6.8M):**



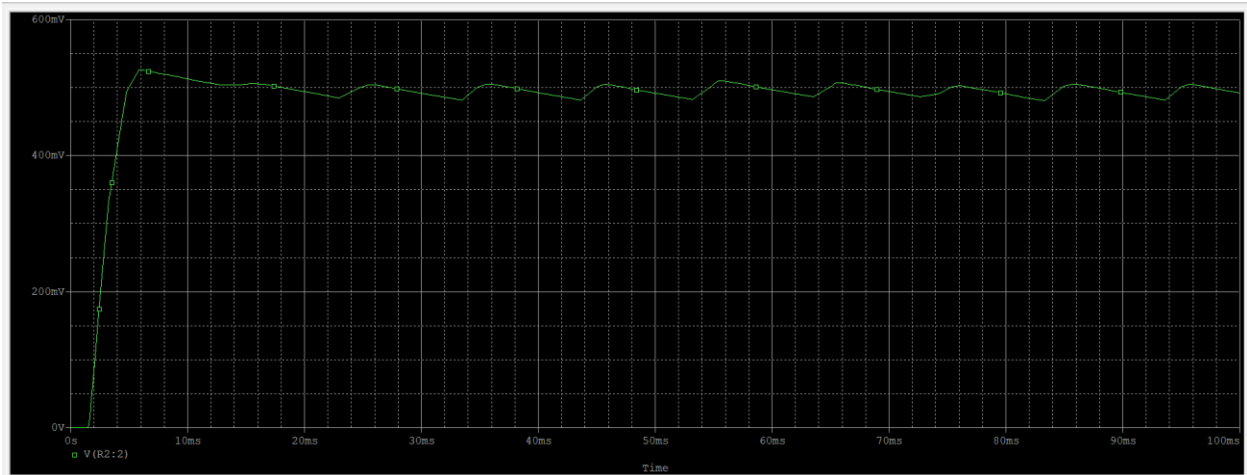
**When  $R_x= 288.08K$  (322.5k parallel with 2.7M):**



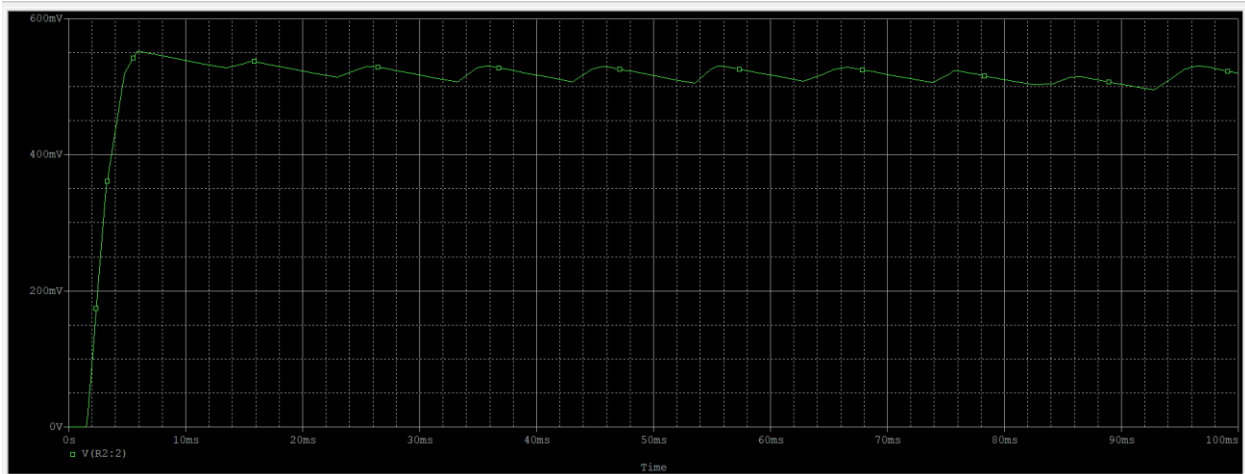**When  $R_x=276.3\text{K}$  (288.08K Parallel with 6.8M):**




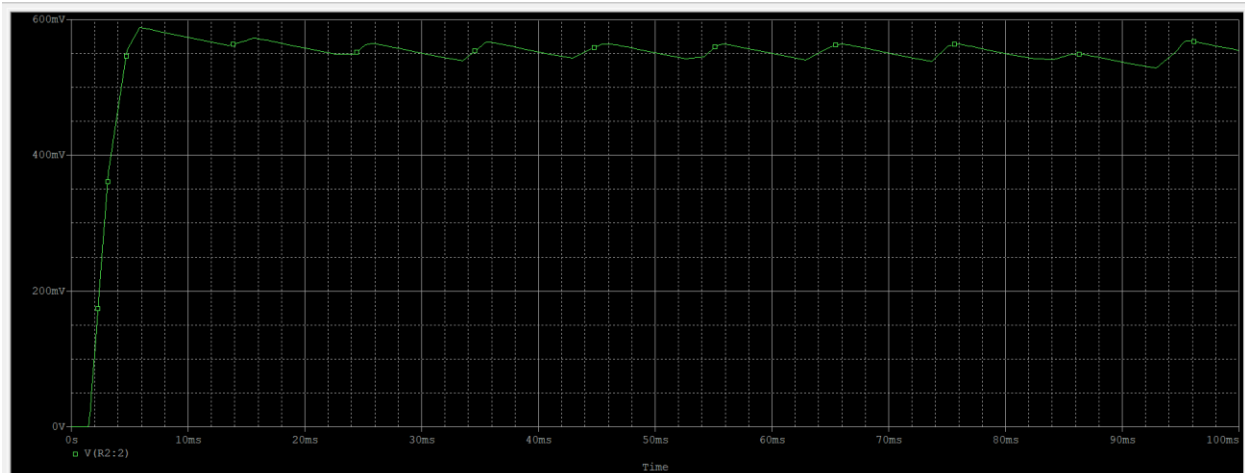**When  $R_x=260.9\text{K}$  (276.3K Parallel with 4.7M):**






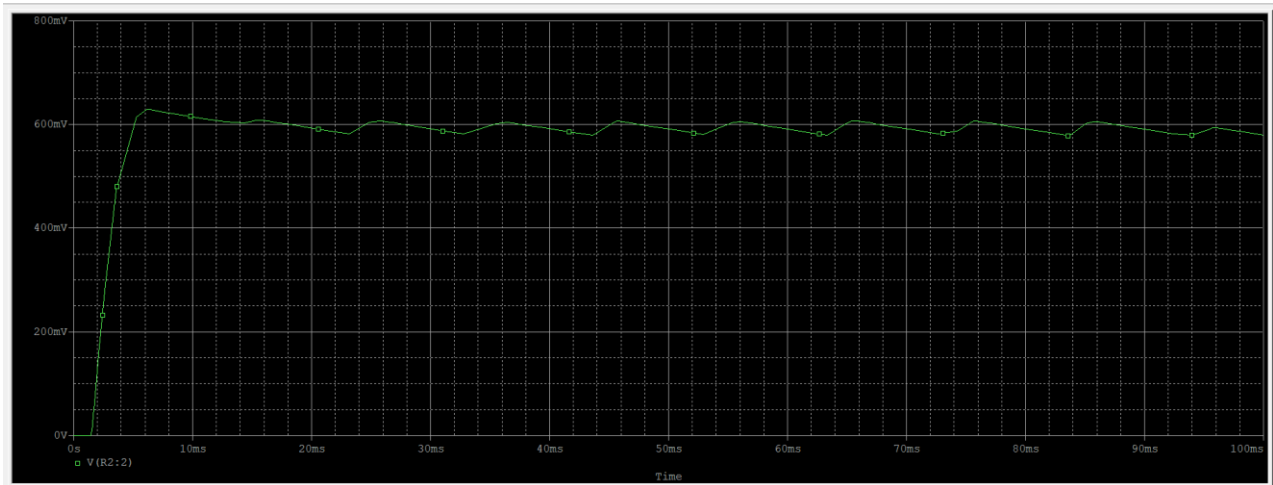When  $R_x = 244.45\text{K}$  (260.9k Parallel with 3.9M):



## Analysis and calculations:

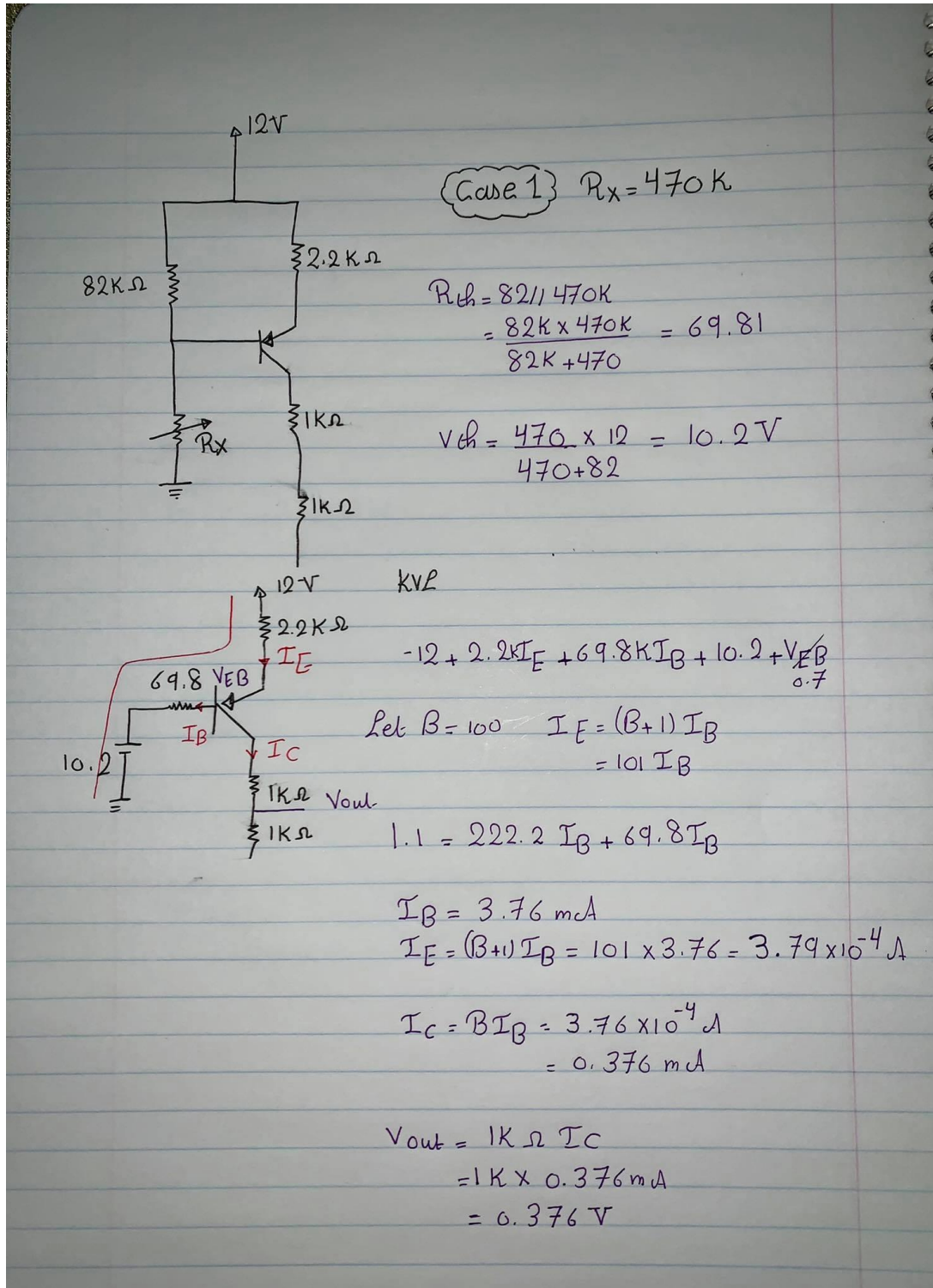

Case 1  $R_X = 470k$

$$R_{th} = 82 || 470k$$

$$= \frac{82k \times 470k}{82k + 470k} = 69.81$$

$$V_{be} = \frac{470 \times 12}{470 + 82} = 10.2V$$

KVL

$$-12 + 2.2kI_E + 69.8kI_B + 10.2 + V_{BE} = 0$$

Let  $\beta = 100$   $I_E = (\beta + 1)I_B$

$$= 101I_B$$

$$1.1 = 222.2I_B + 69.8I_B$$

$$I_B = 3.76 \text{ mA}$$

$$I_E = (\beta + 1)I_B = 101 \times 3.76 = 3.79 \times 10^{-4} \text{ A}$$

$$I_C = \beta I_B = 3.76 \times 10^{-4} \text{ A}$$

$$= 0.376 \text{ mA}$$

$$V_{out} = 1k \Omega I_C$$

$$= 1k \times 0.376 \text{ mA}$$

$$= 0.376 \text{ V}$$

Case 2

$$R_x = 3.9 \text{ M} \parallel 470 \text{ k}$$

$$R_x = \frac{3.9 \times 10^6 \times 470 \times 10^3}{(3.9 \times 10^6) + (470 \times 10^3)} = 419.45 \text{ k}$$

$$R_{th} = 419.45 \text{ k} \parallel 82 \text{ k}$$

$$= 68.59 \text{ k}$$

$$V_{th} = \frac{419.45}{419.45 + 82} \times 12 = 10 \text{ V}$$

$$-12 + 222.2 I_B + 0.7 + 68.59 I_B + 10 = 0$$

$$1.3 = 290.79 I_B \Rightarrow I_B = 4.47 \mu\text{A}$$


$$I_E = 4.51 \times 10^{-4} \text{ A}$$

$$I_C = 4.47 \times 10^{-4} \text{ A}$$

$$V_{out} = (1 \text{ k}) \times I_C$$

$$= 1 \times 10^3 \times 4.47 \times 10^{-4}$$

$$= 0.447 \text{ V}$$

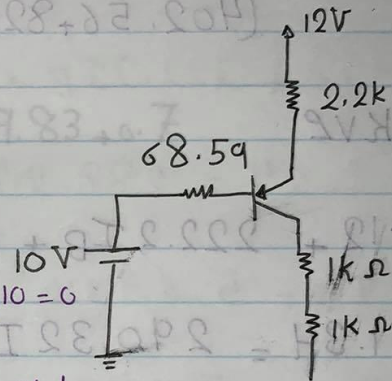


Case 3)  $R_x = 419.45k // 10M \Omega$  Case 2

$$R_x = 402.56k$$

$$R_{th} = 402.56k // 82k$$

$$= 68.12k$$
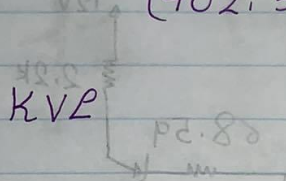
$$V_{th} = \frac{402.56k}{(402.56k + 82k)} \times 12 = 9.96V$$



$$-12 + 222.2 I_B + 68.12 I_B + 9.96 + 0.7 = 0$$

$$1.34 = 290.32 I_B$$

$$I_B = 4.615 \times 10^{-6} A$$

$$I_E = 4.66 \times 10^{-4} A$$

$$I_C = 4.615 \times 10^{-4} A$$

$$V_{out} = 0.4615 V$$

Case 4  $R_x = 402.56k / 4.7M = R_x$  Case 5

$R_x = 370.80k$   $R_x = 338.6k$

$R_{th} = 370.80k // 82k = 338.6k // 82k = 67.15k$

$V_{th} = \frac{370.80k \times 12}{(370.80 + 82)k} = 9.83V$

$12 = 222.2I_B + 67.15kI_B + 9.83 + 0.7$

$I_B = 5.08 \times 10^{-6}$

$I_E = 5.13 \times 10^{-4}$

$I_C = 5.08 \times 10^{-4}$

$V_{out} = I_C \times 1k = 0.508V$

Case 6  $R_x = 338.6k // 82k = 338.6k // 82k = 67.15k$

$R_x = 338.6k$

$R_{th} = 338.6k // 82k = 67.15k$

Case 5)  $R_x = 370.80k / 3.9M$

$$R_x = 338.6 k\Omega$$

$$R_{th} = 338.6 // 82 = 66 k\Omega$$

$$V_{th} = \frac{338.6 \times 10^3}{(338.6 + 82) \times 10^3} \times 12 = 9.66 V$$

$$-12 + 222.2 I_B + 66 I_B + 9.66 + 0.7 = 0$$

$$1.64 = 288.2 I_B$$

$$I_B = 5.69 \times 10^{-6} A$$

$$I_E = 5.747 \times 10^{-4} A$$

$$I_C = 0.569 mA$$

$$V_{out} = (1k) \times (I_C) \\ = 0.569 V$$

Case 6)  $R_x = 338.6k / 6.8M$

$$R_x = 322.5 k\Omega$$

$$R_{th} = 322.5 // 82 = 65.37 k\Omega$$

$$V_{th} = \frac{322.5 \times 10^3}{(322.5 + 82) \times 10^3} \times 12 = 9.56 V$$

$$-12 + 222.2 I_B + 65.37 I_B + 0.7 + 9.56$$

$$I_B = 6.05 \times 10^{-6} \text{ A}$$

$$I_E = (B+1)I_B \\ = 6.1105 \times 10^{-4} \text{ A}$$

$$I_C = 0.6 \text{ mA}$$

$$V_{out} = R I_C \\ = 1 \times 10^3 \times 0.6 \times 10^{-3} \\ = 0.6 \text{ V}$$

Case 7  $R_x = 322.5 \text{ k} / 2.7 \text{ M}$

$$R_x = 288.08$$

$$R_{th} = 288.08 \text{ k} // 82 \text{ k} = 63.83 \text{ k}$$

$$V_{th} = \frac{288.08 \text{ k} \times 12}{(288.08 + 82) \text{ k}} = 9.34 \text{ V}$$

$$-12 + 2.2 I_E + 63.83 \text{ k} I_B + 0.7 + 9.34 = 0$$

$$I_B = 6.85 \times 10^{-6} \text{ A}$$

$$I_E = 6.9185 \times 10^{-4} \text{ A}$$

$$I_C = 6.85 \times 10^{-4} \text{ A}$$

$$V_{out} = I_C \times 1 \times 10^3 \\ = 0.685 \text{ V}$$

Case 8)  $R_x = 288.08k // 6.8M \times 20 \times 10^{-3} = 9.7$

$R_x = 276.3k$

$R_{th} = 276.3 // 82 = 63.3k$

$V_{th} = \frac{276.3 \times 10^3 \times 12}{(276.3 + 82) \times 10^3} = 9.25V$

KVL  $\Rightarrow -12 + 222.2 I_B + 63.3 I_B + 9.25 + 0.7 = 0$

$2.05 = 285.5 I_B$

$I_B = 7.18 \times 10^{-6} A$

$I_E = 7.252 \times 10^{-4} A$

$I_C = 0.718 mA$

$V_{out} = 1k \times I_C$

$= 0.718V$

Case 9)  $R_x = 276.3 // 4.7 \times 10^3 = 4.7$

$R_x = 260.9k \Omega$

$R_{th} = 260.9 // 82k = 62.39k \Omega$

$V_{th} = \frac{260.9k \times 12}{(260.9 + 82)k} = 9.13V$

$-12 + 222.2 I_B + 62.3 I_B + 0.7 + 9.13 = 0$



$$I_B = 7.66 \times 10^{-6} \text{ V}$$

$$I_E = 7.739 \times 10^{-4} \text{ V}$$

$$I_C = 0.766 \text{ mA}$$

$$V_{out} = I_C \cdot 1\text{K}$$

$$= 0.766 \text{ V}$$

$$\text{Case 10} \quad R_x = 260.9 \text{ M} / 3.9 \text{ M}$$

$$R_x = 244.45 \text{ K}$$

$$R_{th} = 244.45 \text{ K} // 82 \text{ K} = 61.4 \text{ K}$$

$$V_{th} = \frac{244.45 \text{ K} \times 12}{(244.45 + 82) \text{ K}} = 8.98 \text{ V}$$

$$-12 + 222.2 I_B + 61.4 I_B + 0.7 + 8.98 = 0$$

$$2.32 = 283.6 I_B$$

$$I_B = 8.18 \times 10^{-6} \text{ A}$$

$$I_E = 8.26 \times 10^{-4} \text{ A}$$

$$I_C = 8.1805 \times 10^{-4} \text{ A}$$

$$V_{out} = I_C \times 1\text{K}^3$$
$$= 0.81805 \text{ V}$$

## Conclusion:

The project was very useful, it provided to us more information about how we can analyze, design and build the circuit and make the simulation on OrCad PSpice. The function of this electronic circuit also helped us to learn how we can know the water level in the tank by using LEDs\_ lights work with sensors. In addition, through this project we learned new uses for diodes and improved our analysis skills and simplification the complex circuits.