
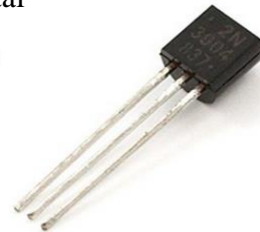


Bipolar junction Transistor _ (BJT):

Bipolar junction Transistor _ (BJT):


BJT:

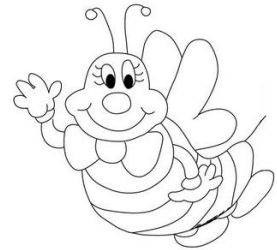1. It's a semiconductor device that can amplify electrical signals such as radio or television signals.
2. Its essential ingredient of every electronic circuits; from the simplest amplifier or oscillator to the most elaborate digital computer.
3. It's a three terminal device; **Base**, **Emitter**, and **Collector**.




There are two type of BJT:

- **npn** type
- **pnp** type

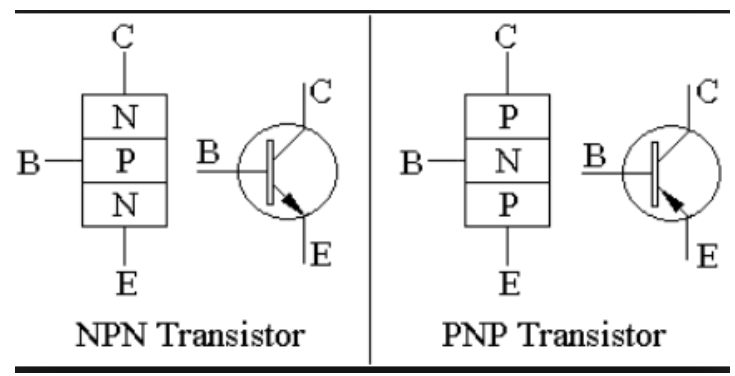


Transistor structure:

- **npn** type

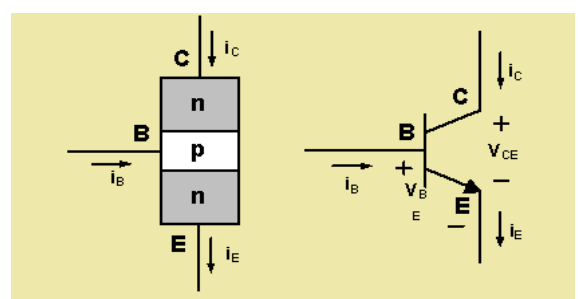

- **pnp** type

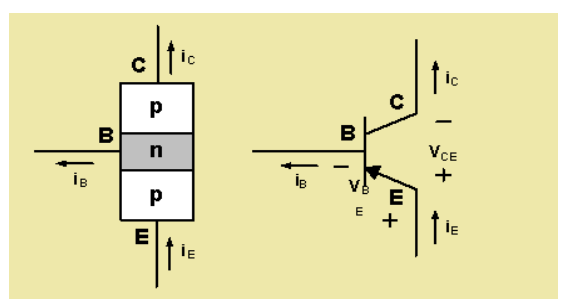



Transistor biasing:

- ✓ In order to operate properly as an amplifier, it's necessary to correctly bias the two pn-junctions with external voltages.
- ✓ Depending upon external bias voltage polarities used; the transistor works in one of **four regions** (modes).
- ✓ For transistor to be used as an Active device (**Amplifier**); the **emitter-base** junction must be **forward** bias, while the **collector-base** junction must be **reverse** biased.

Region	Base-Emitter junction	Base-collector junction
Active	Forward Bias	Revers Bias
Saturation	Forward Bias	Forward Bias
Cut-off	Revers Bias	Revers Bias
Invers	Revers Bias	Forward Bias

In active region

- ✓ The base region is thin and lightly doped
- ✓ The **emitter-base** junction is **forward biased**, thus the depletion region at this junction **is reduced**.
- ✓ The **base-collector** junction is **revers** biased, thus the depletion region at this junction **is increased**.
- ✓ The **forward** biased **BE-junction** causes the electrons in the **n-type** emitter to flow **toward the base**; this constitutes the emitter current I_E .
- ✓ As these electrons flow through the **P-type** base; they tend to recombine with holes in **p-type** base.

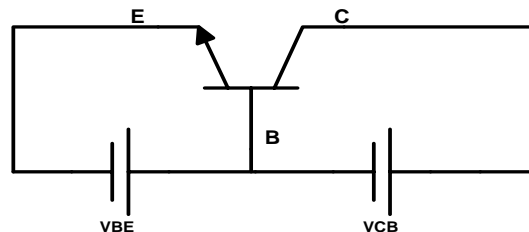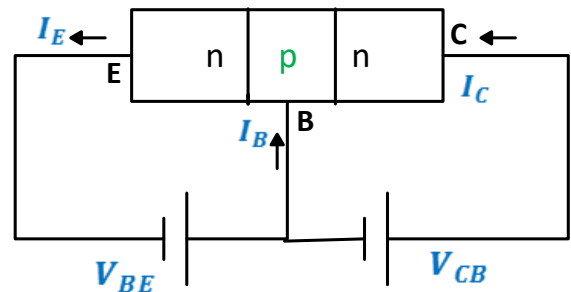

- ✓ Since the **base** region is **lightly doped**; very few of the electrons injected into the base from the emitter recombine with holes to constitute base current I_B and the remaining large number of electrons cross the base and move through the collector region to the positive terminal of the external DC source; this constitute collector current I_C
- ✓ There is another component for I_C due to the minority carrier; I_{CBO}

$$I_C = \alpha I_E + I_{CBO}$$

Majority
Minority

$0.998 > \alpha > 0.9$

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = I_C + I_B$$

$$I_C = \alpha(I_C + I_B) + I_{CBO}$$

$$\diamond I_C = \frac{\alpha}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBO}$$

Let Beta, $\beta = \frac{\alpha}{1-\alpha}$

$$\diamond I_C = \beta I_B + (\beta + 1)I_{CBO}$$

$$I_C = \beta I_B + I_{CE0}$$

$$\beta = \frac{\alpha}{1-\alpha}$$

If $\alpha = 0.99 \rightarrow \beta = 99$

If $\alpha = 0.995 \rightarrow \beta = 199$



In active region:

$$I_C = \alpha I_E + I_{CBO}$$

$$I_C = \beta I_B + (\beta + 1)I_{CBO}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$I_C = \beta I_B + I_{CEO}$$

$$I_E = I_C + I_B$$

Approximate relationships:



$$I_C \cong \alpha I_E \cong I_E$$

$$I_C \cong \beta I_B$$

$$I_E \cong (\beta + 1)I_B$$



Input characteristic curve:

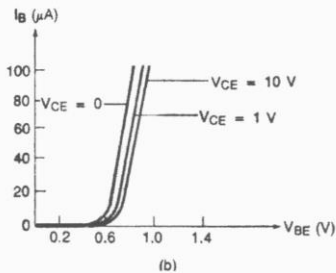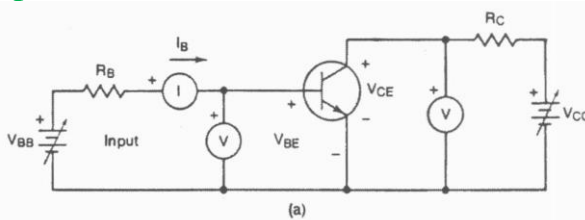


$$i_B(t) = I_{B0} \left(e^{\frac{V_{BE}(t)}{\eta V_T}} - 1 \right)$$

$$i_B(t) \cong I_{B0} \left(e^{\frac{V_{BE}(t)}{\eta V_T}} \right)$$

$$i_C(t) \cong I_S \left(e^{\frac{V_{BE}(t)}{\eta V_T}} \right)$$

Output characteristic curve:

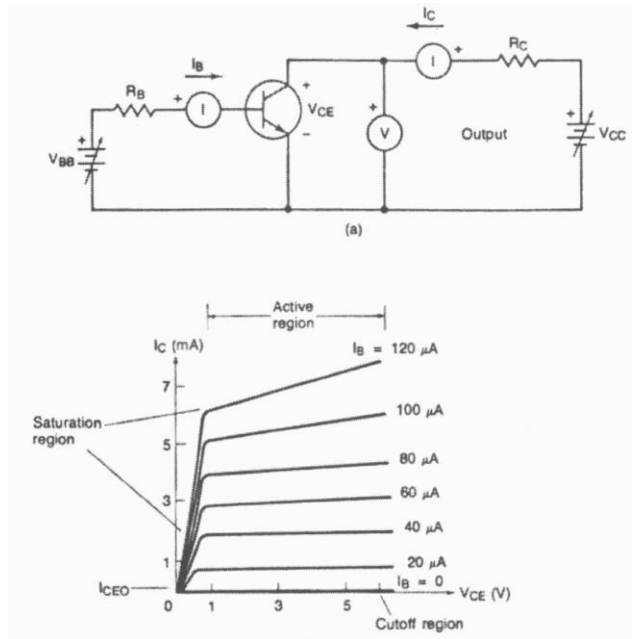

1. In the **cutoff** region :

$$I_B = I_C = I_E = 0$$

2. In the **active** region :

$$I_C = \alpha I_E$$

$$I_C = \beta I_B$$

$$I_E = (\beta + 1) I_B$$

$$V_{BE} = 0.7 \text{ v} \quad , \quad \text{Si} \quad , \quad \text{npn}$$

$$V_{BE} = -0.7 \text{ v} \quad , \quad \text{Si} \quad , \quad \text{pnp}$$

$$V_{CE} > V_{CE,sat} = 0.2 \text{ v} \quad , \quad \text{Si} \quad , \quad \text{npn}$$


$$V_{CE} < V_{CE,sat} = -0.2 \text{ v} \quad , \quad \text{Si} \quad , \quad \text{pnp}$$

3. In the **saturation** region :

$$V_{CE} = V_{CE,sat}$$



$$V_{BE} = 0.8 \text{ v} \quad , \quad \text{Si} \quad , \quad \text{npn}$$
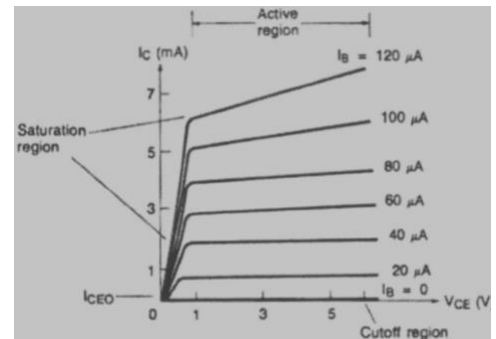
$$V_{BE} = -0.8 \text{ v} \quad , \quad \text{Si} \quad , \quad \text{pnp}$$



Example:

Find the Q point V_{CEQ} , I_{CQ}

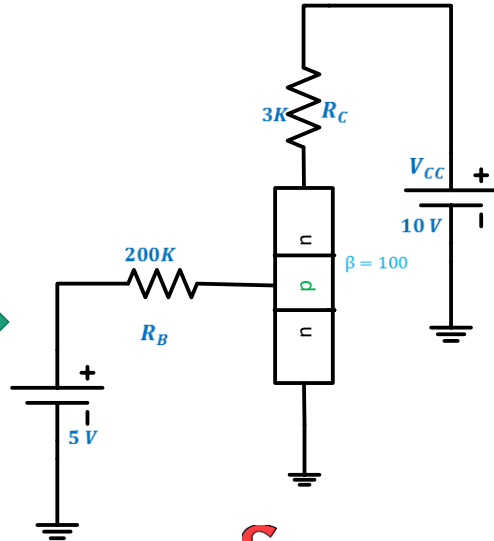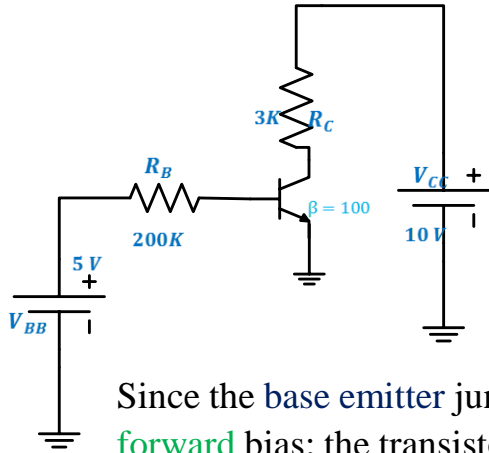

Since the base emitter junction is forward bias; the transistor could be either in the active or the saturation region



➤ Assume that the transistor in the active region:

KVL: $5 = 200k I_B + V_{BE}$

$$I_B = \frac{5 - 0.7}{200k} = 0.0215 \text{ mA}$$


$$I_C = \beta I_B = 100 * 0.0215 = 2.15 \text{ mA}$$

KVL: $10 = R_C I_C + V_{CE}$

$$V_{CE} = 10 - R_C I_C$$

$$\diamond V_{CE} = 10 - 3k * 2.15 \text{ mA}$$

$$\diamond V_{CE} = 3.55 \text{ Volt}$$

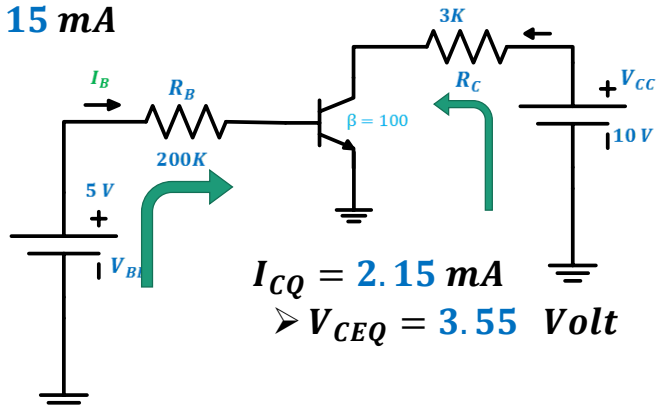

$$I_{CQ} = 2.15 \text{ mA}$$


$$\triangleright V_{CEQ} = 3.55 \text{ Volt}$$

➤ Since $V_{CE} > V_{CE,sat} \gg \gg$ The transistor is in the active region

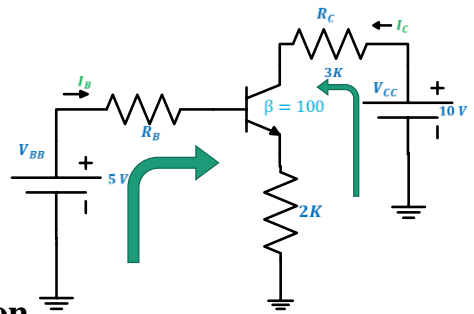Example Find the Q point V_{CEQ} , I_{CQ}

Solution:

Since the base emitter junction is forward bias ; the transistor could be either in the active or the saturation region



➤ Assume that the transistor in the active region

KVL: $5 = 200k I_B + V_{BE} + 2k I_E$

KVL: $10 = R_C I_C + V_{CE} + R_E I_E$

$$I_E = (\beta + 1) I_B$$

$$V_{CE} = 10 - R_C I_C - R_E I_E$$

❖ $V_{CE} = 4.63 \text{ Volt}$

Since $V_{CE} > V_{CE,sat} \gg \gg$ The transistor is in the active region V_{CEQ}

$$I_B = \frac{5 - 0.7}{200k + 101 * 2k} = 0.0107 \text{ mA}$$

$= 4.63 \text{ Volt}$ and $I_{CQ} = 1.07 \text{ mA}$

$$I_C = \beta I_B = 100 * 0.0107 = 1.07 \text{ mA}$$


Second method:

1) In the active region:

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - R_C I_C$$

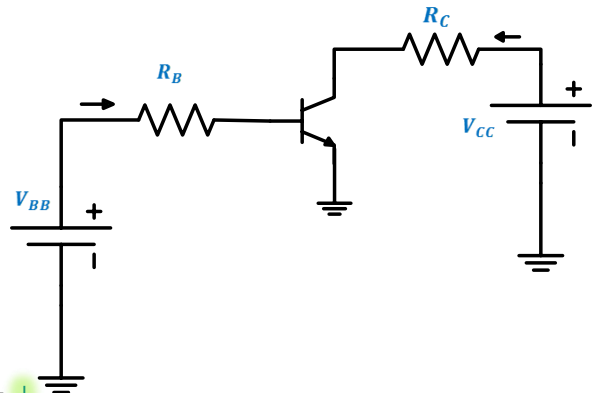


As : $R_B \downarrow$, $I_B \uparrow$, $I_C \uparrow$, $V_{CE} \downarrow$

2) In the saturation region:

$$V_{CE} = V_{CE,sat} = 0.2 \text{ v} \quad , \quad \text{Si} \quad , \quad \text{nnp}$$

$$I_C = I_{C,sat} = \frac{V_{CC} - V_{CE,sat}}{R_C}$$

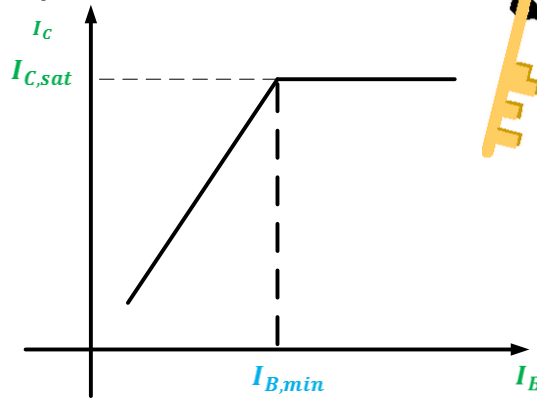Let define: $I_B(min) = \frac{I_{C,sat}}{\beta}$





$$I_B(min) = \frac{I_{C,sat}}{\beta}$$

- ✚ If $I_B > I_B(min)$ the transistor is in the **saturation** region.
- ✚ If $I_B < I_B(min)$ the transistor is in the **Active** region.

BJT as switch:

Example:



Find $V_o(t)$ for the input given below:

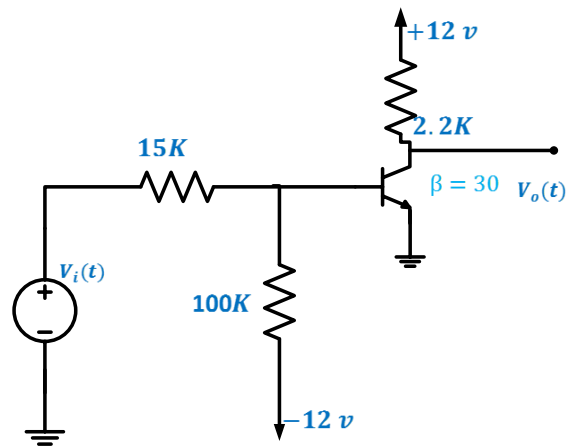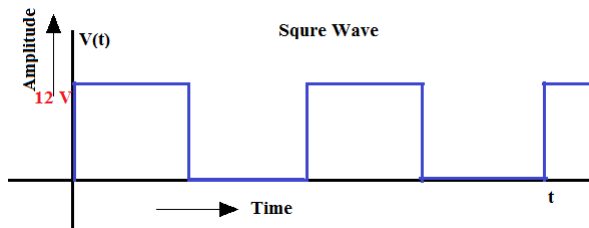

Solution:

❖ Let $V_i(t) = +12 \text{ volt}$

Calculate V_{th} & R_{th}

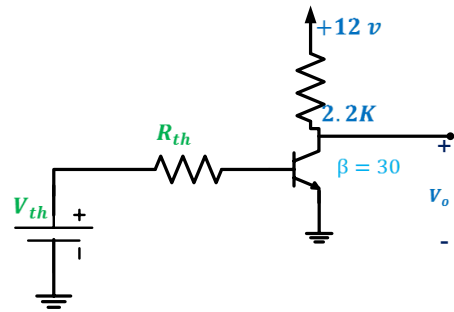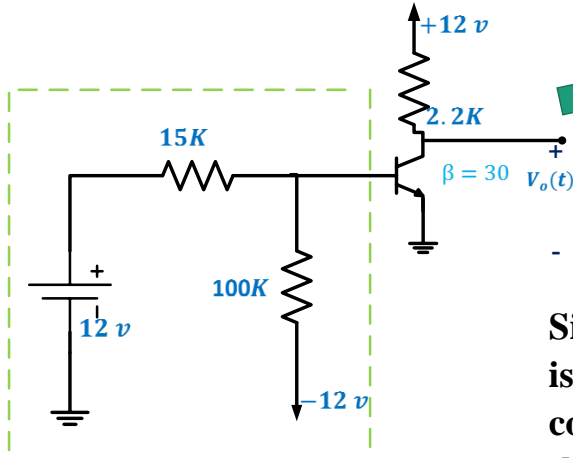

$$R_{th} = 15k // 100k = \frac{100k \cdot 15k}{15k + 100k} = 13k$$

$$V_{th} = 8.9 \text{ volt} \quad \text{Proof!!}$$




Since the **base emitter junction** is **forward bias**; the transistor could be either in the **active** or the **saturation** region

➤ Assume that the transistor in the **saturation** region

$$I_C = I_{C,sat} = \frac{V_{CC} - V_{CE,sat}}{R_C} = \frac{12 - 0.2}{2.2k} = 5.36 \text{ mA}$$

$$I_B(\text{min}) = \frac{I_{C,sat}}{\beta} = \frac{5.36 \text{ mA}}{30} = 0.18 \text{ mA}$$
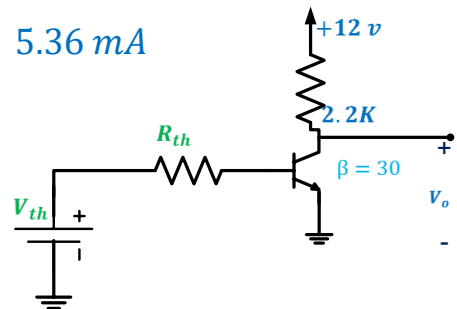
$$I_B = \frac{V_{th} - V_{BE}}{R_{TH}} = \frac{8.9 - 0.8}{13k} = 0.62 \text{ mA}$$




✚ Since $I_B > I_B(\text{min})$ the transistor is in the **saturation** region.

✓ $V_o = V_{CE,sat} = 0.2 \text{ volt}$

✓ $I_C = 5.36 \text{ mA}$

❖ Let $V_i(t) = 0$ volt

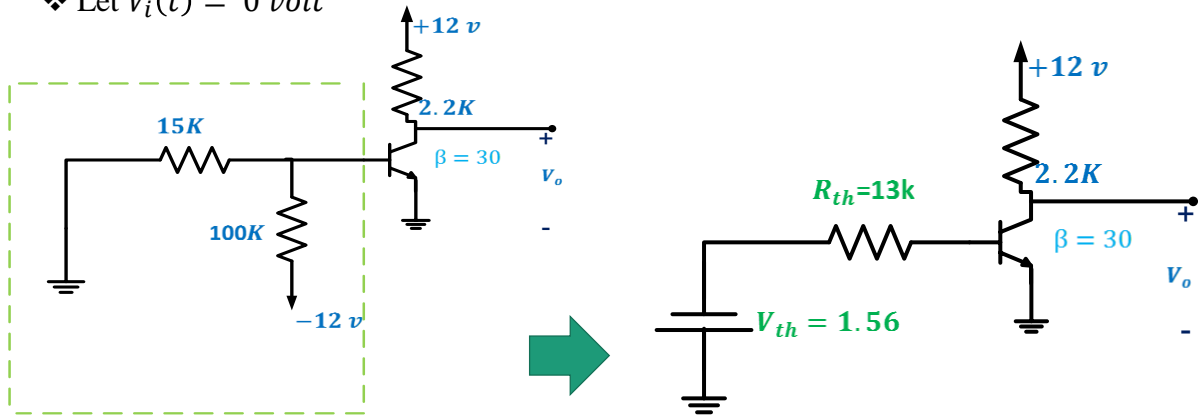


Since $V_{th} = -1.56$ volt

Base emitter junction is revers biased the transistor in cutoff region

✓ $V_o = V_{CE} = 12$ volt , $I_C = 0$ mA

The circuit acts as inverter or not gate

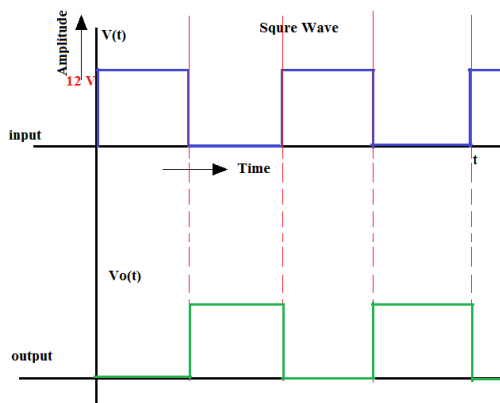

NOT gate truth table

Input Output

Input	Output
0	1
1	0

Transistor biasing circuits:

1. Fixed current bias circuit


KVL: $V_{CC} = R_B I_B + V_{BE}$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

KVL: $V_{CC} = R_C I_C + V_{CE}$

$$V_{CE} = V_{CC} - R_C I_C$$

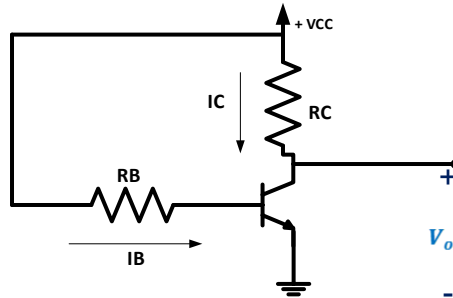

Transistor biasing circuits:

Example: Design a fixed current bias circuit using a silicon transistor having

$$\beta(\min) = 25, \quad \beta(\max) = 75$$

Such that $I_C = 1mA$, and $V_{CE} = 5\text{ volt}$ given $V_{CC} = 10\text{ volt}$

Solution:

Using equations of the fixed current bias circuit:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}, \quad V_{BE} = 0.7\text{ v} \quad - (1)$$

$$V_{CE} = V_{CC} - R_C I_C \quad - (2)$$

From eq.2:

$$5 = 10 - R_C(1mA)$$

$$\rightarrow R_C = 5k\Omega$$

$$I_C = \beta I_B$$

$$\text{Let } \beta = \frac{25+75}{2} = 50$$

the average between max && min

$$I_B = \frac{I_C}{\beta} = \frac{1mA}{50} = 20\ \mu A$$

From eq.1

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{10 - 0.7}{R_B}$$

$$\rightarrow R_B = 465\text{ k}\Omega$$

Transistor biasing circuits:

⚡ If $\beta = 50 \gg \gg R_c = 5k\Omega, R_B = 465k\Omega, I_C = 1mA, V_{CE} = 5v$

BUT:

⚡ When $\beta = \beta(\min) = 25$

$$\begin{aligned} I_B &= 20 \mu A \\ I_C &= 0.5mA \\ V_{CE} &= 7.5v \end{aligned}$$

For:

$$\begin{aligned} 75 &\geq \beta \geq 25 \\ 1.5mA &\geq I_C \geq 0.5mA \end{aligned}$$

⚡ When $\beta = \beta(\max) = 75$

$$\begin{aligned} I_B &= 20 \mu A \\ I_C &= 1.5mA \\ V_{CE} &= 2.5v \end{aligned}$$



❖ The fixed current bias circuit is **not** a very satisfactory circuit of obtaining good bias point stability.

Transistor biasing circuits:

2. Collector to base feedback bias circuit:

KVL: $V_{CC} = R_c I + R_B I_B + V_{BE}$



$$I = I_B + I_C$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_c} \dots (1)$$

$$I_C = \beta I_B$$

KVL: $V_{CC} = R_c(I_B + I_C) + V_{CE}$
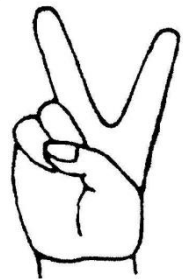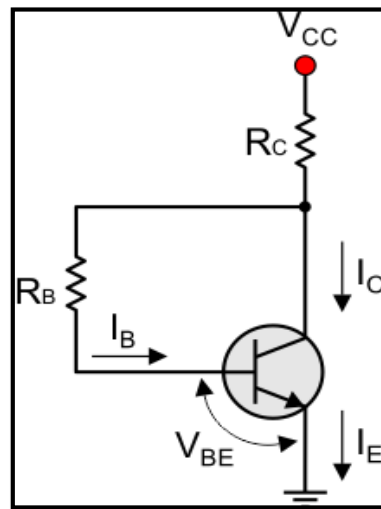
$$V_{CE} = V_{CC} - R_c(I_B + I_C) \dots (2)$$



Transistor biasing circuits:

Example: Design a collector to base feedback bias circuit using a silicon transistor having

$$\beta(\text{min}) = 25, \quad \beta(\text{max}) = 75$$

Such that $I_c = 1\text{mA}$, and $V_{CE} = 5\text{ volt}$ given $V_{CC} = 10\text{ volt}$

Solution:

Let $\beta = \frac{25+75}{2} = 50$ the average between max && min

$$I_B = \frac{I_C}{\beta} = \frac{1\text{mA}}{50} = 20\ \mu\text{A}$$

From eq.2:

$$V_{CE} = V_{CC} - R_c(I_B + I_c)$$

$$5 = 10 - R_c(1\text{mA} + 20\ \mu\text{A})$$

➤ $R_c \approx 4.9\text{k}\Omega$



From eq.1:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_c}$$

$$= \frac{10 - 0.7}{R_B + (50 + 1) \cdot 4.9\text{k}} \dots, I_B = 20\ \mu\text{A}$$

➤ $R_B \approx 215\text{k}\Omega$

As before we can proof that:

$$75 \geq \beta \geq 25$$

$$1.19\text{mA} \geq I_c \geq 0.68\text{mA}$$

There is an improvement over the fixed bias circuit.

Transistor biasing circuits:

3. Biasing circuit with stabilization resistor (R_E):

KVL: $V_{CC} = R_B I_B + V_{BE} + R_E I_E$



$$I_E = (\beta + 1) I_B$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E} \dots (1)$$

$$I_C = \beta I_B$$

KVL: $V_{CC} = R_c I_c + V_{CE} + R_E I_E$
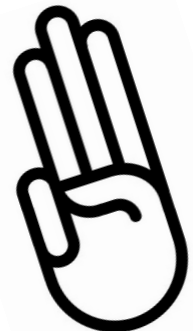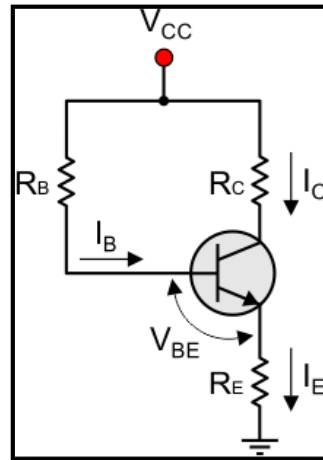
$$V_{CE} = V_{CC} - R_c I_c - R_E I_E \dots (2)$$



Transistor biasing circuits:

Example: Design Biasing circuit with stabilization resistor (R_E) using a silicon transistor having

$$\beta(\min) = 25, \quad \beta(\max) = 75$$

Such that $I_c = 1mA$, and $V_{CE} = 5 \text{ volt}$ given $V_{CC} = 10 \text{ volt}$

From eq.2 :

$$V_{CE} = V_{CC} - R_c I_c - R_E I_E$$

$$\rightarrow R_c = 3k\Omega$$

Solution:

In this circuit we have **3-unknowns** (R_B, R_c, R_E) & **two equations!**



From eq.1 : $I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$

$$\rightarrow R_B = 365k\Omega$$

We must make a new assumption :

$$\frac{V_{CC}}{5} \geq V_{RE} \geq \frac{V_{CC}}{10} \quad ; \quad \beta = 50$$

$$\text{let } V_{RE} = \frac{V_{CC}}{5} = \frac{10}{5} = 2 \text{ volt}$$

$$V_{RE} = R_E I_E$$

$$\rightarrow R_E = \frac{2}{1.02 \text{ mA}} \cong 2k\Omega$$



Proof that :

$$75 \geq \beta \geq 25$$

$$1.349 \text{ mA} \geq I_c \geq 0.55755 \text{ mA}$$

There is an improvement over the fixed bias circuit.

Transistor biasing circuits:

4) Voltage divider bias circuit:

a) Approximate method:

$$I_B \text{ Very small } \gg \gg I_B = 0$$

$$\diamond I_1 = I_2$$

$$V_B = \frac{R_2}{R_2 + R_1} V_{CC} \quad \text{Voltage divider}$$



$$V_{BE} = V_B - V_E$$

$$\diamond V_E = V_B - V_{BE}$$

$$I_{E1} = \frac{V_E}{R_E} = \frac{V_B - V_{BE}}{R_E}$$

$$I_C = \alpha I_E = I_E$$

$$V_{CE} = V_{CC} - R_c I_c - R_E I_E$$

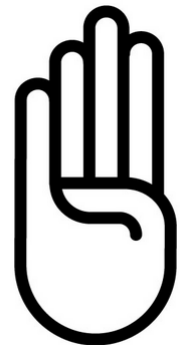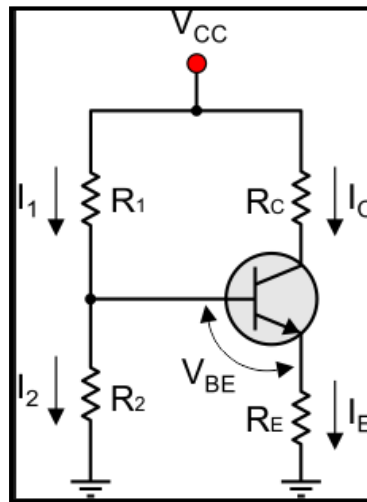


Transistor biasing circuits:

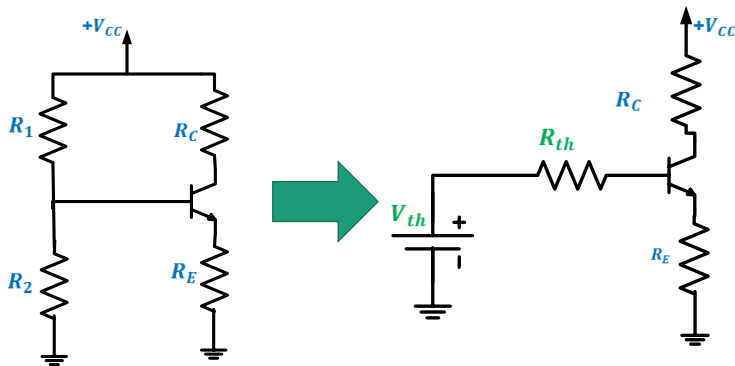b) Exact method:

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{th} = \frac{R_2}{R_1 + R_2} V_{CC}$$



KVL: $V_{th} = R_{th} I_B + V_{BE} + R_E I_E$

$$I_E = (\beta + 1) I_B$$

$$I_{E2} = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta + 1} + R_E}$$

Transistor biasing circuits:

Using approximate method, we get:

$$I_{E1} = \frac{V_B - V_{BE}}{R_E}$$

Where:

$$V_B = \frac{R_2}{R_2 + R_1} V_{CC}$$

Using exact method, we get:

$$I_{E2} = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta + 1} + R_E}$$

Where:

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} \quad \text{,,,} \quad V_{th} = \frac{R_2}{R_1 + R_2} V_{CC}$$

To make $I_{E2} \cong I_{E1}$:

$$\frac{R_{th}}{\beta + 1} + R_E \cong R_E$$

$$\frac{R_{th}}{\beta + 1} \ll R_E$$

$$R_{th} \ll (\beta + 1) R_E$$

$$R_{th} = \frac{(\beta + 1) R_E}{10, 20, 30..}$$



Example: Design a Voltage divider bias circuit using a silicon transistor having

$$\beta(\min) = 25, \quad \beta(\max) = 75$$

Such that $I_C = 1\text{mA}$, and $V_{CE} = 5\text{ volt}$ given $V_{CC} = 10\text{ volt}$

Solution:

$$\text{Let } V_{RE} = \frac{V_{CC}}{10} = \frac{10}{10} = 1\text{ volt}$$

$$V_{RE} = R_E I_E$$

$$\triangleright R_E = \frac{1}{1.02\text{mA}} \cong 1\text{k}\Omega$$

$$\text{From : } R_{th} = \frac{(\beta+1)R_E}{10,20,30..}$$

$$\text{Let } R_{th} = \frac{(\beta)R_E}{50}, \text{ where } \beta = 50$$

$$\triangleright R_{th} = 1\text{k}\Omega$$

$$\text{KVL: } V_{CC} = V_{CE} + R_C I_C + R_E I_E$$

$$\triangleright R_C = 4\text{k}\Omega$$

To find R_1, R_2 , we need to find R_{th}, V_{th} :

$$\text{From: } I_E = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta+1} + R_E}$$

$$\text{We find } V_{th} = 1.72\text{ volt}$$

$$\text{We have : } V_{th} = 1.72\text{ volt} \quad \&\& \quad R_{th} = 1\text{k}\Omega$$

From:

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} \quad \text{and} \quad V_{th} = \frac{R_2}{R_1 + R_2} V_{CC}$$

We get:

$$\triangleright R_1 = 5.8\text{ k}\Omega$$

$$\triangleright R_2 = 1.2\text{ k}\Omega$$

Our design @ $\beta = 50$

$$\triangleright R_E = 1\text{k}\Omega$$

$$\triangleright R_C = 4\text{k}\Omega$$

$$\triangleright R_1 = 5.8\text{ k}\Omega$$

$$\triangleright R_2 = 1.2\text{ k}\Omega$$

$$\triangleright I_C = 1\text{mA},$$

$$\triangleright V_{CE} = 5\text{ volt}$$

But:

$$75 \geq \beta \geq 25$$


$$1.0067\text{mA} \geq I_C \geq 0.982\text{mA}$$



Circuit using pnp transistor:

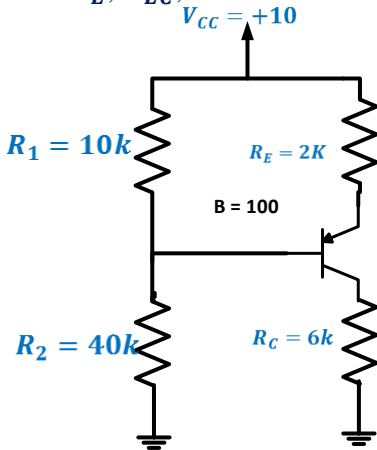
Example:

Find I_E , V_{EC} , for the circuit below:



solution

Using thevenin's theorem:

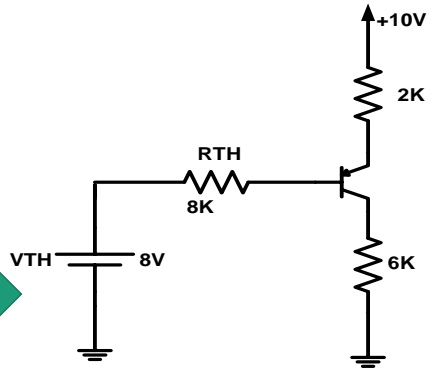

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{10 * 40}{10 + 40} k = 8k\Omega$$

$$V_{th} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{40}{10 + 40} * 10 = 8 \text{ volt}$$

$$\text{KVL: } 10 = 2kI_E + V_{EB} + R_{th}I_B + V_{th}$$

$$\text{➤ } I_E = 0.625 \text{ mA}$$

$$\text{KVL: } 10 = 2kI_E + V_{EC} + 6kI_C$$

$$\text{➤ } V_{EC} = 5 \text{ volt}$$


Example:

Design the given circuit so that


$$I_{CQ} = 2 \text{ mA}, \text{ and } V_C = 5 \text{ volt}$$

Given that $V_{BE} = 0.7 \text{ volt}$ @ $I_C = 1 \text{ mA}$

$$\beta = \infty$$

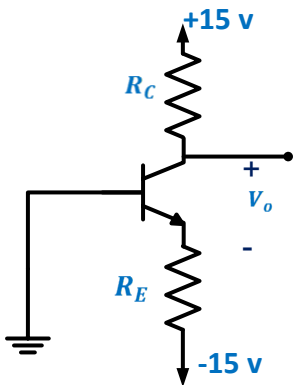

Solution:

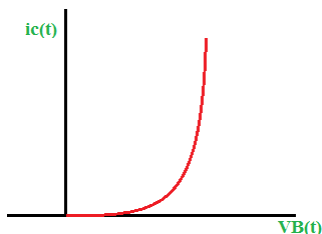

$$i_C(t) \cong I_S e^{\frac{V_{BE}(t)}{V_T}}$$

$$I_C \cong I_S e^{\frac{V_{BE}}{V_T}}$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right)$$

In our circuit $I_C = 2mA$ we must find the corresponding $V_{BE}??$

$V_{BE} @ I_C = 2mA ??$

$$V_{BE1} = 0.7 = V_T \ln\left(\frac{1mA}{I_S}\right)$$

$$V_{BE2} = V_T \ln\left(\frac{2mA}{I_S}\right)$$

$$V_{BE2} - V_{BE1} = V_T \ln\left(\frac{I_{C2}}{I_{C1}}\right)$$

$$V_{BE2} = V_{BE1} + V_T \ln\left(\frac{2mA}{1mA}\right)$$

$$\text{➤ } V_{BE2} = 0.717 V$$




$$V_{BE2} = 0.717 @ I_C = 2mA$$

$$\text{KVL: } V_C = V_{CC} - R_C I_C$$

$$R_C = \frac{(V_{CC} - V_C)}{I_C}$$

$$R_C = \frac{(15 - 5)}{2mA}$$

$$\text{➤ } R_C = 5k\Omega$$

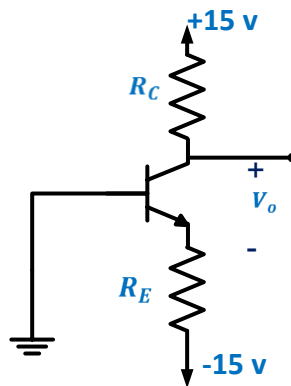


$$\text{KVL: } V_{BE} + R_E I_E - 15 = 0$$

$$R_E = \frac{15 - V_{BE}}{I_E}$$

$$\text{➤ } R_E = 7k\Omega$$

Example:

Find I_{E1}, I_{E2}

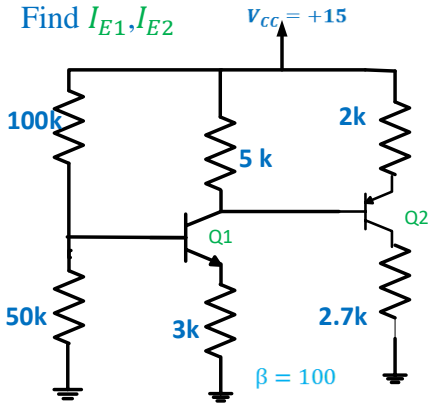


Solution

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{50 * 100}{50 + 100} k = 33.3 k\Omega$$

$$V_{th} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{50}{50 + 100} * 15 = 5 \text{ volt}$$

KVL:

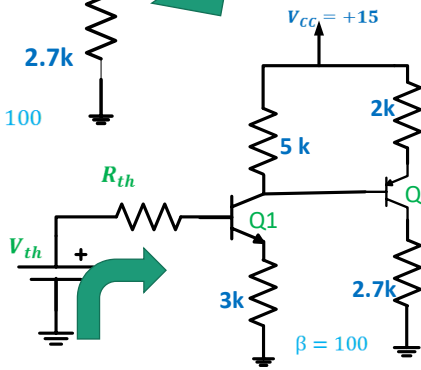

$$I_{E1} = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta + 1} + R_E} = \frac{5 - 0.7}{\left(\frac{33.3k}{101}\right) + 3k} = 1.28 \text{ mA}$$




KVL:

$$2k I_{E2} + V_{EB} - 5k(I_{C1} - I_{B2}) = 0$$

$$I_{E2} = 2.78 \text{ mA}$$

The first project

Automatic Light Controller

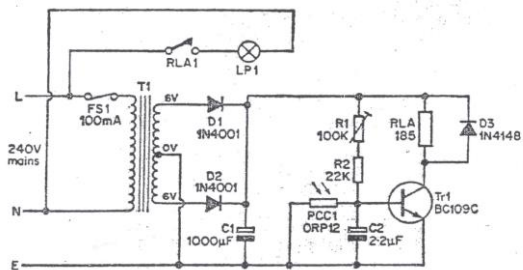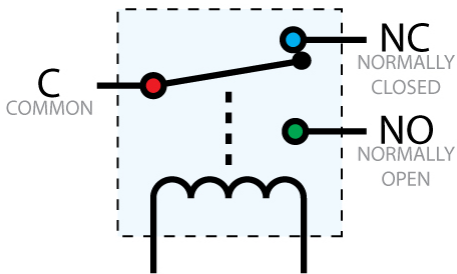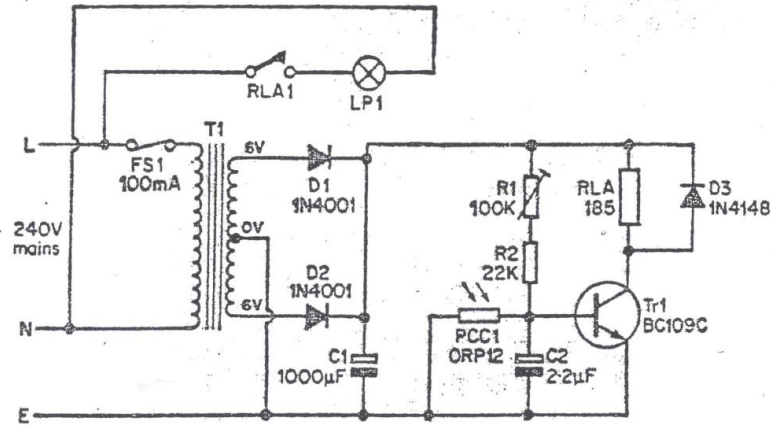

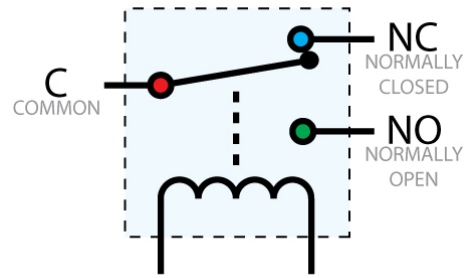


FIGURE 1


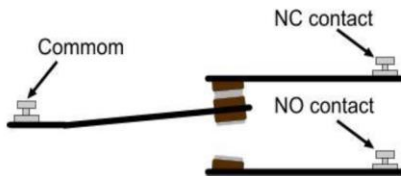


FIGURE 2

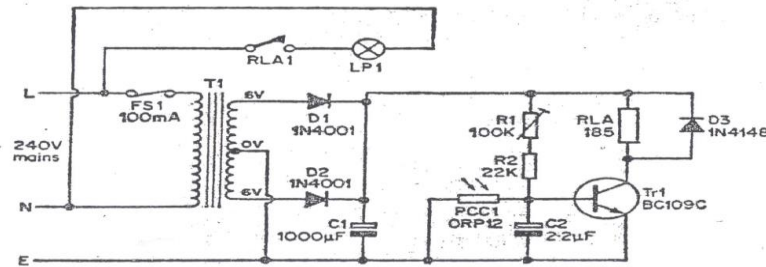

In day time

- R_p is small, so that $V_{BE} < 0.7V$
- \therefore Transistor is in cutoff
- \therefore Relay is deenergized
- \therefore Switch is open
- \therefore Lamp is OFF

At night




- R_p becomes large, so that $V_{BE} \approx 0.7V$
- \therefore The Transistor is on
- \therefore Relay is energized
- \therefore Switch is close

BJT Ac-Small signal analysis using Graphical method:

Graphical method:

KVL: $V_{CC} = R_c I_c + V_{CE}$
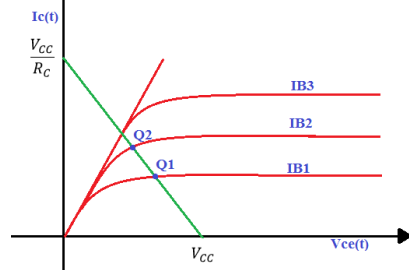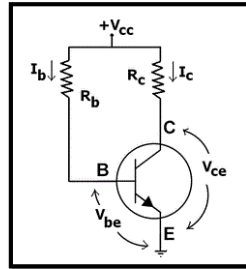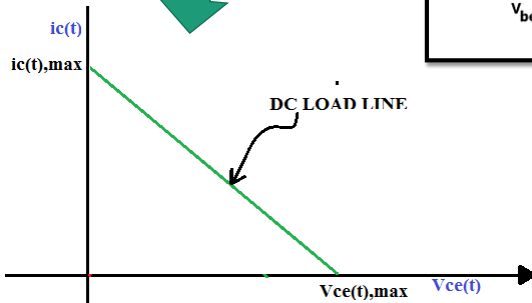
$$I_c = -\frac{1}{R_c} V_{CE} + \frac{V_{CC}}{R_c}$$



$$i_c(t),_{max} = \frac{V_{CC}}{R_c} \quad \text{Saturation}$$

$$V_{CE(t),max} = V_{CC} \quad \text{Cutoff}$$

Small signal BJT amplifier:

DC Analysis:

From **KVL:**

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{18 - 0.65}{576k}$$

➤ $I_B = 30\mu A$


But: $I_C = \beta I_B$


➤ $I_C = 3mA$

KVL:

$$V_{CC} = R_c I_c + V_{CE}$$

➤ $V_{CE} = 9 \text{ volt}$

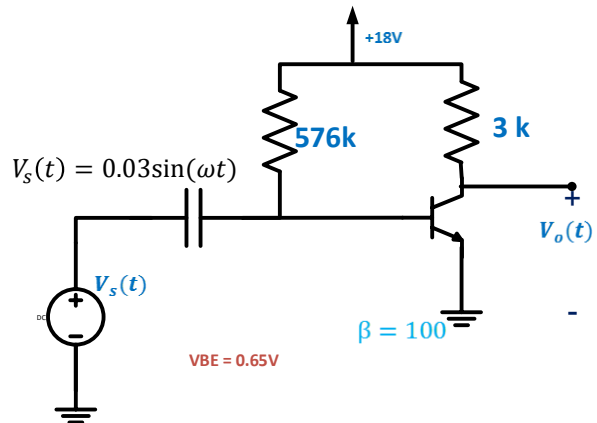

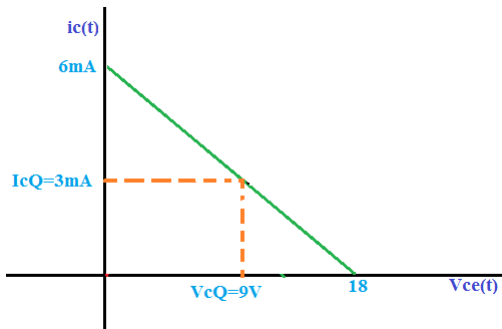


$$V_{BE}(t) = V_{BE} + v_{be}$$

$$i_C(t) = I_{CQ} + i_c$$

$$V_{CE}(t) = V_{CEQ} + v_{ce}$$


Ac analysis:

Ac equivalent circuit:



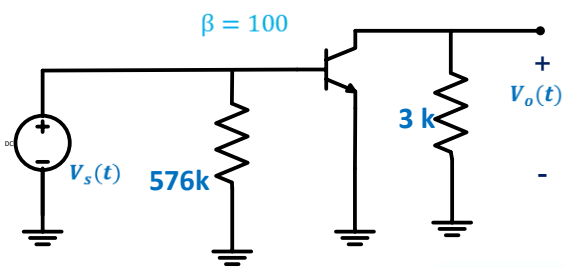


$$v_{be} = V_s(t) = 0.03\sin(\omega t)$$
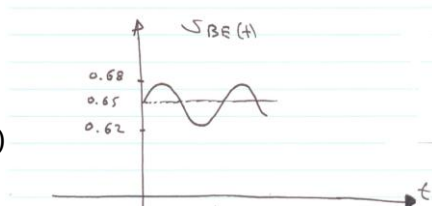
$$V_{BE}(t) = 0.65 + 0.03\sin(\omega t)$$



Ac small signal analysis

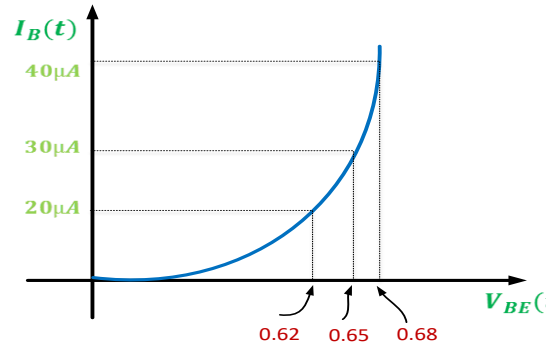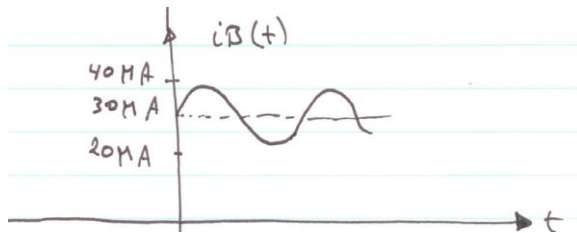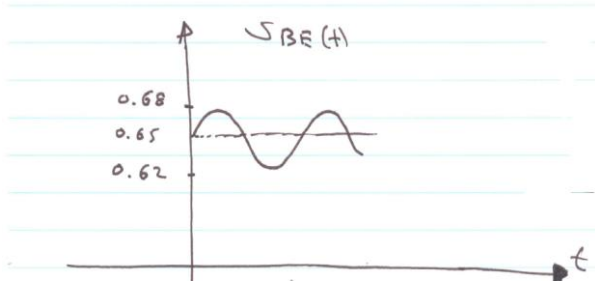

When: $V_{BE}(t) = 0.65$; $i_B(t) = 30\mu A$

$V_{BE}(t) = 0.68$; $i_B(t) = 40\mu A$

$V_{BE}(t) = 0.62$; $i_B(t) = 20\mu A$

Using:

$$i_C(t) = \beta i_B(t)$$

$$V_{CE}(t) = V_{CC} - R_C i_C$$

When : $i_B(t) = 30\mu A$; $i_C(t) = 3mA$


$$V_{CE}(t) = 9 \text{ volt}$$



When : $i_B(t) = 40\mu A$; $i_C(t) = 4mA$

$$V_{CE}(t) = 6 \text{ volt}$$

When : $i_B(t) = 20\mu A$; $i_C(t) = 2mA$

$$V_{CE}(t) = 12 \text{ volt}$$

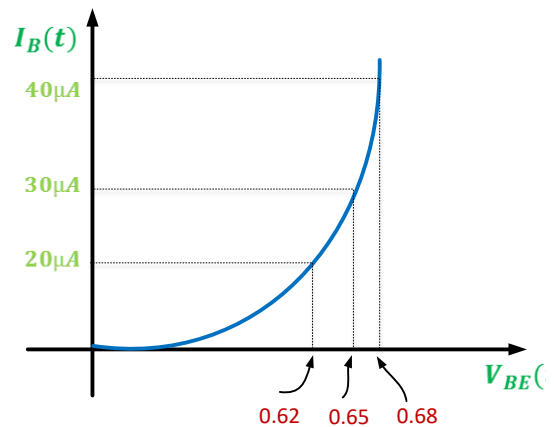

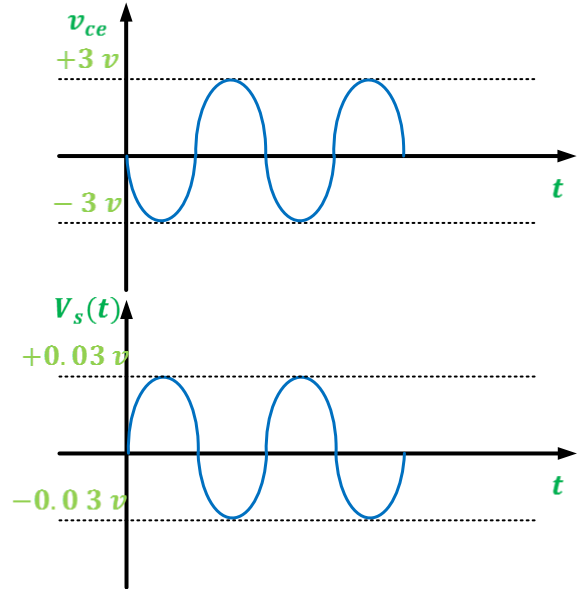
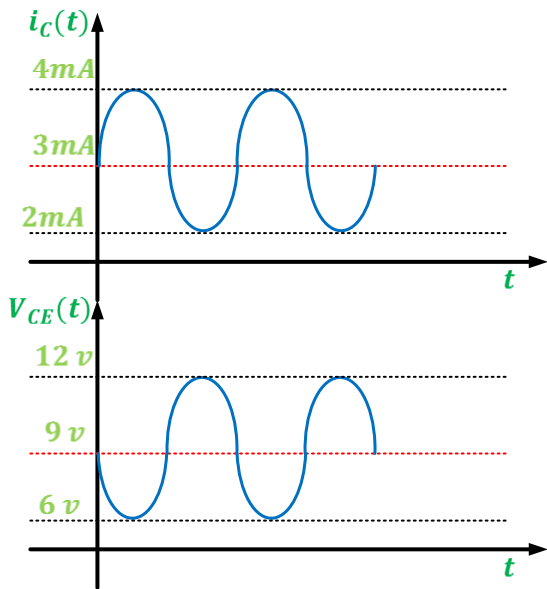




Let $R_B = 3.47M\Omega$

$$I_B = \frac{18 - 0.65}{3.47M} = 5\mu A$$


$$I_C = 0.5mA$$

$$V_{CE} = 16.5 \text{ volt}$$

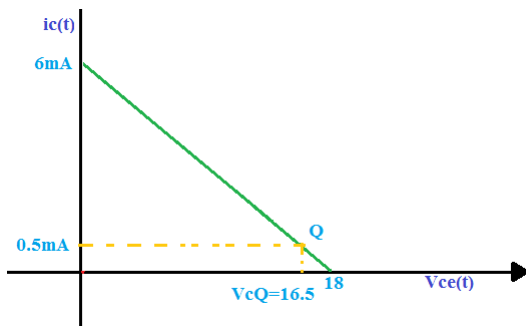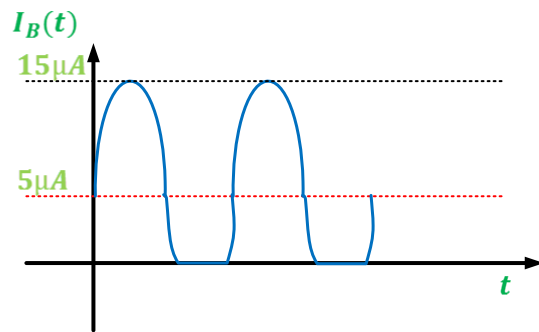


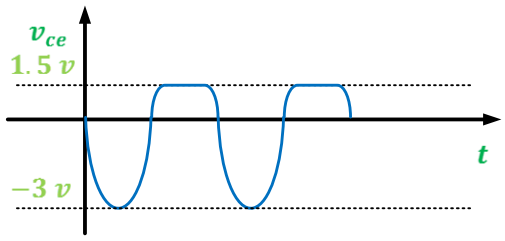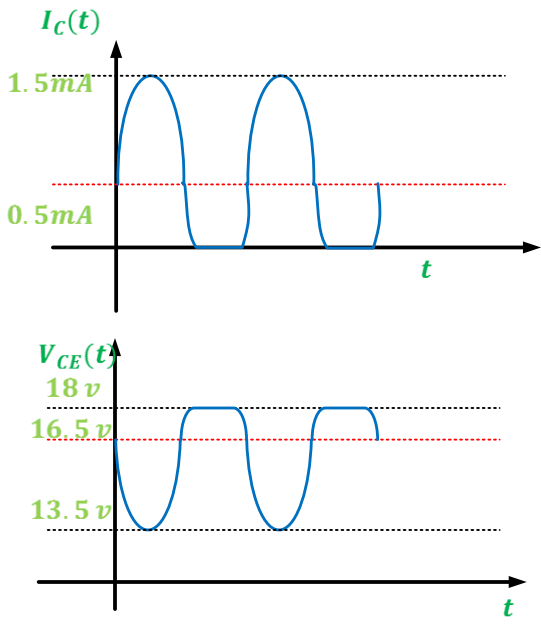

Maximum possibility swing:

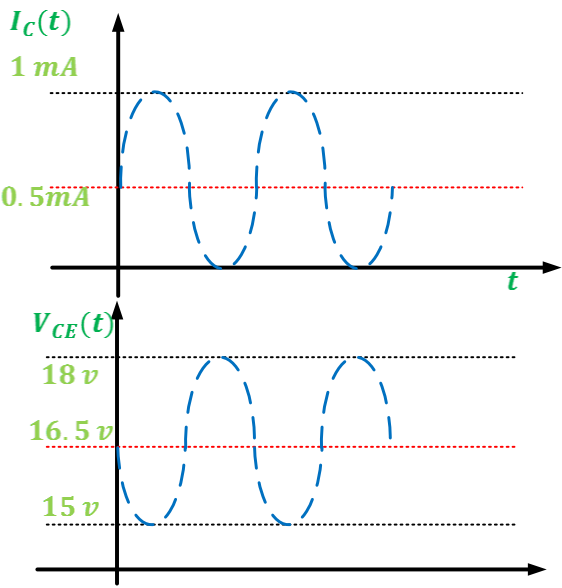

Ac load line:

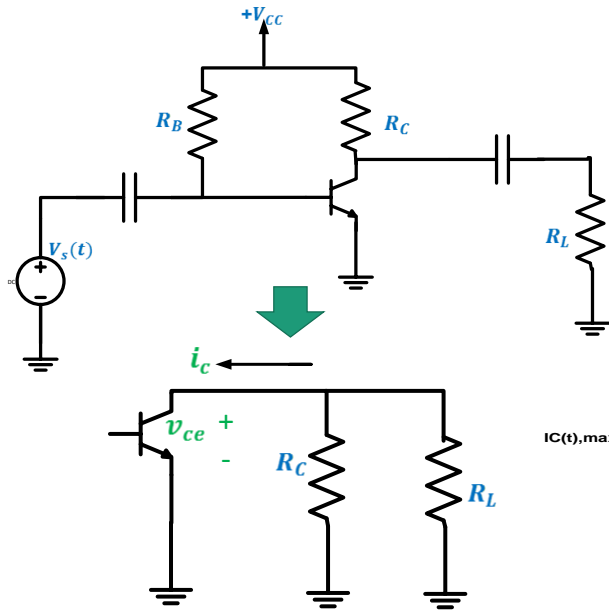

$$v_{ce} = -(R_C || R_L) i_c ;$$

$$v_{ce} = -R_{ac} i_c ;$$


$$V_{CE}(t) - V_{CEQ} = -R_{ac}(i_c(t) - I_{CQ})$$

To find $i_{c,max}(t)$ set $V_{CE}(t) = V_{CE,sat} \cong 0$

$$\triangleright i_{c,max}(t) = I_{CQ} + \frac{V_{CEQ}}{R_{ac}}$$

To find $V_{CE,max}(t)$ set $i_c(t) = 0$
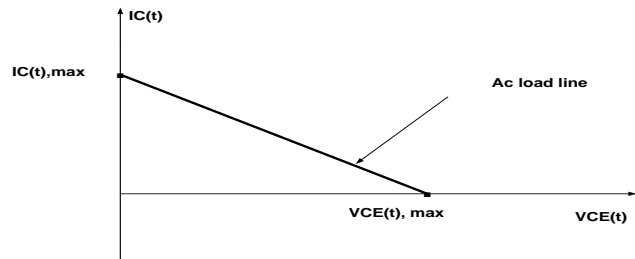
$$\triangleright V_{CE,max}(t) = V_{CEQ} + R_{ac} I_{CQ}$$



For maximum symmetrical swing:

$$I_{CQ} = \frac{1}{2} i_{c,max}(t)$$

$$i_{c,max}(t) = I_{CQ} + \frac{V_{CEQ}}{R_{ac}} = 2I_{CQ}$$

$$\triangleright I_{CQ} = \frac{V_{CEQ}}{R_{ac}}$$

For DC condition:

$$V_{CC} = R_C I_C + V_{CE}$$

$$V_{CC} = R_{dc} I_C + V_{CE}$$


$$V_{CC} = R_{dc} I_C + R_{ac} I_C$$

$$\triangleright I_C = \frac{V_{CC}}{R_{dc} + R_{ac}}$$

Example:

Find R_{dc} , R_{ac}

For maximum symmetrical swing:

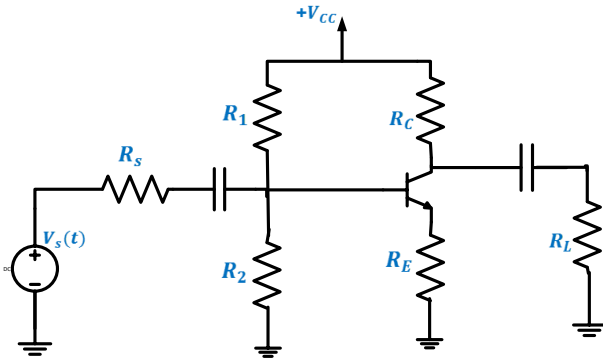

$$I_C = \frac{V_{CC}}{R_{dc} + R_{ac}}$$

$$R_{dc} = R_C + R_E$$

$$R_{ac} = R_E + (R_C || R_L)$$

$$V_{CEQ} = R_{ac} * I_{CQ}$$

Ac small signal equivalent circuits for BJT configuration:



Hybrid parameters “h- parameters”:

$$v_1 = h_{11}i_1 + h_{12}v_2$$


$$i_2 = h_{21}i_1 + h_{22}v_2$$

$$h_{11} = \left. \frac{v_1}{i_1} \right|_{v_2 = 0} \text{ Short circuit input impedance, } \Omega (h_i)$$

$$h_{12} = \left. \frac{v_1}{v_2} \right|_{i_1 = 0} \text{ Open circuit reverse voltage ratio, } (h_r)$$


$$h_{21} = \left. \frac{i_2}{i_1} \right|_{v_2 = 0} \text{ Short circuit forward current ratio, } (h_f)$$

$$h_{22} = \left. \frac{i_2}{v_2} \right|_{i_1 = 0} \text{ Open circuit output admittance, } S (h_o)$$

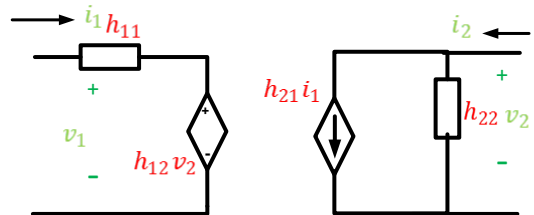


Transistor configuration:


1. common emitter:

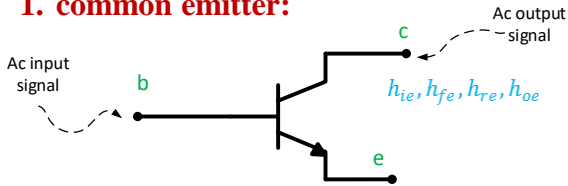


2. common collector

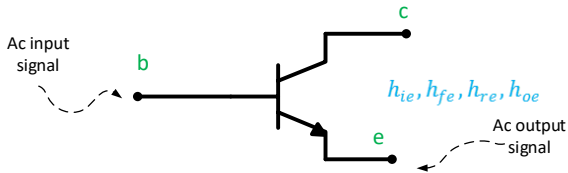

3. common base

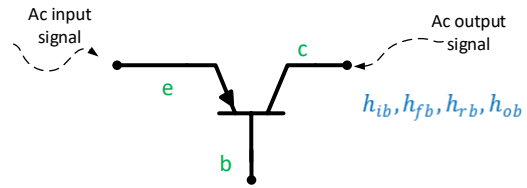


Common emitter & common collector:

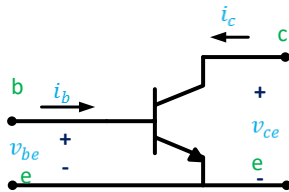


$$v_{be} = h_{ie}i_b + h_{re}v_{ce}$$

$$i_c = h_{fe}i_b + h_{oe}v_{ce}$$

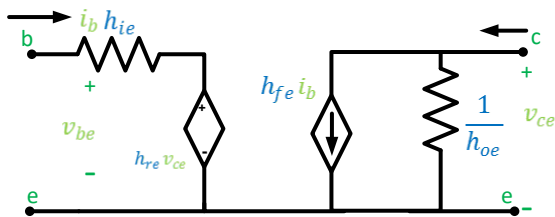


Common base:

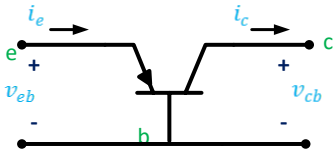

$$v_{eb} = h_{ib}i_e + h_{rb}v_{cb}$$

$$i_c = h_{fb}i_e + h_{ob}v_{cb}$$

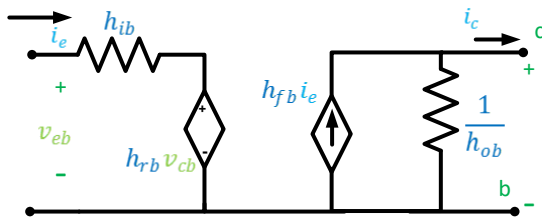

h-parameter typical value:

$$h_{ie} = 1600\Omega$$

$$h_{oe} = 20 * 10^{-6} \text{ S}$$

$$h_{fe} = 80$$

$$h_{re} = 20 * 10^{-4}$$

$$h_{oe} = 20 * 10^{-6} \text{ S} \longrightarrow 0;$$



We replace $\frac{1}{h_{oe}}$ with open circuit.

$$h_{re} = 20 * 10^{-4} \longrightarrow 0;$$



We replace $h_{re}v_{ce}$ with short circuit.

Approximate BJT models:

1) Common emitter & common collector:

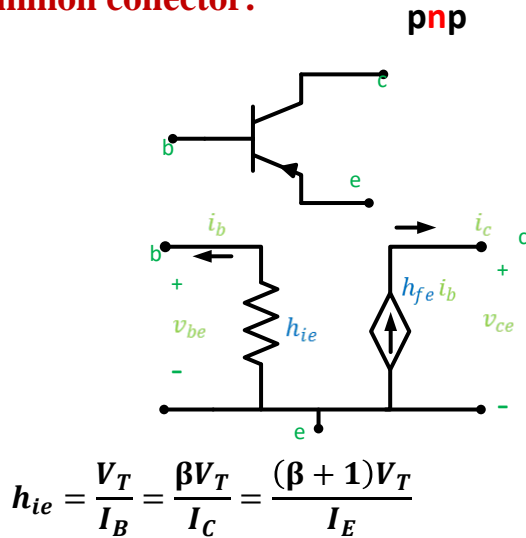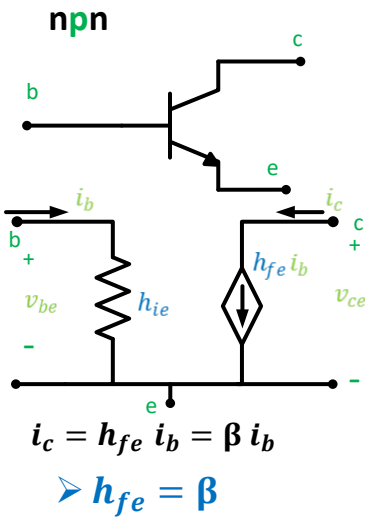

2-common base:

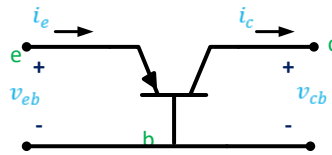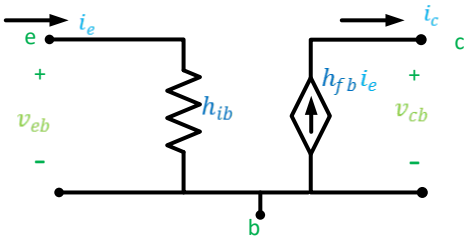

$i_c = h_{fb} i_e = \alpha i_e$
 $\triangleright h_{fb} = \alpha$

$h_{ib} = \frac{V_T}{I_E}$

$h_{ie} = (h_{fe} + 1)h_{ib}$



BJT ac amplifiers:

1-common base amplifiers:



Find :

1. voltage gain
2. Current gain
3. output impedance
4. Input impedance

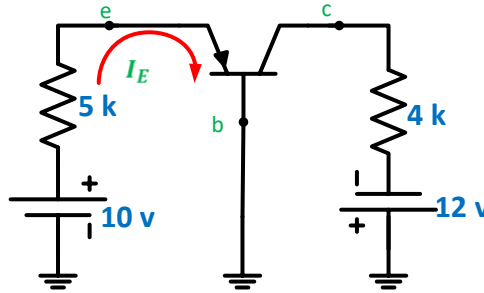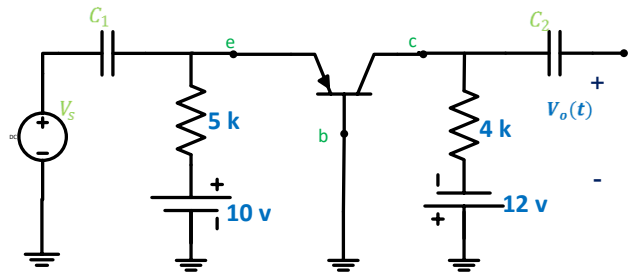a) Dc analysis:

$$I_E = \frac{10 - V_{EB}}{5k} = \frac{10 - 0.7}{5k} = 1.86mA$$

$$h_{ib} = \frac{V_T}{I_{EQ}} = 13.98\Omega$$



BJT ac amplifiers:

1-common base amplifiers:

b) Ac small signal analysis:



Ac small signal equivalent circuit:

1. Voltage gain $A_v = \frac{V_o}{V_s}$

$$V_o = h_{fb} i_e (4k)$$

$$i_e = \frac{V_s}{h_{ib}}$$
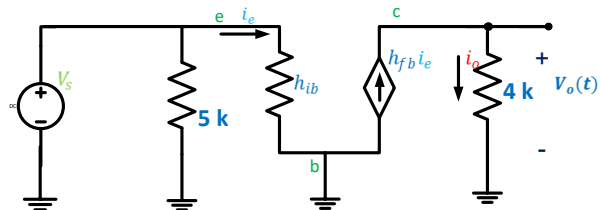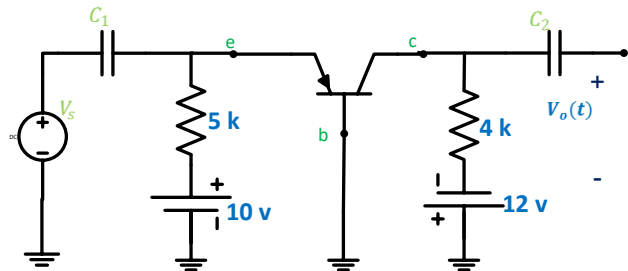
$$A_v = \frac{V_o}{V_s} = \frac{h_{fb}(4k)}{h_{ib}} = 286 > 1$$




V_s Is in phase with V_o

2. Current gain $A_i = \frac{i_o}{i_{in}}$

$$i_o = h_{fb} i_e$$

$$i_e = i_{in} \frac{5k}{5k + h_{ib}}$$
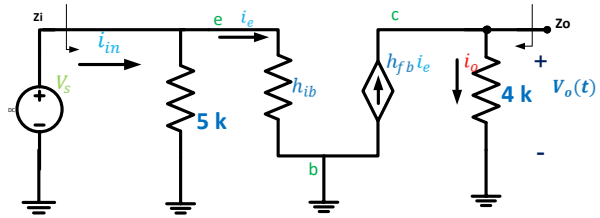
$$A_i = \frac{5k}{5k + h_{ib}} h_{fb} < 1$$



3. Input impedance Z_i

$$Z_i = \frac{V_s}{i_{in}}$$

$$i_{in} = \frac{V_s}{5k} + \frac{V_s}{h_{ib}}$$


$$\frac{V_s}{i_{in}} = (5k || h_{ib}) \cong h_{ib}$$

$Z_i \cong h_{ib}$ Very small;

Output impedance Z_o

Z_o Is R_{th} seen by the load


$$Z_o = \left. \frac{V_T}{I_T} \right| V_s = 0$$

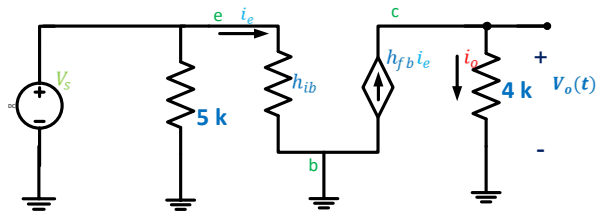

$$I_T = \frac{V_T}{4k} - h_{fb} i_e$$

$$i_e = 0$$
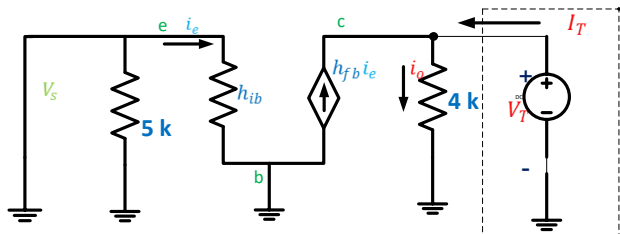
$$\frac{V_T}{I_T} = 4k \quad (\text{Large})$$



Common base amplifier


$$A_v = \frac{V_o}{V_s} = \frac{h_{fb}(4k)}{h_{ib}} = 286 > 1$$

$$A_i = \frac{5k}{5k + h_{ib}} h_{fb} < 1$$

$$Z_i = (5k || h_{ib})$$

$Z_i \cong h_{ib}$ Very small;

$Z_o = 4k$ (Large)

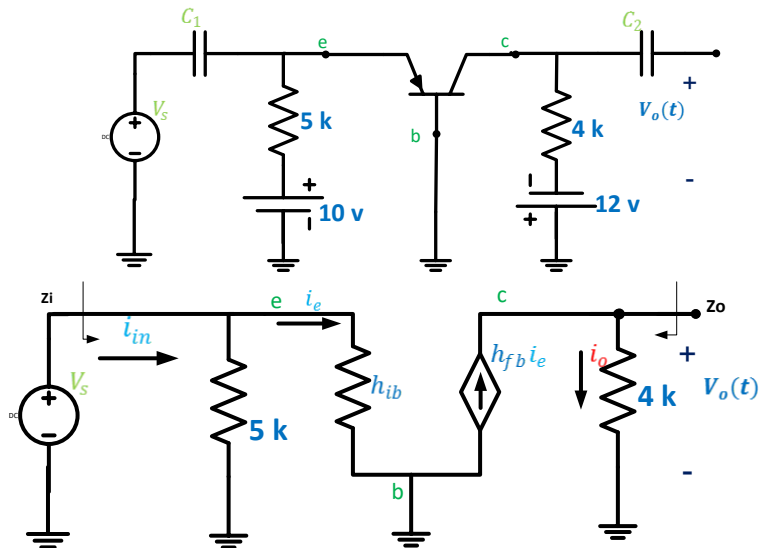

The effect of R_s

$$V_o = h_{fb} i_e (4k)$$

$$i_e = \frac{V_i}{h_{ib}}$$


$$V_i = (5k || h_{ib}) / ((5k || h_{ib}) + R_s) V_s$$

$$V_i = \frac{Z_i}{Z_i + R_s} * V_s$$

$$A_{vs} = \frac{V_o}{V_s} = \frac{h_{fb}(4k)}{h_{ib}} \frac{Z_i}{Z_i + R_s}$$

$$A_{vs} = \begin{cases} 62.5 & R_s = 50\Omega \\ 0.4 & R_s = 10k\Omega \end{cases}$$


Ac small signal equivalent circuit:

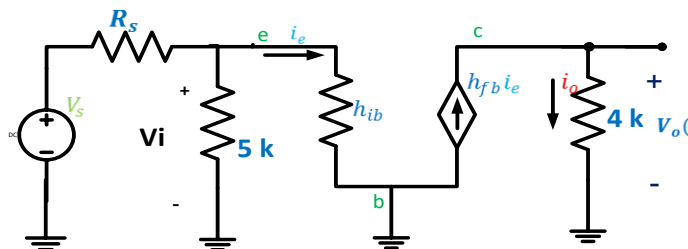

$$V_o = 286 V_i$$

$$V_i = \frac{Z_i}{Z_i + R_s} * V_s$$


$$V_o = \frac{Z_i}{Z_i + R_s} 286 V_i$$

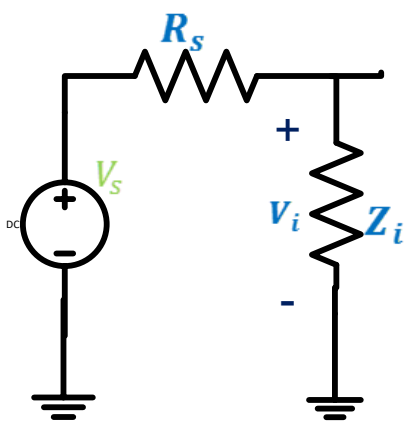

Z_i Must be as large as could be 


The effect of R_L

Using thevenin's theorem:

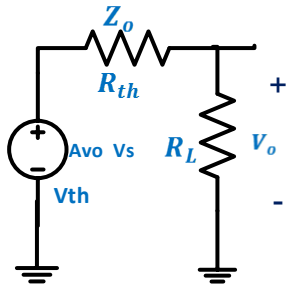


$$V_o = \frac{R_L}{R_L + Z_o} A_{V_o} V_s$$

Z_o Must be as small as co 

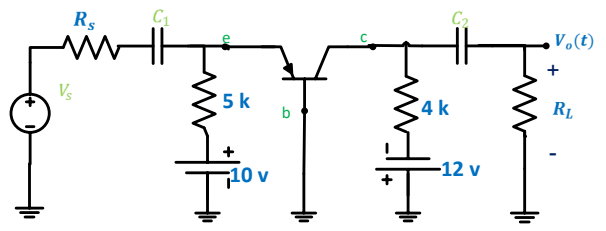


Ac small signal equivalent circuit:

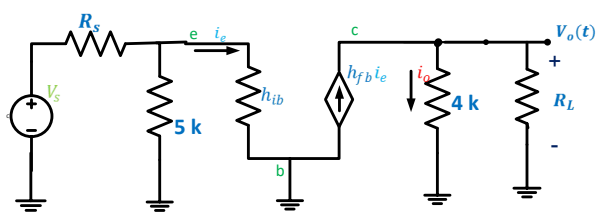


2) Common emitter amplifier:

Find:

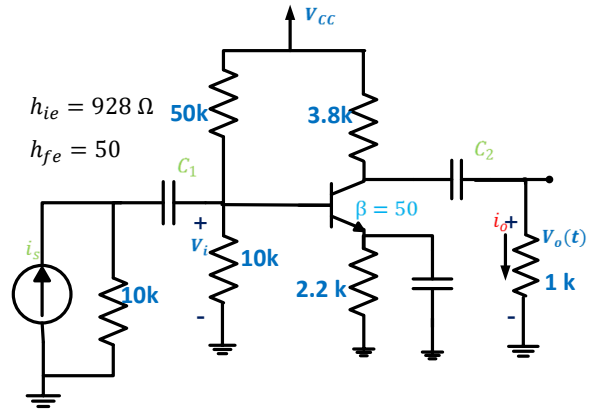1. voltage gain
2. Current gain
3. output impedance
4. Input impedance



Ac small signal equivalent circuit:

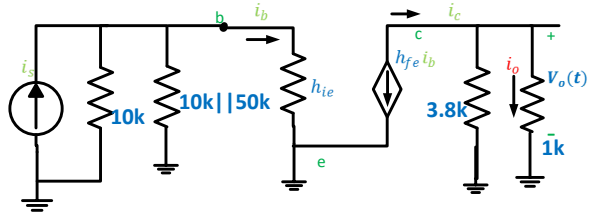

$$A_i = \frac{i_o}{i_s}$$

$$i_o = -h_{fe}i_b * \frac{3.8k}{3.8 + 1k}$$

$$i_b = i_s \cdot \frac{10k || 10k || 50k}{10k || 10k || 50k + h_{ie}}$$

➤ $A_i = -33$

$$A_v = \frac{V_o}{V_i}$$

$$V_o = -h_{fe}i_b(1k || 3.8k)$$

$$i_b = \frac{V_i}{h_{ie}}$$

➤ $A_v = \frac{V_o}{V_i} = -42.7$


For Common emitter amplifier:

- $|A_v| > 1$
- $|A_i| > 1$
- Z_i Large
- Z_o Large




➤ $Z_i = 10k || 50k || h_{ie}$


➤ $Z_o = 3.8k$

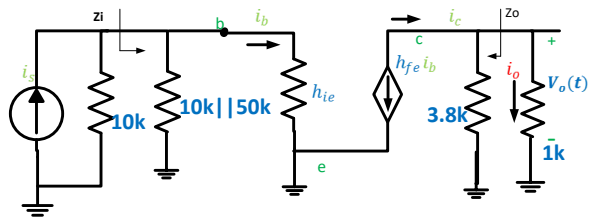

Impedance reflection:

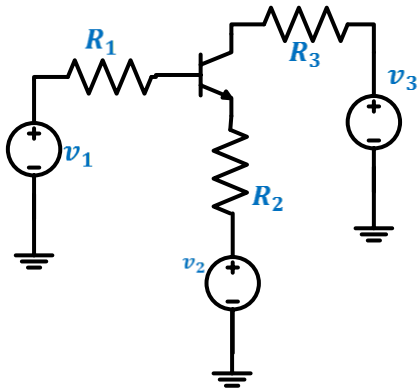


Ac small signal equivalent circuit:

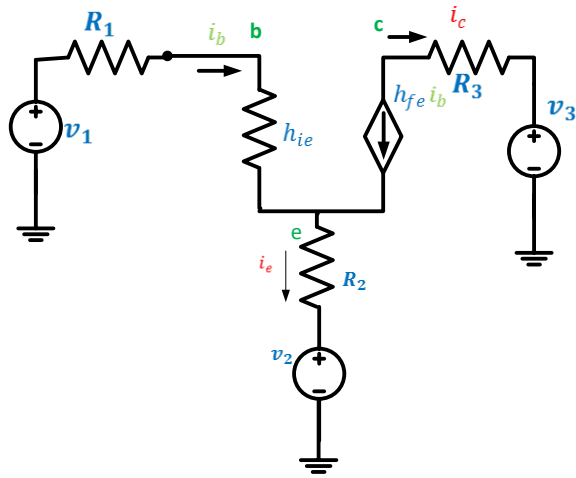


Base equivalent circuit:
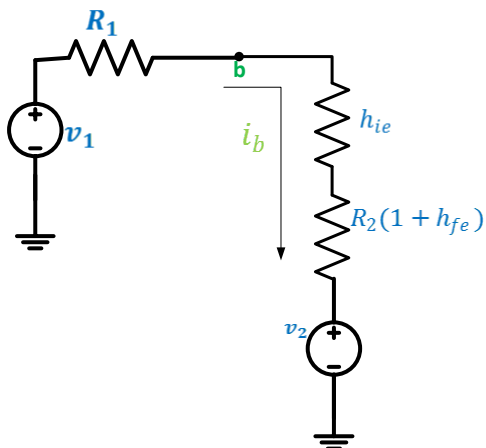
$$i_b = \frac{v_1 - v_2}{R_2(1 + h_{fe}) + R_1 + h_{ie}}$$




Emitter equivalent circuit:

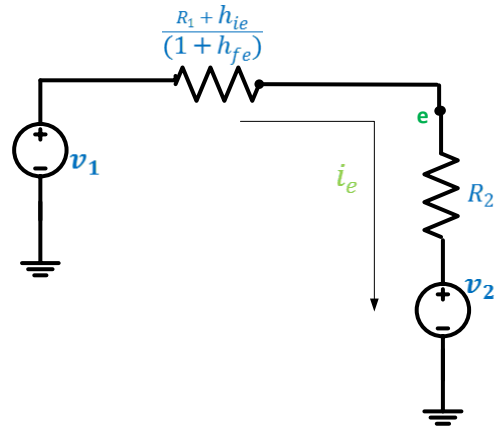
$$i_e = \frac{v_1 - v_2}{R_2 + \frac{R_1 + h_{ie}}{(1 + h_{fe})}}$$




Collector equivalent circuit:

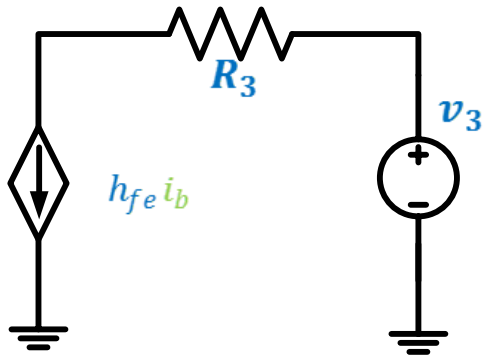

3) Common collector amplifier:

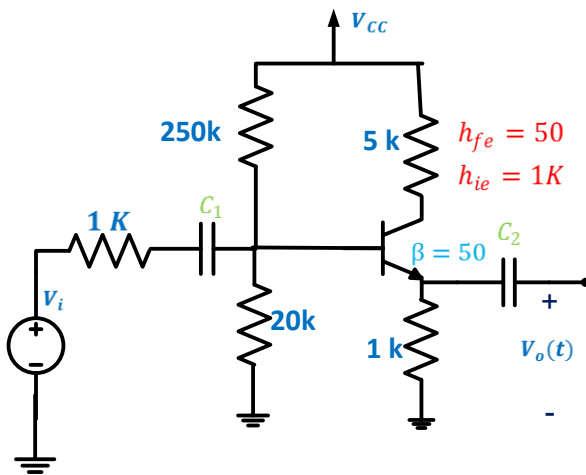

Ac small signal equivalent circuit

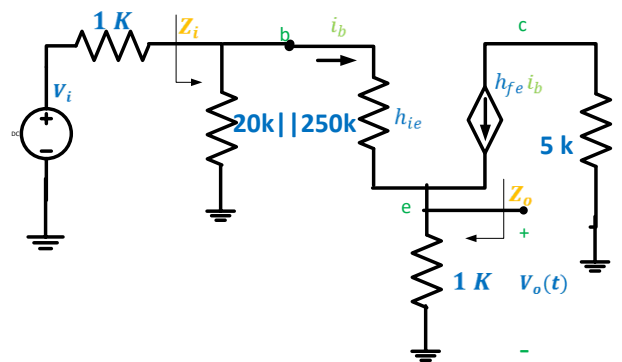

$$A_v = \frac{V_o}{V_{in}}$$

$$V_o = 1k * i_e$$


$$i_e = (1 + h_{fe})i_b$$

To find i_b  base equivalent circuit:


$$i_b = \frac{(20k || 250k) i_{in}}{(20k || 250k) + h_{ie} + 1k(1 + h_{fe})}$$

$$i_{in} = \frac{v_{in}}{1k + Z_{in}}$$

$$Z_{in} = [(20k || 250k) || [h_{ie} + 1k(1 + h_{fe})]]$$

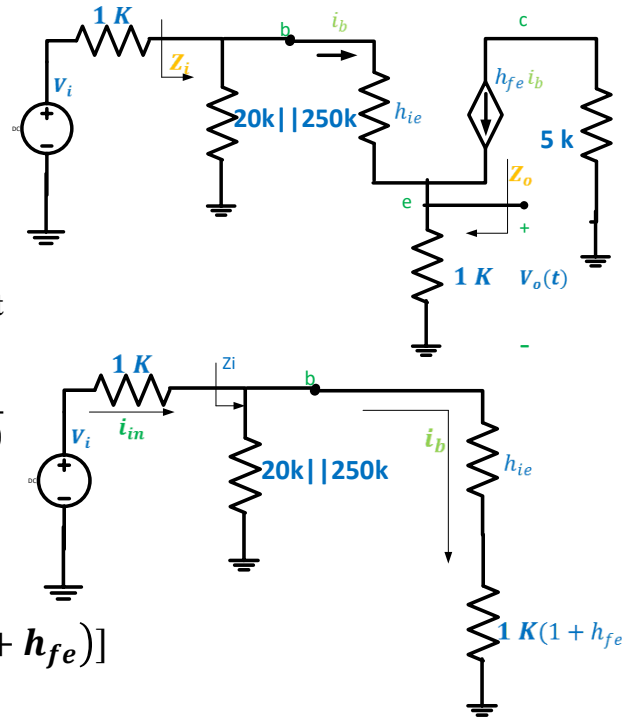

$$i_{in} = \frac{v_{in}}{1k + [(20k || 250k) || [h_{ie} + 1k(1 + h_{fe})]]}$$

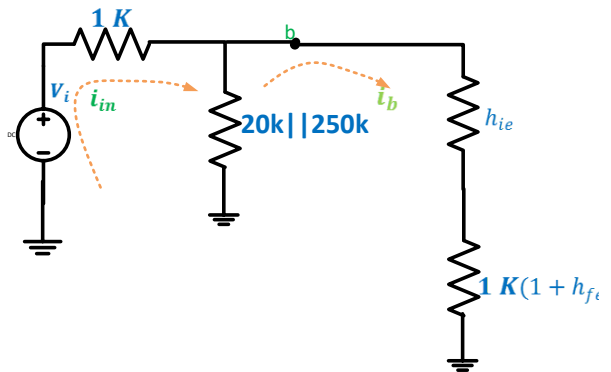

➤ $Z_{in} = 13.66K$

➤ $A_v = \frac{V_o}{V_{in}} = 0.9149$


➤ $A_i = \frac{i_o}{i_{in}} = 13.9$

To find Z_o ; emitter equivalent circuit:



$$R_{th} = 1k \parallel 20k \parallel 250k$$

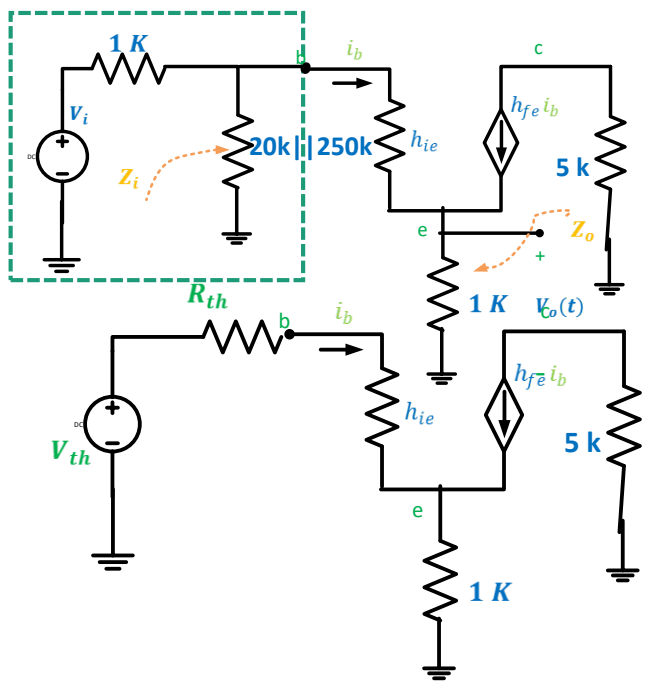
$$V_{th} = \frac{(20k \parallel 250k)}{(20k \parallel 250k) + 1k} V_{in}$$




Emitter equivalent circuit:

To find Z_o we set $V_{in} = 0$

❖ $V_{th} = 0$

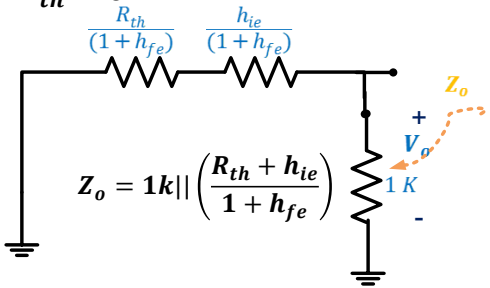
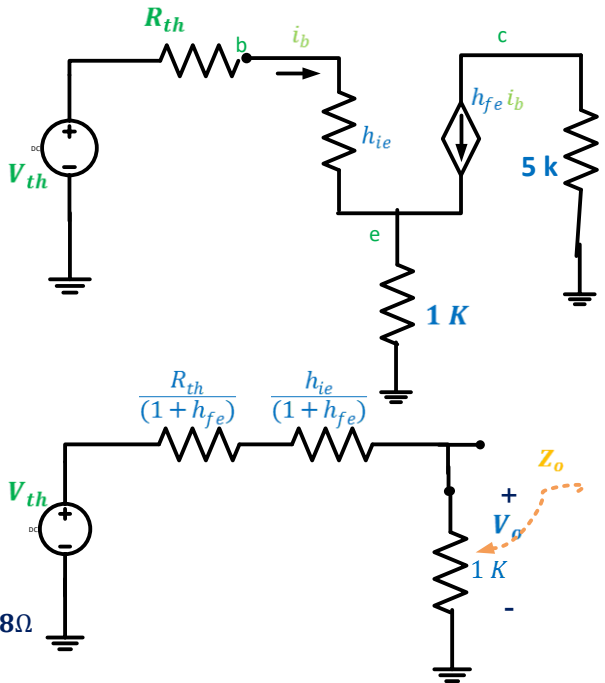
$$Z_o = 1k \parallel \left(\frac{1k \parallel 20k \parallel 250k + h_{ie}}{1 + h_{fe}} \right) = 36.8\Omega$$




For common collector amplifier:

- $A_v < 1$
- $A_i > 1$
- Z_o very small
- $Z_i =$ very larg



The common collector as a buffer:

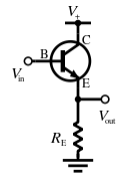Although the small signal voltage gain of the common collector (emitter follower) is less than 1, it can be used to improve the total voltage gain of a multistage amplifier.




Common emitter amplifier


$$A_v = \frac{V_o}{V_{in}} = -140$$





Proof!!

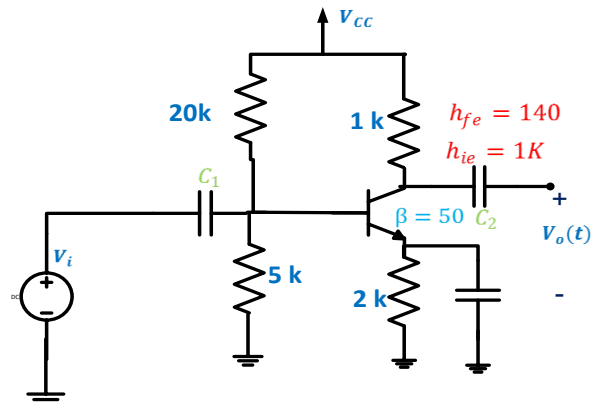


Ac small signal equivalent circuit:

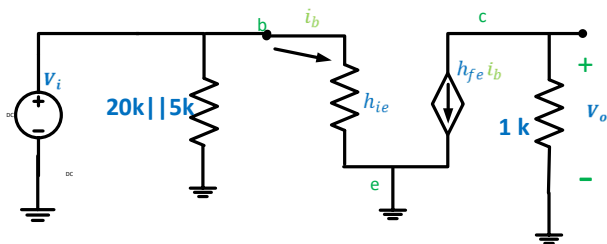

Common emitter amplifier with R_L :

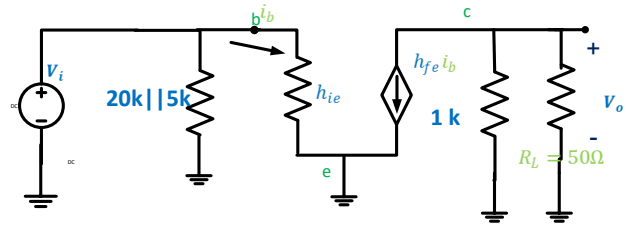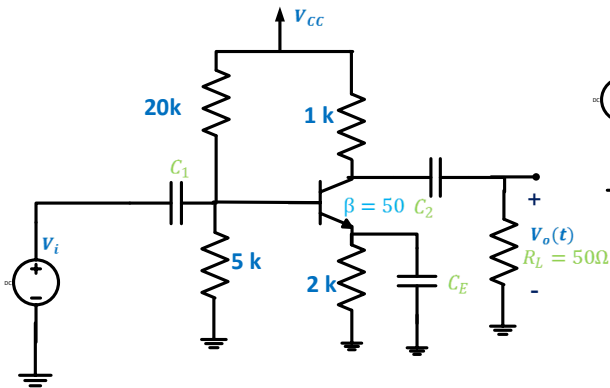

$$A_v = \frac{V_o}{V_{in}} = -6.67$$

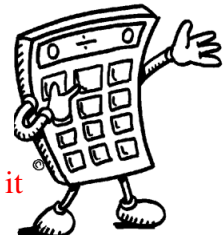

Do it


Ac small signal equivalent circuit:

Multistage amplifier:



Find the voltage gain

$$h_{ie1} = 1k, h_{ie2} = 2.24k, h_{fe1} = 140, h_{fe2} = 100$$

Ac small signal equivalent circuit:

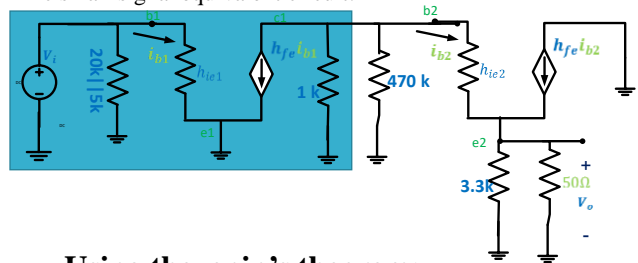


Using thevenin's theorem:

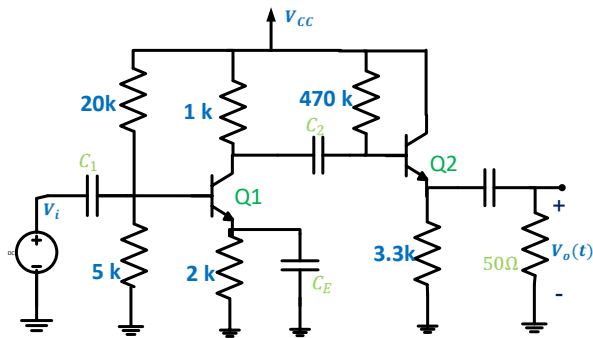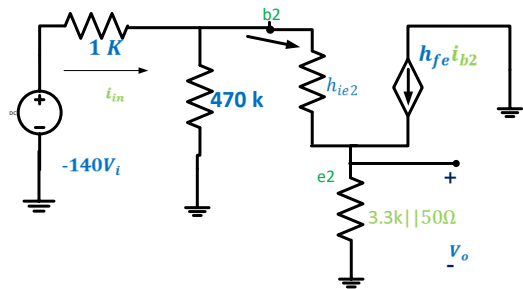

$$V_o = (3.3k \parallel 50\Omega)(1 + h_{fe2})i_{b2}$$

$$i_{b2} = i_{in} * \frac{470k}{470k + h_{ie2} + (3.3k \parallel 50\Omega)(1 + h_{fe2})}$$
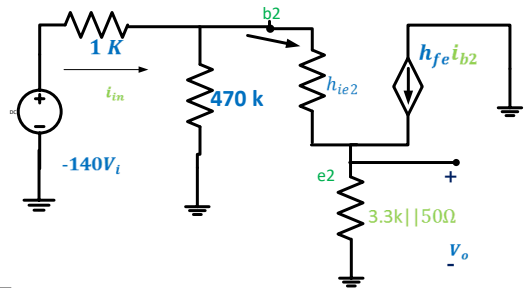
$$i_{in} = \frac{-140v_{in}}{1k + 470k \parallel [h_{ie2} + (3.3k \parallel 50\Omega)(1 + h_{fe2})]}$$



$$\rightarrow A_v = \frac{V_o}{V_{in}} = -85$$

The common emitter amplifier design:


Design a common emitter amplifier using a transistor having

$$\beta(\min) = 480, \quad \beta(\max) = 1500$$

To provide a voltage gain $\left| \frac{V_o}{V_s} \right| \geq 200$, between a small signal voltage source having a resistance 500Ω and load $R_L = 5k$

Its specified that $Z_{in} \geq 5k$

Solution :

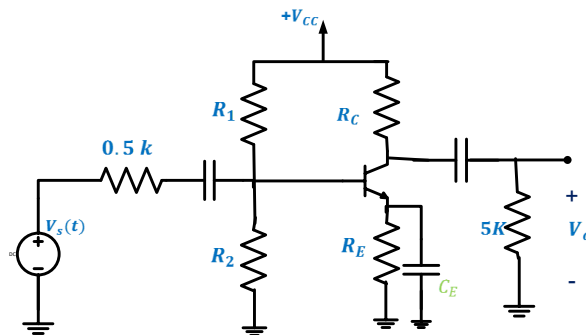

Solution:

Ac small signal equivalent circuit:

$$V_o = -(R_C \parallel R_L) h_{fe} i_b$$

$$i_b = \frac{V_i}{h_{ie}}$$



$$V_i = \frac{Z_i}{Z_i + R_s} V_s$$

$$\ast |A_v| = \frac{h_{fe}}{h_{ie}} \frac{Z_i}{Z_i + R_s} (R_C \parallel R_L)$$

$$1 > \frac{Z_i}{Z_i + R_s} > 0.9$$

$$\ast |A_v| = \frac{h_{fe}}{h_{ie}} (0.9) (R_C \parallel 5k)$$
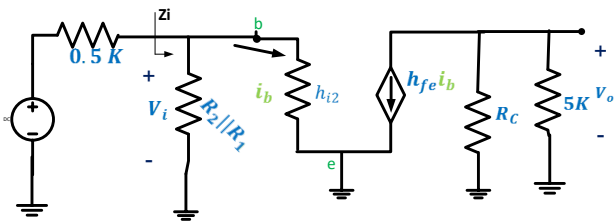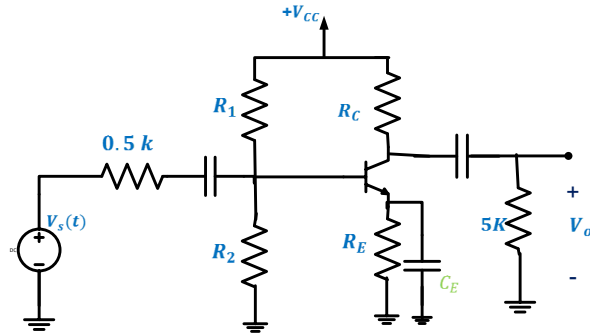
$$\text{Let } g_m = \frac{h_{fe}}{h_{ie}} = 38.92 I_{CQ}$$



$$\ast |A_v| = (g_m)(0.9)(R_C \parallel 5k) \geq 200$$

$$\text{Let } R_C = 8k, \text{ then: } g_m \geq 72.2$$

$$\text{Let } g_m = 77.86, \text{ then } I_{CQ} = 2mA$$

$$\text{Since } V_{RC} = 16v; \text{ let } V_{CC} = 30v$$

$$\text{Let } V_{RE} = \frac{V_{CC}}{5} = 6v$$

$$R_E = \frac{V_{RE}}{I_E} = 3k\Omega$$

$$R_{th} = \frac{\beta(\min)R_E}{20} = 72k\Omega$$

$$\text{From: } I_E = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta+1} + R_E}$$

$$V_{th} = 7 \text{ volt}$$

$$V_{th} = \frac{R_2}{R_1 + R_2} V_{CC}$$


$$R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\text{➤ } R_1 = 93.9k$$

$$\text{➤ } R_2 = 308.6k$$

Example :


Find voltage gain

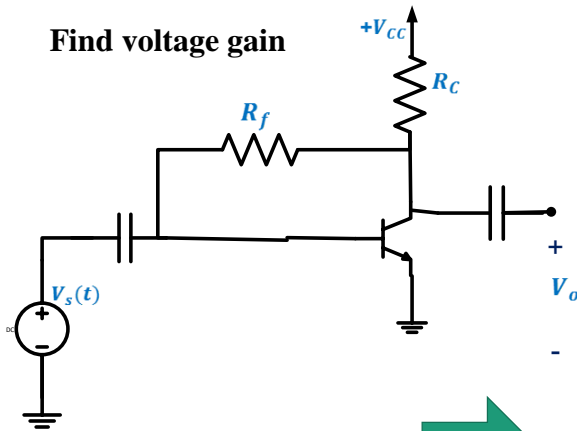


$$V_o = -R_C i_o$$

$$i_o = h_{fe} i_b + i_f$$

$$i_f = \frac{V_o - V_s}{R_f}$$

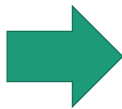

Ac small signal equivalent circuit:

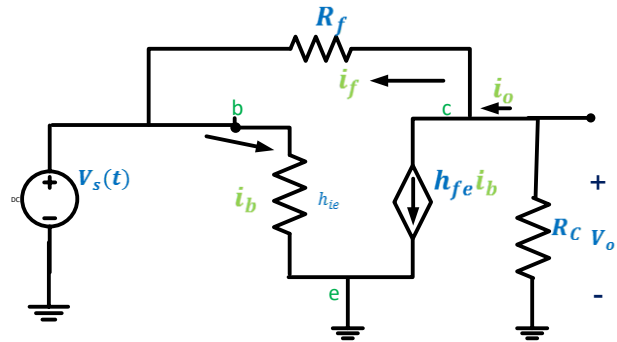

$$i_b = \frac{V_s}{h_{ie}}$$

$$A_v = -\frac{\frac{R_C}{R_E} - R_C \frac{h_{fe}}{h_{ie}}}{1 + \frac{R_C}{R_E}}$$

Early voltage V_A

$$\frac{1}{h_{oe}} = \frac{V_{CEQ} + V_A}{I_{CQ}}$$

$$\frac{1}{h_{oe}} \cong \frac{V_A}{I_{CQ}}$$

$$V_A = 100, 150, 200$$

**If V_A is given, we must include $\frac{1}{h_{oe}}$ in
Ac small signal equivalent circuit:**

