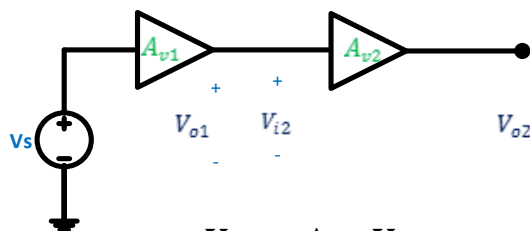


Multistage Amplifiers



- 1) Additional Amplification can be required .
- 2) Improving the performance of the amplifier (**high input impedance ,high gain , small output impedance**) .
- 3) Increasing the Bandwidth .

Multistage Amplifiers



$$V_{O2} = Av_2 V_{i2}$$


$$V_{i2} = V_{O1}$$

$$V_{O1} = Av_1 V_S$$

$$\frac{V_{O2}}{V_S} = Av_1 \cdot Av_2$$



Multistage Amplifiers

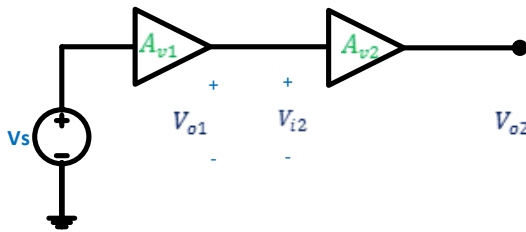

- ❖ When the output of one amplifier stage is connected to the input of another, the amplifier stages are said to be in **cascade**.
- ❖ $A_{v_T} = A_{v_1} \cdot A_{v_2} \cdot A_{v_3} \dots A_{v_n}$
 A_{v_1} , A_{v_2} , and A_{v_n} are the in-circuit gains.

Multistage Amplifiers

Methods of Coupling:

- Capacitor Coupling.
- Direct Coupling.
- Transformer Coupling.




Capacitor Coupled Multistage Amplifier

Advantages:



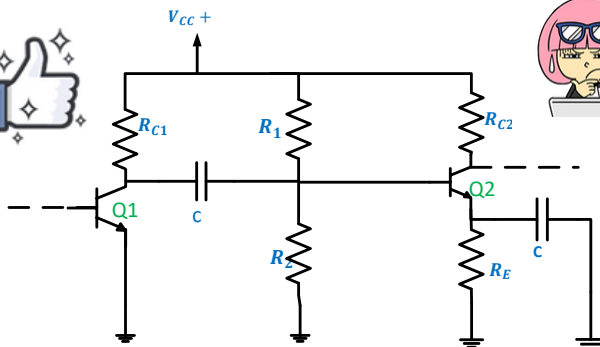- ❖ the coupling capacitor **blocks** the flow of **DC** current while it **permits** the flow of **Ac** signal between stages .




- ❖ It makes it possible to have a dc bias voltage at the output of one stage that is different from the dc bias voltage at the input to the next stage
- ❖ (stage isolation) .

Capacitor Coupled Multistage Amplifier

Disadvantages:



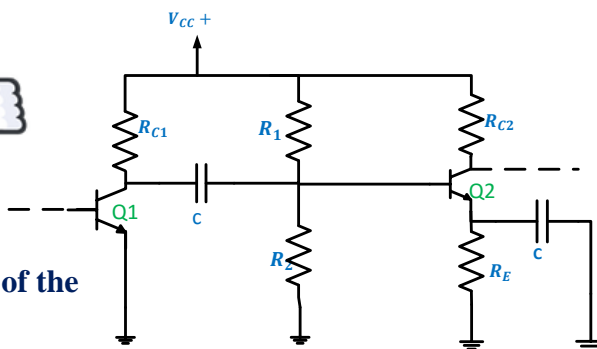
- ❖ It effects the low – frequency response of the amplifier .



- ❖ It **not** used in integrated circuit , because it is difficult and uneconomical to fabricate capacitors on a chip .

Capacitor Coupled Multistage Amplifier

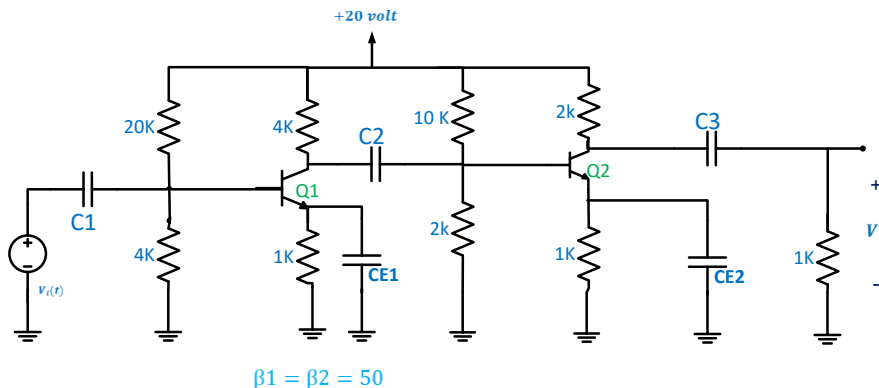Example: find the gain of the multistage amplifier




Capacitor Coupled Multistage Amplifier

Solution:



DC Analysis:

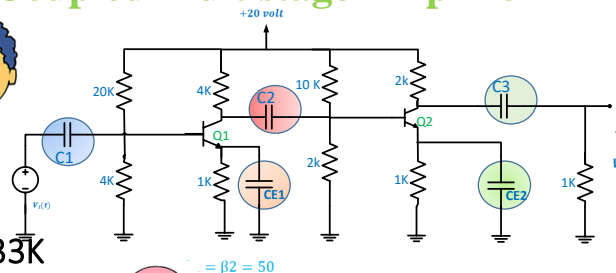

$$R_{TH1} = 4K \parallel 20K = 3.33K$$

$$V_{TH1} = \frac{4K}{4K + 20K} (20) = 3.33v$$


$$I_{E1} = 2.47 \text{ mA} \quad \therefore h_{ie1} = 0.51K$$

Open Circuit!

$$R_{TH2} = 2K \parallel 10K = 1.67 K$$


$$V_{TH2} = \frac{2K}{2K + 10K} (20) = 3.33v$$
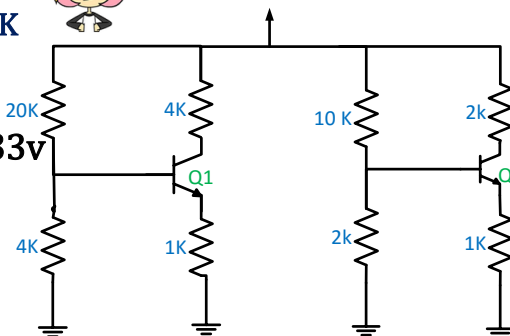
$$I_{E2} = 2.55 \text{ mA} \quad \therefore h_{ie2} \approx 0.51K$$



Capacitor Coupled Multistage Amplifier



Ac small signal equivalent circuit

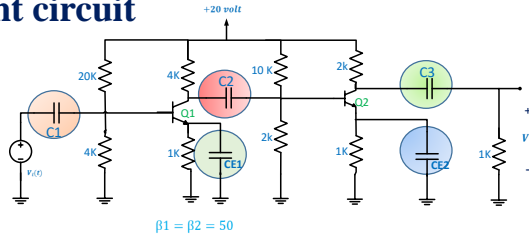

Short Circuit


Capacitor Coupled Multistage Amplifier

Ac small signal equivalent circuit

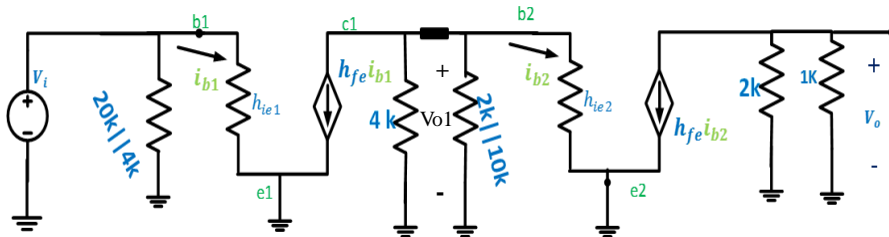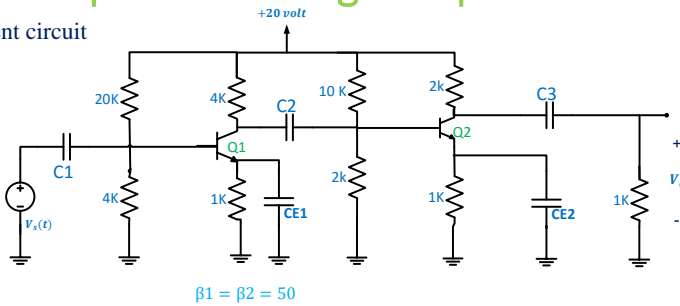

Capacitor Coupled Multistage Amplifier

$$Av_T = Av_1 \cdot Av_2$$

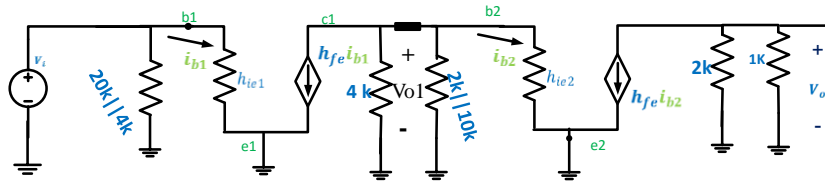

- $Av_1 = \frac{V_{O1}}{V_i}$

$$V_{O1} = -h_{fe1} i_{b1} (4k || 2k || 10k || h_{ie2})$$

$$i_{b1} = \frac{V_i}{h_{ie1}}$$

- $Av_1 = -34.14$

- $Av_2 = \frac{V_{O2}}{V_{i2}} = \frac{V_{O2}}{V_{O1}} = \frac{V_O}{V_{O1}}$

$$V_{O2} = -h_{fe2} i_{b2} (1k || 2k)$$

$$i_{b2} = \frac{V_{O1}}{h_{ie2}}$$

- $Av_2 = -66.66$


$$Av_T = Av_1 \cdot Av_2$$

- ❖ $Av_T = 2342$

2) Direct – coupled multistage Amplifier

2) Direct – coupled multistage Amplifier

Advantages

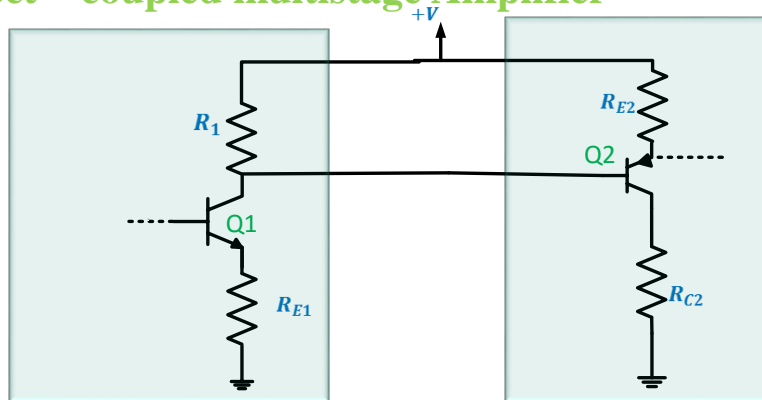


- ❖ Used in differential and operational amplifier .
- ❖ Used in low and high frequency applications .

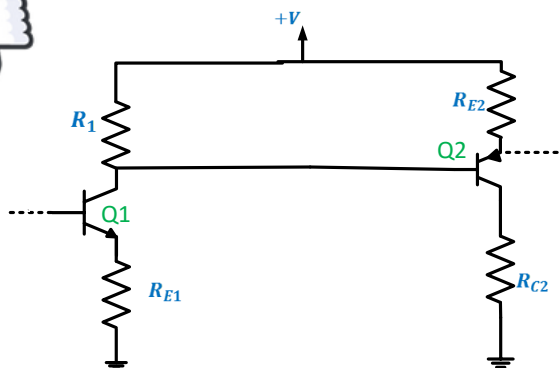2) Direct – coupled multistage Amplifier

Disadvantages



- ❖ Any change in the dc voltage at the output of one stage produce an identical change in dc voltage at the input to the next stage



- We must use R_E .
- We must use alternating transistor types (npn, pnp) .

2) Direct – coupled multistage Amplifier

Darlington compound configuration

DC Analysis :




$$V_{cc} = R_B I_{B1} + V_{BE1} + V_{BE2} + R_E I_{E2}$$

$$I_{E2} = (\beta_2 + 1) I_{B2}$$

$$I_{B2} = I_{E1}$$



$$I_{E1} = (\beta_1 + 1) I_{B1}$$
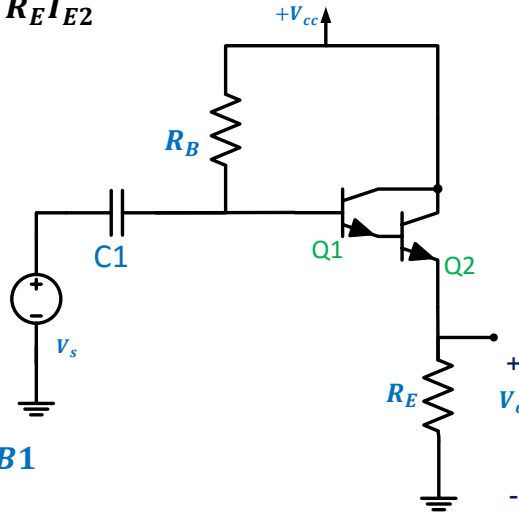
$$\therefore I_{E2} = (\beta_2 + 1) (\beta_1 + 1) I_{B1}$$



Darlington compound configuration

Ac small signal equivalent circuit

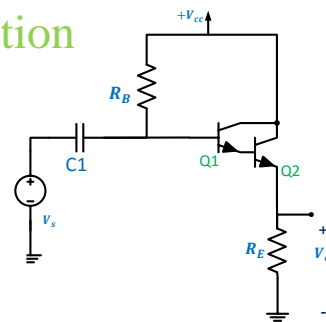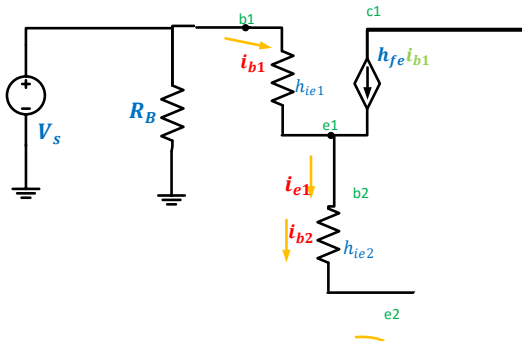

2) Direct – coupled multistage Amplifier

Darlington compound configuration

$$A_i = \frac{i_o}{i_{b1}} = \frac{i_{e2}}{i_{b1}}$$

$$i_{e2} = (1+h_{fe2}) i_{b2}$$

$$i_{b2} = i_{e1}$$


$$i_{e1} = (1+h_{fe1}) i_{b1}$$

$$A_i = \frac{i_o}{i_{b1}} = (1+h_{fe2}) (1+h_{fe1})$$

$$A_v = \frac{V_o}{V_s}$$


$$V_o = R_E i_o$$
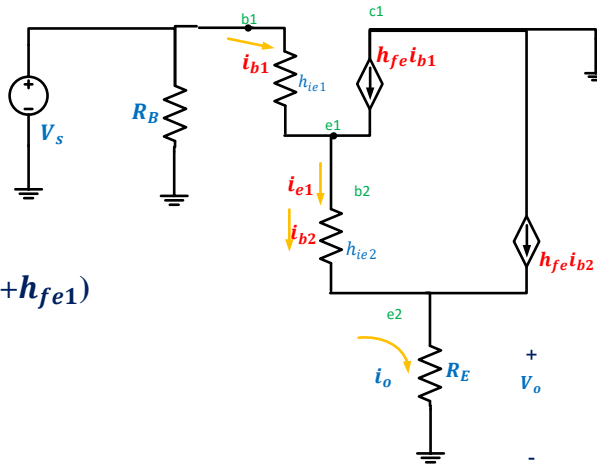
$$i_o = (1 + h_{fe2}) (1 + h_{fe1}) i_{b1}$$




Darlington compound configuration

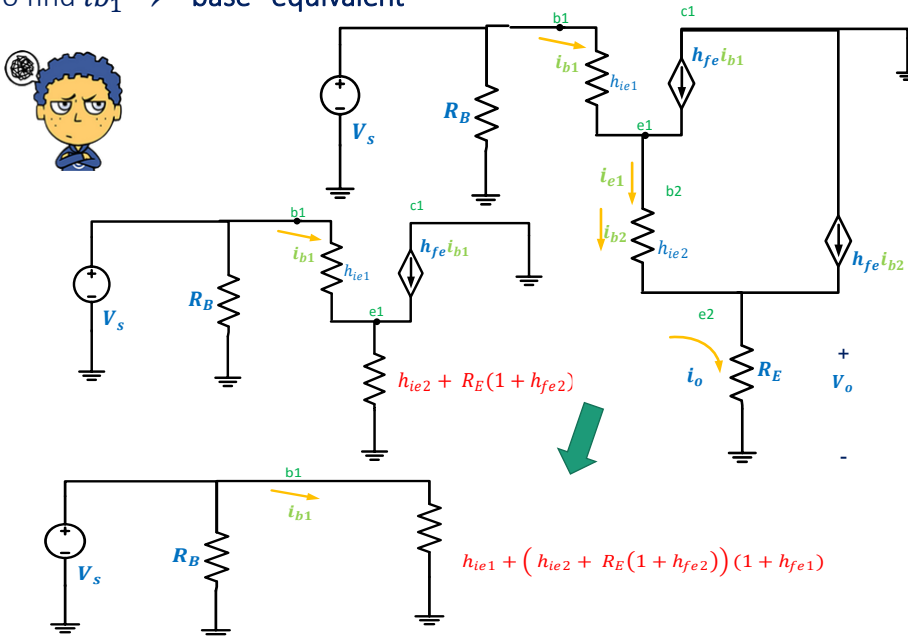To find $i_{b1} \rightarrow$ base equivalent




2) Direct – coupled multistage Amplifier

Darlington compound configuration

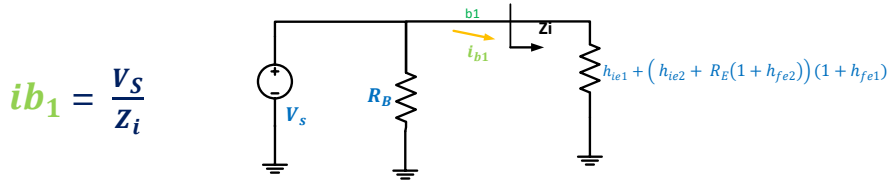
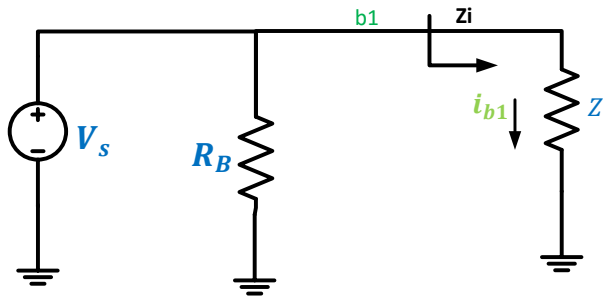
$$Z_i = h_{ie1} + (h_{ie2} + R_E (1 + h_{fe2})) (1 + h_{fe1})$$




Darlington compound configuration

$$A_v = \frac{R_E (1 + h_{fe2}) (1 + h_{fe1})}{h_{ie1} + (R_E (1 + h_{fe2}) + h_{ie2}) (1 + h_{fe1})} < 1$$

To find Z_O , set $V_S = 0$

$$Z_O = \left(\frac{h_{ie1} + h_{ie2}}{1 + h_{fe1}} \right) || R_E$$

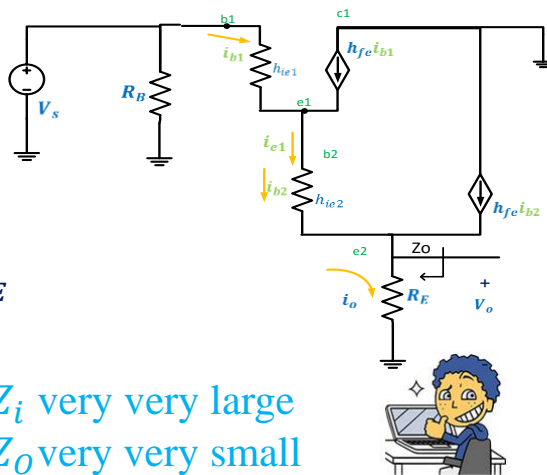

$$\therefore A_i > 1$$

$$A_v < 1$$


Z_i very very large
 Z_O very very small
 modified buffer



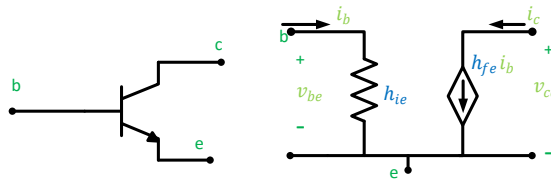
2) Direct – coupled multistage Amplifier

Darlington compound configuration

Ac small signal equivalent circuit of the BJT



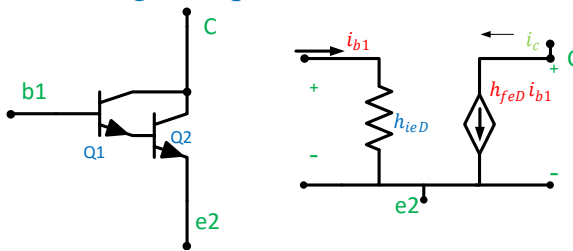Ac small signal equivalent circuit of the Darlington



Darlington compound configuration

$$h_{ieD} = 2 h_{ie1}$$

$$h_{feD} = h_{fe1} \cdot h_{fe2}$$

$$h_{feD} = \frac{i_c}{i_{b1}}$$

$$h_{ieD} = Z_i \text{ with } R_E = 0$$

2) Direct – coupled multistage Amplifier

Darlington compound configuration

$$h_{feD} = \frac{i_c}{i_{b1}}$$

$$i_c = i_{c1} + i_{c2}$$

$$i_c = h_{fe1} i_{b1} + h_{fe2} i_{b2}$$



$$i_c = h_{fe1} i_{b1} + h_{fe2} i_{e1}$$

$$i_c = h_{fe1} i_{b1} + h_{fe2} (1 + h_{fe1}) i_{b1}$$

$$i_c = (h_{fe1} + h_{fe2} + h_{fe2} h_{fe1}) i_{b1}$$

$$h_{feD} = h_{fe1} + h_{fe2} + h_{fe2} h_{fe1}$$

$$h_{feD} \approx h_{fe2} h_{fe1}$$

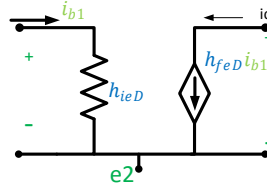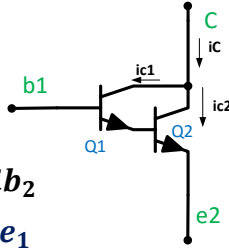

Darlington compound configuration

$$h_{ieD} = Z_i \Big|_{R_E=0}$$



$$Z_i = h_{ie1} + (R_E (1 + h_{fe2}) + h_{ie2})(1 + h_{fe1})$$


$$\therefore h_{ieD} = h_{ie1} + (1 + h_{fe1}) h_{ie2}$$

$$= h_{ie1} + (1 + h_{fe1}) \frac{(1 + h_{fe2}) V_T}{I_{E2}}$$

$$= h_{ie1} + (1 + h_{fe1}) \frac{(1 + h_{fe2}) V_T}{(1 + h_{fe2}) I_{E1}}$$

2) Direct – coupled multistage Amplifier

Darlington compound configuration

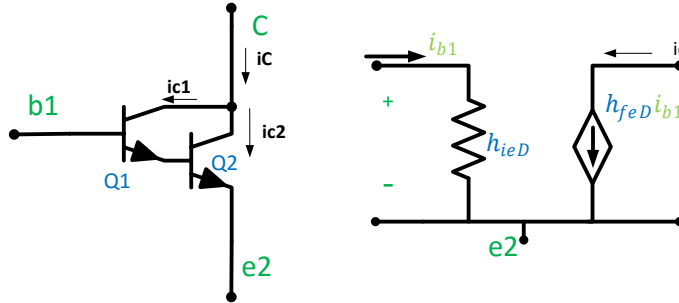

$$\therefore h_{ieD} = h_{ie1} + \frac{(1+h_{fe1})V_T}{I_{E1}}$$


$$h_{ieD} = h_{ie1} + h_{ie1}$$

$$= 2h_{ie1}$$



Cascode Amplifier


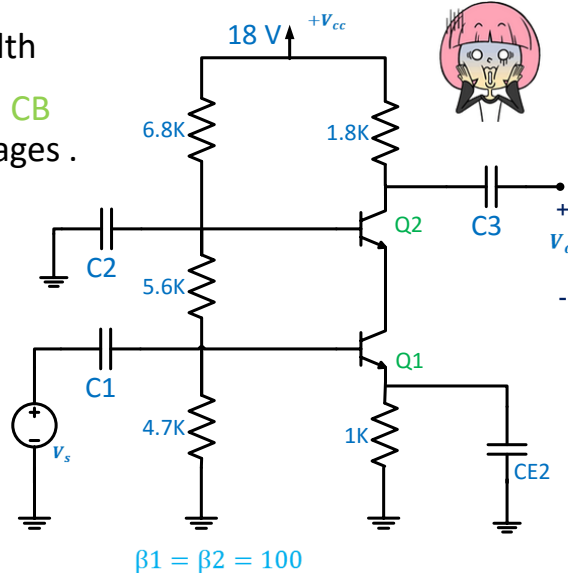
- ◆ Used to amplify video signal
- ◆ It has a wide bandwidth
- ◆ It consists of a CE and CB stages .



2) Direct – coupled multistage Amplifier

Cascode Amplifier

DC Analysis :

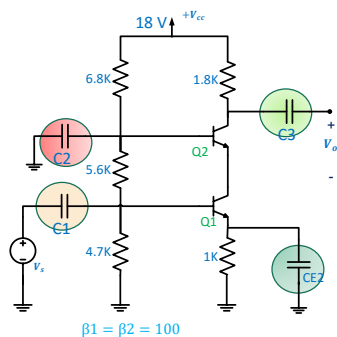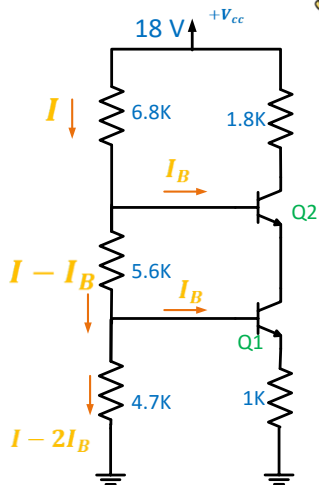

$\beta_1 = \beta_2 = 100$

Open Circuit!



$$I_{C1} = I_{E2} \approx I_{C2}$$

Since $\beta_1 = \beta_2$

$$I_{B1} = I_{B2} = I_B$$

Cascode Amplifier

DC Analysis :

$$I_{C1} = I_{E2} = I_{C2}$$


And since $\beta_1 = \beta_2$

$$I_{B1} = I_{B2} = I_B$$

$$18 = 6.8k I + 5.6k(I - I_B) + 4.7k(I - 2I_B)$$

$$18 = 6.8k I + 5.6k(I - I_B) + V_{BE1} + 1k I_{E1}$$

Solving for $I_E = 4mA$

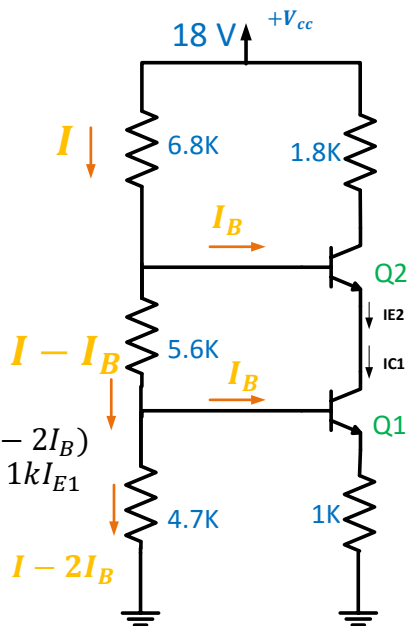

2) Direct – coupled multistage Amplifier

Cascode Amplifier


Ac small signal analysis

$$V_O = -h_{fb} i_{e2} (1.8K)$$


$$i_{e2} = h_{fe1} i_{b1}$$

$$i_{b1} = \frac{V_S}{h_{ie1}}$$

$$\therefore A_v = -294$$

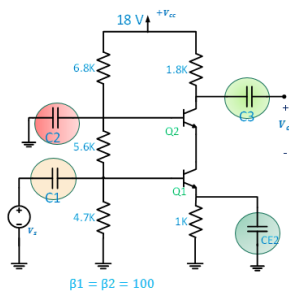

Short Circuit!

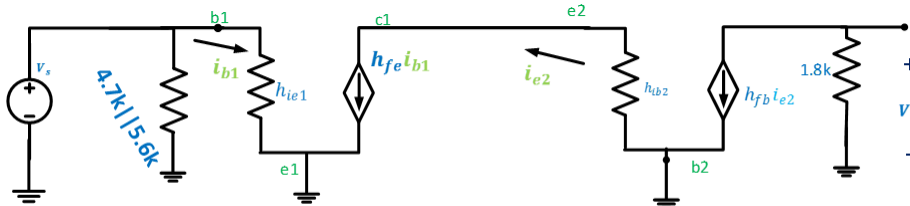


Transformer coupled multistage amplifier

3) Transformer coupled multistage amplifier

$h_{fe} = 50$

$\frac{1}{h_{oe}} = 50k$

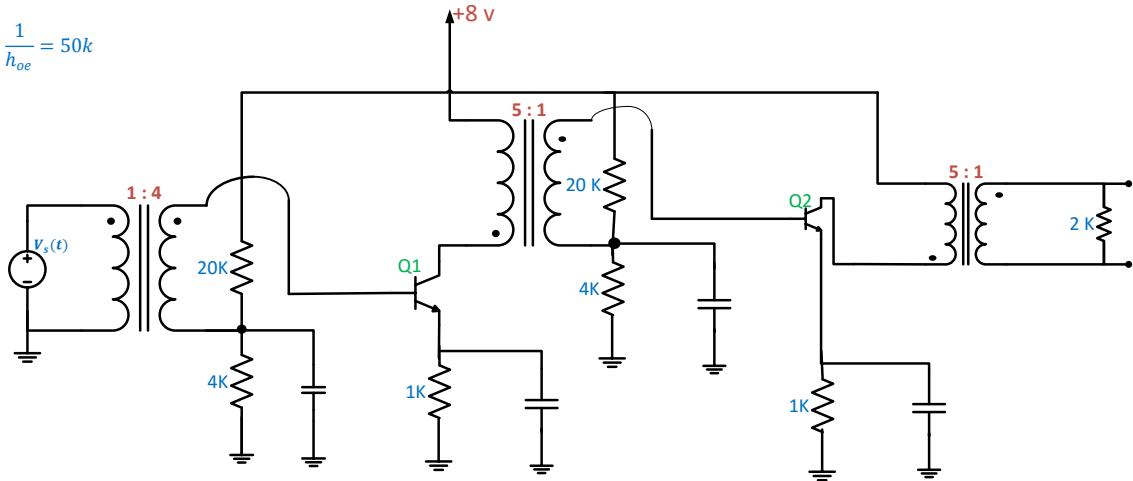

3) Transformer coupled multistage amplifier

Advantages:




- 1) The coupling transformer is used to pass the ac signal from one stage to the next, while blocking the DC voltages.
- 2) DC isolation.
- 3) matching for maximum power transfer.
- 4) low dc power dissipation ($R_C = 0$).

Disadvantages



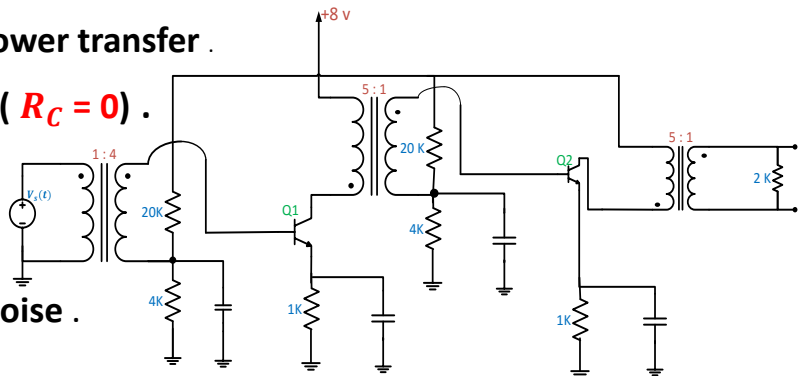
- 1) cost, weight, size, and noise.
- 2) poor frequency response.



Transformer coupled multistage amplifier

3) Transformer coupled multistage amplifier

DC Analysis:

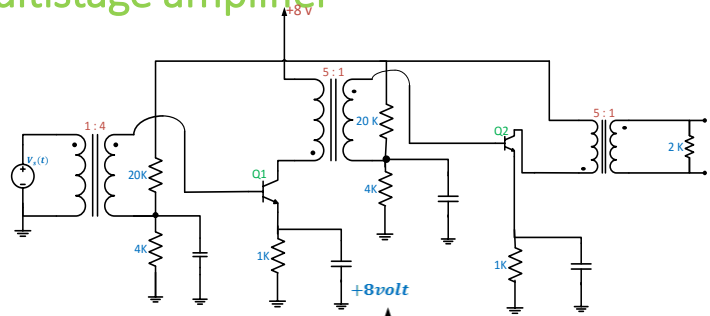


$$R_{TH1} = R_{TH2} = 4K \parallel 20K = 3.33K$$

$$V_{TH1} = V_{TH2} = \frac{4K}{4K + 20K} (+8) = 1.33V$$



$$I_{E1} = I_{E2} = \frac{4K}{\frac{R_{TH}}{\beta + 1} + 1K} = 0.595\text{ mA}$$

$$\therefore h_{ie1} = h_{ie2} = 2K$$

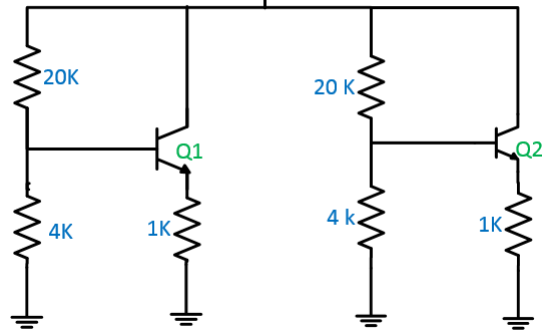

3) Transformer coupled multistage amplifier


Ac small signal equivalent circuit

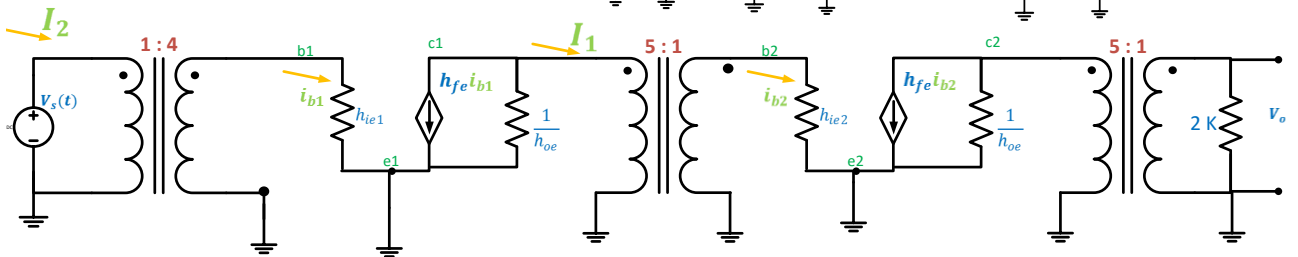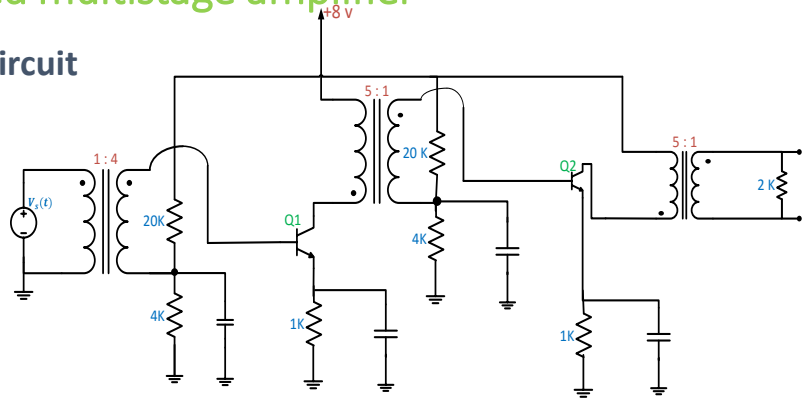

Transformer coupled multistage amplifier

3) Transformer coupled multistage amplifier


Transformation

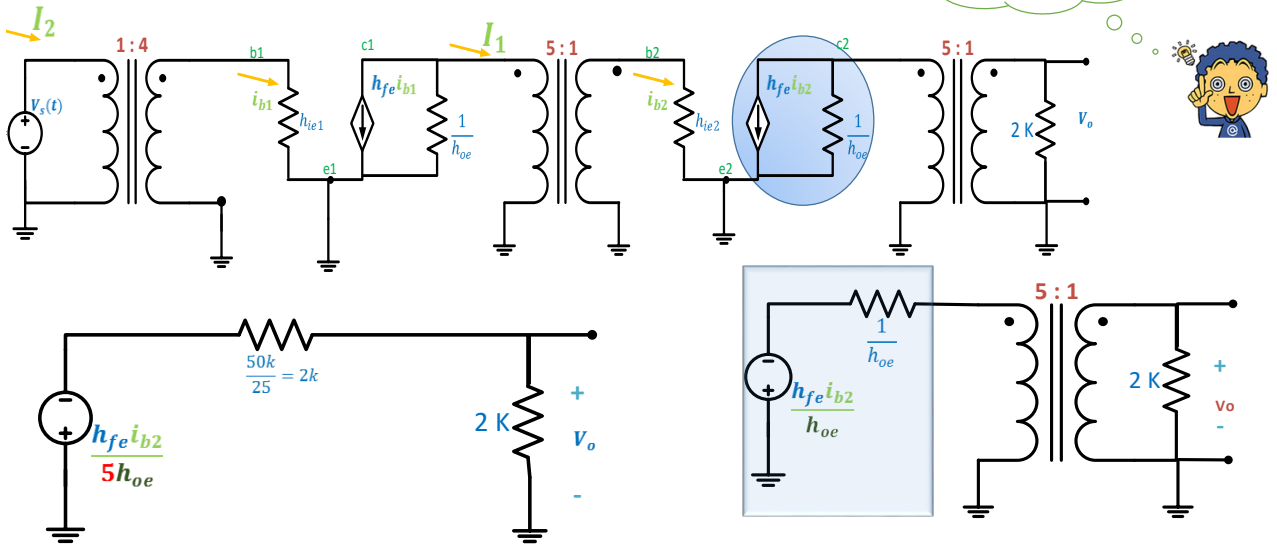

$$V_o = - \frac{2K}{2K+2K} \frac{hfe ib_2}{5h_{oe}}$$


3) Transformer coupled multistage amplifier

To find ib_2

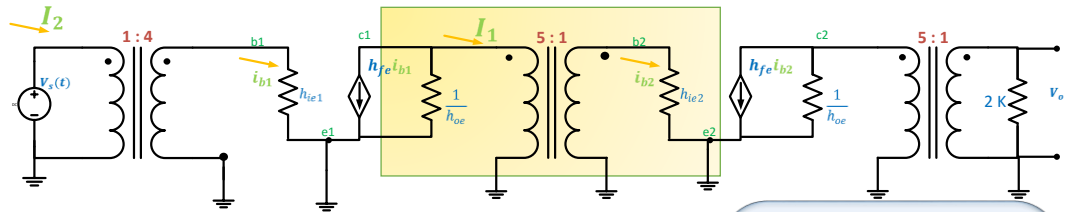

$$ib_2 = 5I_1$$

To find I_1

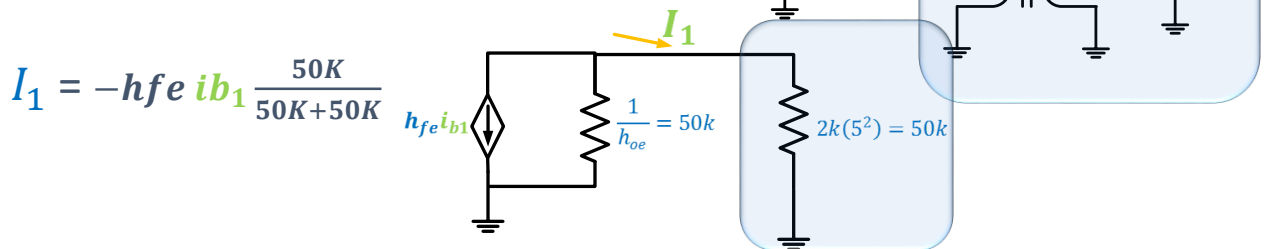


$$I_1 = -hfe ib_1 \frac{50K}{50K+50K}$$

Transformer coupled multistage amplifier

3) Transformer coupled multistage amplifier

To find i_{b1}

$$i_{b1} = +\frac{1}{4} I_2$$

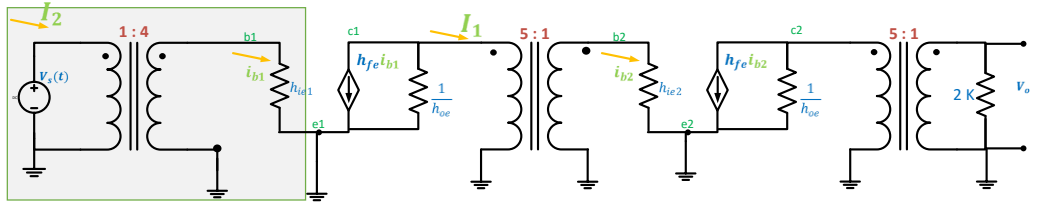

To find I_2

$$I_2 = \frac{V_S}{\frac{h_{ie1}}{16}}$$

$$\therefore A_v = \frac{V_0}{V_S} = +62.5$$

