

Experiment 3
Network analysis 1
The superposition principle and Kirchhoff's rules

Student's name:

Student's No.:

Partner's name:

Partners No.:

Section:

Instructor:

Date:

Abstract:

Theory:

Calculations:

- 1) Using Kirchhoff's rules find the values of the currents passing through the three carbon resistors.
- 2) Using superposition principle, find the value of the current passing through R_3 when each source acting alone.

Data:

(a) Measure the current passing through the three carbon resistors:

$$I_1(\text{K-exp}) =$$

$$I_2(\text{K-exp}) =$$

$$I_3(\text{K-exp}) =$$

(b) Measure the current passing through R_1 :

-when ε_1 acting alone: $I_{11} =$

- when ε_2 acting alone: $I_{12} =$
 $I_1(\text{spp-exp}) =$

(c) Measure the current passing through R_2 :

-when ε_1 acting alone: $I_{21} =$

- when ε_2 acting alone: $I_{22} =$
 $I_2(\text{spp-exp}) =$

(d) Measure the current passing through R_3 :

-when ε_1 acting alone: $I_{31} =$

- when ε_2 acting alone: $I_{32} =$
 $I_3(\text{spp-exp}) =$

Results and conclusion: