

Experiment2
**Source internal resistance, loading problems
and circuit impedance matching**

Student's name:
Student's No.:

Partner's name:
Partners No.:

Section:

Instructor:

Date:

Abstract:

Theory:

Results and conclusion:

Preliminary Laboratory Questions

1. Show that the power P developed across a resistance R is $P=I^2R$, where I is the current flowing across the resistance.
2. Define the emf of a voltage source.
3. Define the internal resistance of a voltage source.
4. What is meant by, "loaded source"?
5. For the circuit you use in the experiment find an expression for the power developed across the load resistance.
6. If you vary the load resistance, when the power developed across the load resistance is maximum?