

# linear and non linear circuit components

• Components used :-


↳ Carbon resistance, light bulb and a diode

Components are

• linear components (Carbon resistance)

- The slope of the line


$$= \frac{1}{R}$$

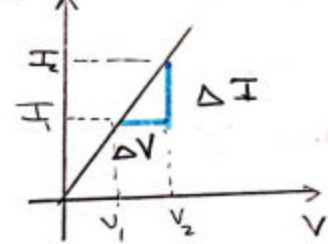

• non-linear components (light bulb, diode)


Diode: \*  $I = I_0 (e^{V/K} - 1)$

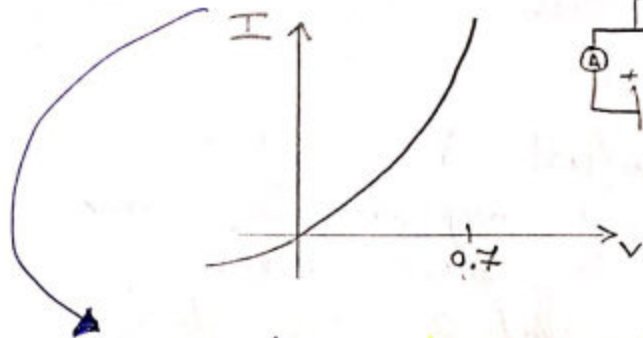For the light bulb \*  $R = R_0 [1 + \alpha(T - T_0)]$




light bulb: \*

low current

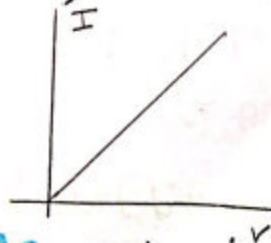

high current

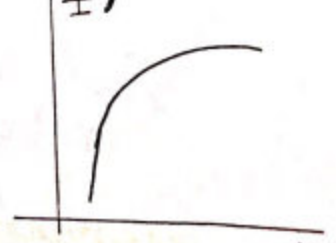

**Note** • A semi conducting consists of two pieces: a p-type piece and a n-type piece

→ p-type with battery = forward biased

→ n-type with battery = reverse biased

• What we used :-


- A decade box Resistance (مقاومة متغيرة / صندوق المقاومات)
- A voltage source
- An element (Carbon Resistance, light bulb, Si diode)
- Ammeter & Voltmeter

• Procedure :-

1- element 1 (Carbon Resistance)

• keep changing

The value of R

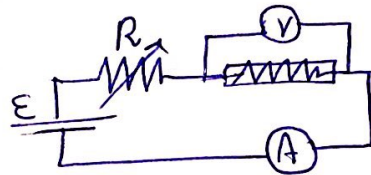

to adjust V to (0.2, 0.4, ...) and measure I then draw I vs V.

2- element 2 (Si diode)

• same as Resistance carbon

And draw I vs V (V (0.4 — 0.7))

3- element 3 (light bulb)

• same but this time we need to measure high and low currents so voltage Range will be (0.01 — 3) Volts

1- العنصر الأول (المقاومة الكربونية)

قم بتغيير قيم المقاومة المتغيرة حتى تصبح V تساوي

(0.2, 0.4, ... 2) V

و قم بقياس I عند كل قيمة

V ↓

ثم قم برسم I vs V

2- العنصر الثاني (الثنائي)

نفس الخطوات التي قمنا بها مع المقاومة الكربونية

ثم رسم I vs V

3- العنصر الثالث (الصباح)

نفس الخطوات السابقة لكن نحتاج إلى قياس تيار عالي ومنخفض

لذلك يكون مدى الجهد (0.01 — 3) Volts