

Experiment 4: Network Analysis II


The Thevenin and Norton Techniques

Thevenin: "any network of resistors and supplies having two output terminals and supplies having two output terminals can be replaced by a series combination of E_{eq} & R_{eq} By three steps:- **starting by R_3** "

Step 1:- you consider that E_1, E_2 does not exist:-

$$R_{eq} = R_1 + R_2$$


$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

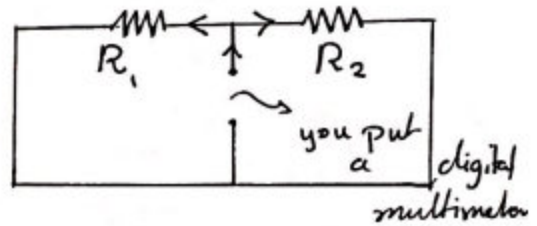

Step 2:- you consider that E_1, E_2 exist


$$E_{eq} = E_1 - I R_1 \quad \text{--- ①}$$
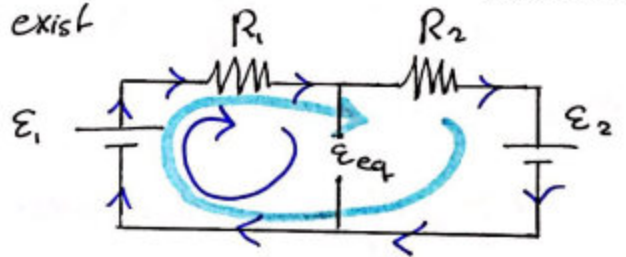
$$\text{you find } I \quad \text{--- ②}$$



Step 3:- you find I_{eq3}
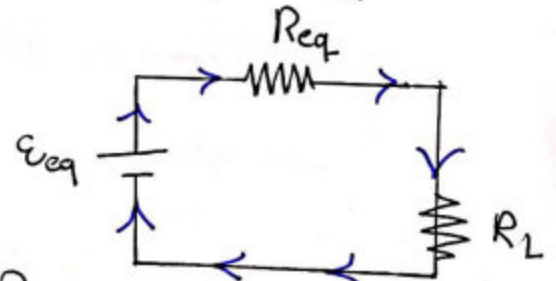
$$I_{eq3} = \frac{E_{eq}}{R_{eq} + R_L}$$




You do the same for R_1 and R_2 and you find I_{eq1} and I_{eq2}

2- **Norton's** for R_3

Step 1:- The same

$$\begin{aligned} \text{Step 2:- } I_{eq3} &= I_1 + I_2 \\ &= \frac{E_1}{R_1} + \frac{E_2}{R_2} \end{aligned}$$


Step 3: get rid of E_1, E_2

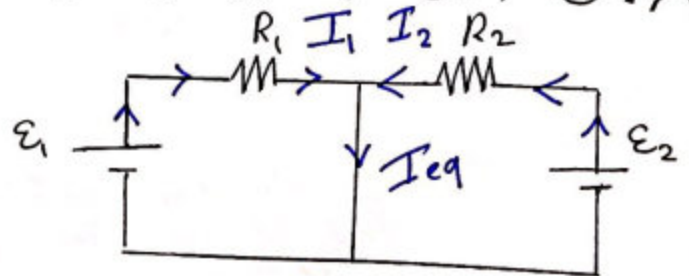

• you replace R_1, R_2 with R_{eq3}

• $I_{L3} R_3 = (I_{eq3} - I_{L3}) R_{eq3}$

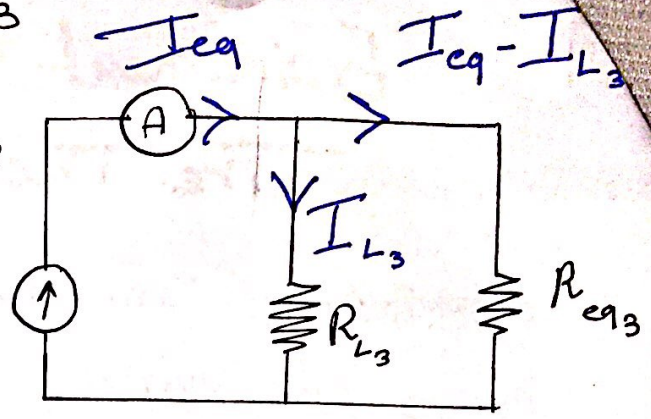• على مبدأ تساوي الجهد عند التوصل على التوازي




$$I_{L3} (R_3) = I_{eq3} R_{eq3} - I_{L3} R_{eq3}$$

$$I_{L3} (R_3 + R_{eq3}) = I_{eq3} R_{eq3}$$



you have it you have it you have it
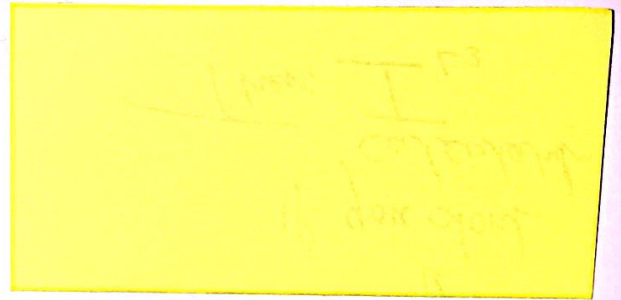
$$I_{L3} = \frac{I_{eq3} R_{eq3}}{R_3 + R_{eq3}}$$



Difference between

Theremin & Norton

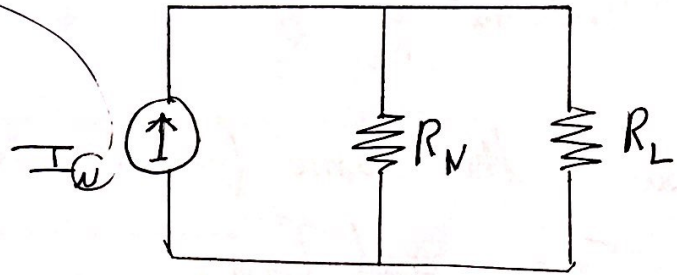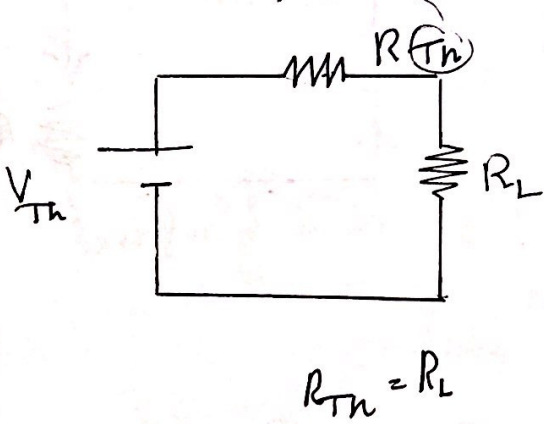

- what we use
 - 2 voltage sources
 - 3 carbon Resistances
 - Circuit board
 - digital Multimeter

• DMM, digital Multimeter

• Procedure


Theremin :-

There are 3 currents to measure each one we have 3 steps:- let's say we want to measure I_3

Step 1:- Calculate R_{eq} :-

• first circuit :-

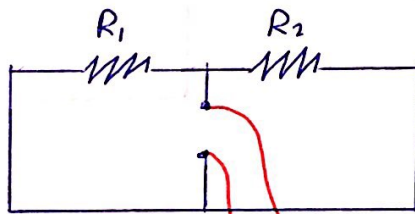- Take E_1 and E_2 off
- Put a DMM in the place of R_3



$$I_L = I_3$$


$$R_L = R_3$$

To a DMM to measure R_{eq3}

Step 2:- Calculate E_{eq} :-

• second circuit:-

- Take R_3 off and put E_1 and E_2 back

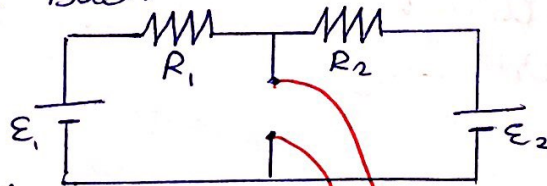


To a DMM to measure E_{eq3}

Step 3:-

• connect the circuit

$$R_L = R_3$$

R_{eq} = you get it from the box

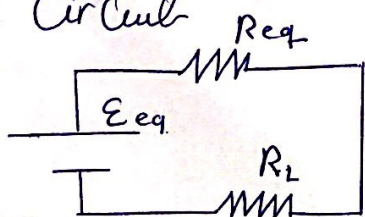


To measure I_{eq3}

E_{eq} = Power supply


Arabic notes:
 - في الخطوة الأولى :- تم إزالة E_2, E_1 و R_3 و تم إضافة R_3 و E_2, E_1 و R_3 في مكانها.
 - في الخطوة الثانية :- تم إضافة E_2, E_1 و R_3 في مكانها.

Norton :-

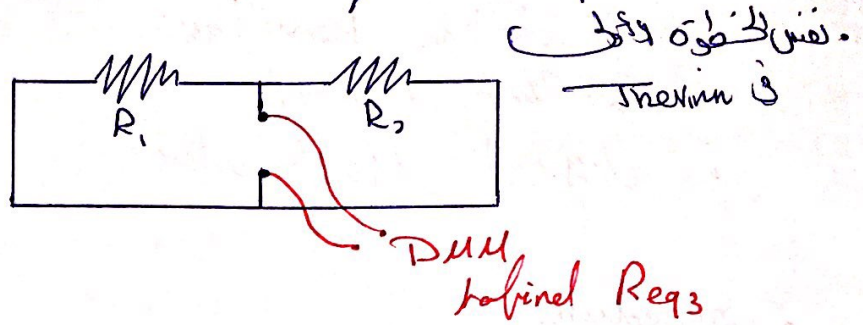Step 1 :- The same as Thevenin's first step



Step 2 :- measure I_{eq3} :- I_{eq3} us.

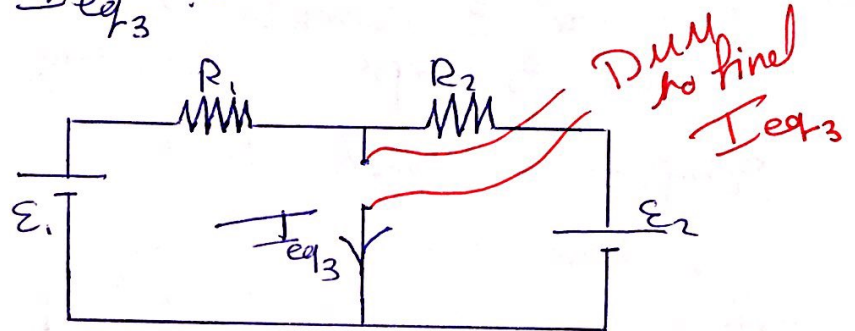

Step 3 :- Connect this circuit

