



① Ex: linear and non-linear Components.

→ Ohm's law: R indepⁿ on V and I .



$$R = \frac{V}{I}$$

① Carbon R :-



$$\text{error} = \frac{| \text{true} - \text{expl} |}{\text{true}} \times 100\%$$

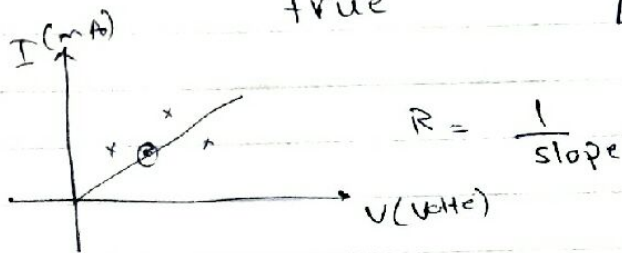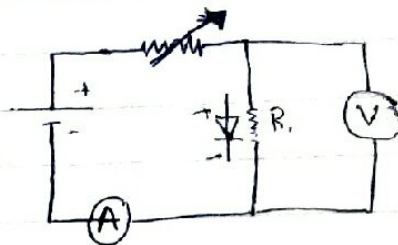

② Diode :-

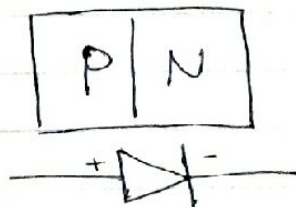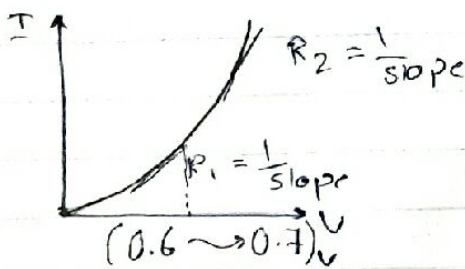

③ Light bulb

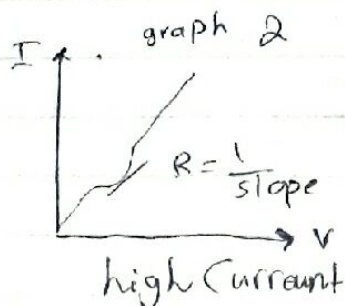
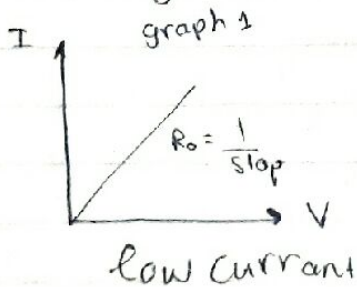


graph 2

$$R = \frac{R_0}{\text{graph 1}} \left[1 + \frac{\alpha}{4.5 \times 10^{-3}} (T - T_0) \right]$$

↳ 300 K

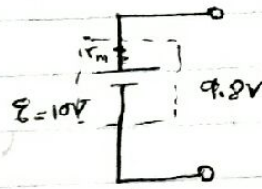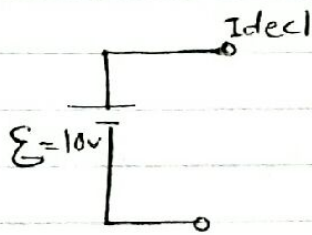Exp 2: Source Internal R, loading problem and Impedance matching.



$$I = \frac{\mathcal{E}}{(r_{in} + R_L)}$$

$$V_{R_L} = \frac{\mathcal{E}}{(r_{in} + R_L)} R_L$$


↳ ohm's law
 $V = IR$

• if $r_{in} \ll R_L \Rightarrow V_{R_L} \sim \mathcal{E}$

• if $r_{in} \approx R_L \Rightarrow V_{R_L} \sim \frac{\mathcal{E}}{2}$ "loading problem"

solve by adding

another resistance

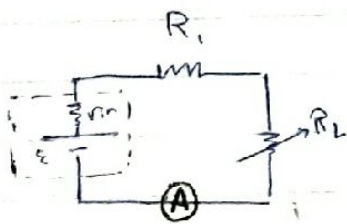


$$R_{in} = R_i + r_{in} \rightarrow 1k\Omega$$

$$I = \frac{\mathcal{E}}{(R_L + R_{in})}$$

$$\frac{1}{I} = \frac{R_L + R_{in}}{\mathcal{E}}$$

$$\frac{1}{I} = \frac{R_L}{\mathcal{E}} + \frac{R_{in}}{\mathcal{E}}$$


\downarrow \downarrow
 $y = mx + b$

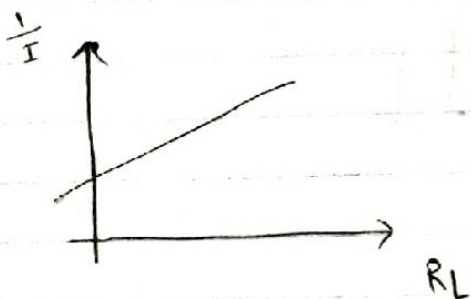

• slope = $\frac{1}{\mathcal{E}} \rightarrow 10V$

• y intercept = $\frac{R_{in}}{\mathcal{E}} \rightarrow 10k\Omega$
 $\mathcal{E} \rightarrow$ slope time

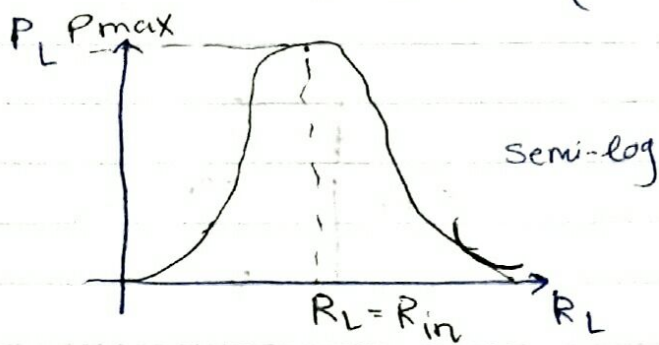- power (R_L) = $I V = I^2 R_L$
 $= \left(\frac{\mathcal{E}}{R_L + R_{in}} \right)^2 R_L$




$$P = \left(\frac{\mathcal{E}}{R_L + R_{in}} \right)^2 R_L \quad \text{. must be in conclusion.}$$

$$\frac{dP}{dR_L} = 0$$

power (maximum) when $\Rightarrow R_L = R_i + r_{in}$

- error $R_{in} = \frac{|R_{in th} - R_{in exp}|}{R_{in th}} \times 100\%$

Exp 3:

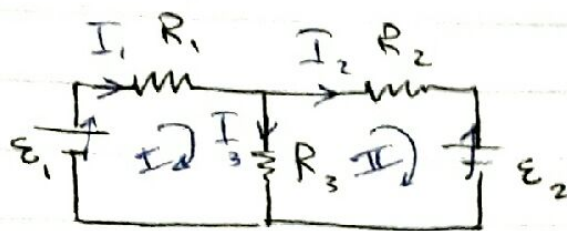

- $\epsilon_1 = 10 \text{ V}$
- $\epsilon_2 = 5 \text{ V}$
- $R_1 = 1 \text{ k}\Omega$, $R_2 = 2.2 \text{ k}\Omega$
- $R_3 = 5.1 \text{ k}\Omega$

Kirchoff's law

$$\sum_{\text{loop}} V = 0$$

$$\sum_{\text{node}} I = 0$$


(I): $\epsilon_1 - I_1 R_1 - I_3 R_3 = 0$ ——— ①

(II): $\epsilon_2 + I_2 R_2 - I_3 R_3 = 0$ ----- ②

(III) $I_1 = I_2 + I_3$ ——— ③

Super position:-

⇒ Kill ϵ_2

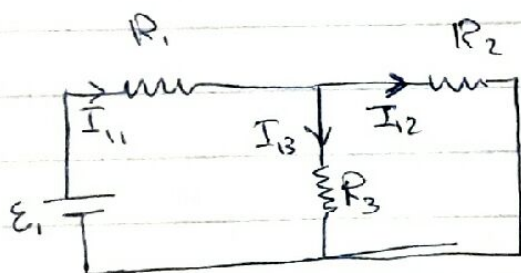


⊛ $I_{11} = \frac{\epsilon_1}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$

⊛ $I_{13} R_3 = I_{12} R_2$

⊛ $I_{11} = I_{13} + I_{12}$

$I_{12} = I_{11} - I_{13}$ ←

⇒ Kill ϵ_1

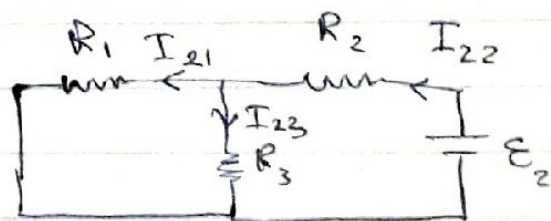

⊛ $I_{22} = \frac{\epsilon_2}{R_2 + \frac{R_1 R_3}{R_1 + R_3}}$


⊛ $I_{23} R_3 = I_{21} R_1$

⊛ $I_{22} = I_{23} + I_{21}$


⊛

AC


Sin wave

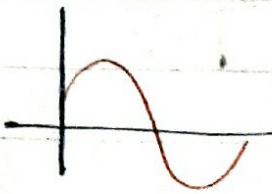


triangle wave

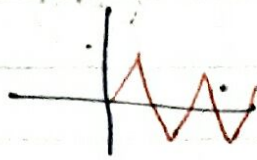

Square wave

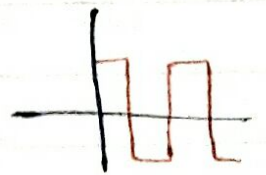

• Sin wave :-

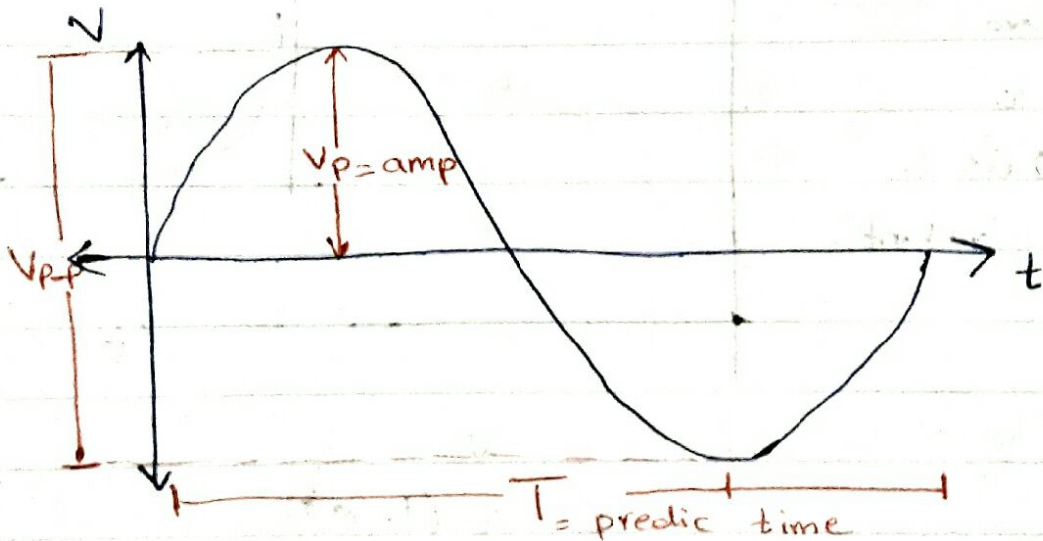


• Frequency = $\frac{1}{T}$

(1)

Ex 6: Capacitors and Inductors

PART A RC circuit:

$$\Rightarrow \mathcal{E} = V_R + V_C$$

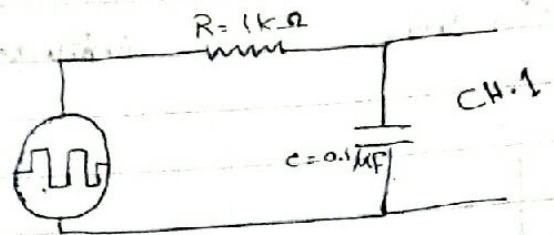

The Capacitor's while charging:-


$$\Rightarrow V_C(t) = \mathcal{E} (1 - e^{-t/RC})$$

• when $t = \text{zero} \Rightarrow \mathcal{E}(t) = \text{zero}$

• when $t = \infty \Rightarrow \mathcal{E}(t) = \mathcal{E}$

• when $t = RC \Rightarrow \mathcal{E}(t) = 0.63 \mathcal{E}$

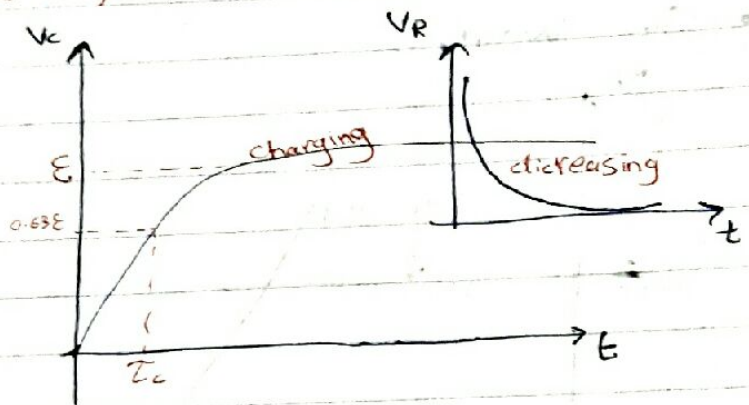$t = RC = \tau_c \Rightarrow$ "time constant"




$$\begin{aligned} \Rightarrow \text{when } t = RC = \tau_c \Rightarrow V_R &= \mathcal{E} - V_C \\ &= \mathcal{E} - \mathcal{E} (1 - e^{-t/RC}) \\ &= \mathcal{E} e^{-t/RC} \text{ Volte} \end{aligned}$$


The Capacitor's while discharging:-

$$\Rightarrow V_C = \mathcal{E} e^{-t/RC}$$

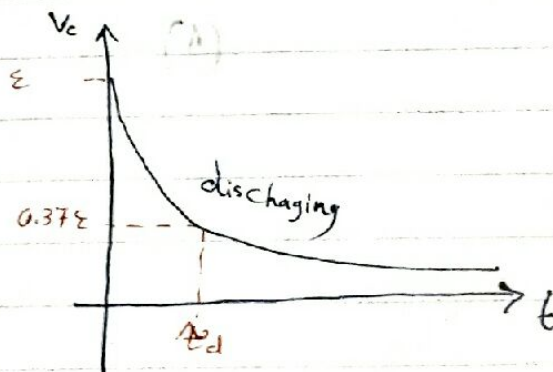• when $t = \tau_d \Rightarrow \mathcal{E}(t) = 0.37 \mathcal{E}$


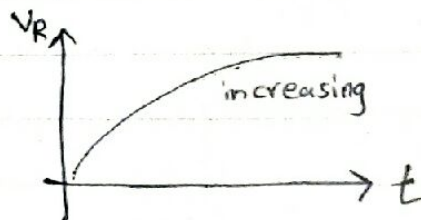
$$\Rightarrow \tau = \frac{\tau_d + \tau_c}{2}$$




(2)

PART C LC circuit.

$$\rightarrow \omega_0 = \frac{1}{\sqrt{LC}} = 2\pi f_0$$

angular frequency

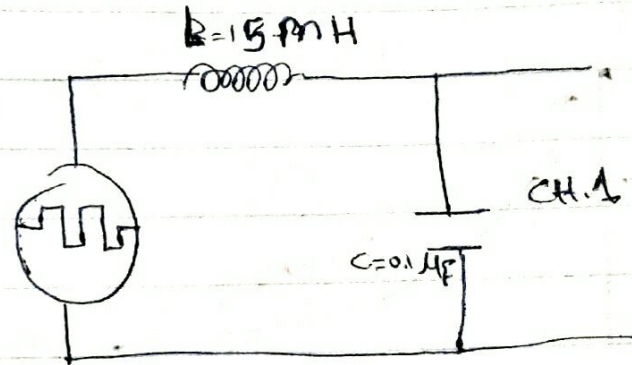

• $f_0 = \text{Resonance freq}$

• حساب f_0 علياً في الدارة لمجاورة نقوم بزيادة التردد
تسرياً مما يترتب عليه زيادة الجهد ثم يتوقف فجأة
ليعود للصفر دد هنا تكون قيمة f_0 .


(4)

Case (II): Critical damping :-

$$\left(\frac{R_c}{2L}\right)^2 = \frac{1}{LC}$$


• $\tau = \frac{\ln 2}{t/2}$ decay constant.

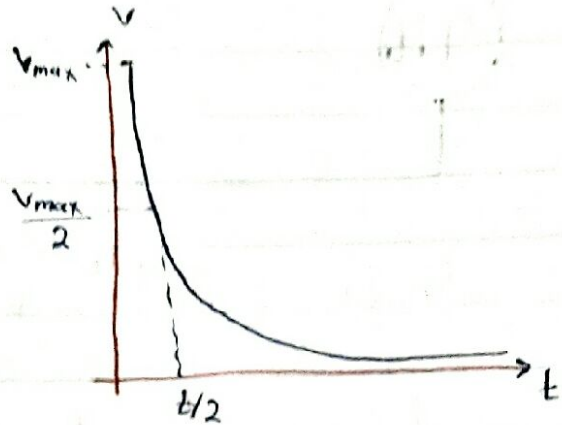• $R_{\text{crit}} = R_0 + R_{\text{ext}}$



Case (III): Over damping :: $\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$


• $\tau = \frac{\ln 2}{t/2}$

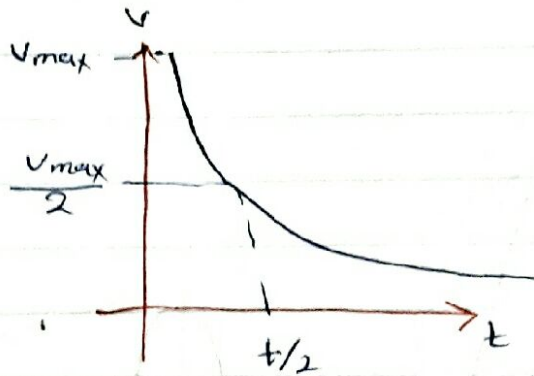

$\tau_{\text{under}} < \tau_{\text{over}} < \tau_{\text{critical}}$

Ex 8

Impedance and reactance:

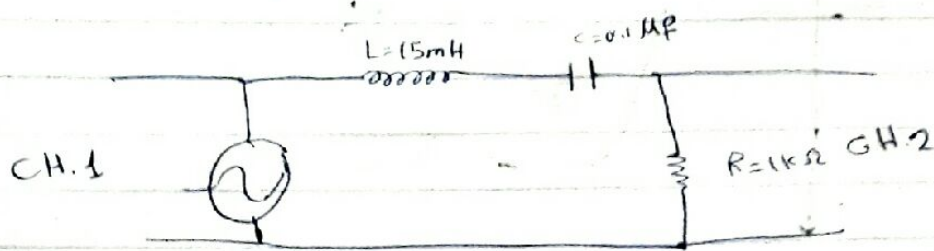

$\Rightarrow Z_R = R$

$\Rightarrow Z_C = -\frac{1}{\omega C} j$
(inversely)

$\Rightarrow Z_L = \omega L j$
(directly)

$\Rightarrow Q_R = R$

$\Rightarrow Q_C = \frac{1}{\omega C}$

$\Rightarrow Q_L = \omega L$


$\Rightarrow Z_{eq} = R + (\omega L - \frac{1}{\omega C}) j$

$|Z_{eq}| = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$

$\Rightarrow I = \frac{\epsilon}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$


$\Rightarrow \Phi = \tan^{-1} \left(\frac{+\frac{1}{\omega C} - \omega L}{R} \right)$

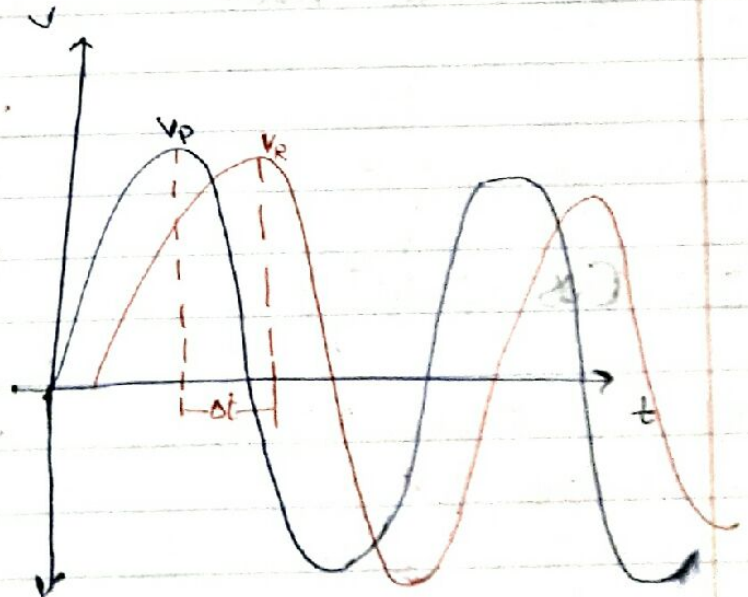$\Phi = \omega \Delta t$
 $= 2\pi f \Delta t$
↳ phasa shift



(7)




when $\omega = 0$... $\frac{\pi}{2}$

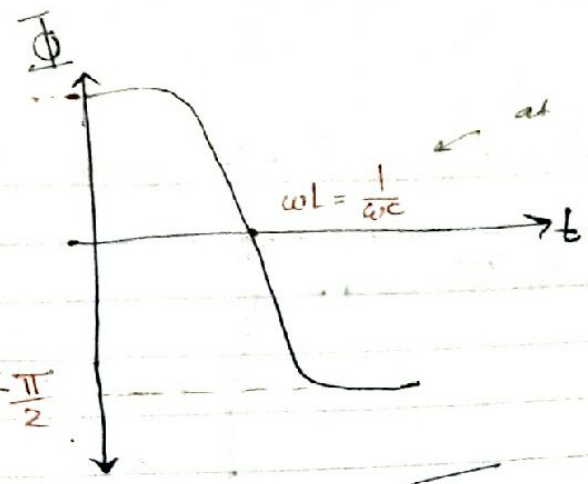

when $\omega = \infty$... $-\frac{\pi}{2}$

• $\omega L = \frac{1}{\omega C} \Rightarrow \omega_0 = \sqrt{\frac{1}{LC}} \Rightarrow$ when $\Phi = 0$

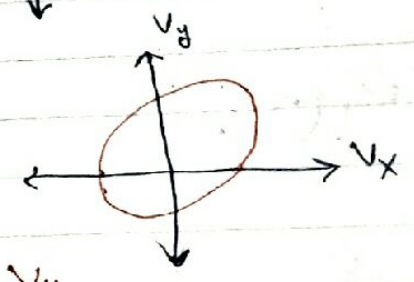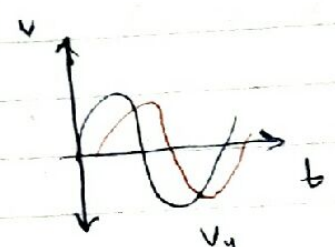
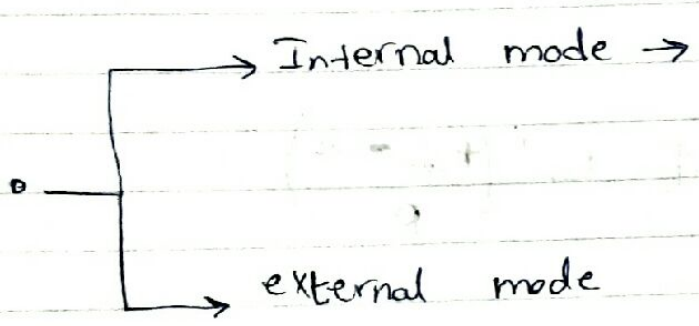
بالسرعة المتغيرة ← zero = Φ ← بالسرعة المتغيرة
 ← Δt ← تغير سرعة الموجة في تغير موقعها




• In external mode

$\Phi = \cos^{-1} \left(\frac{V_{y0}}{V_{y0}} \right)$

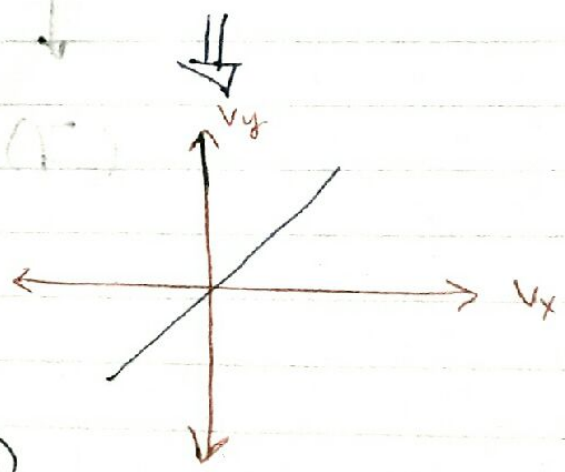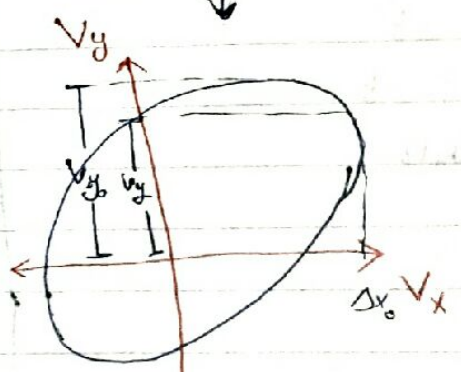→ At f_0 (Resonance) the ellipses turn to a line.




• At f resonance

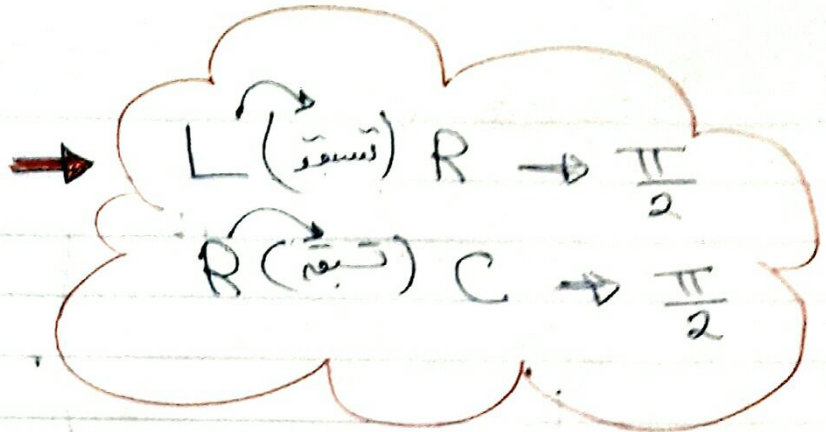

• At external mode


the ellipses turn to circles

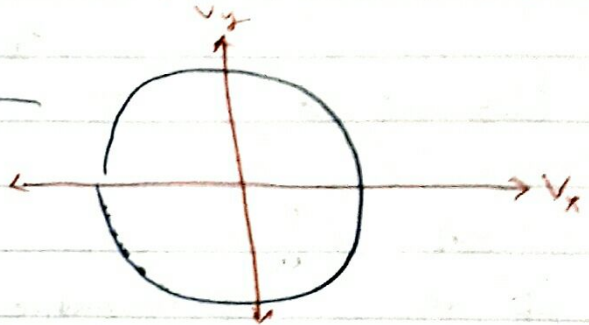

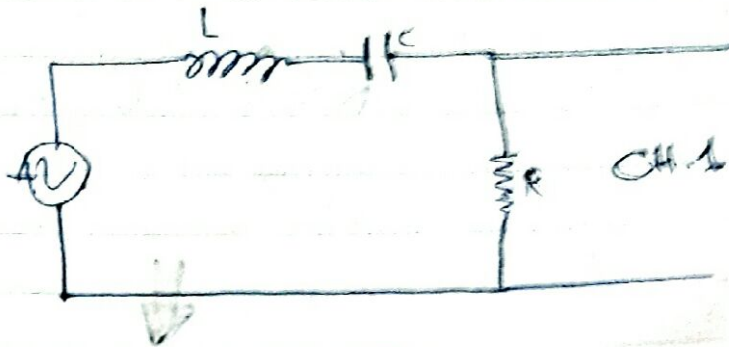(9)

Exp 9 Resonance:


$$I = \frac{\epsilon}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$



• When $\omega = 0 \Rightarrow I = 0$

• When $\omega = \infty \Rightarrow I = 0$

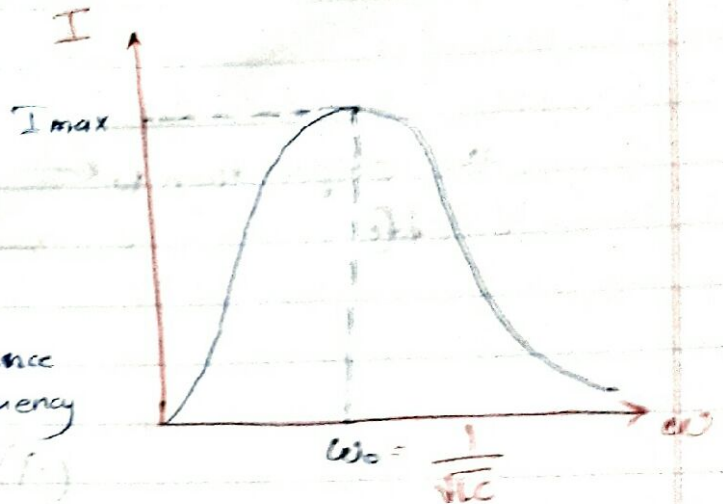
• I_{max} when $\omega L = \frac{1}{\omega C}$
 $\Rightarrow \omega = \frac{1}{\sqrt{LC}} \Rightarrow$ Resonance frequency



Quality factor: $\frac{\text{Energy stored}}{\text{Energy dissipated}}$

$$\Rightarrow Q_{exp} = \frac{\omega_0}{\Delta\omega} = \frac{\omega_0}{\omega_2 - \omega_1}$$
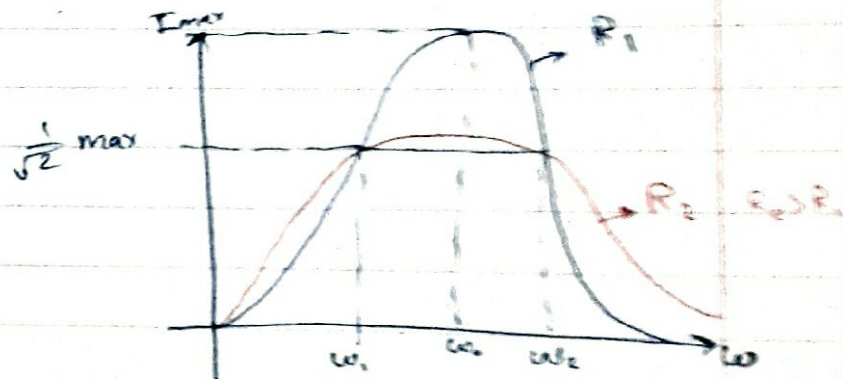
$$\Rightarrow Q_{th} = \frac{1}{R_1} \sqrt{\frac{L}{C}}$$




• ω_0 (resonance frequency) $\Rightarrow \sqrt{\frac{1}{LC}}$

Ex 10 Filters

□ low-pass filters:-

$Z_R = R$, $Z_C = -\frac{1}{\omega c}$

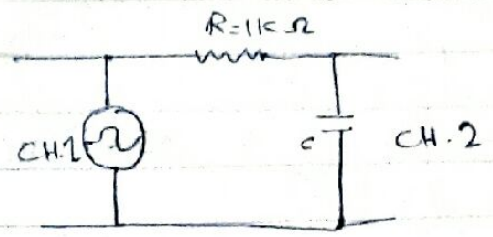$\Rightarrow Z_{eq} = R - \frac{1}{\omega c} j$



$\Rightarrow V_c = \frac{Z_c}{R + Z_c} \epsilon = \frac{-\frac{1}{\omega c} j}{R - \frac{1}{\omega c} j} V_{in}$ \Rightarrow *نقد الی*

$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{1 + RC\omega j} \Rightarrow \left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (RC\omega)^2}}$


Atenuation factor (A)
 $A = \frac{1}{\sqrt{1 + (RC\omega)^2}}$

• $\omega_{-3dB} = \frac{1}{RC} \Rightarrow R^2 C^2 = \frac{1}{\omega_{-3dB}^2}$

$\Rightarrow A = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_{-3dB}}\right)^2}}$



• when $\omega = \omega_{-3dB} \Rightarrow V_{out} = \frac{1}{\sqrt{2}} V_{in}$

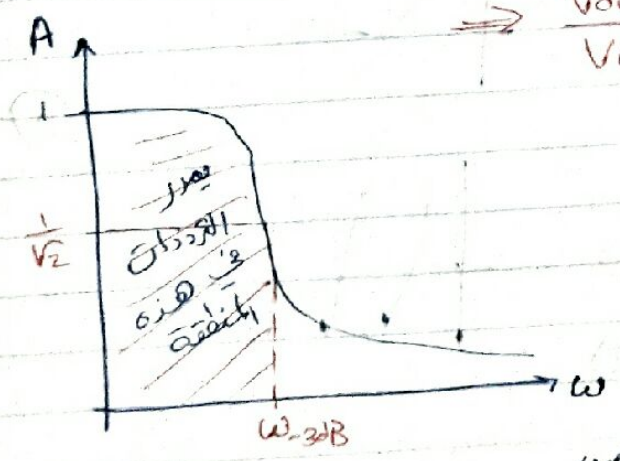$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{2}} \Rightarrow \frac{1}{RC} = \omega_{-3dB}$
 $\hookrightarrow A$





(17)

12] high pass filters

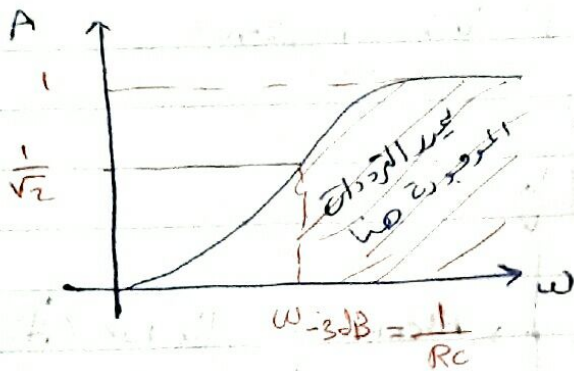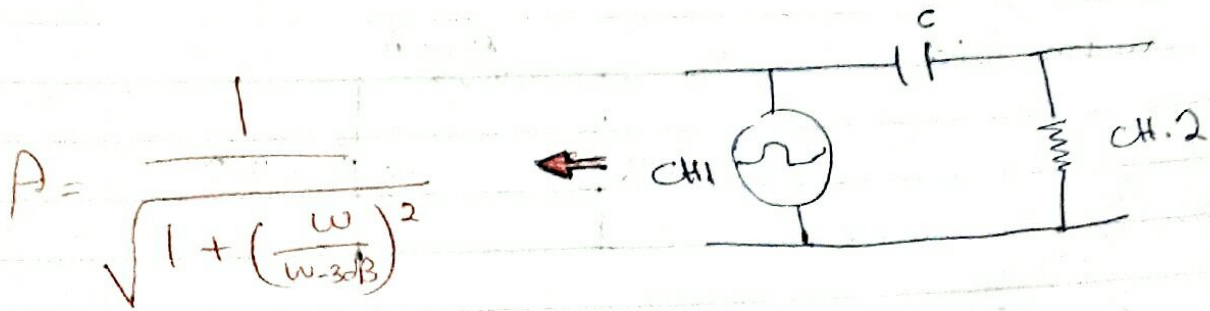

• low pass at high frequency $\approx 70 \text{ kHz}$




input \Rightarrow output

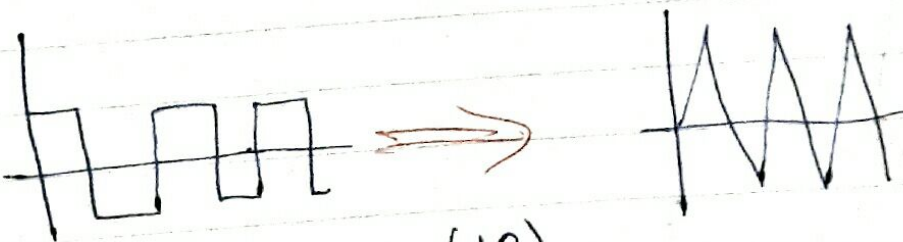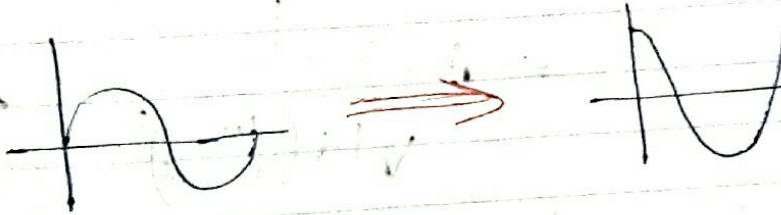

work as a ~~low pass filter~~
Integrators

- high pass at low frequency ≈ 200 Hz

input \Rightarrow out put

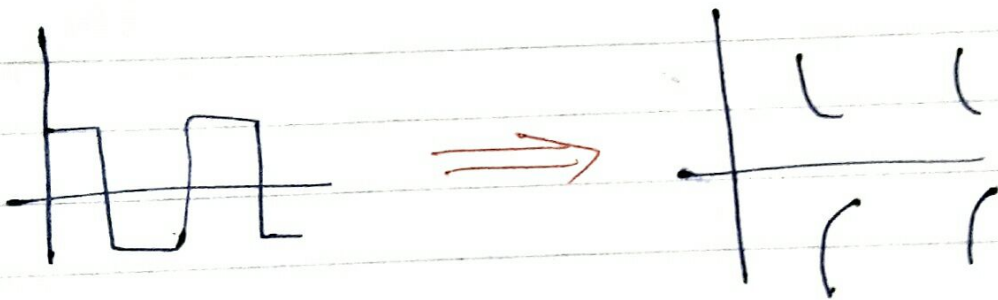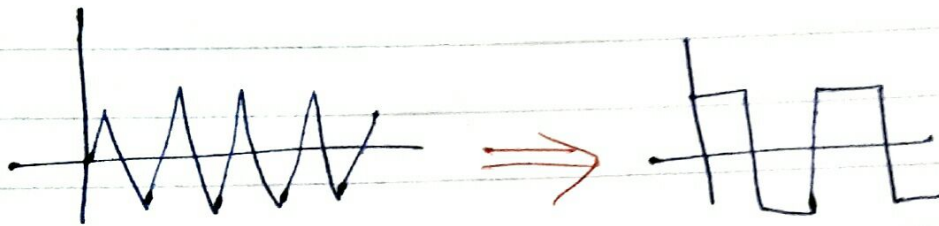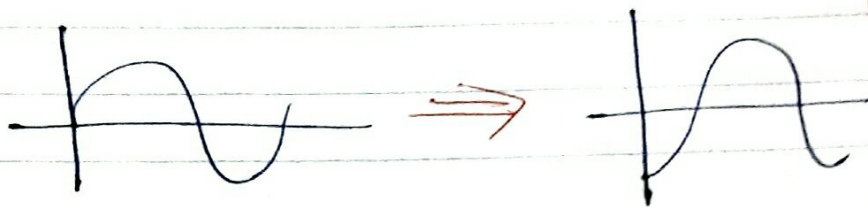

work as an
~~integrator~~
Differentiators