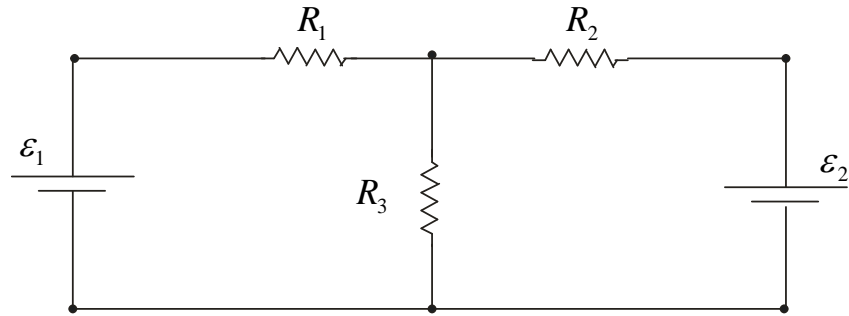


Physics 112  
 Preliminary Laboratory Questions Exp.4  
 network analysis II : Thevenin and Norton techniques

For the circuit shown:



$\varepsilon_1 = 8$  volt,  $\varepsilon_2 = 4$  volt,  $R_1 = 1$  K $\Omega$ ,  $R_2 = 2$  K $\Omega$ ,  $R_3 = 4$  K $\Omega$ .

- a) Use Thevenin's equivalent circuit techniques to find the current passing through  $R_3$ .

$$R_{eq} = \frac{R_1 + R_2}{R_1 R_2} = \frac{R_L = R_3}{(1 + 2) \times 10^3} = \frac{2}{3} \Omega$$

$$\varepsilon_{eq} = \varepsilon_1 - \frac{(\varepsilon_1 - \varepsilon_2)R_1}{R_1 + R_2} = 8 - \frac{(8 - 4) \times 1 \times 10^3}{(1 + 2) \times 10^3} = \frac{20}{3} \text{ volt}$$

$$I_{R_L} = I_{R_3} = \frac{\varepsilon_{eq}}{R_{eq} + R_L} = \frac{\varepsilon_{eq}}{R_{eq} + R_3} = \frac{20/3}{2/3 + (4 \times 10^3)} = 1.67 \text{ mA}$$

- b) Use Norton's equivalent circuit techniques to find the current passing through  $R_3$ .

$$\varepsilon_{eq} = \frac{\varepsilon_1}{R_1} + \frac{\varepsilon_2}{R_2} = \frac{8}{1 \times 10^3} + \frac{4}{2 \times 10^3} = 10 \text{ mA}$$

$$I_{R_L} = \frac{I_{eq} R_{eq}}{R_{eq} + R_L}$$

$$I_3 = \frac{I_{eq} R_{eq}}{R_{eq} + R_3} = \frac{10 \times 10^{-3} \times 2/3}{2/3 + (4 \times 10^3)} = 1.67 \mu\text{A}$$