



Physics Department

Physics 112

Experiment no.2

**Source Internal Resistance, Loading Problems And
Circuit Impedance Matching**

Student's Name: Ahmad Jundi

Student's NO:1150665

Partner's Name:

Partner's No:

Section:- 18

Date1/3/2017

Instructor: Dr.Ghassan Abbas

Abstract:

- 1) **the aim of the experiment is:** to find the value of the load resistance R_L that satisfies the condition of the maximum power transfer which is $R_L = R + R_{in}$
- 2) **the method used:** by reading different measurements of the current passing through the circuit in different values of the R_L (variable resistance in the circuit).

3) the main result is:

Theory:

Electromotive force (emf) is the open circuit voltage difference between voltage source terminals.

A voltage source is characterized by its electromotive force and the maximum value of the current it can deliver to a short circuit. An ideal voltage source is the one in which the internal resistance is zero ($R \sim 0$), so when it is connected to a short circuit it should, according to Ohm's law $\left(I = \frac{V}{R} \right)$, be able to provide an almost infinite current. But in real circuit a voltage source connected to a short circuit can't neither maintain its (emf) as a voltage difference across its terminals nor can it provide the circuit with unlimited current, and that's because there is some kind of

resistance inside the voltage source which is called internal resistance (r_{in}) as shown in fig.1.

Any circuit component that consumes electrical power to produce useful work is called a load and its resistance is called load resistance (R_L).

In the simple series circuit shown in fig.2 the current is:

$$I = \frac{\varepsilon}{R_L + r_{in}} \dots\dots\dots 1$$

and the voltage difference between its terminals is:

$$V_{RL} = \frac{\varepsilon}{(R_L + r_{in})} R_L \dots\dots\dots 2$$

If (R_L) is comparable to (r_{in}) then (V_{RL}) is smaller than (ε), and so a considerable amount of power is consumed inside the source and converted to unuseful heat energy. And in this case the source is said to be loaded and this is what is known as the loading problem. In practical circuits we usually want to avoid loading the source, therefore, choosing ($R_L \geq 10R_{in}$) is recommended.

In fig.2 the power consumed in the load resistor is given by:

$$P = I^2 R_L \dots\dots\dots 3$$

Therefore,

$$P = \frac{\varepsilon^2 R_L}{(R_L + r_{in})^2} \dots\dots\dots 4$$

the last equation shows the power consumed in the load as a function of the load resistance itself. And this function has a maximum value which

can be obtained by setting $\left(\frac{dP}{dR_L} = 0 \right)$ as in fig.3 and this gives:

$$R_L = r_{in}$$

as the condition for transferring maximum power to the load resistance. This choice of load resistance is called impedance matching.

As in the internal resistance of voltage sources is usually small (a few Ohms), in practical circuits an additional resistor is connected in series with the source as shown in fig.4 in order to produce the maximum power transfer condition for large values of (R_L). While this additional resistance appears to (R_L) as an additional internal resistance, it is seen by the source as an additional load resistance. Consequently, this resistance helps in avoiding loading problems and fulfilling the condition of impedance matching for large load values. The only disadvantage is that this additional resistance consumes part of the power delivered to the circuit by the source.

Now if we apply conservation of energy to the circuit in fig.4, we get:

$$\varepsilon = Ir_{in} + IR + IR_L \dots\dots\dots 5$$

and rearranging we get:

$$\frac{1}{I} = R_L \frac{1}{\varepsilon} + \frac{r_{in} + R}{\varepsilon} \dots\dots\dots 6$$

A plot of ($\frac{1}{I}$ vs. R_L) gives a straight line with $\left(\frac{1}{\varepsilon}\right)$ as its slope and $\left(\frac{r_{in} + R}{\varepsilon}\right)$ as its y-intercept.

And now if we apply the condition of maximum power transfer to the load resistance of the same circuit we get:

$$R_L = R + r_{in}$$

A useful concept to use with power is that of efficiency (η). The efficiency of a component with impedance (resistance) (R_L) operated from a source with internal resistance (r_{in}) is the power dissipated in (R_L) divided by the power dissipated in the circuit. Therefore:

$$\eta(R_L) = \frac{I^2 R_L}{I^2 (R_L + r_{in})}$$

$$\eta(R_L) = \frac{R_L}{R_L + r_{in}} \dots\dots\dots 7$$