



Physics Department

Physics 112

Experiment #7

CAPACITORS AND INDUCTORS

Student's Name :Ahmad Jundi

Student's NO:1150665

Partner's Name:Saleem Abufarha

Partner's No: 1120076

Section:- 18

Date:5/4/2017

Instructor: Dr.Ghassan Abbas

Abstract:

The aim of the experiment: is to find out the time constant in RC, RL, and LC circuits.

The method used: is by using the DCO to measure the voltage in the RC and RL circuits and to measure the frequency in the LC circuit.

The main result:

(RC circuit) $\tau_{th} = 0.1\text{msec}$ $\tau_{ex} = 0.15\text{msec}$

(RL circuit) $\tau_{th} = 10\mu\text{sec}$ $\tau_{ex} = 17\mu\text{sec}$

(LC circuit)

$$f_{th} = 5\text{KHZ}$$

$$f_{ex} = 5.05\text{KHZ}$$

$$\omega_{th} = 31.7\text{KHZ}$$

$$\omega_{ex} = 31.714$$

Theory:

RC circuits:


Charging a capacitor:

The voltage across the capacitor's plates is defined by $V_C = \frac{Q}{C}$, and

while $Q(t) = C\varepsilon\left(1 - e^{-\frac{t}{RC}}\right)$ (when we are talking about the

positive half period of the square wave), then $V_C = \varepsilon\left(1 - e^{-\frac{t}{RC}}\right)$

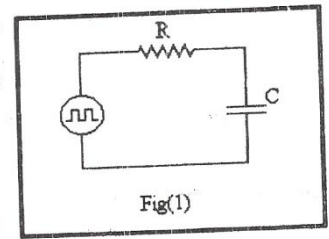.The value of **RC** is usually called the time constant (**τ**) of the **RC** circuit like the one shown in fig.1. **τ** is a measure of how fast the voltage across the capacitor rises. When $t = \tau$, $V_C = 0.63\varepsilon$.



The current passing through the circuit is given by: $I(t) = \frac{dQ}{dt} = \frac{\varepsilon}{R}e^{-\frac{t}{RC}}$, and

while the voltage across the resistor is $V_R = I(t)R = \varepsilon e^{-\frac{t}{RC}}$.

Discharging a capacitor:

Now, during the negative period of the square wave, the capacitor, the capacitor discharges according to the following formula:

$$Q(t) = C\varepsilon e^{-\frac{t}{RC}}$$

And so the voltage across the capacitor's plates is:

$$V_C = 0.37\varepsilon$$

In this case the voltage decays to **0.37** of its maximum value within a time **τ** , which equals **RC** (the time constant).

The current passing through the circuit is:

$$I(t) = \frac{dQ}{dt} = -\frac{\varepsilon}{R}e^{-\frac{t}{RC}}$$


and so, the voltage is given by:

$$V_R = I(t)R = -\varepsilon e^{-\frac{t}{RC}}$$

RL circuits:

The current passing through the **RL** circuit shown in fig.3 rises with time according to the following equation:
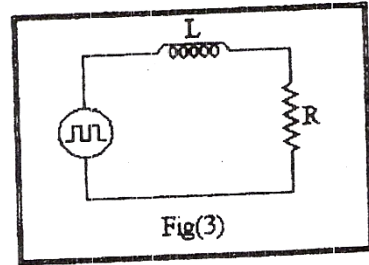
$$I = \frac{\varepsilon}{R} \left(1 - e^{-\frac{Rt}{L}} \right)$$



The voltage across the resistor is $V_R = IR = \varepsilon \left(1 - e^{-\frac{Rt}{L}} \right)$ and across

the inductor is $V_L = L \frac{dI}{dt} = \varepsilon e^{-\frac{Rt}{L}}$.

In this case the time constant equals $\frac{L}{R}$. When $t = \tau$,

$$\text{and } V_L = 0.37\varepsilon . V_R = 0.63\varepsilon$$



LC circuits:

The following equation describes the voltage across the capacitor's plates of the one in the circuit shown in fig.5,

$$V_C = V_{Co} \cos(\omega t + \Phi)$$

where V_{Co} is the amplitude (constant) and $\omega = \frac{1}{\sqrt{LC}}$.

Fig.6 shows the voltage across the capacitor as a function of time

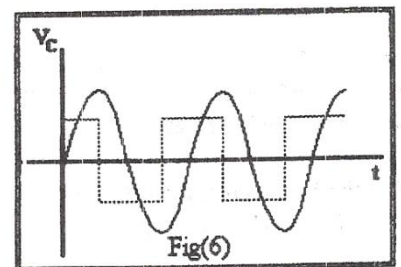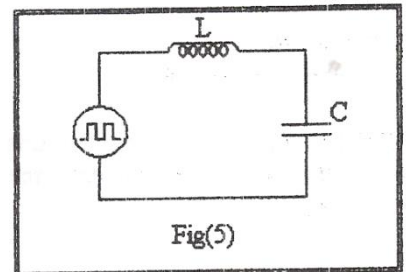

Calculations:

RC circuit:

. (Theoretically, in the two cases; $\tau = R \times C = 1000 \times 0.1 \times 10^{-6} = 0.1 \text{msec}$ charging and discharging).

. (The practical values of time constant that we $\tau_1 = 0.1 \text{msec}$
 $\tau_2 = 0.1 \text{msec}$

obtained by measuring the voltage across the capacitor and the resistance).

RL circuit:

. (Theoretically) $\tau = \frac{L}{R} = \frac{10 \times 10^{-3}}{1000} = 10 \times 10^{-6} \text{ sec}$

. (The practical values of time constant that we $\tau_1 = 10 \times 10^{-6} \text{ sec}$
 $\tau_2 = 10 \times 10^{-6} \text{ sec}$

obtained by measuring the voltage across the resistance and the inductor e).

LC circuit:

The value of frequency as we read from the signal generator is $5 \times 10^3 \text{ Hz}$.

Amplitude = $3.4 \times 2 = 6.8 \text{ volt}$

Period = 4.1

Time for period = $4.1 \times 50 \times 10^{-6} = 2.05 \times 10^{-4}$

$$= \frac{1}{T} = \frac{10000}{2.05} = 4.9 \times 10^3 \text{ Hz. } f_o$$

$$\omega_o = 2\pi f_o = 2 \times \frac{22}{7} \times 4900 = 30800 \text{ Hz}$$

Theoretically:

$$\omega_o = 2\pi f_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10 \times 10^{-3} \times 0.1 \times 10^{-6}}} = \frac{1}{\sqrt{10^{-9}}} = 31622.7766 \text{ Hz}$$

$$f_o = \frac{31622.7766}{2\pi} \approx 5033 \text{ Hz}$$

Analysis of results:

As we saw from the results of the three circuits the values were somehow close to those of the theoretical ones, the small difference may be because of the visual inaccuracy while looking on the CRO.

Q1) $\tau \rightarrow 0$

$$\text{charging} \Rightarrow V_C = \varepsilon(1 - e^{-\frac{t}{RC}}) = \varepsilon(1 - e^0) = 0$$

$$\text{discharging} \Rightarrow V_C = \varepsilon e^{-\frac{t}{RC}} = \varepsilon$$

$\tau \rightarrow \infty$

$$\text{charging} \Rightarrow V_C = \varepsilon(1 - e^{-\frac{t}{RC}}) = \varepsilon$$

$$\text{discharging} \Rightarrow V_C = \varepsilon e^{-\frac{t}{RC}} = 0$$