
جامعۃ بئر زیت
BIRZEIT UNIVERSITY
Physics Department
Physics 112

Experiment 3
Network analysis II
The Thevenin and Norton techniques

Student's name:
Student's No.:

Partner's name:
Partners No.:

Section:


Instructor:

Date:

Abstract:

Theory:

Calculations:

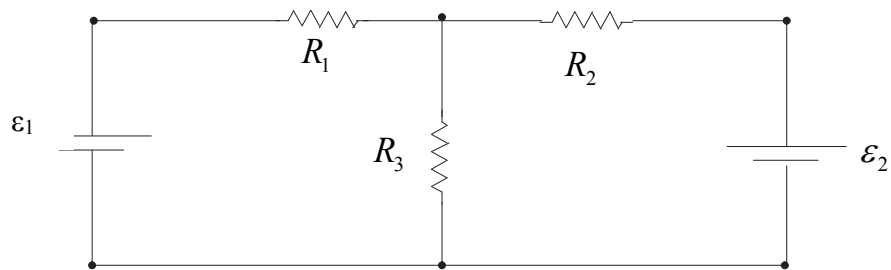

For the circuit shown:

- Use Thevenin's equivalent circuit techniques to find the current passing through R_3 .
- Use Norton's equivalent circuit techniques to find the current passing through R_2 .

Data:

$$R_1 = \quad , R_2 = \quad , R_3 =$$
$$\varepsilon_1 = \quad \varepsilon_2 =$$

- (a) Remove R_3 , kill both sources and measure R_{eq} :

$$R_{eq} =$$

- (b) Connect the sources back and measure ε_{eq} :

$$\varepsilon_{eq} =$$

- (c) Measure I_{eq} :

$$I_{eq} =$$

- (d) Construct Thevenin's equivalent circuit:

$$\text{Measure } I_{RL} =$$

- (e) Construct Norton's equivalent circuit:

$$\text{Measure } I_{RL} =$$

Results and conclusion: