


**Physics 112**  
**Exp.#10: Resonance**  
**Preliminary Laboratory Questions**

1) Consider a series RLC circuit with a sinusoidal input:  $\varepsilon(t) = 2\cos(\omega t)$  Volts. If  $R=1\text{ K}\Omega$ ,  $L= 10\text{ mH}$  and  $C=0.1\text{ }\mu\text{F}$ .

a) Find the maximum value of the current amplitude  $I_0$  in the circuit.

b) Find  $\omega$  for which, the current amplitude  $I_0$  in circuit is maximum.

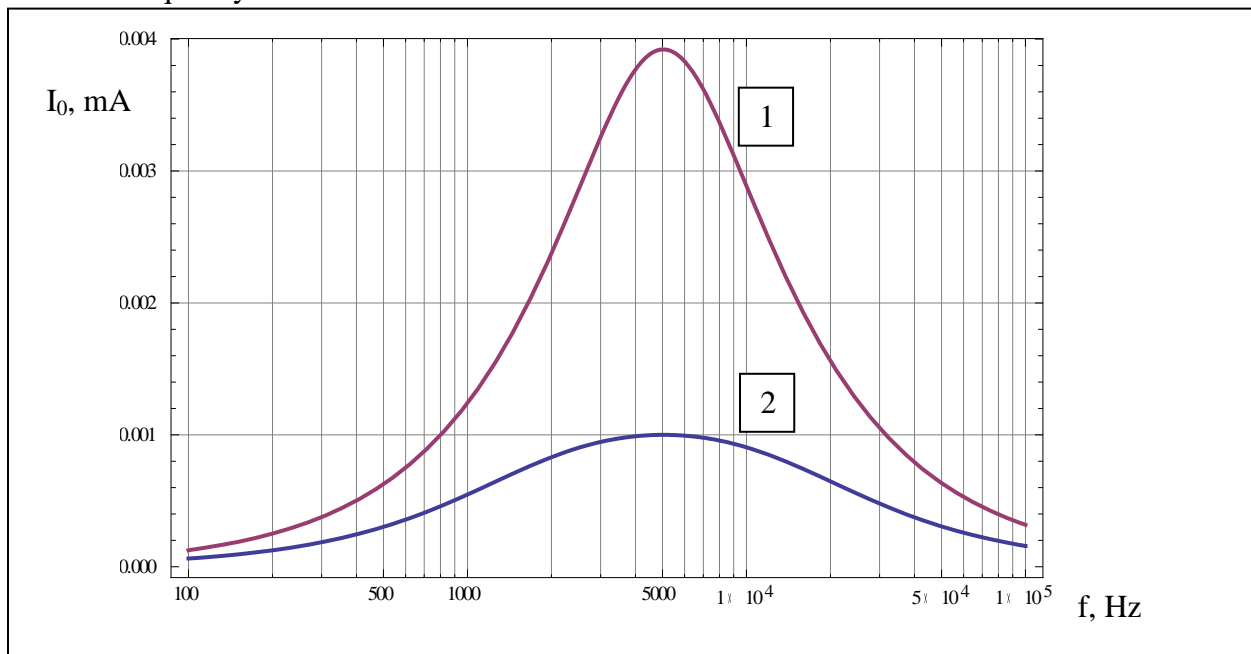2) Consider the same circuit in q1. The plot below shows two curves of current amplitude  $I_0$  versus the frequency  $f$  : one for  $R=1000\Omega$  and the other for  $R=510\Omega$ .



a) Which of the curves for  $R=1000\Omega$  and which for  $R=510\Omega$ ?

b) Estimate the resonance frequency from the curves.

c) Estimate the bandwidth for both curves

c) Estimate the quality factors for both resonance curves.