

Chapter 27 :-

Circuits

Electromotive force (\mathcal{E}) :-

→ Work done by the Power source (s.a battery) in moving $+1\text{ C}$ from (-) terminal to (+) positive terminal.

$$\mathcal{E} = \frac{dW}{dq} \quad \text{V (J/C)}$$

ideal device is a device that lacks any internal resistance

A real emf device has an internal resistance

Calculating I in a single-loop circuit

$$\mathcal{E} dq = dW$$

derivation to dt

$$\mathcal{E}I = \frac{dW}{dt} \rightarrow P_{\mathcal{E}}$$


$$P_{\mathcal{E}} = P_R \quad \text{Conservation of Energy}$$

$\mathcal{E}I$ → thermal energy

$$\mathcal{E}I = I^2 R$$



$$\boxed{I = \frac{\mathcal{E}}{R}} \quad \text{for an ideal battery} \quad \text{and} \quad \boxed{V = \mathcal{E}}$$

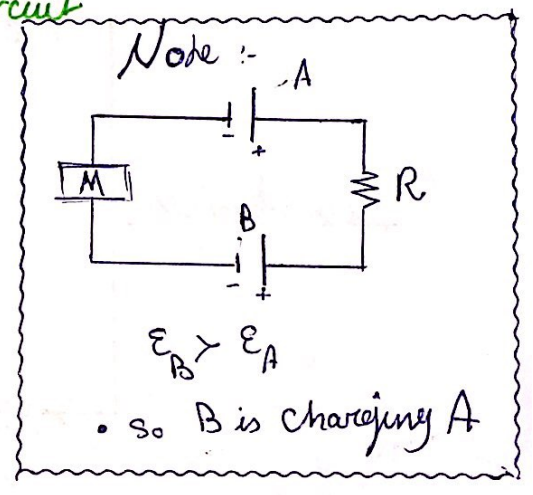→ Loop Rule : $\sum V = 0$ in a closed loop
↳ (Kirchoff's voltage law)



Alaa Etawi

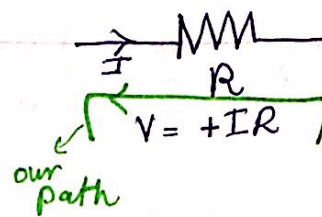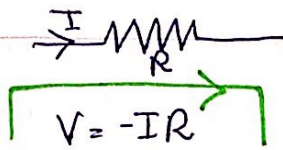In a loop :- If the more through the Resistance is the same as the direction of I The potential change $= -IR$ if opposite it equals $+IR$



If the battery is not ideal and $r_{in} \neq 0$


Then

$$I = \frac{\mathcal{E}}{R + r_{in}}$$

and $V = \mathcal{E} - ir_{in}$

Resistances

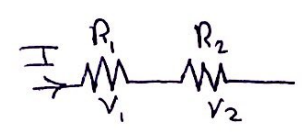→ on series :-
 I is the same for All R
 V is not the same $V_{applied} = V_1 + V_2$




$$R_{eq} = R_1 + R_2$$

$$R_{eq} > R_1$$

$$R_{eq} > R_2$$

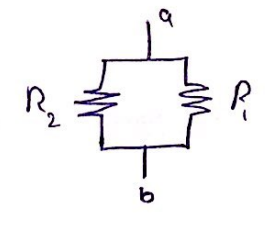→ on parallel :-
 V is the same for all R
 I is not the same $I_{app} = I_1 + I_2$



$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Alaa Haidwi

Multiloop Circuits

At Any Junction

$$\sum I_{in} = \sum I_{out}$$

$$\sum_{\text{closed loop}} V = 0$$

$$1 - V_a - \mathcal{E}_1 - i_3 R_3 + i_1 R_1 = V_a$$

$$\mathcal{E}_1 + i_3 R_3 - i_1 R_1 = 0$$

$$\mathcal{E}_1 = i_1 R_1 - i_3 R_3 \quad \text{--- (1)}$$

$$2 - V_b + \mathcal{E}_2 + i_2 R_2 + i_3 R_3 = V_b$$

$$\mathcal{E}_2 = -i_2 R_2 - i_3 R_3 \quad \text{--- (2)}$$


solve 1 & 2 by substituting $i_1 = i_2 - i_3$

$$\mathcal{E}_1 = R_1 i_2 - R_1 i_3 - i_3 R_3$$

$$\mathcal{E}_1 = R_1 i_2 - i_3 (R_1 + R_3)$$

$$\mathcal{E}_2 = -i_2 R_2 - i_3 R_3$$

→ You can solve them knowing R & E.

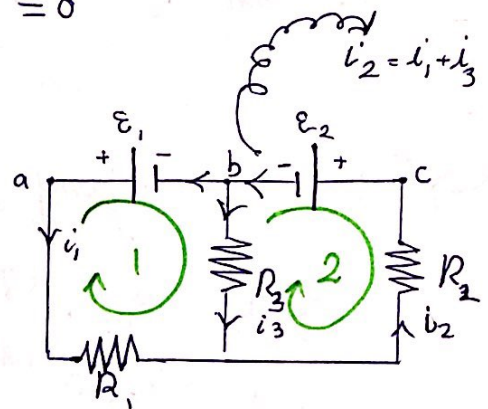

RC - Circuits

→ Charging a capacitor :-

$$t=0 \rightarrow q=0$$



After a long time q is max = $\mathcal{E}C$

At Any time $\mathcal{E} = V_R + V_C$

$$Q(t) = C\mathcal{E} (1 - e^{-t/RC})$$

$$V_C(t) = \mathcal{E} (1 - e^{-t/RC})$$

$$V_R(t) = \mathcal{E} e^{-t/RC}$$

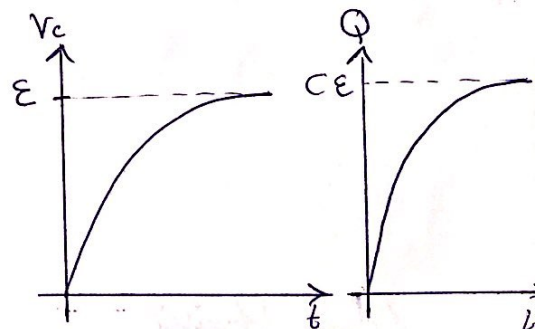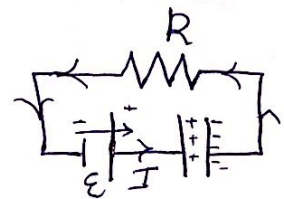

Maa Itaiwi


• Generally :-

$$i_0 = \frac{\mathcal{E}}{R}$$

and

$$\tau = RC$$

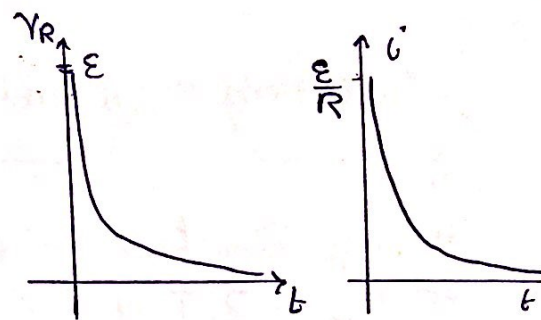→ when $V_C = 0.63 \mathcal{E} \rightarrow t = \tau$



↳ Discharging A Capacitor


$$Q(t) = q_0 e^{-t/RC}$$

$$V_C(t) = V_0 e^{-t/RC}$$

$$i(t) = \frac{-q_0}{RC} e^{-t/RC}$$

The rest charge

(qawab iswli)

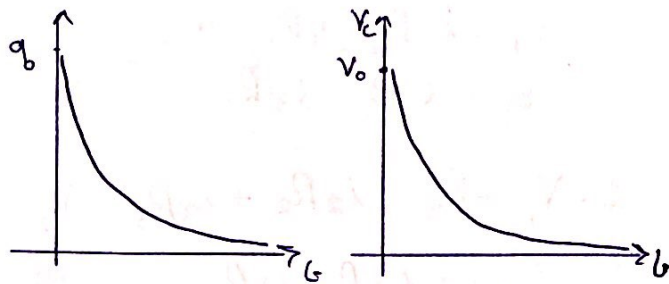

• stored energy

Alaa Etaiwi