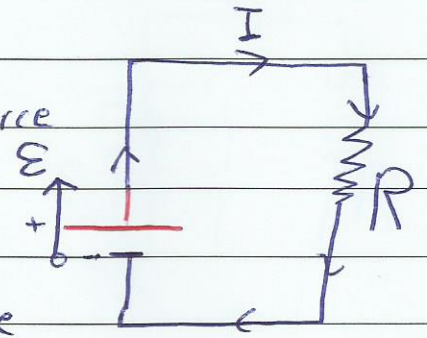


Chapter 27 - Circuits

Single-loop circuit:

Electromotive force of the Power source (Battery) is the work done by the Battery to move $+1C$ from negative terminal \rightarrow to positive terminal inside the source



$$\mathcal{E} = \frac{dW}{dq} \text{ J/C} = \text{Volt}$$

$dW = \mathcal{E} dq$ is the work done by the Battery to move dq from $(-)$ \rightarrow $(+)$ inside the Battery

$$\frac{dW}{dt} = \mathcal{E} \frac{dq}{dt}$$

Power of the Battery = $\mathcal{E} I$ Watt.

$P_{\mathcal{E}} = \mathcal{E} I$ The amount of Power supplied by \mathcal{E} to the circuit

$P_R = I^2 R$ The thermal Power in R @
The Power Consumed by R
from Conservation of Energy.


$$P_{\mathcal{E}} (\text{supplied}) = P_R (\text{consumed})$$
$$\mathcal{E} I = I^2 R$$

$I = \frac{\mathcal{E}}{R}$ Single-loop circuit equation for ideal Power source

Real Power Sources (Real Battery)
has internal resistance = r

$$I = \frac{\mathcal{E}}{R+r}$$


Single-loop circuit equation

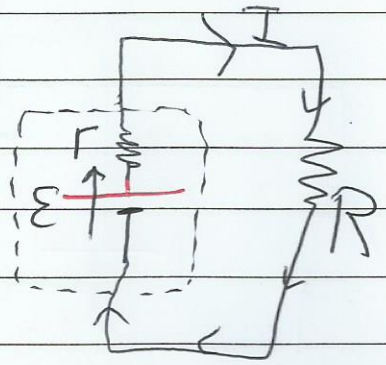

Resistance in Series

① The same current is passing through each resistor

$$I = I_1 = I_2 = I_3$$

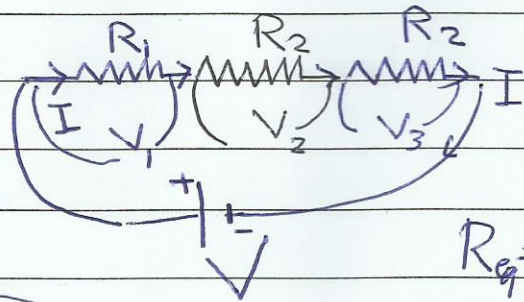

$$R_{eq} = \sum_{j=1}^n R_j$$

$$V = RI$$

OHM'S LAW

$$\textcircled{2} V = V_1 + V_2 + V_3$$

$$V = IR_1 + IR_2 + IR_3$$

$$V = I(R_1 + R_2 + R_3)$$

$$\frac{V}{I} = R_1 + R_2 + R_3 \quad \rightarrow \quad R_{eq} = \frac{V}{I}$$

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

Resistance in Parallel:

$$V = V_1 = V_2 = V_3$$



$$V = IR$$

OHM'S LAW

$$I = I_1 + I_2 + I_3$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$
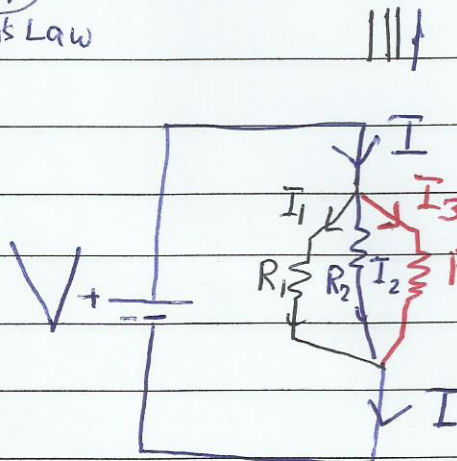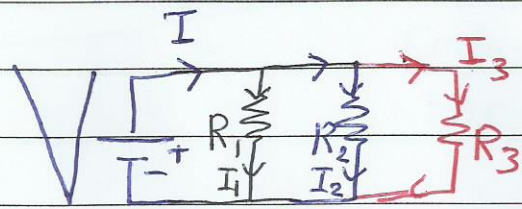
$$I = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$



$$\frac{1}{R_{eq}} = \sum_{j=1}^n \frac{1}{R_j}$$

$$\frac{I}{V} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Problem (27-61)

$$\mathcal{E}_1 = 12V, \mathcal{E}_2 = 4V$$

$$I = \frac{\sum \mathcal{E}}{R_{eq}}$$
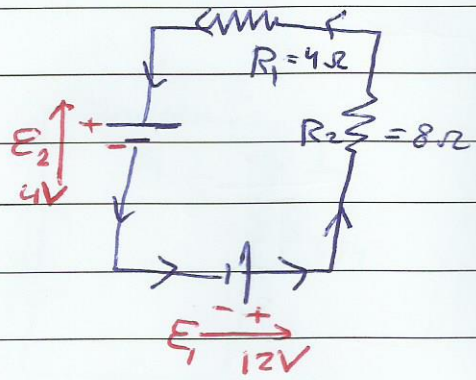
$$= \frac{12 + (-4)}{4 + 8} = \frac{8}{12} = 0.67A$$





$I = I_1 = I_2 = 0.67A$ in each resistor

$$P_{R_1} = I^2 R_1 = (0.67)^2 (4) = 1.78 \text{ Watt thermal Power}$$


$$P_{R_2} = I^2 R_2 = (0.67)^2 (8) = 3.56 \text{ Watt, thermal Power}$$

$$P_{\mathcal{E}_1} = I \mathcal{E}_1 = (0.67)(12) = 8 \text{ Watt}$$
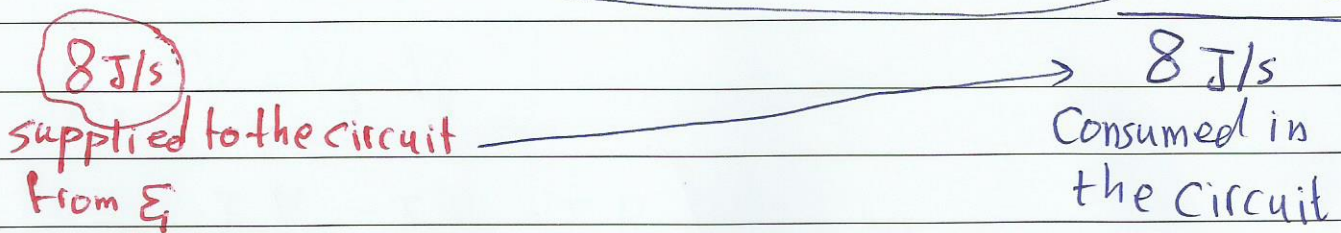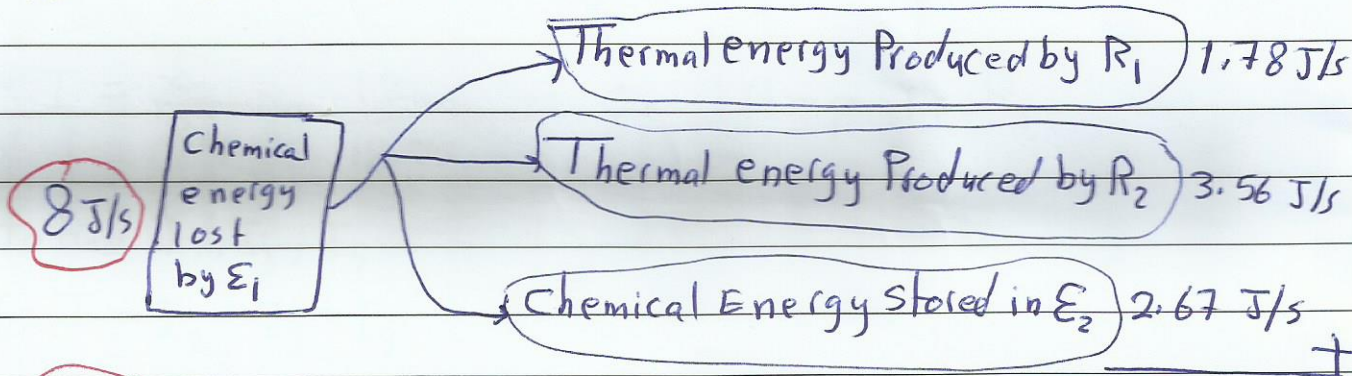
$$P_{\mathcal{E}_2} = I \mathcal{E}_2 = (0.67)(4) = 2.67 \text{ Watt}$$



Problem (27-8)

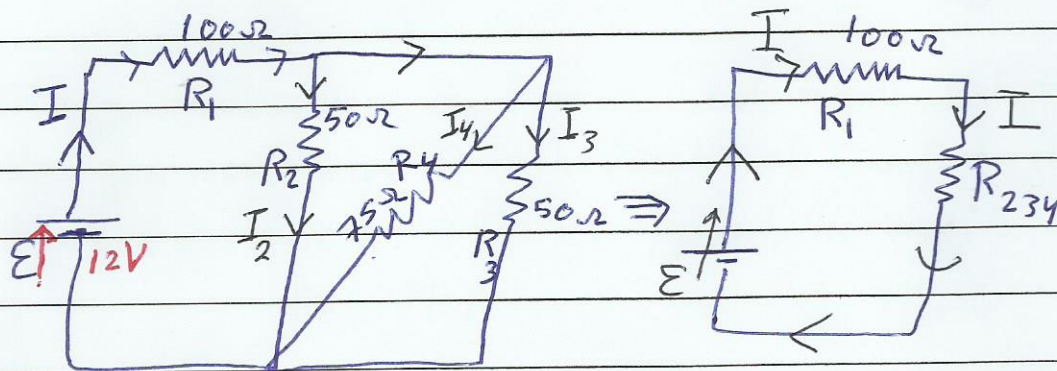

R_2, R_3, R_4 all in parallel

$$\frac{1}{R_{234}} = \frac{1}{50} + \frac{1}{50} + \frac{1}{75} = \frac{3+3+2}{150} = \frac{8}{150}$$

$$R_{234} = \frac{150}{8} = \frac{75}{4} = 18.75 \Omega$$

$$R_{eq} = R_1 + R_{234} = 118.75 \Omega$$

$$I = \frac{E}{R_{eq}} = \frac{12}{118.75} = 0.1 \text{ Amp in } R_1$$

to find I_2, I_3, I_4

$$\textcircled{1} I = I_2 + I_3 + I_4$$

$$V_{234} = V_2 = V_3 = V_4$$

$$I R_{234} = I_2 R_2 = I_3 R_3 = I_4 R_4$$

$$(0.1)(18.75) = 50 I_2 = 50 I_3 = 75 I_4$$

$$I_2 = \frac{(0.1)(18.75)}{50} = 0.0375 \text{ A} = 3.75 \times 10^{-3} \text{ A}$$

$$I_3 = \frac{(0.1)(18.75)}{50} = 0.0375 \text{ A} = 3.75 \times 10^{-3} \text{ A}$$

$$I_4 = \frac{(0.1)(18.75)}{75} = 0.025 \text{ A} = 25 \times 10^{-3} \text{ A}$$

Solve Sample Problem 27.02

0.1 A

④

Potential difference between 2 points ($V_{ab} = V_a - V_b$)

- When you move across \mathcal{E} from (-) \rightarrow (+) terminals put $+\mathcal{E}$
- When you move across R in the direction of I , put $-RI$
- When you move across R in the opposite direction of I put $+RI$

Sample Problem 27.01


$$\mathcal{E}_1 = 4.4 \text{ V}$$

$$\mathcal{E}_2 = 2.1 \text{ V}$$

$$r_1 = 2.3 \Omega$$

$$r_2 = 1.8 \Omega$$

$$R = 5.5 \Omega$$

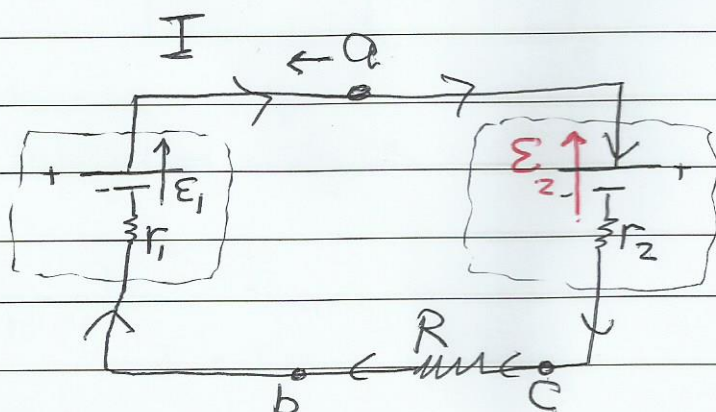

$$\text{Find } I? \quad I = \frac{\sum \mathcal{E}}{r_1 + r_2 + R} = \frac{+4.4 + -2.1}{2.3 + 1.8 + 5.5} = \frac{2.3}{9.6}$$

$$I = 0.24 \text{ A}$$

find V_{ab} ? find $V_a - V_b$?

$$V_a + -\mathcal{E}_1 + +I r_1 = V_b$$

$$V_a - 4.4 + (0.24)(2.3) = V_b \Rightarrow V_a - 4.4 + 0.55 = V_b$$

$$V_a - 3.85 = V_b$$

$$\boxed{V_a - V_b = +3.85 \text{ V}} \quad \text{Note that } V_b - V_a = -3.85 \text{ V} = V_{ba}$$

find V_{ac} ? find $V_a - V_c$?

$$V_a + -\mathcal{E}_2 + -I r_2 = V_c$$

$$V_a - 2.1 - (0.24 \times 1.8) = V_c \Rightarrow V_a - 2.1 - 0.43 = V_c$$

$$V_a - 2.53 = V_c \Rightarrow V_a - V_c = 2.53 \text{ V}$$

Note that $\boxed{V_{ab} = -V_{ba}}$ Note that $V_c - V_a = -2.53 \text{ V}$


Multiloop Circuits

Kirchhoff's rules:

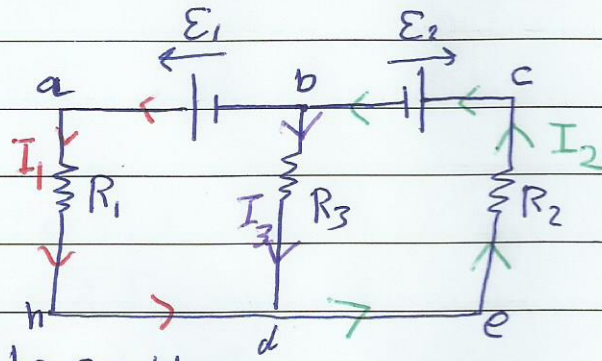1) Junction Rule:

From Conservation of Charge

"The sum of the currents entering any junction must be equal to the sum of currents leaving that junction"



At a point (b) $\sum I_{\text{entering}} = \sum I_{\text{leaving}}$
 $I_2 = I_1 + I_3$ (1)

From Conservation of energy

2) Loop Rule: "The algebraic sum of the changes in Potential encountered in a complete traversal of any loop of a circuit must be zero"

$$\sum V = 0 \text{ around any closed loop}$$

$$\sum V_{abdha} = 0 \Rightarrow -\mathcal{E}_1 + -I_3 R_3 + I_1 R_1 = 0 \quad (2)$$

$$\sum V_{acedb} = 0 \Rightarrow +\mathcal{E}_2 + +I_2 R_2 + +I_3 R_3 = 0 \quad (3)$$

also you can consider the third loop aceha

$$\sum V_{aceha} = 0 \Rightarrow -\mathcal{E}_1 + +\mathcal{E}_2 + I_2 R_2 + I_1 R_1 = 0 \quad (4)$$

equation (4) is the sum of (2) + (3), you will not need it if you write (3) + (2)

Solve Sample Problem 27.04

Problem (27-3)

$\mathcal{E}_1 = 1V, \mathcal{E}_2 = 3V$

$R_1 = 4\Omega, R_2 = 2\Omega, R_3 = 5\Omega$

What is the rate at which energy dissipated in:

a) R_1 ? b) R_2 ? c) R_3 ?

What is the power of d) \mathcal{E}_1 ? e) \mathcal{E}_2 ?

At point b $\sum I_{\text{entering}} = \sum I_{\text{leaving}}$

$I_2 = I_1 + I_3$ ①

$\sum V_{\text{abcd}} = 0 \Rightarrow +I_1 R_1 - I_3 R_3 + \mathcal{E}_1 = 0$
 $4I_1 - 5I_3 + 1 = 0$

$1 = 5I_3 - 4I_1$ ②

$\sum V_{\text{bhec}} = 0 \Rightarrow +I_2 R_2 - \mathcal{E}_2 + I_3 R_3 = 0$
 $2I_2 - 3 + 5I_3 = 0$

$3 = 2I_2 + 5I_3$ ③

From ① in ③ $\Rightarrow 3 = 2(I_1 + I_3) + 5I_3$

$3 = 2I_1 + 7I_3$ ③'

you have to solve ② with ③' \Rightarrow multiply ③' by 2 \Rightarrow

$6 = 4I_1 + 14I_3$ ③''

$1 = -4I_1 + 5I_3$ ②

$7 = 19I_3$

$I_3 = \frac{7}{19} = 0.368 \text{ A}$

$I_3 = 0.368 \text{ A}$ in ② \Rightarrow

$4I_1 = 5I_3 - 1$

$I_1 = \frac{5(0.368) - 1}{4} = 0.211 \text{ A}$

$I_1 = 0.211 \text{ A}$

from ① $I_2 = I_1 + I_3$

$I_2 = 0.579 \text{ A}$


a) $P_{R_1} = I_1^2 R_1 = (0.211)^2 (4) = 0.178 \text{ Watt}$

b) $P_{R_2} = I_2^2 R_2 = (0.579)^2 (2) = 0.670 \text{ Watt}$

c) $P_{R_3} = I_3^2 R_3 = (0.368)^2 (5) = 0.677 \text{ Watt}$

d) $P_{\mathcal{E}_1} = I_1 \mathcal{E}_1 = (-)(0.211)(1) = -0.211 \text{ Watt}$
 absorbed

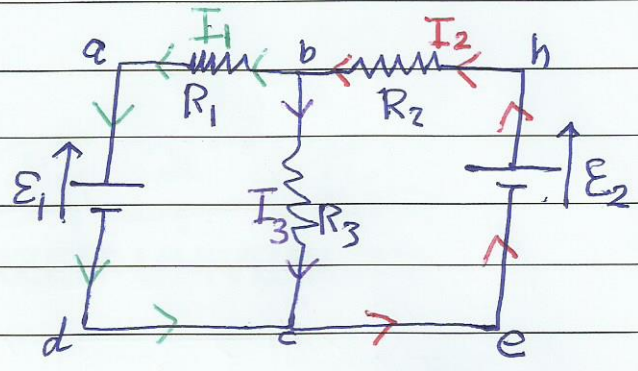e) $P_{\mathcal{E}_2} = I_2 \mathcal{E}_2 = 0.579(3) = +1.737 \text{ Watt}$
 Provided



Note: that

- $I_1^2 R_1$
- $I_2^2 R_2$
- $I_3^2 R_3$
- $P_{\mathcal{E}_2}$
- $P_{\mathcal{E}_1}$



(L.O)

$P_{\mathcal{E}_2} = P_{\mathcal{E}_1} + I_1^2 R_1 + I_2^2 R_2 + I_3^2 R_3$

RC - Circuits:-

Charging a Capacitor;

Connecting (S to a)

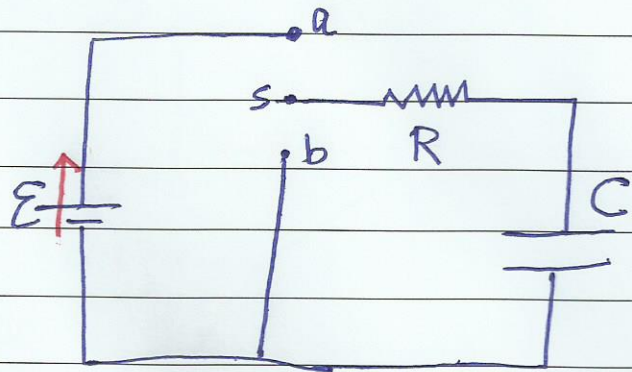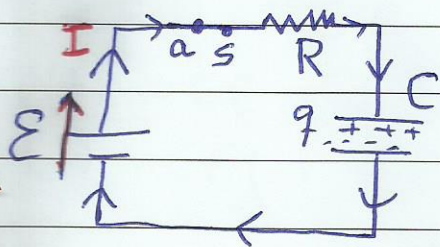

Remember $V_C = \frac{q}{C}$
 $V_R = RI$

$q_0 = 0$ initial charge on the Capacitor,
 the charge will increase gradually on the Capacitor to
 reach q_{max} after a long time

$$q_{max} = C\varepsilon$$

To find the charge on the Capacitor at any time

$\sum V = 0$ around the closed loop.

$$\varepsilon - RI + \frac{q}{C} = 0, \quad I = \frac{dq}{dt}$$

$$\varepsilon = \frac{q}{C} + R \frac{dq}{dt}$$

$$\varepsilon - \frac{q}{C} = R \frac{dq}{dt} \Rightarrow \frac{\varepsilon C - q}{C} = R \frac{dq}{dt}$$

$$\frac{\varepsilon C - q}{RC} = \frac{dq}{dt} \Rightarrow \frac{q - \varepsilon C}{RC} = (-) \frac{dq}{dt}$$

$$\frac{dq}{q - \varepsilon C} = (-) \frac{dt}{RC}$$

integrate from $t=0 \rightarrow t=t$

$$\int_0^q \frac{dq}{q - \varepsilon C} = (-) \frac{1}{RC} \int_0^t dt$$

$$\ln [q - \varepsilon C]_0^q = -\frac{t}{RC}$$

$$\ln(q - \varepsilon C) - \ln(-\varepsilon C) = -\frac{t}{RC}$$

$$\ln\left(\frac{Q - CE}{-CE}\right) = -\frac{t}{RC}$$


$$\frac{Q - CE}{-CE} = e^{-t/RC}$$

$$Q - CE = -CE e^{-t/RC}$$

$$Q(t) = CE - CE e^{-t/RC}$$

$$Q(t) = CE(1 - e^{-t/RC}) \quad \textcircled{I}$$

charging a capacitor

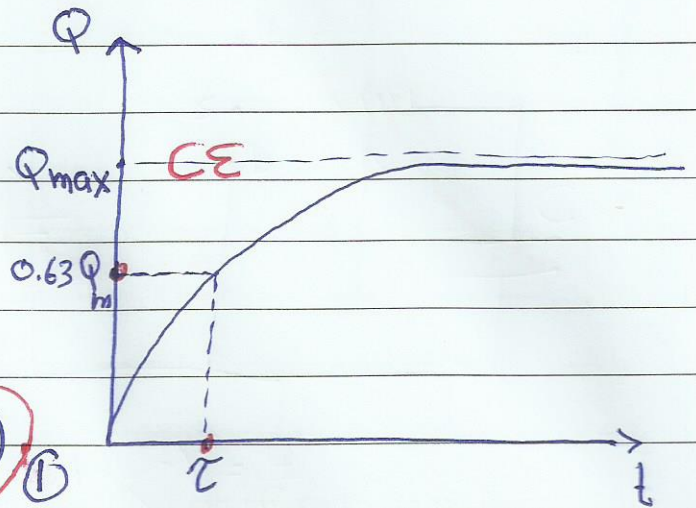

The time constant of the circuit = RC
 $\Omega F = \text{sec.}$

$$\tau = RC$$

$$Q(t) = CE(1 - e^{-t/\tau}) \quad \textcircled{II}$$


1) to find Q_{\max} , put $t \rightarrow \infty$ $Q_{\max} = CE$

2) Find Q at $t = \tau \Rightarrow Q(\tau) = CE(1 - e^{-1})$
 $= CE(1 - 0.37)$

$$Q(\tau) = 0.63 CE = 0.63 Q_{\max}$$

\Rightarrow At $t = \tau \Rightarrow$ the charge on the capacitor will reach $0.63 Q_{\max}$
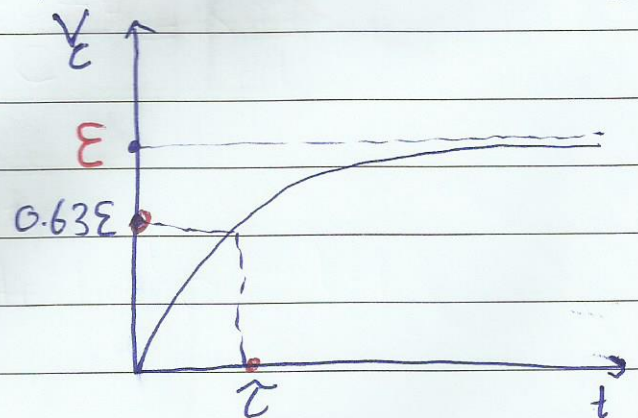
$$V_c(t) = \frac{Q(t)}{C} = \varepsilon(1 - e^{-t/\tau})$$



Find the current at any time?

$$I = \frac{dQ}{dt} = \frac{d}{dt} [CE(1 - e^{-t/RC})]$$

$$= 0 - CE(-\frac{1}{RC}) e^{-t/RC}$$

$$I(t) = \frac{\varepsilon}{R} e^{-t/RC}$$

charging C

$$\frac{\varepsilon}{R} = I_0 \text{ at } t=0$$

$$V_R = RI$$



$$V_R(t) = \varepsilon e^{-t/RC}$$

$$I(t) = \frac{\mathcal{E}}{R} (e^{-t/\tau})$$

$$V_R(t) = \mathcal{E} e^{-t/\tau}$$

$$\text{as } t \rightarrow \infty \quad I = 0$$

$$V_R = 0$$

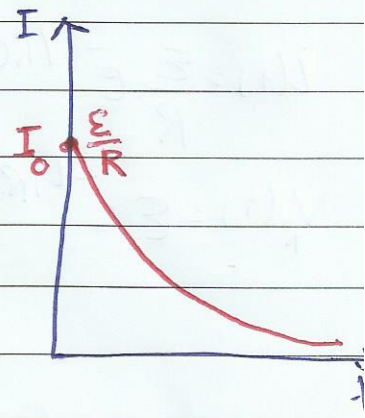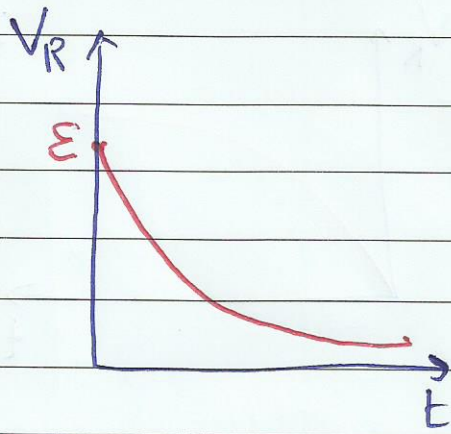


Discharging a Capacitor

Connect b & S

The charge will move from (+) plate
 → (-) plate through R

$$q_0 = C\mathcal{E} = q_m$$
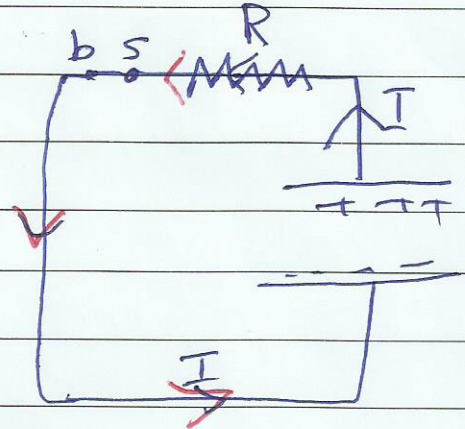
$$q_{\text{finally}} = 0 \text{ as } t \rightarrow \infty$$



find q at any time.

$$RI + \frac{q}{C} = 0 \Rightarrow R \frac{dq}{dt} = -q/C$$

$$\frac{dq}{q} = -\frac{dt}{RC} \quad \text{integrate}$$

$$\int_{q_0}^q \frac{dq}{q} = -\frac{1}{RC} \int_0^t dt$$




$$\ln\left(\frac{q}{q_0}\right) = -\frac{t}{RC} \Rightarrow \frac{q}{q_0} = e^{-t/RC}$$

$$q(t) = q_0 e^{-t/RC} \Rightarrow q(t) = q_0 e^{-t/\tau}$$

$$i(t) = \frac{dq}{dt} = q_0 \left(-\frac{1}{RC}\right) e^{-t/RC} = \left(-\frac{q_0}{RC}\right) e^{-t/\tau}$$

$$I_0 = \frac{q_0}{RC}$$

$$I_{\text{finally}} = 0$$

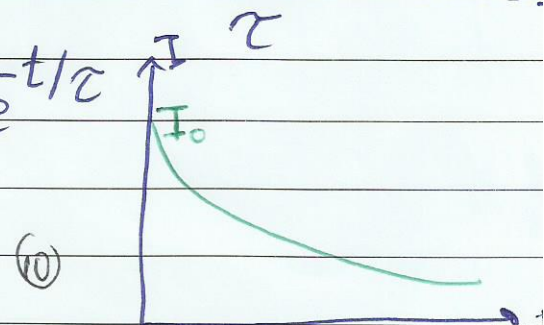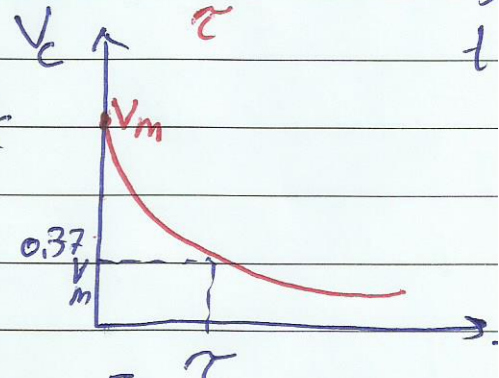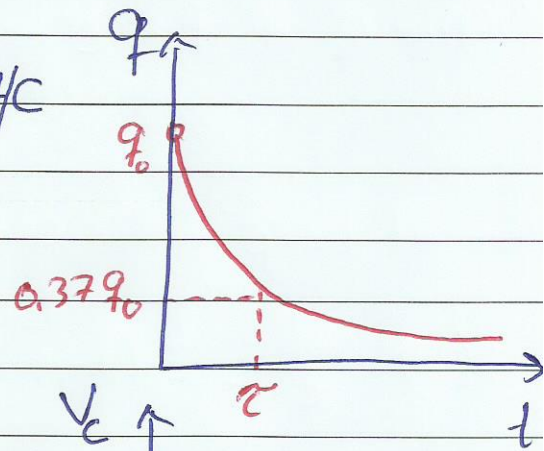

(10)

Problem (27-40)

$$R = 1.4 \text{ M}\Omega, C = 2.7 \mu\text{F}$$

Find

a) τ ?

$$\tau = RC = (1.4 \times 10^6)(2.7 \times 10^{-6}) = 3.78 \text{ sec.}$$

b) $Q(t) = CE(1 - e^{-t/\tau})$

$$Q_{\max} \text{ at } t \rightarrow \infty \Rightarrow Q_{\max} = CE = (2.7 \times 10^{-6})(12) = 32.4 \times 10^{-6} \text{ C}$$

c) Find t ? When $Q = 16 \mu\text{C}$

$$Q(t) = CE(1 - e^{-t/\tau})$$


$$16 \times 10^{-6} = 32.4 \times 10^{-6} (1 - e^{-t/\tau})$$

$$0.494 = 1 - e^{-t/\tau} \Rightarrow e^{-t/\tau} = 1 - 0.494 = 0.506$$

$$-\frac{t}{\tau} = \ln(0.506) \Rightarrow t = -\tau \ln(0.506) = -\tau(-0.68)$$

$$t = 0.68(3.78)$$

$$t = 2.575 \text{ s}$$

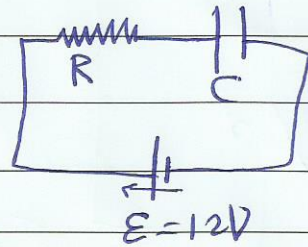

Problem (27-18)

at $t=0, V_{C0} = 80\text{V}$

at $t=10\text{s}, V_C = 1\text{V}$

a) Find τ ?

$$q(t) = q_0 e^{-t/\tau}$$

$$V(t) = V_{C0} e^{-t/\tau}$$

$$V_C(t) = 80 e^{-t/\tau}$$

$$1 = 80 e^{-10/\tau} \Rightarrow \frac{1}{80} = e^{-10/\tau} \Rightarrow -\frac{10}{\tau} = \ln\left(\frac{1}{80}\right)$$


$$\tau = \frac{-10}{\ln(1/80)} = \frac{-10}{-4.382} = 2.28\text{s}$$

$$\tau = 2.28\text{s}$$

b) Find V_C ? at $t = 17\text{s}$. $V_C = 80 e^{-17/2.28} = 80 e^{-7.45} = 4.65 \times 10^{-2} \text{ V}$


(11)

$$V_C = 46.5 \text{ mV}$$

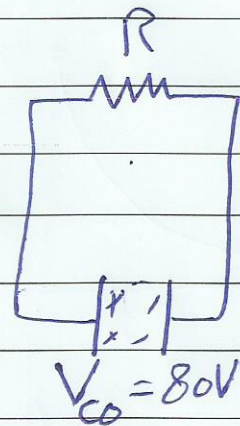

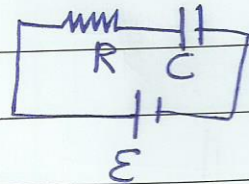Problem (27-15)

Find t in terms of τ
for C to reach 89% Q_f



$$Q(t) = CE(1 - e^{-t/\tau})$$

$$\frac{89}{100}(CE) = CE(1 - e^{-t/\tau})$$

$$0.89 = 1 - e^{-t/\tau} \Rightarrow e^{-t/\tau} = 1 - 0.89 = 0.11$$

$$-\frac{t}{\tau} = \ln 0.11 \Rightarrow t = -\tau \ln 0.11$$

$$t = 2.21\tau \text{ for } Q = 0.89 Q_{\max}$$

b)*

Find t ? for $Q = 99\% Q_0$


$$0.99CE = CE(1 - e^{-t/\tau}) \Rightarrow$$

$$t = \tau \ln(0.01)$$

$$t = 4.6\tau \text{ for } Q = 0.99 Q_{\max}$$

Problem (27-30)

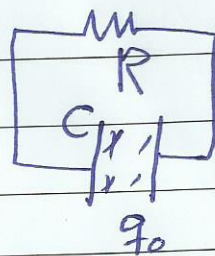a) Find t ? for the Capacitor to
lose the first 25% of its q_0



$$q(t) = q_0 e^{-t/\tau}$$

$$0.75q_0 = q_0 e^{-t/\tau} \Rightarrow 0.75 = e^{-t/\tau}$$

$$-\frac{t}{\tau} = \ln 0.75 \Rightarrow t = -\tau \ln 0.75$$

$$t = 0.29\tau \text{ to lose 25\%}$$

b) Find t ? to lose 50% q_0

$$0.5q_0 = q_0 e^{-t/\tau} \Rightarrow t = -\tau \ln 0.5 = 0.69\tau \text{ to lose 50\%}$$

c) Find t ? to lose one third of its q_0 .

$$\frac{2}{3}q_0 = q_0 e^{-t/\tau} \Rightarrow t = -\tau \ln\left(\frac{2}{3}\right) = 0.41\tau \text{ to lose } \frac{1}{3}q_0$$