


# Chapter 27: Circuits

•  $\mathcal{E} = \frac{dW}{dq}$ , 1 Volt = 1 J/sec  $\Rightarrow$

ideal battery ( $r_{in} = 0$ )  
Real battery ( $r_{in}$ )


$\Rightarrow$  Battery

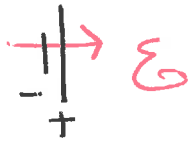- supplies energy  $\rightarrow$  current with emf
- absorbs energy  $\rightarrow$  current & emf are in opposite direction



• Loop Rule  $\Rightarrow$  conservation of energy  $\Rightarrow$  closed loop  $\sum V = 0$

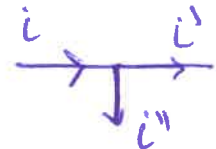• Junction Rule  $\Rightarrow$  conservation of charge



$i = i' + i''$

$\Rightarrow$  Series Resistances  $R_{eq} = \sum_{i=1}^N R_i$

Parallel Resistances  $\frac{1}{R_{eq}} = \sum_{i=1}^N \frac{1}{R_i}$

\* RC - Circuits,  $\tau_c \equiv$  capacitive time constant = RC



• charging a capacitor

$q = C\mathcal{E}(1 - e^{-t/RC})$


$V_c = \mathcal{E}(1 - e^{-t/RC})$

• Discharging a capacitor

$V_c = \mathcal{E} e^{-t/RC}$

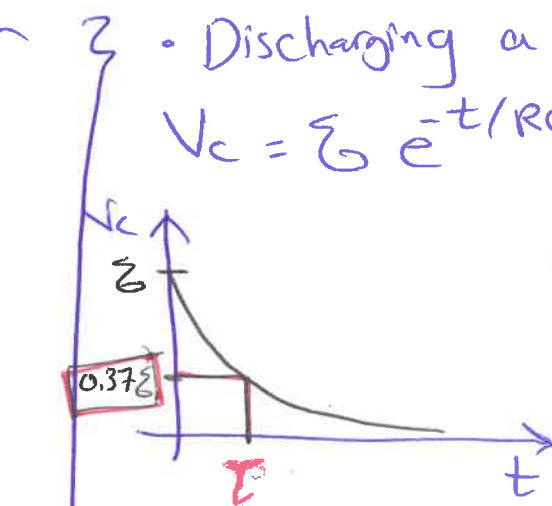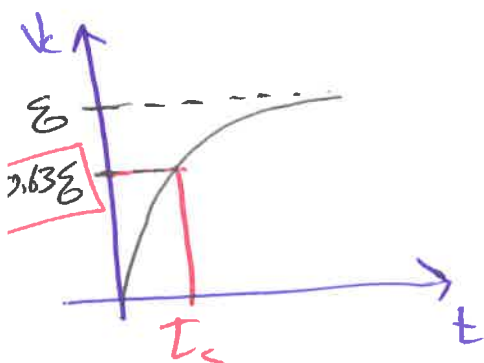

$t_{1/2} = \tau \ln 2$

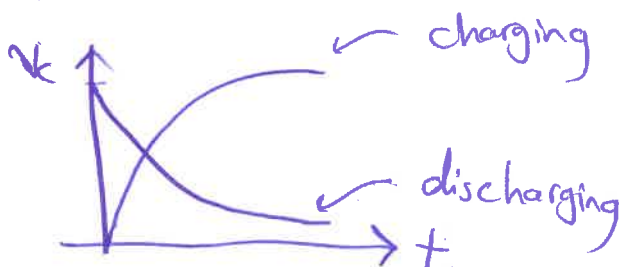

27-2 In the below figure, the ideal batteries have emfs

$\mathcal{E}_1 = 12V$  and  $\mathcal{E}_2 = 0.500\mathcal{E}_1$ , and the resistances are each  $4.00\Omega$ .


What is the current in a) resistance 2 and b) resistance 3?

• Junction Rule  $\Rightarrow i_1 = i_2 + i_3$

• Loop Rule  $\Rightarrow$

$$\textcircled{1} \quad \mathcal{E}_1 - i_1 R_1 - i_3 R_3 = 0$$
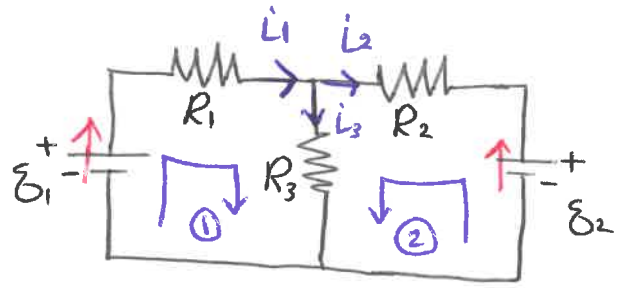
$$\textcircled{2} \quad \mathcal{E}_2 + i_2 R_2 - i_3 R_3 = 0$$



$$\longrightarrow i_1 = i_2 + i_3$$

$$12 - i_2 R_1 - i_3 R_1 - i_3 R_3 = 0$$

$$6 + i_2 R_2 - i_3 R_3 = 0$$

$$\longrightarrow 12 - 4i_2 - 8i_3 = 0$$

$$6 + 4i_2 - 4i_3 = 0$$

$$\longrightarrow 18 = 12i_3$$


$$\boxed{i_3 = 1.5 \text{ A}} \text{ downward}$$

$$\Rightarrow 6 + 4i_2 - 4(1.5) = 0$$

$$\boxed{i_2 = 0 \text{ A}}$$

$$\boxed{i_1 = 1.5 \text{ A, rightward}}$$

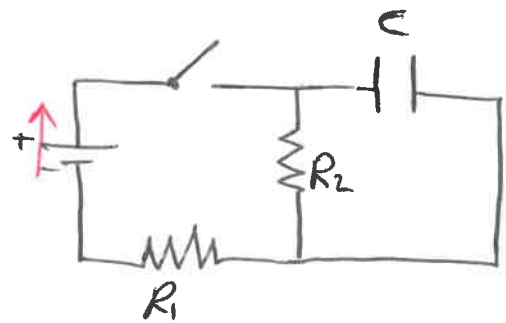27-9 In the below figure,  $R_1 = 10.0 \text{ k}\Omega$ ,  $R_2 = 15.0 \text{ k}\Omega$ ,  $C = 0.40 \text{ MF}$  and the ideal battery has emf  $\mathcal{E} = 20.0 \text{ V}$ . First, the switch is closed a long time so that the steady state is reached. Then the switch is opened at time  $t=0$ . For resistor 2 and at time  $t=4.0 \text{ ms}$ , what are a) the current, b) the rate at which the current is changing, and c) the rate at which the dissipation rate is changing?



a)  $V_{\text{Capacitor}} = V_{R_2}$  "parallel" steady state

$$\Rightarrow V_{\text{Capacitor}} = \frac{\mathcal{E} R_2}{R_1 + R_2} = \frac{20 (15)}{10 + 15}$$


(open circuit)

$$i = \frac{\mathcal{E}}{R_1 + R_2}$$

$$V_{R_2} = i R_2$$

$$V_{\text{Capacitor}} = 12 \text{ V}$$

• Switch is opened

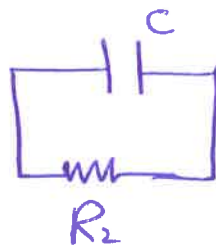

Discharging a capacitor

$$i = \frac{dq}{dt} = \left( -\frac{q_0}{RC} \right) e^{-t/RC}$$

$$\begin{aligned} \underline{OR} \quad V_{\text{Discharging}} &= V_0 e^{-t/RC} \\ &= 12 e^{-(4 \times 10^{-3} / [15 \times 10^3 \times 0.4 \times 10^{-6}])} \end{aligned}$$

$$V = 6.16 \text{ V}$$

• Using ohm's Law  $\Rightarrow i = \frac{V}{R_2} = \frac{6.16}{15 \times 10^3} = 4.11 \times 10^{-4} \text{ A}$

b) The rate at which the current is changing

$$\frac{di}{dt} = \frac{d^2q}{dt^2} \Rightarrow q(t) = CV_0 e^{-t/\tau}$$

$$i = \frac{dq(t)}{dt} = \frac{-CV_0}{\tau} e^{-t/\tau}$$

$$\frac{d^2q}{dt^2} = \frac{CV_0}{\tau^2} e^{-t/\tau}$$



$$\frac{di}{dt} = \frac{0.4 \times 10^{-6} \times 12}{(15 \times 10^3 \times 0.4 \times 10^{-6})^2} e^{-(4 \times 10^{-3} / (15 \times 10^3 \times 0.4 \times 10^{-6}))}$$

$$\frac{di}{dt} = 0.0685 \text{ A/s} = 68.5 \text{ mA/s}$$

c)  $P = i^2 R \Rightarrow \frac{dP}{dt} = \frac{d}{dt}(i^2 R) = 2iR \frac{di}{dt}$

$$\frac{dP}{dt} = 2 \times 4.11 \times 10^{-4} \times 15 \times 10^3 \times 68.5 \times 10^{-3} = 0.845 \frac{\text{W}}{\text{Sec}}$$

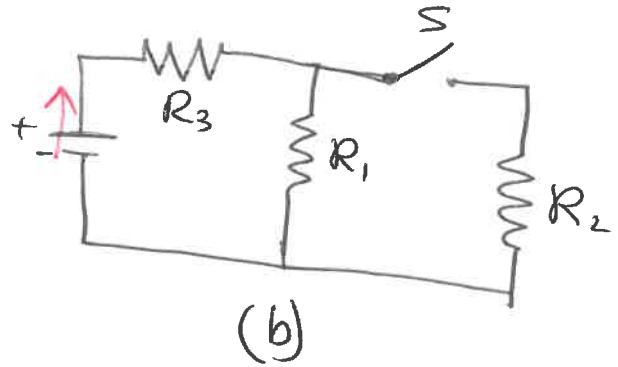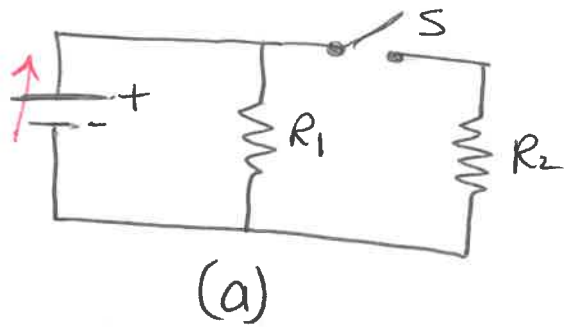27-14 The resistances in the below figure are all  $4.0\ \Omega$ , and the batteries are ideal  $12\text{ V}$  batteries. a) When switch  $S$  in Figure (a) is closed, what is the change in the electric potential  $V_1$  across resistor 1, or does  $V_1$  remain the same? b) When switch  $S$  in figure part b is closed, what is the change in  $V_1$  across resistor 1, or does  $V_1$  remain the same?



a) By loop theorem, it remains the same  
 $R_1$  in parallel with  $R_2$

b) Switch is closed  $R_1, R_2$  parallel and their combination is in series with  $R_3$

$$R_{123} = R_3 + \frac{R_1 \times R_2}{R_1 + R_2} = 6.0\ \Omega$$

$$R_{12} = \frac{R_1 R_2}{R_1 + R_2} = 2\ \Omega \quad \Rightarrow \quad i = \frac{12\text{ V}}{6\ \Omega} = 2\text{ A}$$

$$V_{R_3} + V_{R_{12}} = 12 \quad \Rightarrow$$


$$V_{R_3} = i R_3 = 2 \times 4 = 8\text{ V}$$

$$V_{R_{12}} = i R_{12} = 2 \times 2 = 4\text{ V}$$

$\Rightarrow R_1$  and  $R_2$  in parallel

$$V_{R_1} = V_{R_2} = 4\text{ V}$$

- Switch is open

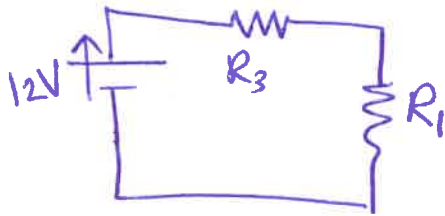

$$12 = V_{R_3} + V_{R_1}$$
$$\Rightarrow V_{R_3} = V_{R_1} = 6V$$


$$\text{Since } R_1 = R_3$$

$$\Rightarrow V_{R_1} \text{ "switch is open"} = 6V$$

$$V_{R_1} \text{ "switch is closed"} = 4V$$

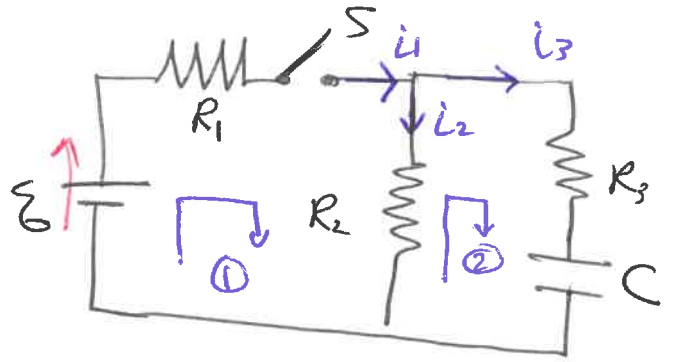27-47 In the below circuit,  $\mathcal{E} = 1.2 \text{ kV}$ ,  $C = 6.5 \mu\text{F}$ ,

$R_1 = R_2 = R_3 = 0.73 \text{ M}\Omega$ . with  $C$  completely uncharged, switch  $S$  is suddenly closed (at  $t=0$ ). At  $t=0$ , what are a) current  $i_1$  in resistor 1 b) current  $i_2$  in resistor  $R_2$ , and c) current  $i_3$  in resistor 3? At  $t=\infty$  (that is, after many time constants), what are  $i_1$ ,  $i_2$  and  $i_3$ ? What is the potential difference  $V_2$  across resistor 2 at  $t=0$  and  $t=\infty$ ?



\* Junction Rule

$$i_1 = i_2 + i_3$$

\* Loop Rule

$$\textcircled{1} \quad 1.2 \text{ kV} = 0.73 \text{ M}\Omega i_1 + 0.73 \text{ M}\Omega i_2$$

$$\textcircled{2} \quad 0 = 0.73 \text{ M}\Omega i_3 - 0.73 \text{ M}\Omega i_2$$

$$\xrightarrow{\text{use } i_3 = i_1 - i_2} \quad 1.2 \text{ kV} = 0.73 \text{ M}\Omega i_1 + 0.73 \text{ M}\Omega i_2$$

$$- \left( 0 = 0.73 \text{ M}\Omega i_1 - 2(0.73 \text{ M}\Omega) i_2 \right)$$

$$\xrightarrow{\hspace{10em}} \quad 1.2 \text{ kV} = 3(0.73 \text{ M}\Omega) i_2$$

$$i_2 = 0.55 \text{ mA}$$

$$i_1 = 2 i_2 = 1.1 \text{ mA}$$

$$i_3 = 0.55 \text{ mA}$$

$t=0$

$$V_{R_2} = i R_2$$


$$\text{at } t=0, V_{R_2} = 402 \text{ V}$$

$$\text{at } t=\infty, V_{R_2} = 598.6 \text{ V}$$

At  $t=\infty$ ,  $i_3 = 0$  (Capacitor is fully charged  
current = 0 "open circuit")

$$i_1 = i_2 = \frac{1.2 \text{ kV}}{2(0.73 \text{ M}\Omega)} = 0.82 \text{ mA}$$

P20-27) In Fig,  $\varepsilon_1 = 12.0 \text{ V}$ ,  $\varepsilon_2 = 12.0 \text{ V}$ ,  $R_1 = 100 \ \Omega$ ,  $R_2 = 200 \ \Omega$ , and  $R_3 = 300 \ \Omega$ . One point of the circuit is grounded ( $V = 0$ ). What are the (a) size and (b) direction (up or down) of the current through resistance 1, the (c) size and (d) direction (left or right) of the current through resistance 2, and the (e) size and (f) direction of the current through resistance 3? (g) What is the electric potential at point A?

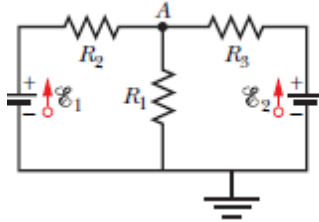

20. (a) Using the junction rule ( $i_1 = i_2 + i_3$ ) we write two loop rule equations:

$$\varepsilon_1 - i_2 R_2 - (i_2 + i_3) R_1 = 0$$

$$\varepsilon_2 - i_3 R_3 - (i_2 + i_3) R_1 = 0.$$

Solving, we find  $i_2 = 0.0182 \text{ A}$  (rightward, as was assumed in writing the equations as we did),  $i_3 = 0.02545 \text{ A}$  (leftward), and  $i_1 = i_2 + i_3 = 0.04365 \text{ A}$  (downward).

(b) The direction is downward. See the results in part (a).

(c)  $I_2 = 0.0182 \text{ A}$ . See the results in part (a).

(d) The direction is rightward. See the results in part (a).


(e)  $i_3 = 0.0254 \text{ A}$ . See the results in part (a).

(f) The direction is leftward. See the results in part (a).

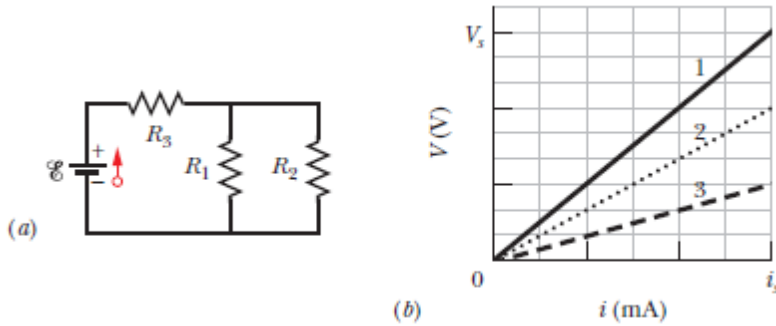(g) The voltage across  $R_1$  equals  $V_A$ :  $(0.0382 \text{ A})(100 \ \Omega) = +4.37 \text{ V}$ .



P56-27) The ideal battery in Fig. 27-39a has emf  $\varepsilon_1 = 10.0 \text{ V}$ . Plot 1 in Fig. 27-39b gives the electric potential difference  $V$  that can appear across resistor 1 of the circuit versus the current  $i$  in that resistor. The scale of the  $V$  axis is set by  $V_s = 18.0 \text{ V}$ , and the scale of the  $i$  axis is set by  $i_s = 3.00 \text{ mA}$ . Plots 2 and 3 are similar plots for resistors 2 and 3, respectively. What is the current in resistor 2?



56. Line 1 has slope  $R_1 = 6.0 \text{ k}\Omega$ . Line 2 has slope  $R_2 = 4.0 \text{ k}\Omega$ . Line 3 has slope  $R_3 = 2.0 \text{ k}\Omega$ . The parallel pair equivalence is  $R_{12} = R_1 R_2 / (R_1 + R_2) = 2.4 \text{ k}\Omega$ . That in series with  $R_3$  gives an equivalence of

$$R_{123} = R_{12} + R_3 = 2.4 \text{ k}\Omega + 2.0 \text{ k}\Omega = 4.4 \text{ k}\Omega.$$


The current through the battery is therefore  $i = \varepsilon / R_{123} = (10 \text{ V}) / (4.4 \text{ k}\Omega) = 2.27 \text{ mA}$  and the voltage drop across  $R_3$  is  $V_3 = i R_3 = (2.27 \times 10^{-3} \text{ A})(2.0 \text{ k}\Omega) = 4.55 \text{ V}$ . Subtracting this (because of the loop rule) from the battery voltage leaves us with the voltage across  $R_2$ :

$$V_2 = \varepsilon - V_3 = 10.0 \text{ V} - 4.55 \text{ V} = 5.45 \text{ V}.$$

Then Ohm's law gives the current through  $R_2$ :

$$i_2 = \frac{V_2}{R_2} = \frac{5.45 \text{ V}}{4.0 \text{ k}\Omega} = 1.4 \text{ mA}.$$

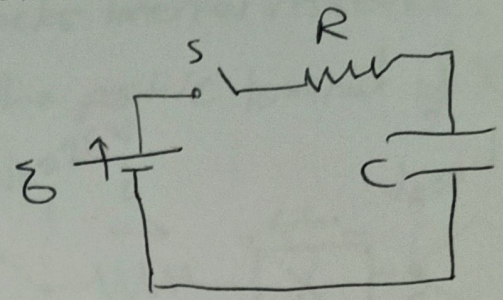27-21) Switch S in the below circuit is closed at  $t=0$ , to begin charging an initially uncharged capacitor of capacitance  $C = 49.0 \mu\text{F}$  through a resistor of resistance  $R = 32.0 \Omega$ . At what time is the potential across the capacitor equal to that across the resistor?



$$V_R = V_C$$

$\Rightarrow t_{1/2}$  "Half time"

$$t_{1/2} = \tau \ln 2 = RC \ln 2$$

$$t_{1/2} = (32 \Omega)(49 \times 10^{-6} \text{F}) \ln 2 = 1.09 \times 10^{-3} \text{ sec}$$

$$t = 1.09 \text{ ms}$$

$$\text{or } V_C = V_R$$

$$\mathcal{E}(1 - e^{-t/\tau}) = \mathcal{E} e^{-t/\tau}$$

$$1 = 2 e^{-t/\tau}$$


$$\frac{1}{2} = e^{-t/\tau}$$

$$\ln \frac{1}{2} = -\frac{t}{\tau}$$

$$-\ln 2 = -\frac{t}{\tau}$$

$$t = \tau \ln 2$$

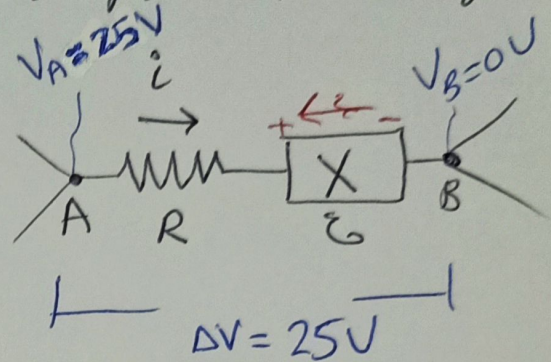27-33 In the below figure, circuit section AB absorbs energy at a rate of 50W when current  $i = 2.0\text{A}$  through it is in the indicated direction. Resistance  $R = 2.0\ \Omega$ . (a) What is the potential difference between A and B? Emf device X lacks internal resistance. (b) What is its emf? (c) Is point B connected to the positive terminal of X or to the negative terminal?



(a)  $P = i \Delta V$

50 watt = 2.0A  $\Delta V$

$\Delta V = 25.0\text{V}$

$V_A - V_B = 25\text{V}$

(b)  $V_A - V_B = 25.0\text{ volts}$


$-iR - \mathcal{E} = 25$

A = Higher V  
B = Lower V

$\mathcal{E} = 25 - iR = 25 - [2 \times 2] = 21\text{V}$

(c) point B connected to the negative terminal of X

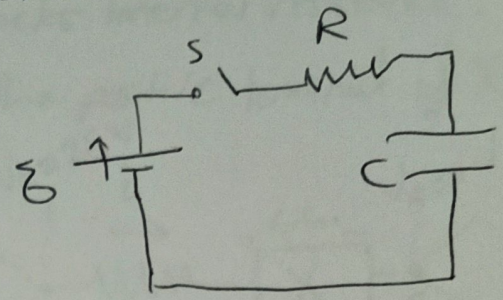27-21) Switch S in the below circuit is closed at  $t=0$ , to begin charging an initially uncharged capacitor of capacitance  $C = 49.0 \mu\text{F}$  through a resistor of resistance  $R = 32.0 \Omega$ . At what time is the potential across the capacitor equal to that across the resistor?



$$V_R = V_C$$

$\Rightarrow t_{1/2}$  "Half time"

$$t_{1/2} = \tau \ln 2 = RC \ln 2$$

$$t_{1/2} = (32 \Omega)(49 \times 10^{-6} \text{F}) \ln 2 = 1.09 \times 10^{-3} \text{ sec}$$

$$t = 1.09 \text{ ms}$$

$$\text{or } V_C = V_R$$

$$\mathcal{E}(1 - e^{-t/\tau}) = \mathcal{E} e^{-t/\tau}$$

$$1 = 2 e^{-t/\tau}$$

$$\frac{1}{2} = e^{-t/\tau}$$

$$\ln \frac{1}{2} = -\frac{t}{\tau}$$

$$-\ln 2 = -\frac{t}{\tau}$$

$$t = \tau \ln 2$$