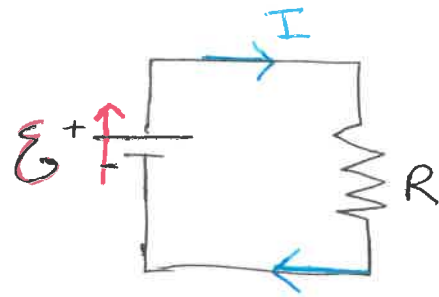


# Chapter 27: Circuits

- Single loop circuit

Electromotive force of the power supply " $\mathcal{E}$ "

- emf device "Battery" does work on charges to maintain a potential difference between its output terminals.



$\Rightarrow dW$  is the work the device does to force (move) positive charge  $dq$  from the negative to the positive terminal [inside the source].

emf (work per unit charge) of the device is

$$\mathcal{E} = \frac{dW}{dq}, \quad [\mathcal{E}] = \frac{J}{C} = \text{volt}$$

emf device

Ideal emf device

Lacks any internal resistance  
The potential difference between its terminals is equal to the emf.


Real emf device

- Has internal Resistance
- The potential difference between its terminals is equal to the emf only if there is no current through the device.

• Calculating current in a single-loop circuit "Energy method"

$$\Rightarrow P = i^2 R \quad \text{"Resistive Dissipation"}$$

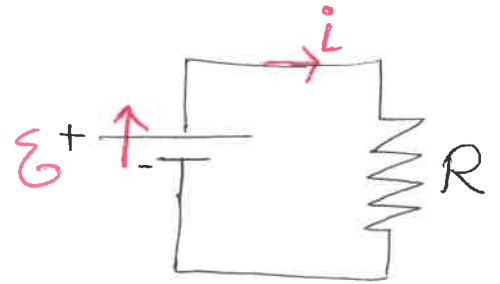$i^2 R dt \equiv$  Amount of energy will appear in the resistor in a time interval  $dt$ .



• During the same interval, a charge  $dq = i dt$  will have moved through battery, and the work that the battery will have done on this charge is

$$dW = \mathcal{E} dq = \mathcal{E} i dt$$

$P_{\mathcal{E}} = i\mathcal{E}$  "The amount of power supplied by emf device to the circuit"

By using Conservation of Energy principle  $\Rightarrow$


$$\mathcal{E} i dt = i^2 R dt \quad \text{"} P_{\mathcal{E}} (\text{supplied}) = P_R (\text{consumed}) \text{"}$$

$$i = \frac{\mathcal{E}}{R}$$

single-loop circuit current for ideal power supply

\* Real power supply "Has internal resistance"

$$i = \frac{\mathcal{E}}{R+r}$$

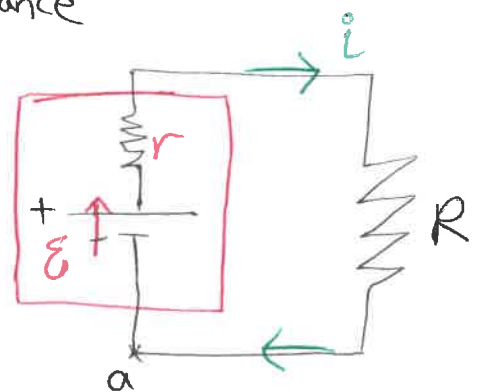

$$\mathcal{E} - ir - iR = 0$$

$$i = \frac{\mathcal{E}}{r+R}$$

• Potential difference between two points ( $V_{ab} = V_a - V_b$ )

Loop Rule  $\Rightarrow$  The algebraic sum of the changes in potential encountered in a complete traversal of any loop of a circuit - must be zero

Resistance Rule  $\Rightarrow$  For a move through a resistance in the direction of the current, the change in potential is  $-iR$ ; in the opposite direction it is  $+iR$

Emf Rule  $\Rightarrow$  For a move through an ideal emf device in the direction of the emf arrow, the change in potential is  $+\mathcal{E}$ , in the opposite direction it is  $-\mathcal{E}$ .

• Resistances in Series

1) The same current is passing through each resistor.

$$i = i_1 = i_2 = i_3$$



2) By using loop Rule

$$\mathcal{E} - iR_1 - iR_2 - iR_3 = 0$$

$$i = \frac{\mathcal{E}}{R_1 + R_2 + R_3}$$

$$\Rightarrow i R_{eq} = \mathcal{E} \Rightarrow i = \frac{\mathcal{E}}{R_{eq}}$$

$$R_{eq} = R_1 + R_2 + R_3$$

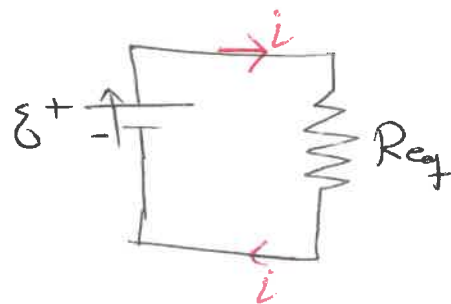
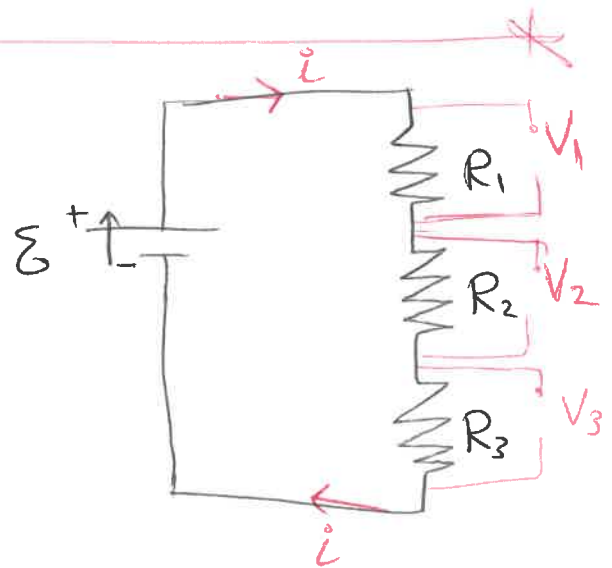


Ohm's law  $\Rightarrow R = \frac{V}{i}$

$$R_{eq} = \sum_{j=1}^N R_j \quad \text{"N-resistances in series"}$$
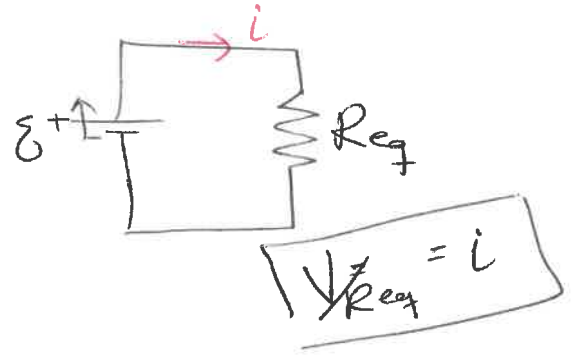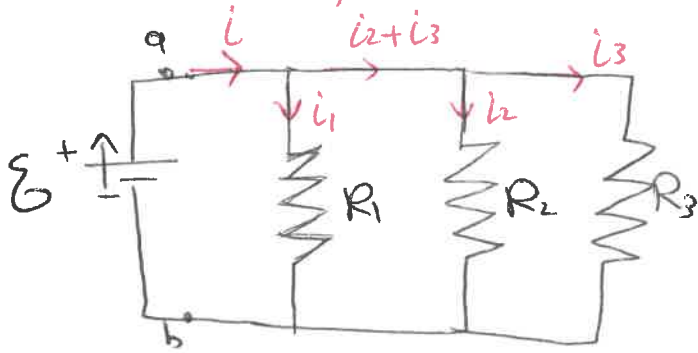
# Resistances in Parallel - Multiloop Circuit

Junction Rule  $\Rightarrow$  The sum of the currents entering any junction must be equal to the sum of the currents leaving that junction



$$\textcircled{1} V = V_1 = V_2 = V_3$$

$$i_1 = \frac{V}{R_1}, \quad i_2 = \frac{V}{R_2}, \quad i_3 = \frac{V}{R_3}$$

$$V_{ab} = V$$

$$\textcircled{2} i = i_1 + i_2 + i_3$$

$$i = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = V \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{eq}} = \sum_{j=1}^N \frac{1}{R_j} \quad N\text{-Resistors in parallel}$$

# • Multi-loop circuits →


⇒ Kirchhoff's rules

1] Junction Rule ⇒ Conservation of charge

The sum of the currents entering any junction must be equal to the sum of currents leaving that junction.

2] Loop Rule ⇒ Conservation of energy

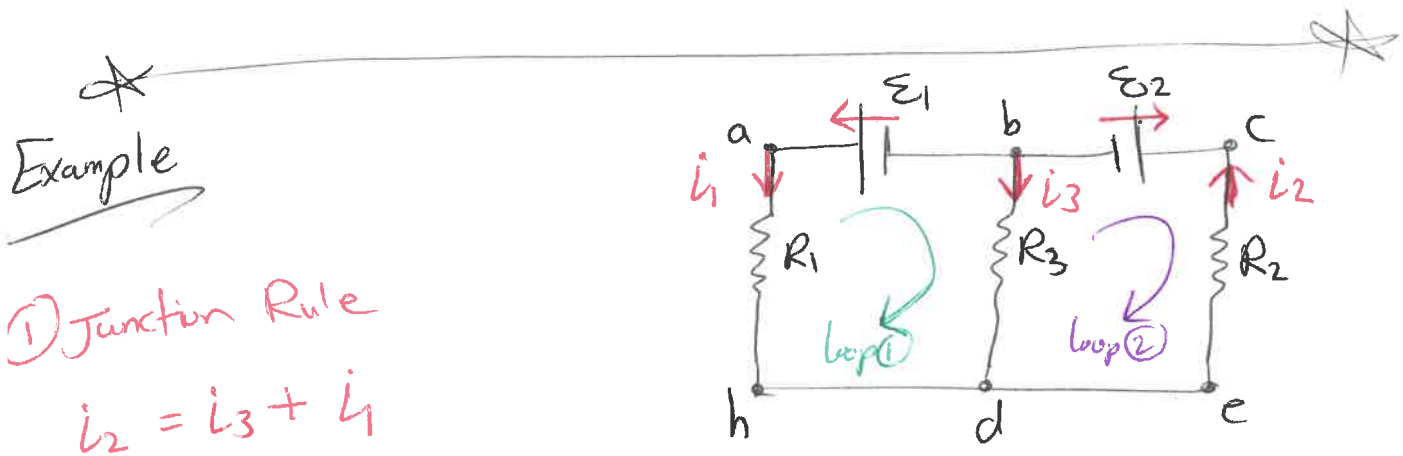The algebraic sum of the changes in potential encountered in a complete traversal of any loop of a circuit must be zero  $\sum V = \text{Zero}$  closed loop



1] Junction Rule

$$i_2 = i_3 + i_1$$

2] Loop Rule

$$\sum V_{abdha} = -\epsilon_1 - i_3 R_3 + i_1 R_1 = \text{Zero} \quad \text{"loop 1"}$$


$$\sum V_{bcdcb} = +\epsilon_2 + i_2 R_2 + i_3 R_3 = \text{Zero} \quad \text{"loop 2"}$$

$$\Rightarrow \sum V_{aceha} = \text{Zero} = -\epsilon_1 + \epsilon_2 + i_2 R_2 + i_1 R_1 = \text{Zero}$$
$$= \text{loop 1} + \text{loop 2}$$

• Sample problem 27.01: Single loop circuit with two Real batteries

$$\mathcal{E}_1 = 4.4\text{V}, \mathcal{E}_2 = 2.1\text{V}$$
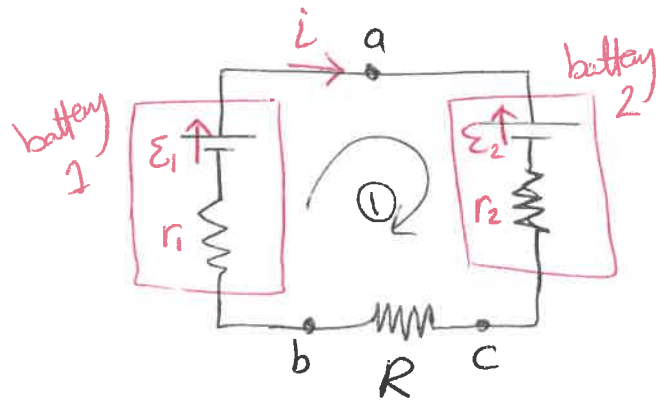
$$r_1 = 2.3\Omega, r_2 = 1.8\Omega, R = 5.5\Omega$$



(a) What is the current in the circuit?

$$\text{loop ①} \Rightarrow \mathcal{E}_1 - \mathcal{E}_2 - i r_2 - i R - i r_1 = 0$$

$$i = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R + r_1 + r_2} = \frac{(4.4 - 2.1)\text{V}}{(5.5 + 2.3 + 1.8)\Omega} = 0.24\text{A}$$

$$i = 240\text{mA}$$

(b) What is the potential difference between the terminals of battery 1?

$$V_{ab} = V_a - V_b$$

$$V_{ab} = V_a - \mathcal{E}_1 + i r_1 - V_b$$

$$V_a - V_b = +\mathcal{E}_1 - i r_1 = 4.4\text{V} - 0.24\text{A}(2.3\Omega)$$

$$V_a - V_b = +3.8\text{V}$$

$$V_{ab} = -V_{ba}$$

$$\bullet V_b - V_a = V_b - i r_1 + \mathcal{E}_1 - V_a$$

$$V_b - V_a = i r_1 - \mathcal{E}_1 = -3.8\text{V}$$

$$\bullet V_{ac} = V_a - V_c = V_a - \mathcal{E}_2 - i r_2 - V_c$$



$$V_a - V_c = \mathcal{E}_2 + i r_2 = (2.1) + (0.24 \times 1.8) = 2.53\text{V}$$

Potential difference across battery 2

# RC - Circuits:-

Charging a Capacitor;

Connecting (S to a)

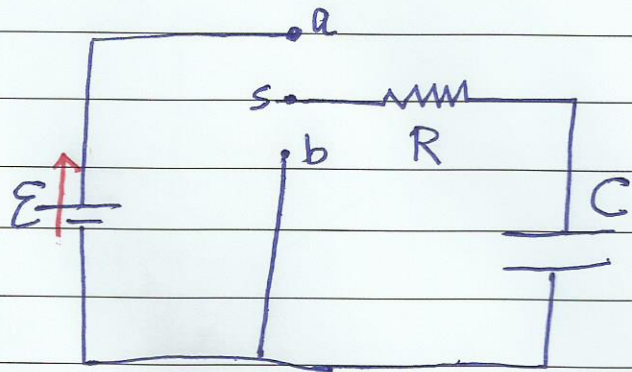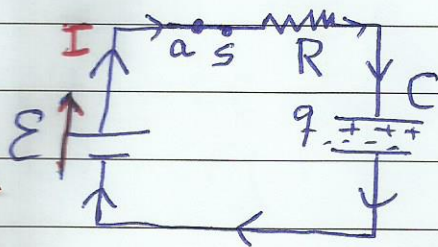

Remember  $V_C = \frac{q}{C}$   
 $V_R = RI$

$q_0 = 0$  initial charge on the Capacitor,  
 the charge will increase gradually on the Capacitor to  
 reach  $q_{max}$  after a long time

$$q_{max} = C\varepsilon$$

To find the charge on the Capacitor at any time ....

$\sum V = 0$  around the closed loop.

$$\varepsilon - RI + \frac{q}{C} = 0, \quad I = \frac{dq}{dt}$$

$$\varepsilon = \frac{q}{C} + R \frac{dq}{dt}$$

$$\varepsilon - \frac{q}{C} = R \frac{dq}{dt} \Rightarrow \frac{\varepsilon C - q}{C} = R \frac{dq}{dt}$$

$$\frac{\varepsilon C - q}{RC} = \frac{dq}{dt} \Rightarrow \frac{q - \varepsilon C}{RC} = (-) \frac{dq}{dt}$$

$$\frac{dq}{q - \varepsilon C} = (-) \frac{dt}{RC}$$

integrate from  $t=0 \rightarrow t=t$

$$\int_0^q \frac{dq}{q - \varepsilon C} = (-) \frac{1}{RC} \int_0^t dt$$

$$\ln [q - \varepsilon C]_0^q = -\frac{t}{RC}$$

$$\ln(q - \varepsilon C) - \ln(-\varepsilon C) = -\frac{t}{RC}$$

$$\ln\left(\frac{Q - CE}{-CE}\right) = -\frac{t}{RC}$$


$$\frac{Q - CE}{-CE} = e^{-t/RC}$$

$$Q - CE = -CE e^{-t/RC}$$

$$Q(t) = CE - CE e^{-t/RC}$$

$$Q(t) = CE(1 - e^{-t/RC}) \quad \textcircled{I}$$

charging a capacitor

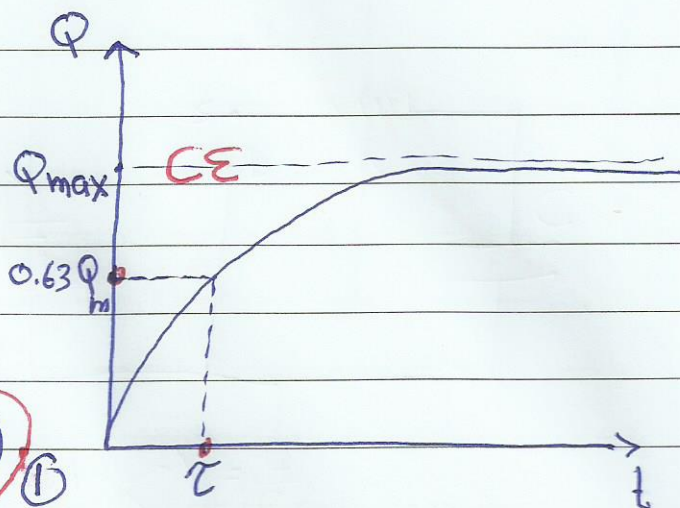

The time constant of the circuit =  $RC$   
 $\Omega \cdot F = \text{sec.}$

$$\tau = RC$$

$$Q(t) = CE(1 - e^{-t/\tau}) \quad \textcircled{II}$$


1) to find  $Q_{\max}$ , put  $t \rightarrow \infty$   $Q_{\max} = CE$

2) Find  $Q$  at  $t = \tau \Rightarrow Q(\tau) = CE(1 - e^{-1})$   
 $= CE(1 - 0.37)$

$$Q(\tau) = 0.63 CE = 0.63 Q_{\max}$$

$\Rightarrow$  At  $t = \tau \Rightarrow$  the charge on the capacitor will reach  $0.63 Q_{\max}$
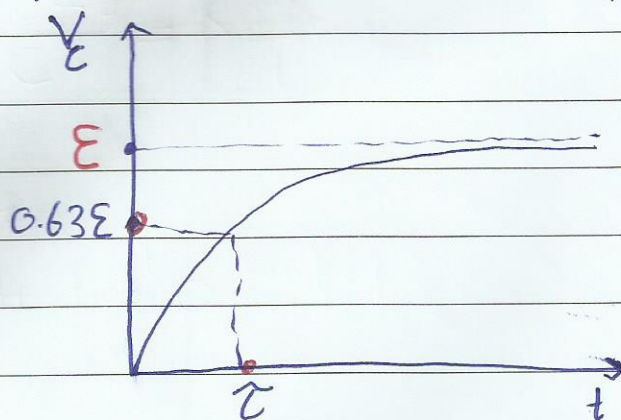
$$V_c(t) = \frac{Q(t)}{C} = \varepsilon(1 - e^{-t/\tau})$$



Find the current at any time?

$$I = \frac{dQ}{dt} = \frac{d}{dt} [CE(1 - e^{-t/RC})]$$

$$= 0 - CE(-\frac{1}{RC}) e^{-t/RC}$$

$$I(t) = \frac{\varepsilon}{R} e^{-t/RC}$$

charging C

$$\frac{\varepsilon}{R} = I_0 \text{ at } t=0$$

$$V_R = RI$$



$$V_R(t) = \varepsilon e^{-t/RC}$$



$$I(t) = \frac{\mathcal{E}}{R} (e^{-t/\tau})$$

$$V_R(t) = \mathcal{E} e^{-t/\tau}$$

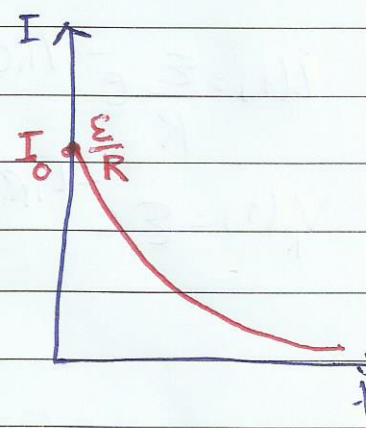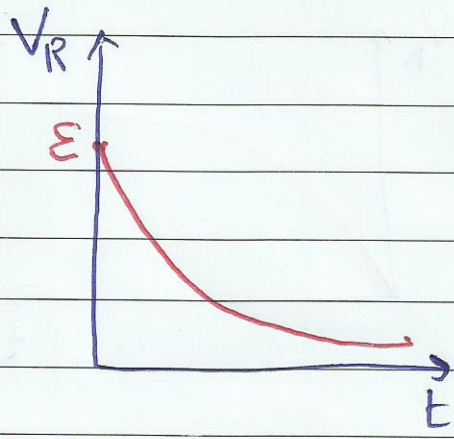as  $t \rightarrow \infty$   $I = 0$   
 $V_R = 0$




### Discharging a Capacitor

Connect  $b \rightarrow S \rightarrow b \rightarrow S$

The charge will move from (+) plate  $\rightarrow$  (-) plate through R

$$q_0 = C\mathcal{E} = q_m$$
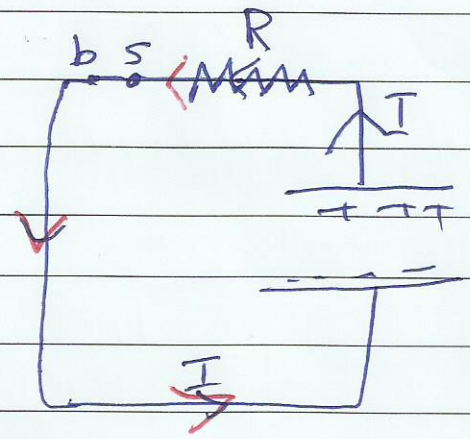
$$q_{\text{finally}} = 0 \text{ as } t \rightarrow \infty$$



find  $q$  at any time.

$$RI + \frac{q}{C} = 0 \Rightarrow R \frac{dq}{dt} = -q/C$$

$$\frac{dq}{q} = -\frac{dt}{RC} \quad \text{integrate}$$

$$\int_{q_0}^q \frac{dq}{q} = -\frac{1}{RC} \int_0^t dt$$




$$\ln\left(\frac{q}{q_0}\right) = -\frac{t}{RC} \Rightarrow \frac{q}{q_0} = e^{-t/RC}$$

$$q(t) = q_0 e^{-t/RC} \Rightarrow q(t) = q_0 e^{-t/\tau}$$

$$i(t) = \frac{dq}{dt} = q_0 \left(-\frac{1}{RC}\right) e^{-t/RC} = \left(-\frac{q_0}{RC}\right) e^{-t/\tau}$$

$$I_0 = \frac{q_0}{RC}$$

$$I_{\text{finally}} = 0$$

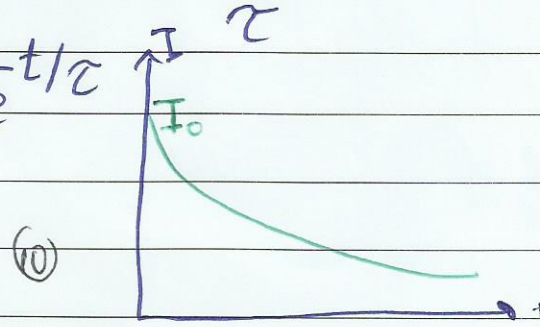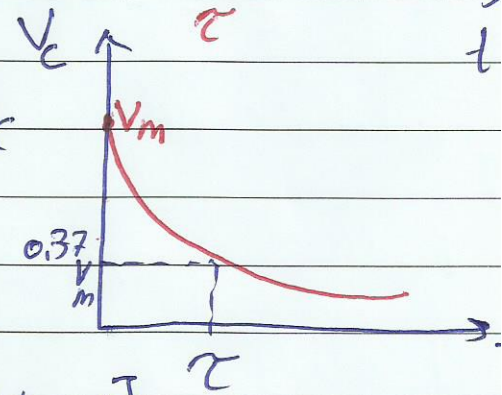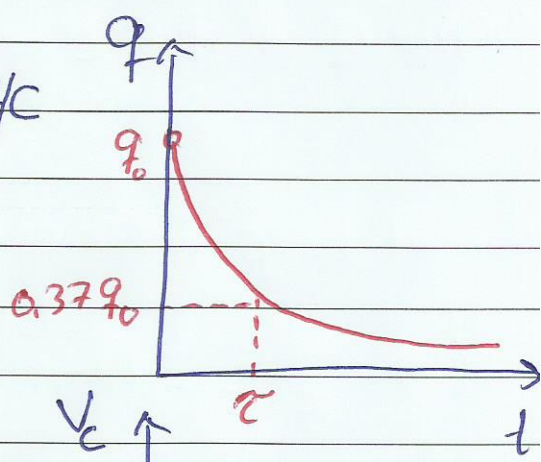


(10)

27-01] In the below figure, the ideal batteries have emfs  $\mathcal{E}_1 = 12\text{ V}$  and  $\mathcal{E}_2 = 4.0\text{ V}$ . What are (a) the current, the dissipation rate in (b) resistor 1 ( $4.0\ \Omega$ ) and (c) resistor 2 ( $8.0\ \Omega$ ), and the energy transfer rate in (d) battery 1 and (e) battery 2? Is energy being supplied or absorbed by (f) battery 1 and (g) battery 2?

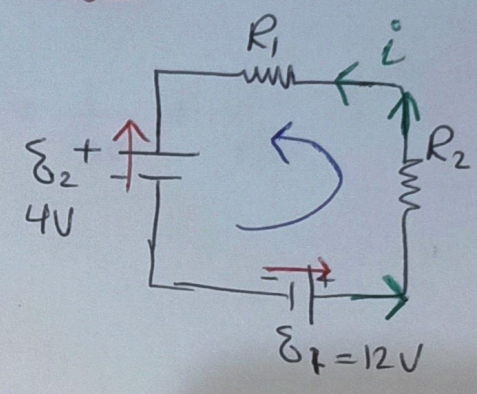(a) Loop Rule  $\Rightarrow$

$$+\mathcal{E}_1 - iR_2 - iR_1 - \mathcal{E}_2 = 0$$

$$i = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R_1 + R_2} = \frac{(12 - 4)\text{ V}}{(4 + 8)\ \Omega} = 0.67\text{ A}$$



$i_1 = i_2 = i$   
 $R_1$  and  $R_2$  in series


(b)  $P_{R_1} = i^2 R_1 = (0.67)^2 (4)$

$P_{R_1} = 1.78\text{ watt}$  (thermal power)

(c)  $P_{R_2} = i^2 R_2 = (0.67)^2 (8) = 3.56\text{ watt}$  (thermal power)


(d)  $P_{\mathcal{E}_1} = i \mathcal{E}_1 = (0.67)(12) = 8.04\text{ watt}$

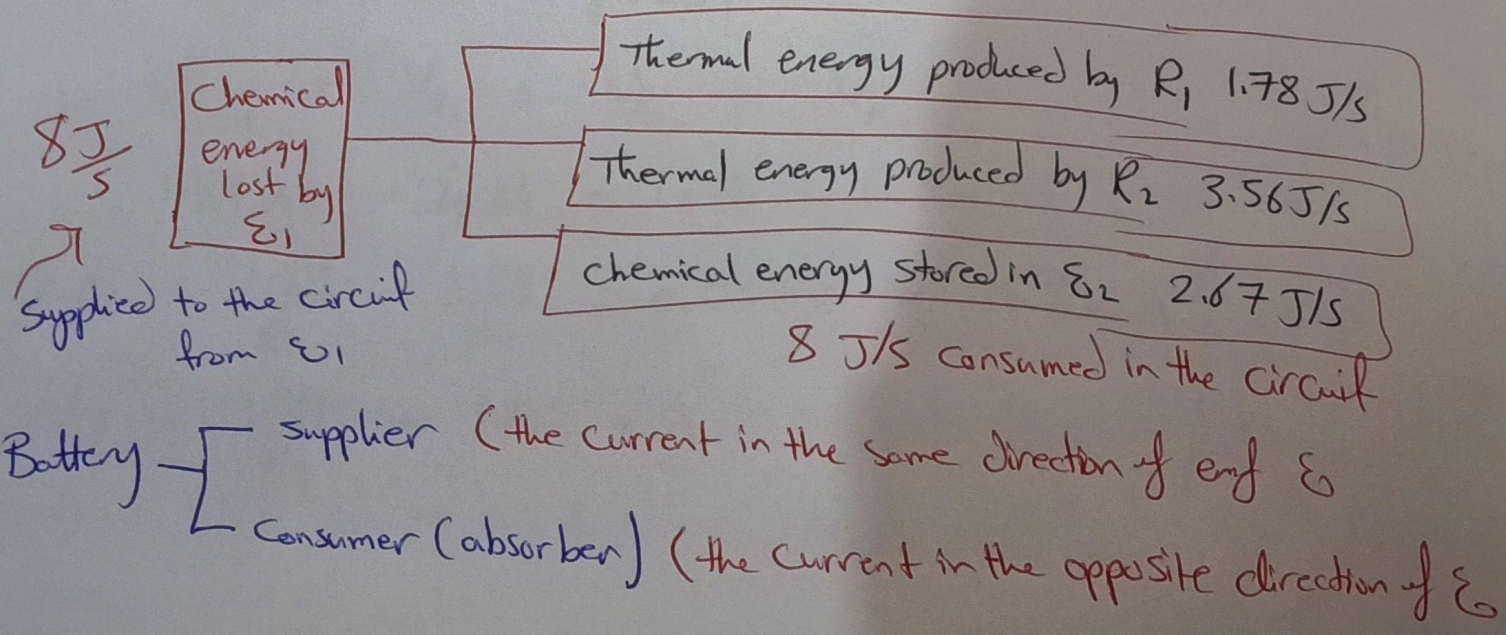(e)  $P_{\mathcal{E}_2} = -i \mathcal{E}_2 = -(0.67)(4) = -2.67\text{ watt}$



27-3  $\mathcal{E}_1 = 1.00\text{V}$ ,  $\mathcal{E}_2 = 3.00\text{V}$ ,  $R_1 = 4\Omega$ ,  $R_2 = 2\Omega$ ,  $R_3 = 5\Omega$

Both batteries are ideal.

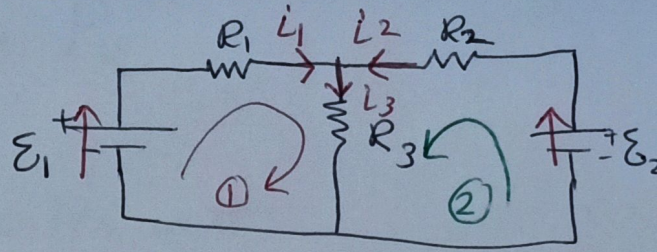

Junction Rule  $\Rightarrow i_1 + i_2 = i_3$

loop ①  $\Rightarrow \mathcal{E}_1 - i_1 R_1 - i_3 R_3 = 0$

loop ②  $\Rightarrow \mathcal{E}_2 - i_2 R_2 - i_3 R_3 = 0$

use  $i_2 = i_3 - i_1 \Rightarrow \mathcal{E}_2 - (i_3 - i_1) R_2 - i_3 R_3 = 0$

$$\mathcal{E}_2 - i_3(R_2 + R_3) + i_1 R_2 = 0$$

$$\mathcal{E}_1 = i_1 R_1 + i_3 R_3$$

$$\mathcal{E}_2 = -i_1 R_2 + i_3 (R_3 + R_2)$$

$$1 = 4i_1 + 5i_3$$

$$(3 = -2i_1 + 7i_3) + 2$$

$$1 = 4i_1 + 5i_3$$

$$+6 = -4i_1 + 14i_3$$

Add  $7 = 19i_3 \Rightarrow i_3 = 0.368\text{A}$

use  $1 = 4i_1 + 5i_3 \Leftrightarrow 1 = 4i_1 + 5(0.368)$

$$i_1 = -0.21\text{A}$$

$$i_2 = i_3 - i_1 = 0.368 - (-0.21) = 0.578\text{A}$$

$i_1 = 0.21\text{A}$  leftward  $\leftarrow$

$i_2 = 0.578\text{A}$  leftward  $\leftarrow$


$i_3 = 0.368\text{A}$  downward  $\downarrow$

⇒ Rate of energy dissipated in R =  $P_R$

$$P_{R_1} = i_1^2 R_1 = (0.21)^2 (4) = 0.176 \text{ watt}$$

$$P_{R_2} = i_2^2 R_2 = (0.578)^2 (2) = 0.668 \text{ watt}$$
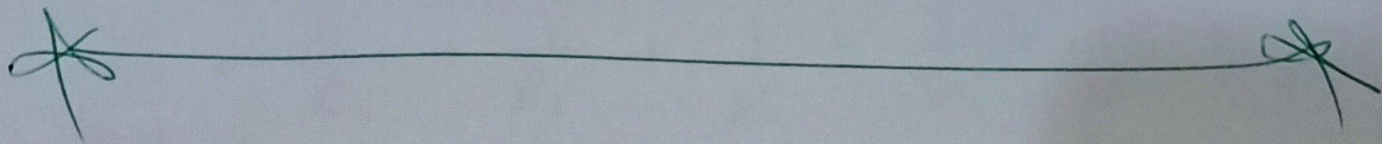
$$P_{R_3} = i_3^2 R_3 = (0.368)^2 (5) = 0.677 \text{ watt}$$




$$P_{\mathcal{E}_1} = i_1 \mathcal{E}_1 = (-0.21)(1) = -0.21 \text{ watt}$$

Absorbed energy

$$P_{\mathcal{E}_2} = i_2 \mathcal{E}_2 = (0.578)(3) = +1.734 \text{ watt}$$

Supplied

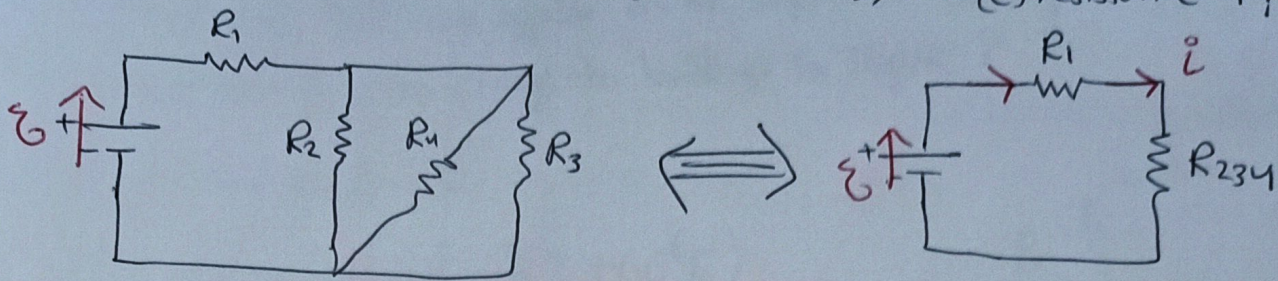27-8]  $R_1 = 100\ \Omega$ ,  $R_2 = R_3 = 50\ \Omega$ ,  $R_4 = 75\ \Omega$ , and the ideal battery has emf  $\mathcal{E} = 12\text{ V}$ . (a) What is the equivalent resistance? What is  $i$  in (b) resistance 1, (c) resistance 2, (d) resistance 3, and (e) resistance 4?



$R_2$ ,  $R_3$  and  $R_4$  are all in parallel

$$\frac{1}{R_{234}} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} = \frac{1}{50} + \frac{1}{50} + \frac{1}{75} = \frac{1.5 + 1.5 + 1}{75}$$

$$R_{234} = \frac{75}{4} = 18.75\ \Omega$$

$R_1$  and  $R_{234}$  are in series

$$R_{eq} = R_1 + R_{234} = 100 + 18.75 = 118.75\ \Omega$$

$$i = \frac{\mathcal{E}}{R_1 + R_{234}} = \frac{12}{118.75} = 0.101\text{ A in } R_1 \text{ and } R_{234}$$

$$\Rightarrow V_{R_{234}} = i R_{234} = (0.101)(18.75) = 1.89\text{ volt}$$

$R_2$ ,  $R_3$  and  $R_4$  in parallel

$$V_{R_{234}} = V_{R_2} = V_{R_3} = V_{R_4}$$

$$1.89\text{ volt} = i_2 R_2 = i_3 R_3 = i_4 R_4$$

$$\Rightarrow i_2 = \frac{1.89}{R_2} = \frac{1.89}{50} = 0.0378 = 37.8\text{ mA}$$

$$i_3 = \frac{1.89}{R_3} = 37.8\text{ mA}$$

$$i_4 = \frac{1.89}{75} = 0.0252 = 25.2\text{ mA}$$


$i_2 + i_3 + i_4 = i$   
Junction Rule

27-40 In an RC series circuit, emf  $\mathcal{E} = 12.0\text{V}$ , resistance  $R = 1.4\text{M}\Omega$  and capacitance  $C = 2.70\mu\text{F}$ . (a) Calculate the time constant. (b) Find the maximum charge that will appear on the capacitor during charging. (c) How long does it take for the charge to build up to  $16.0\mu\text{C}$ ?

(a)  $\tau \equiv$  time constant

$$\tau = RC = (1.4 \times 10^6 \Omega)(2.7 \times 10^{-6} \text{F})$$

$$\tau = 3.78 \text{ sec}$$

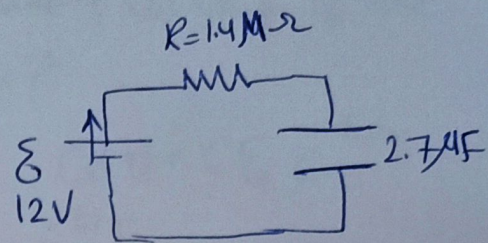

(b)  $Q_{\text{max}}$  at  $t \rightarrow \infty$ ,  $Q(t) = C\mathcal{E}(1 - e^{-t/\tau})$  charging

$$Q_{\text{max}}(t \rightarrow \infty) = C\mathcal{E} = (2.7 \times 10^{-6} \text{F})(12\text{V}) = 32.4 \times 10^{-6} \text{C}$$

$$Q_{\text{max}} = 32.4 \mu\text{C}$$

(c) Find  $t$  when  $Q = 16 \mu\text{C}$ ? [Build up  $\Rightarrow$  charging]

$$Q(t) = Q_{\text{max}}(1 - e^{-t/\tau})$$

$$16 \times 10^{-6} = 32.4 \times 10^{-6}(1 - e^{-t/3.78})$$

$$0.494 = 1 - e^{-t/\tau}$$

$$e^{-t/\tau} = 1 - 0.494 = 0.506$$

$$\frac{-t}{\tau} = \ln(0.506)$$

$$t = -\tau \ln(0.506) = -\tau(-0.68)$$

$$t = 0.68(3.78)$$

$$t = 2.575 \text{ sec}$$

27-18 | A capacitor with an initial potential difference of 80.0 V is discharged through a resistor when a switch between them is closed at  $t=0$ . At  $t=10.0$  sec, the potential difference across the capacitor is 1.00 volt. (a) What is the time constant of the circuit? (b) What is the potential difference across the capacitor at  $t=17.0$  sec?

Discharging of the capacitor  $V_c = \mathcal{E} e^{-t/\tau}$ ,  $Q(t) = C\mathcal{E} e^{-t/\tau}$

(a) at  $t=0$ ,  $V_c = \mathcal{E} = 80.0$  Volts.  $\Rightarrow V_c = 80 e^{-t/\tau}$

at  $t=10$ s,  $V_c = 1$  volt  $\Rightarrow 1 \text{ volt} = 80 \text{ volt } e^{-10/\tau}$

$$\frac{1}{80} = e^{-10/\tau} \Leftrightarrow \frac{-10}{\tau} = -\ln 80$$

$$\tau = \frac{10}{\ln(80)} = 2.28 \text{ sec}$$

$$\tau = 2.28 \text{ s}$$

b)  $V_c = 80 e^{-t/2.28}$

$$V_c(t=17.0 \text{ sec}) = 80 e^{-\frac{17}{2.28}} = 0.0462 \text{ Volts}$$

$$V_c(t=17.0 \text{ sec}) = 46.2 \text{ mV}$$

27-15 What multiple of the time constant  $\tau$  gives the time taken by an initially uncharged capacitor in an RC series circuit to be charged to 89.0% of its final charge?

$$Q(t) = Q_0 (1 - e^{-t/\tau}) \quad , \quad Q_0 \equiv \text{maximum charge} = C\mathcal{E}_0$$

$$0.89Q_0 = Q_0 (1 - e^{-t/\tau})$$

$$0.89 = 1 - e^{-t/\tau}$$

$$e^{-t/\tau} = 1 - 0.89 = 0.11$$

$$-\frac{t}{\tau} = \ln(0.11) = -2.207$$

$$t = 2.207 \tau$$

Find  $t$  in  $Q = 99\% Q_0$

$$0.99Q_0 = Q_0 (1 - e^{-t/\tau})$$

$$1 - 0.99 = e^{-t/\tau}$$

$$t = -\tau \ln(0.01) = 4.6 \tau$$



27-30 A Capacitor with initial charge  $q_0$  is discharged through a resistor. What multiple of the time constant  $\tau$  gives the time the capacitor takes to lose (a) the first 25% of its charge and (b) 50% of its charge? Discharging  $\Rightarrow Q = Q_0 e^{-t/\tau}$

(a) Lose the first 25% of its charge; the remaining charge 75% of its charge

$$Q(t) = Q_0 e^{-t/\tau}$$

$$0.75 Q_0 = Q_0 e^{-t/\tau}$$

$$-\frac{t}{\tau} = \ln(0.75) \Rightarrow t = -\tau \ln(0.75)$$

$$t = 0.29 \tau \text{ to lose the first 25\% of its charge}$$

(b) Lose 50% of its charge

$$0.5 Q_0 = Q_0 e^{-t/\tau}$$

$$t = -\tau \ln(0.5) = 0.69 \tau$$

$$t_{1/2} = \tau \ln 2$$