

# Exp 4: DC circuits

Resistance of a metallic conductor  $R = \frac{\text{Voltage}}{\text{Current}} = \frac{V}{I}$  = potential difference / Current flowing

ohmic :  $V$  depends linearly on  $I$

non-ohmic :  $V$  does not depend linearly on  $I$

## Equivalent Resistance of 2 Resistors


$I$  is the same for  $R_1$  &  $R_2$

$R_{\text{series}} = R_1 + R_2$


$\frac{1}{R_{\text{parallel}}} = \frac{1}{R_1} + \frac{1}{R_2}$

$V$  is the same for  $R_1$  &  $R_2$

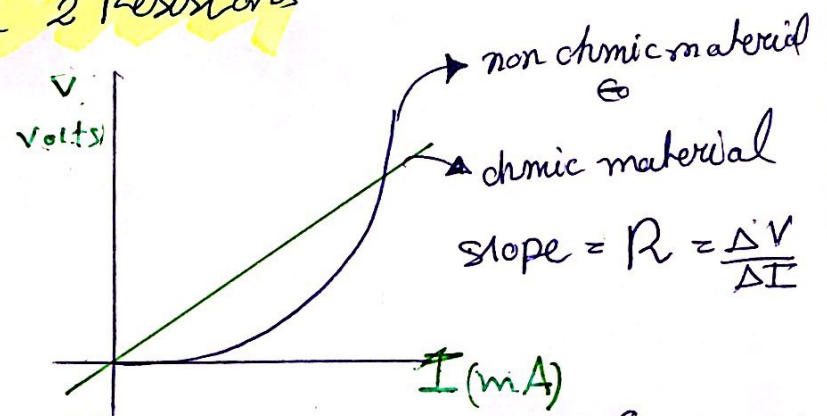$\Rightarrow \frac{\Delta R_2}{R} = \frac{\Delta V}{V} + \frac{\Delta I}{I}$




Color code

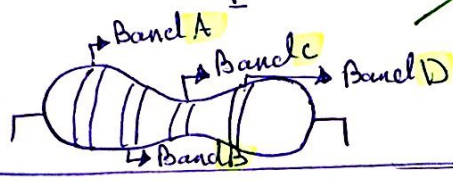

$R \text{ (Theoretically)} = AB \times 10^C \pm (D \times \%R)$

## Exp 5: focal length of a convex lens

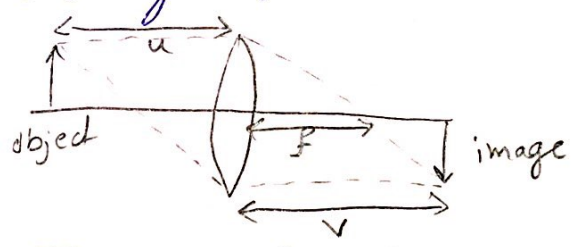

**focal length:**

The distance between the lens and the point of convergence of the light rays coming from the infinity

focal length  $\frac{1}{f} = \frac{1}{u} + \frac{1}{v}$

$\Rightarrow \frac{1}{f} = \frac{1}{x} + \frac{1}{y}$

$\frac{\Delta f}{f^2} = \frac{\Delta u}{u^2} + \frac{\Delta v}{v^2}$

$P_x = f_y$  (theoretically)

$\frac{1}{x \text{ intercept}} = \frac{1}{y \text{ intercept}}$

Alaa Etairwi

