


# Filters

## R-C filters

Note:  $f_{-3dB}$  in both cases should be the same

theoretically

Low pass filters integrator

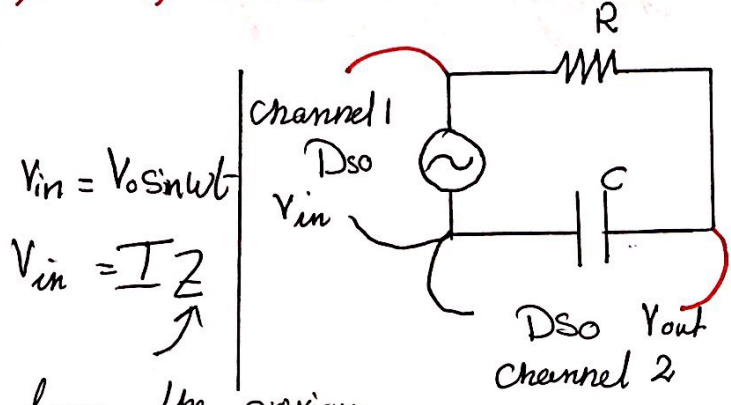

$V_{in} = V_0 \sin \omega t$   
 $V_{in} = I Z$

from the previous Exp  $Z = \sqrt{R^2 + X_c^2}$

$$V_{in} = I \sqrt{R^2 + X_c^2}$$

$$V_{out} = I X_c$$

Remember that  $X_c = \frac{1}{\omega C}$


Attenuation factor :-

$$A = \frac{V_{out}}{V_{in}} = \frac{X_c}{\sqrt{R^2 + X_c^2}}$$


$$A = \frac{1}{\sqrt{R^2 \omega^2 C^2 + 1}}$$

$$\omega_{-3dB} = \frac{1}{RC}$$

$$f_{-3dB} = \frac{1}{2\pi RC}$$

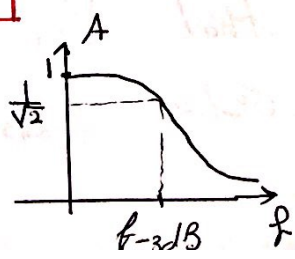


High pass filters differentiator

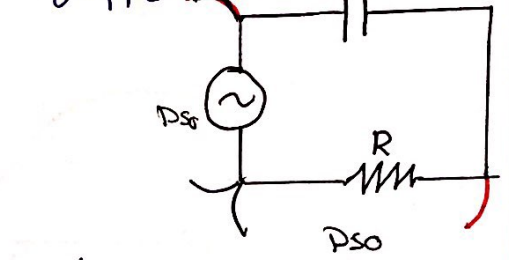

here :-  $V_{out} = I R$

$$A = \frac{R}{\sqrt{R^2 + X_c^2}}$$
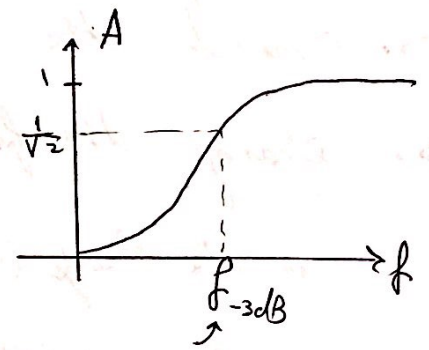
$$A = \frac{1}{\sqrt{1 + \frac{1}{\omega^2 R^2 C^2}}}$$



Alaa Itaiwi

Theoretical explanation :-

- low pass filter only allows low frequency signals to pass
- When the frequency is low the signal travels through the output and when it is high it travels through the capacitor.


what we use :-

- R, C
- signal Generator & DSO

• قم واصل هذه الدارة  
 • غير قيم التردد في المدى (0.2...20)  
 وقس فرق الجهد


Procedure

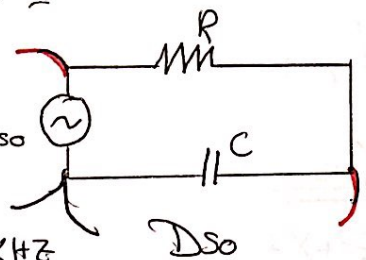- low pass filter :-
- Connect the circuit :-
- Change the frequency of DSO in the Range (0.2...20/KHz and measure V



• اصعب A نسبة  $V_{out}$  على  $V_{in}$   
 • ارسم A vs f و اخرج  $f_{-3dB}$

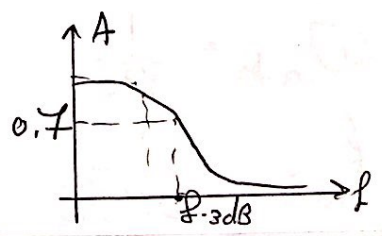- Calculate A by knowing that  $V_{in} = 10$
- Draw A vs f and obtain  $f_{-3dB}$





Alaa Etaiw

• High Pass filter

→ • Connect this Circuit

→ • Same as the previous

• obtain  $f_{-3dB}$

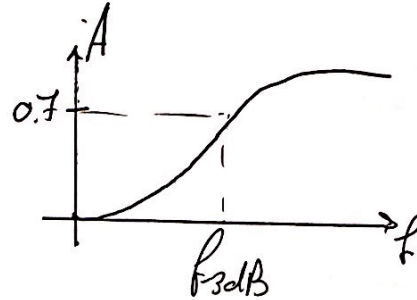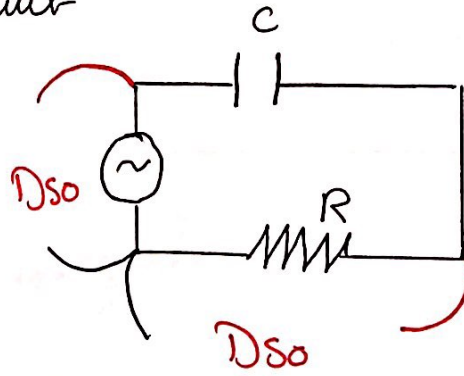

• قم بوصول الدارة ( للقائمة بدل للوضع )

• نفس خطوات التركيب السابق

• احصل على  $f_{-3dB}$

Alaa Etawi