

# Experiment 4: Network Analysis II


## The Thevenin and Norton Techniques

**Thevenin:** "any network of resistors and supplies having two output terminals and supplies having two output terminals can be replaced by a series combination of  $E_{eq}$  &  $R_{eq}$  **By three steps:-** starting by  $R_3$

**Step 1:-** you consider that  $E_1, E_2$  does not exist:-

$$R_{eq} = R_1 + R_2$$


$$R_{eq_3} = \frac{R_1 R_2}{R_1 + R_2}$$

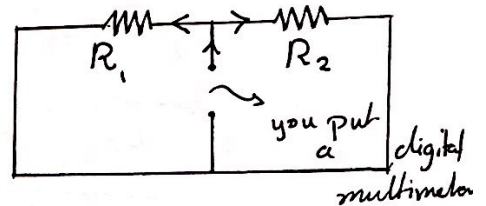

**Step 2:-** you consider that  $E_1, E_2$  exist


$$E_{eq} = E_1 - I R_1 \dots \textcircled{1}$$

you find  $I \dots \textcircled{2}$

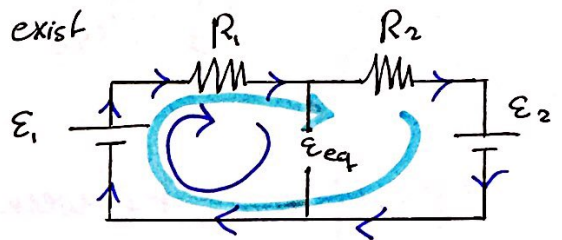

**Step 3:-** you find  $I_{eq_3}$
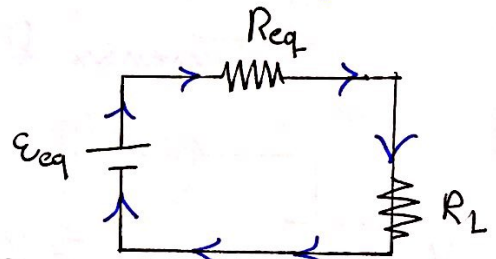
$$I_{eq_3} = \frac{E_{eq}}{R_{eq} + R_L}$$




• You do the same for  $R_1$  and  $R_2$  and you find  $I_{eq_1}$  and  $I_{eq_2}$

### 2- Norton's for $R_3$

**Step 1:-** The same

$$\begin{aligned} \text{Step 2:- } I_{eq_3} &= I_1 + I_2 \\ &= \frac{E_1}{R_1} + \frac{E_2}{R_2} \end{aligned}$$

**Step 3:** get rid of  $E_1, E_2$

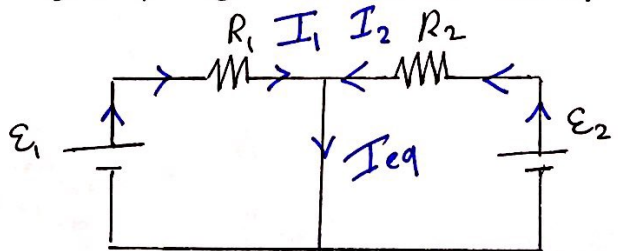


Alaa Etaher

• you replace  $R_1, R_2$  with  $R_{eq3}$

•  $I_{L3} R_3 = (I_{eq3} - I_{L3}) R_{eq3}$

على مصدر الجهد عند التوصل على التوازي

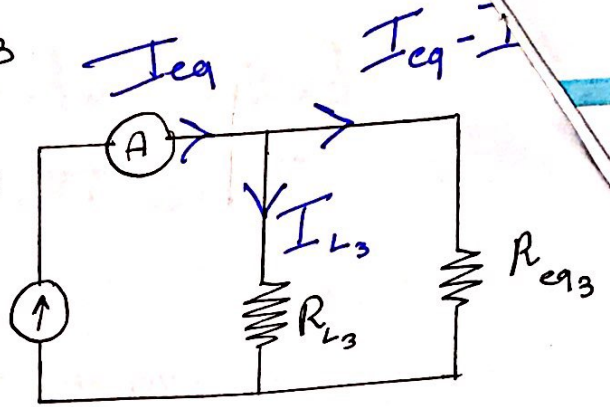

$$I_{L3} (R_3) = I_{eq3} R_{eq3} - I_{L3} R_{eq3}$$

$$I_{L3} (R_3 + R_{eq3}) = I_{eq3} R_{eq3}$$

you have it      you have it


$$I_{L3} = \frac{I_{eq3} R_{eq3}}{R_3 + R_{eq3}}$$

• in Thevenin's


$$I_{L3} = \frac{E_{eq}}{R_{eq} + R_L}$$

if you dont calculate  
Then  $I_{L3}$

### Difference between Thevenin & Norton

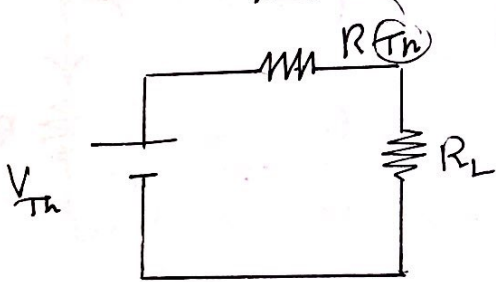

$$R_{th} = R_L$$

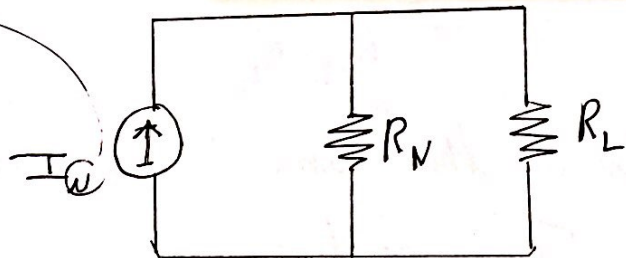

Alaa Itaiwi

- what we use
  - 2 voltage sources
  - 3 carbon Resistances
  - Circuit board
  - digital Multimeter

• DMM: digital Multimeter


• Procedure

Theremin :-

There are 3 currents to measure each one we have 3 steps:- let's say we want to measure  $I_3$

Step 1:- Calculate  $R_{eq}$ :-

• first circuit :-

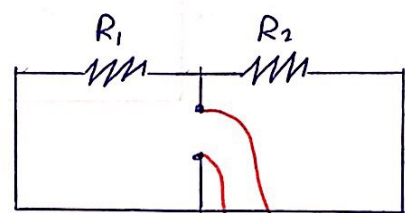

$$I_L = I_3$$

$$R_L = R_3$$


- Take  $E_1$  and  $E_2$  off
- Put a DMM in the place of  $R_3$

to a DMM to measure  $R_{eq3}$

Step 2:- Calculate  $E_{eq}$ :-

• second circuit :-

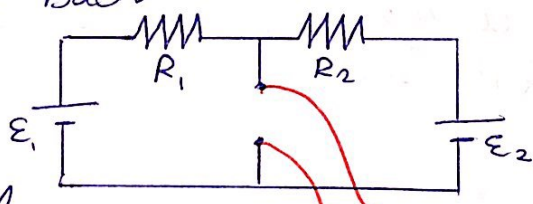- Take  $R_3$  off and put  $E_1$  and  $E_2$  back




to a DMM to measure  $E_{eq3}$

Step 3:-

- connect the circuit

$$R_L = R_3$$

$R_{eq}$  = you get it from the box

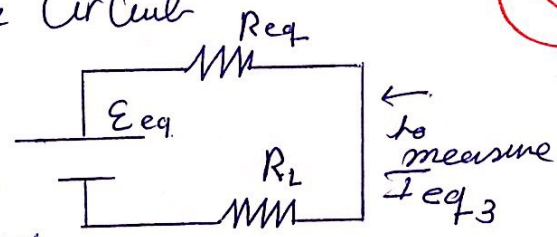


$E_{eq}$  = Power supply  
Alaa Ftairi


• هذه الخطوات الثلاثة هي الخطوات التي نحتاجها لقياس التيار  $I_3$  في المقاومة  $R_3$  في الدارة الأولى.   
 - الخطوة الأولى: نقيس المقاومة  $R_3$  في الدارة الأولى مع وجود  $E_1$  و  $E_2$  مع وجود DMM في مكان  $R_3$  ونقيس  $R_{eq3}$    
 - الخطوة الثانية: نقيس الجهد  $E_{eq}$  في الدارة الثانية مع وجود  $E_1$  و  $E_2$  مع وجود DMM في مكان  $R_2$  ونقيس  $E_{eq3}$    
 - الخطوة الثالثة: نقيس التيار  $I_3$  في الدارة الثالثة مع وجود  $E_{eq}$  و  $R_{eq}$  و  $R_3$  مع وجود DMM في مكان  $R_3$  ونقيس  $I_{eq3}$

Norton :-

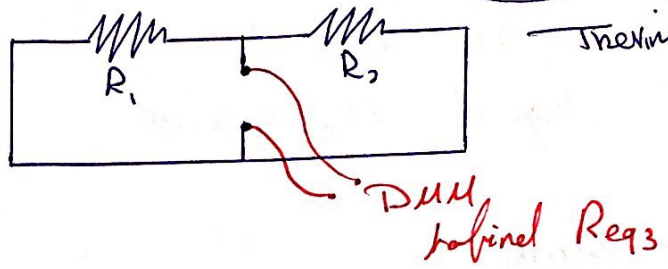
Step 1 :- The same as Thevenin's first step  
 نفس الخطوة الأولى. Thevenin's



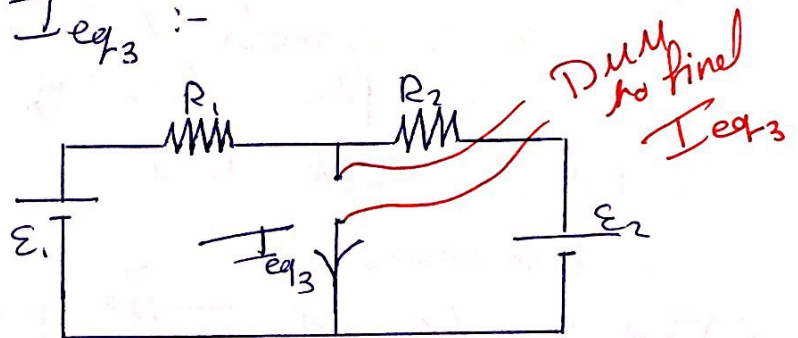Step 2 :- measure  $I_{eq3}$  :-  $I_{eq3}$  is.



Step 3 :- Connect this circuit

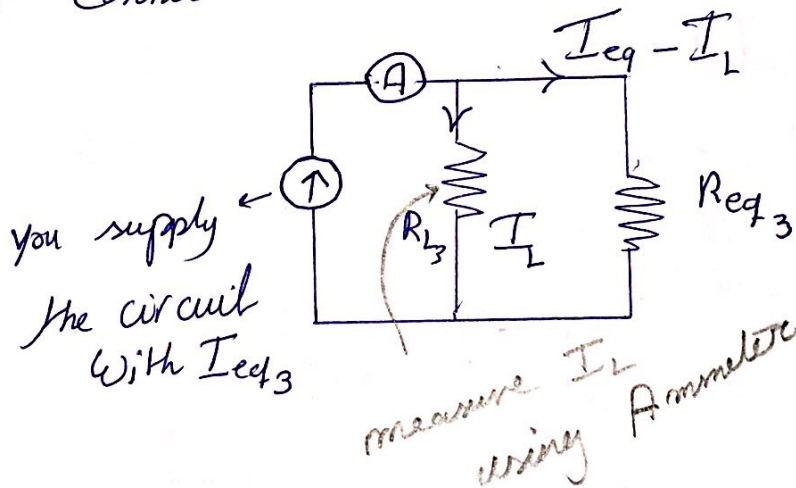

In Norton's

$R_{eq} = R_2 + R_3$  مجموع المقاومات المتصلة

$R_1 =$  is the internal Resistance