



Physics Department  
Physics 112

## Experiment 10: Filters

Student Name:

ID:

Partner Name:

ID:

Section: 8

Instructor: Dr.Gassan Abbas

Date: 21/8/2022

## Abstract:


**The aim of experiment is to** study the effect of the two types of RC-Filters (high and low pass) on output voltage in terms of:

- 1- Attenuation (decreasing the amplitude of the input signal).
- 2- The shape and behavior of the output signal.

**The main result is:**  $\omega_{-3dB} = 1.03 * 10^4 \frac{rad}{s}$

## Calculations:

**GRAPH 1: Low-pass filter: -**

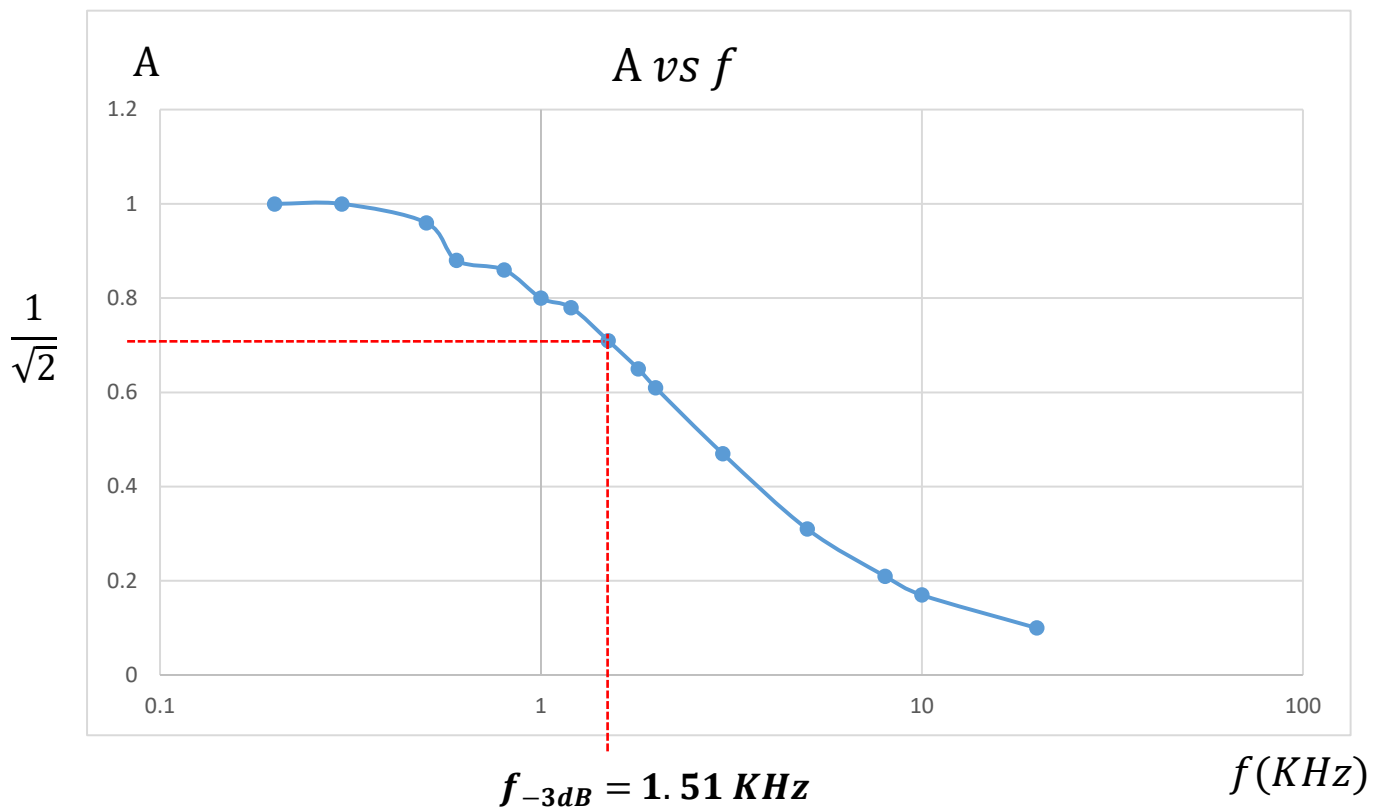

From the graph:


The intersection point is  $f_{-3dB} = 1.51$  KHz  $\gg \omega_{-3dB} = 2\pi f_{-3dB}$   
 $= 2\pi \times 1.51 \times 10^3 = 9.48 * 10^3$  rad/s

Note: (we use desmos to find the intersection point)

**Theoretically:**

$$\omega_{-3dB} = \frac{1}{RC} = \frac{1}{1000 * 0.1 * 10^{-6}} = 1 * 10^4 \frac{rad}{s}.$$

## GRAPH 2: High-pass filter: -

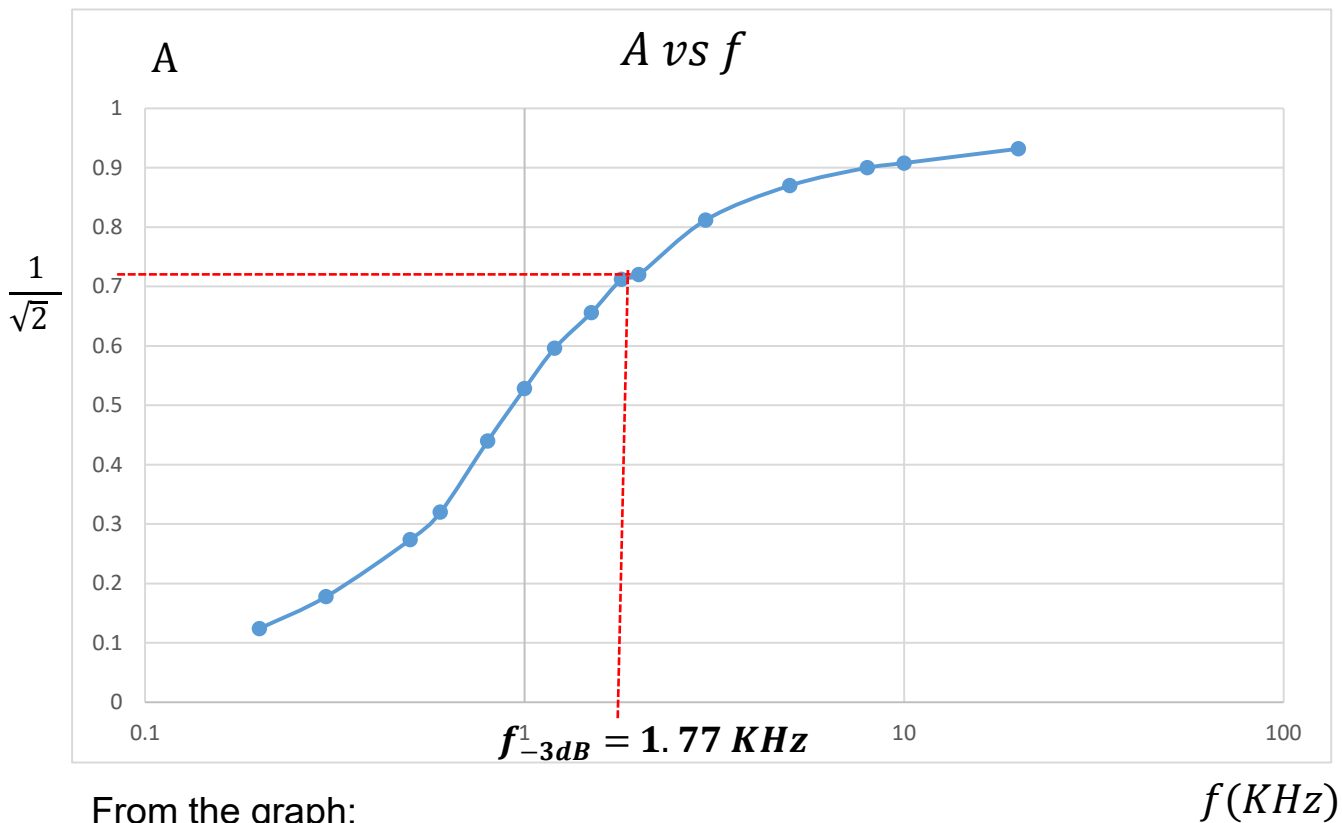

The intersection point is  $f_{-3dB} = 1.77 \text{ KHz} \gg \omega_{-3dB} = 2\pi f_{-3dB}$   
 $= 2\pi \times 1.77 \times 10^3 = 1.11 \times 10^4 \text{ rad/s}$

Note: (we use desmos to find the intersection point)

**Theoretically:**

$$\omega_{-3dB} = \frac{1}{RC} = \frac{1}{1000 \times 0.1 \times 10^{-6}} = 1 \times 10^4 \frac{\text{rad}}{\text{s}}$$

By taking the average value of  $f_{-3dB}$  from high and low pass filters:

$$f_{-3dB} = \frac{f1 + f2}{2} = \frac{1.51 + 1.77}{2} = 1.64 \text{ KHz}$$

$$\text{and } \omega_{-3dB} = 2\pi f_{-3dB} = 2\pi \times 1.64 \times 10^3 = 1.03 \times 10^4 \frac{\text{rad}}{\text{s}}$$

## Results and conclusion:

This experiment discussed: 1) the difference between low-pass and high-pass filters, as well as 2) how to find the integration and differentiation using the filter circuits: Low and High pass filter. To begin, the theoretical value of omega was found to equal to 10000 rad/s which was relatively close to the experimental values found in the Attenuation vs frequency graphs for both circuits. The experimental value of omega from high and low pass filters is  $\omega_{-3dB} = 1.03 * 10^4$  .

In the low-pass filter if  $\omega \gg \omega_{-3dB}$  then A is small and output signal is highly attenuated, and if  $\omega \ll \omega_{-3dB}$  then A is almost 1 and  $V_{out} \approx V_{in}$  and the signal passed without attenuation. Also if  $\omega = \omega_{-3dB}$  then  $A = \frac{1}{\sqrt{2}}$  and  $V_{out} = 0.707 V_{in}$  .

In the High-pass filter if  $\omega \ll \omega_{-3dB}$  then A is small and output signal is highly attenuated, and if  $\omega \gg \omega_{-3dB}$  then A is almost 1 and  $V_{out} \approx V_{in}$  and the signal passed without attenuation. Also if  $\omega = \omega_{-3dB}$  then  $A = \frac{1}{\sqrt{2}}$  and  $V_{out} = 0.707 V_{in}$  .