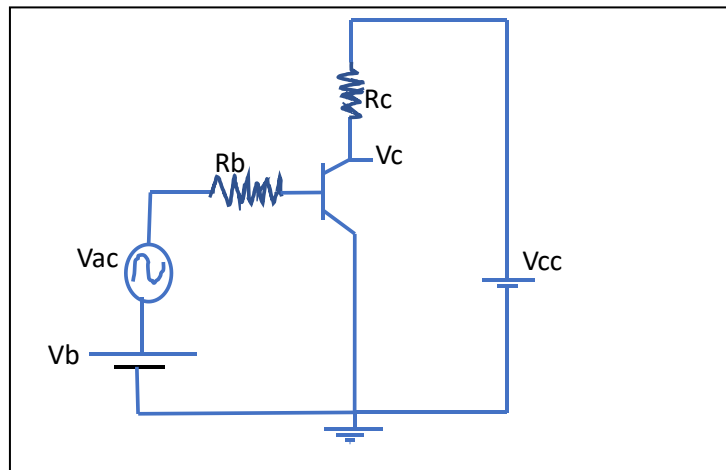


1- In the adjacent cartoon. $R_b=200\text{ k}\Omega$, $R_c=10\text{ k}\Omega$, $V_b=1\text{ V}$, $V_{ac}=0.3\cos t\text{ Volt}$, $V_{cc}=20\text{V}$, $\beta=200$, $V_{BE}=0.7\text{V}$. Find



A) The maximum value of current flowing into R_b


B) The current flowing into the emitter of the transistor

C) The highest voltage for V_c

D) The lowest voltage at V_c

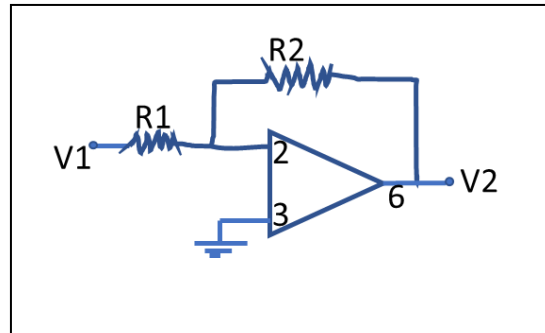
E) Plot $V_C(t)$

2- The adjacent is an Operational Amplifier circuit with $R_1=5\text{ k}\Omega$ and $R_2=200\text{ k}\Omega$.




A) Derive the relation between V2 and V1 (show V2 as a function of V1). Show all your steps.

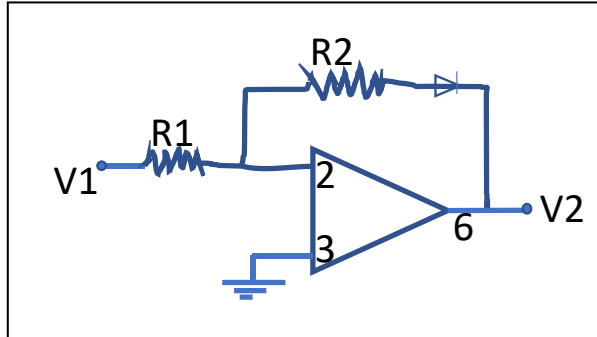B) If a diode with $V_d=0.7V$ forward voltage drop is added between R2 and V2, what is the relation between V2 and V1?



3) In the adjacent diode circuit, $R_1=20\text{k}\Omega$, $R_2=10\text{k}\Omega$, $V_{in}(t)=12 \cos(t)$ Volts, and the forward voltage across diode is 0.65 V .

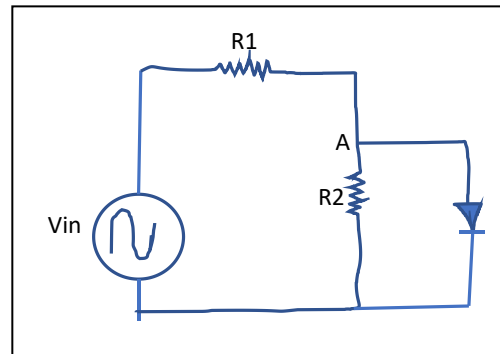a) Plot $V_n(t)$ and $V_D(t)$ showing multiple cycles



b) Find the current through R_2

c) Find the currents through R_1 and through the diode

4) Use sketches to explain the principle of operation of
A) the diode B) The bipolar junction transistor, and C) the field effect
transistor