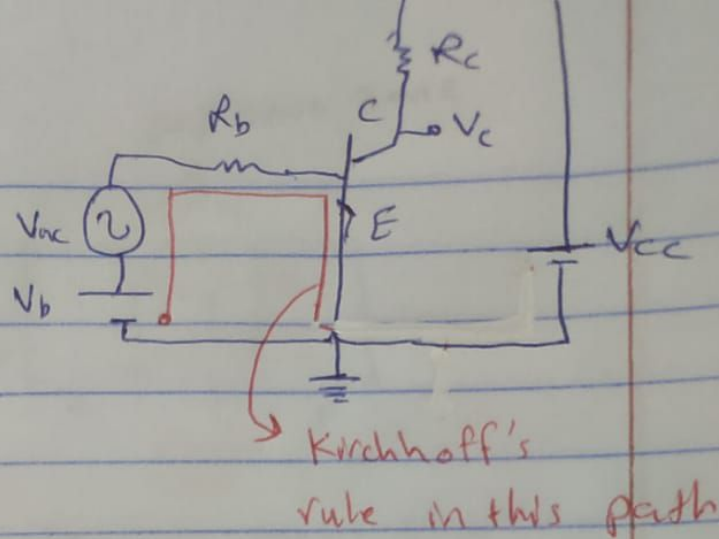


$$\boxed{1} \text{ A) } V_b + V_{ac} - I R_b + 0 = 0 \quad \text{KVL BE}$$

$$1 + 0.3 \cos t - I R_b = 0.7$$

$$I = \frac{1 + 0.3 \cos t - 0.7}{R_b}$$



$$I = \frac{0.3 + 0.3 \cos t}{200} \text{ mA}$$

$$\max(I) = \frac{0.3 + 0.3}{200} \text{ mA} = \frac{0.6}{200} \text{ mA}$$

$$= 0.003 \text{ mA} = 3 \mu\text{A}$$

$$= 3 \mu\text{A}$$

This is I_B

$$\text{B) } I_B + I_c = I_E$$

$$I_c = \beta I_B = 200 \left(\frac{0.3 + 0.3 \cos t}{200} \right)$$

$$\boxed{I_c = 0.3 + 0.3 \cos t \text{ mA}}$$

$$I_E = I_B + I_c$$

$$= \frac{0.3 + 0.3 \cos t}{200} + 0.3 + 0.3 \cos t$$

$$= \left(\frac{1}{200} + 1 \right) (0.3 + 0.3 \cos t)$$

$$\boxed{I_E = 0.3015 + 0.3015 \cos t \text{ mA}}$$

$$\text{C) } V_{cc} - I_c R_c = V_c$$

$$20 - (10 \text{ K})(0.3 + 0.3 \cos t) \text{ mA} = V_c$$

$$\boxed{V_c = 17 - 3 \cos t \text{ Volt}}$$

$$\max(V_c) = 17 + 3 = 20 \text{ Volt (when } \cos t = -1)$$

$$\text{D) } \min(V_c) = 17 - 3 = 14 \text{ Volt (when } \cos t = 1)$$

2) A) $V_2 = V_3 = 0$

$$V_1 = I R_1 \Rightarrow I = \frac{V_1}{R_1}$$

$$V_2 = -I R_2$$

$$V_2 = -V_1 \frac{R_2}{R_1} = -40 V_1$$


B) $V_2 = V_3 = 0$

$$V_1 = I R_1$$

$$V_2 = -I R_2 + V_d$$

$$= -V_1 \frac{R_2}{R_1} - 0.7$$

$$V_2 = -40 V_1 - 0.7$$

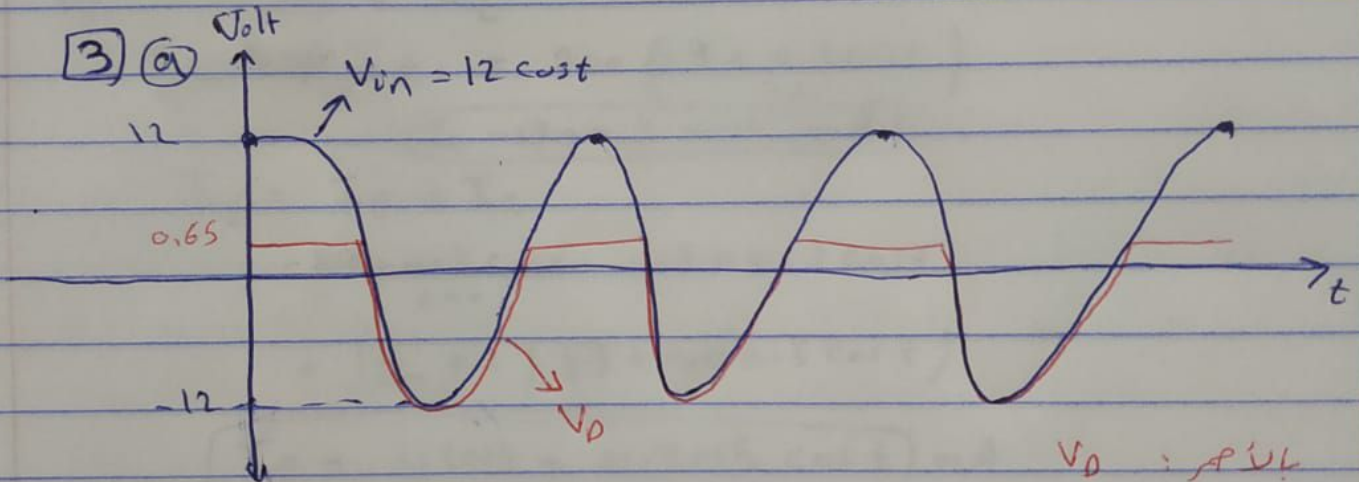


b) $V_D = V_2 = 0.65$ Volt

$$V_1 = V_{in} - V_2$$

$$= 12 \cos t - 0.65 \text{ Volt}$$
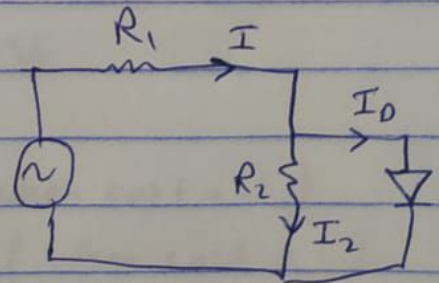
$$I_1 = \frac{V_1}{R_1} = \frac{1}{20} (12 \cos t - 0.65) \text{ mA}$$





$$I_2 = \frac{V_2}{R_2} = \frac{0.65}{10} = 0.065 \text{ mA}$$

$$I_D = I_1 - I_2 = \frac{1}{20} (12 \cos t - 0.65) - 0.065 \text{ mA}$$

c)

4 A) The diode:

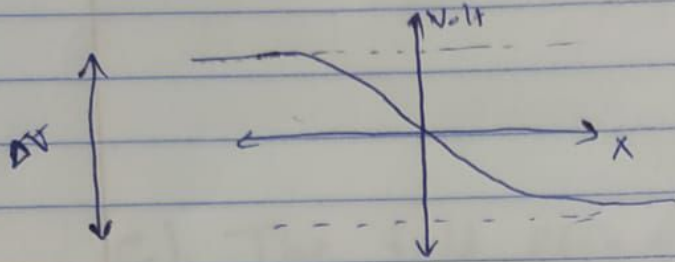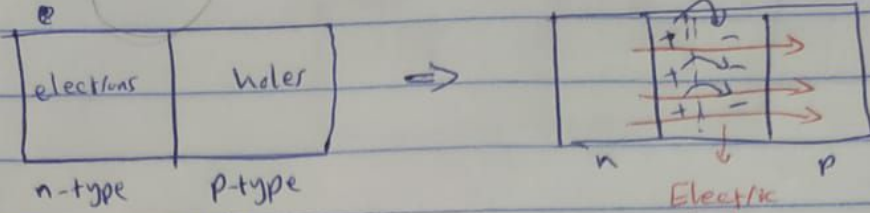

This field prevent electrons from going right. However, they may be electrons having high energy and go right.

This current is I_g (generation)

$I_{ge} \rightarrow I_{gh}$
 electrons holes

Also, they may be electrons in holes' area and holes in electrons' area. With the electric field, a current is created.

It's called I_r (recombination)

I_{re}, I_{rg}


$I_g + I_s = 0$ When $V_b = 0$

$I_g = I_{g0} \exp\left(\frac{-eV}{k_B T}\right)$

$I_s = \text{constant}$

When connecting with battery:

depletion zone increases

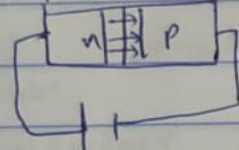


reverse biased junction

يتكون مجال كهربائي عاكس، مما يمنع التيار من الجريان في الاتجاه العكسي.


لا يوجد تيار

No conduction

forward bias

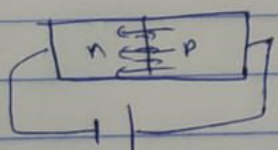


depletion zone decreases

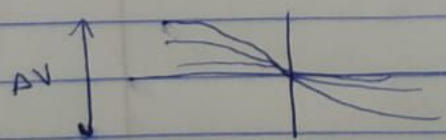

No depletion zone if: $V_{Ext} \geq V_d = \Delta V$

B) The bipolar junction transistor: (using both n and p types)


(BJT)

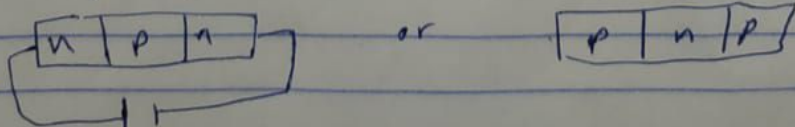

or
 reverse biased
 no current

We need 2 batteries to make the current flow.

الف ب)

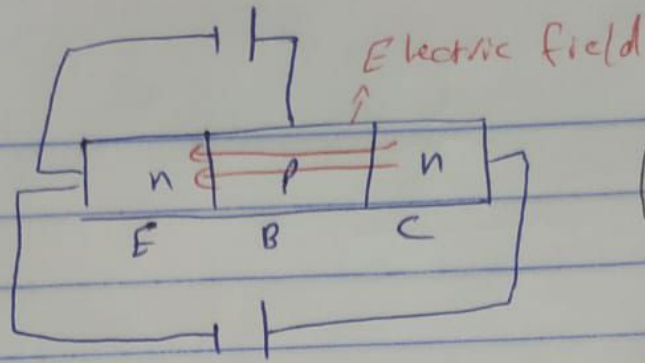


$$I_{CE} = \beta I_{BE}$$

$$\beta \sim 100 - 500$$

$I_{CE} \gg I_{BE}$
 يفتقر إلى التيار


c) The field Effect Transistor (FET):

using either n-type or p-type

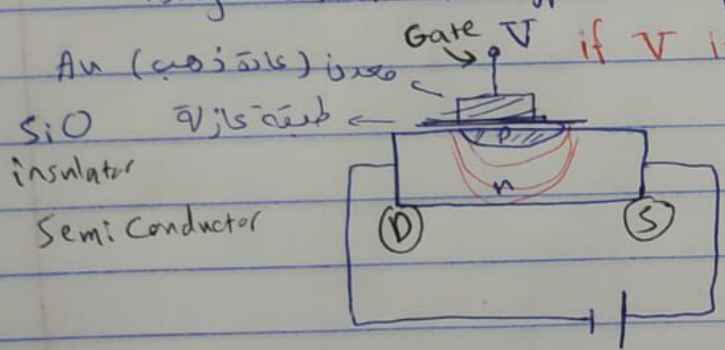

if V is -ve (depletion zone increase)
 if V is +ve (depletion zone disappears)

$$E = \frac{\Delta V}{d}$$

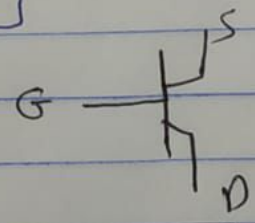

$$I_{SD} \propto V_G$$

E) Plot $V_c(t)$!

$$V_c = 17 - 3 \cos t$$

