
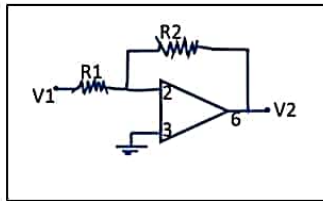


$R2=200k\Omega$ .

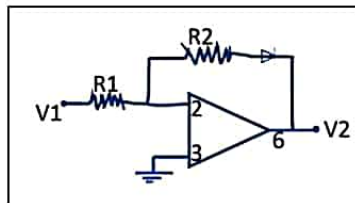


A) Derive the relation between  $V2$  and  $V1$  (show  $V2$  as a function of  $V1$ ). Show all your steps.

B) If a diode with  $V_d=0.7V$  forward voltage drop is added between  $R2$  and  $V2$ , what is the relation between  $V2$  and  $V1$ ?



3) In the adjacent diode circuit,  $R_1=20\text{k}\Omega$ ,  $R_2=10\text{k}\Omega$ ,  $V_{in}(t)=12 \cos(t)$  Volts, and the forward voltage across diode is 0.65 V.

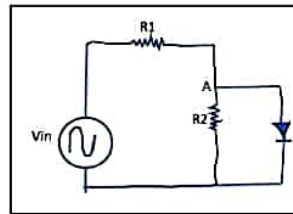a) Plot  $V_n(t)$  and  $V_o(t)$  showing multiple cycles



b) Find the current through  $R_2$

c) Find the currents through  $R_1$  and through the diode




Birzeit University

PHYS336

Final Exam

February 2 2021

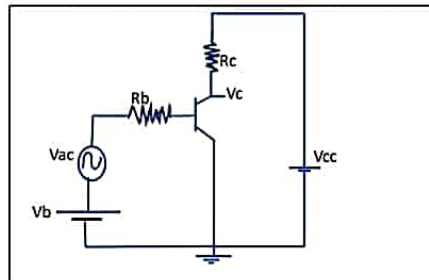1- In the adjacent cartoon.  $R_b=200\text{ k}\Omega$ ,  $R_c=10\text{ k}\Omega$ ,  $V_b=1\text{ V}$ ,  $V_{ac}=0.3\text{cost Volt}$ ,  $V_{cc}=20\text{V}$ ,  $\beta=200$ ,  $V_{BE}=0.7\text{V}$ . Find



A) The maximum value of current flowing into  $R_b$

B) The current flowing into the emitter of the transistor

C) The highest voltage for  $V_c$

D) The lowest voltage at  $V_c$

Q1)

a)  $V_{ac} = 0.3 \cos(t)$

$$I_b = \frac{V_b + V_{ac} - V_{BE}}{R_b} = \frac{1 + 0.3 \cos(t) - 0.7}{200 \text{ K}}$$

$$I_{b_{max}} = \frac{1.3 - 0.7}{200 \text{ K}} = \frac{0.6}{200 \times 10^3} = 3 \times 10^{-6} \text{ Am}$$

max = 1  $\rightarrow$   $t = n\pi$

B)  $I_{EE} = (B+1) I_B$

$$= 201 \times 3 \times 10^{-6} = 6.03 \times 10^{-4} \text{ Am}$$

c)  $V_c = V_{cc} - I_c R_c$

~~$I_{EE} = 6 \times 10^{-4} \text{ Am}$~~   
 ~~$I_B = 6 \times 10^{-6} \text{ Am}$~~   
 ~~$V_c = 20 \text{ V}$~~   
 $I_c = \beta I_B$

من اجل قسمة

$t = \frac{n\pi}{2}$

$$I_b = \frac{V_b - V_{BE} + V_{ac}}{R_b} = \frac{0.3 + 0.3 \cos(t)}{200 \text{ K}}$$

$$I_b = \text{zero} \Rightarrow I_c = 0$$

$$V_c = V_{cc} - \text{zero} = 20 \text{ V}$$

d)  $\rightarrow \cos(t) = 1$

$$I_b = \frac{0.3 + 0.3}{200 \text{ K}} = 3 \times 10^{-6} \text{ Am}$$

$$I_c = I_b \times 200 = 6 \times 10^{-4} \text{ A}$$

$$V_c = V_{cc} - I_c R_c = 20 - 6 = 14 \text{ V}$$

$\pi_2$   $\pi$   $\pi_3$  (b)

B)

$$I_b = \frac{V_B - V_{BE} + V_{AC}}{R_b} = \frac{1 - 0.7 + 0.3 \text{ Cost}}{200k}$$

$$I_b = \frac{0.3 + 0.3 \text{ Cost}}{200k}$$

$$I_E = (\beta + 1) I_b$$


$$= 201 \times \left( \frac{0.3 + 0.3 \text{ Cost}}{200k} \right)$$



Qc)  
a)

$$R_1 = 5 \text{ k}\Omega$$

$$R_2 = 200 \text{ k}\Omega$$

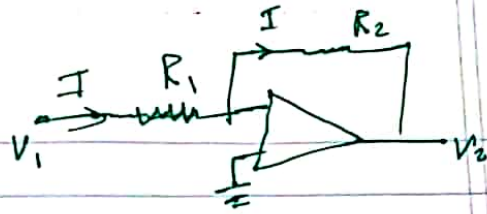

$$I = \frac{V_1}{R_1}$$


$$V_2 + I R_2 = 0$$

$$V_2 = -I R_2$$

$$V_2 = -\frac{V_1 R_2}{R_1} = -\frac{R_2}{R_1} V_1$$

$$V_2 = -\frac{200}{5} V_1 = -40 V_1$$

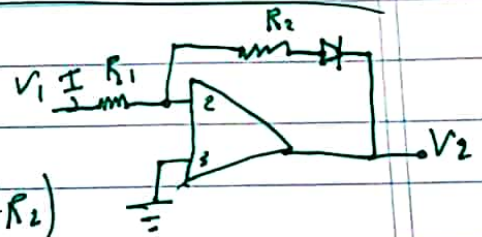B)  $I = \frac{V_1}{R_1}$  ,  $V_2 + V_d + I R_2 = 0$



$$V_d = -(V_2 + I R_2)$$

$$I_D = I_0 \left( e^{\frac{eV_d}{k_B T}} - 1 \right)$$

$$\frac{V_1}{R_1} = I_0 \left( e^{\frac{e \cdot -(V_2 + I R_2)}{k_B T}} - 1 \right)$$


$$\left( e^{\frac{e \cdot -(V_2 + I R_2)}{k_B T}} - 1 \right) = \frac{V_1}{R_1 I_0} + 1$$

$$-e \frac{(V_2 + I R_2)}{k_B T} = \ln \left[ \frac{V_1}{R_1 I_0} + 1 \right]$$

$$V_2 = \frac{k_B T}{-e} \ln \left[ \frac{V_1}{R_1 I_0} + 1 \right] - I R_2$$




# + Field Effect Transistor :-

$$I \propto (V)^2$$

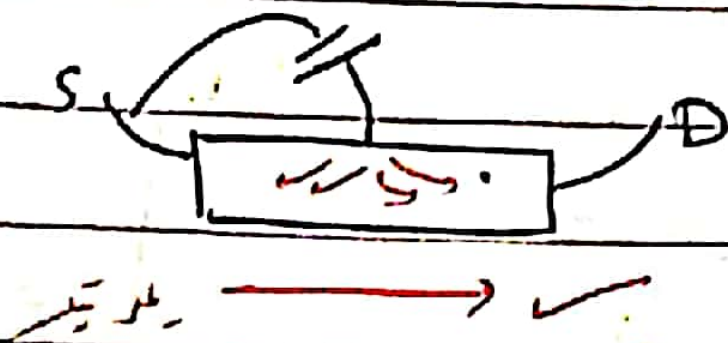

Electron current

# Bipolar Junction Transistor :-

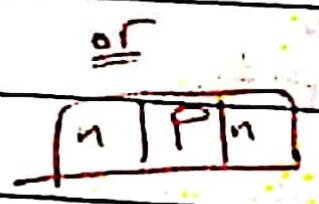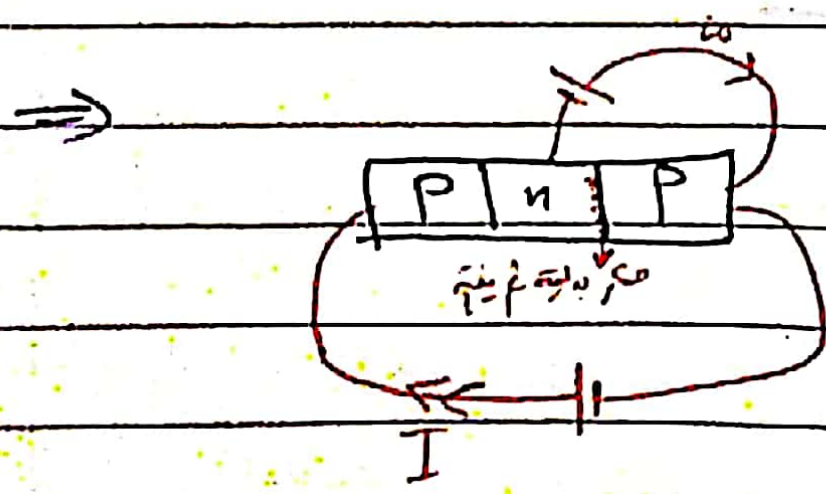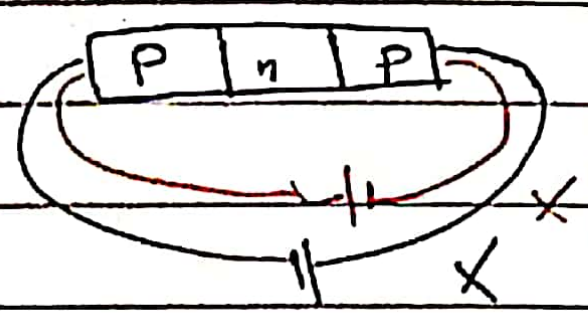



\* Diode :-

