

Birzeit University

Physics 112

Experiment #10

Filter

Student Name: Mujahed AbuAli **#1211047**
Partner's Name: Issa AbuAwada **#1210667**

Section: 6
17\1\2022
Dr. Khalid Eid

Abstract:

- **The aim:** how to find the integration and differentiation using the filter circuits: Low-pass filter and High-pass filter.
- **The method:** by found the border between high and low attenuation for filters by using the CRO to see the plot of the capacitance's voltage vs. time and get the value of the voltage
- **The main Result:**

ω Theoretically: $1/RC = 10000$ rad/sec

ω from the graph of A vs. ω for the low pass filter

(A=0.707) $\approx 10.8 \cdot 10^3$ rad/sec.

ω from the graph of A vs. ω for the high pass filter

(A=0.707) $\approx 11.2 \cdot 10^3$ rad/sec

Introduction:

A filter is an electrical circuit that allows signals with a defined frequency range to pass while blocking others with different frequency ranges. Filters are useful units in many electrical and electronic devices such as radio, TV, etc.

The types of filter :

1- Low-pass RC filter

Using the generalized Ohm's law we can obtain the output voltage, V_{out} , as a function of the input voltage, V_{in} .

$$V_{out}(t) = V_{in}(t) / (1 + j \omega RC)$$

And the attenuation factor takes the following form:


$$A = 1 / (1 + (\omega / \omega_{-3dB})^2)^{0.5}$$

2- High-pass RC filter


The attenuation factor, A can be deduced using exactly the same procedure used in case of the low-pass filter, this gives:

$$A = 1 / (1 + (\omega / \omega_{-3dB})^2)^{0.5}$$

The Graphs

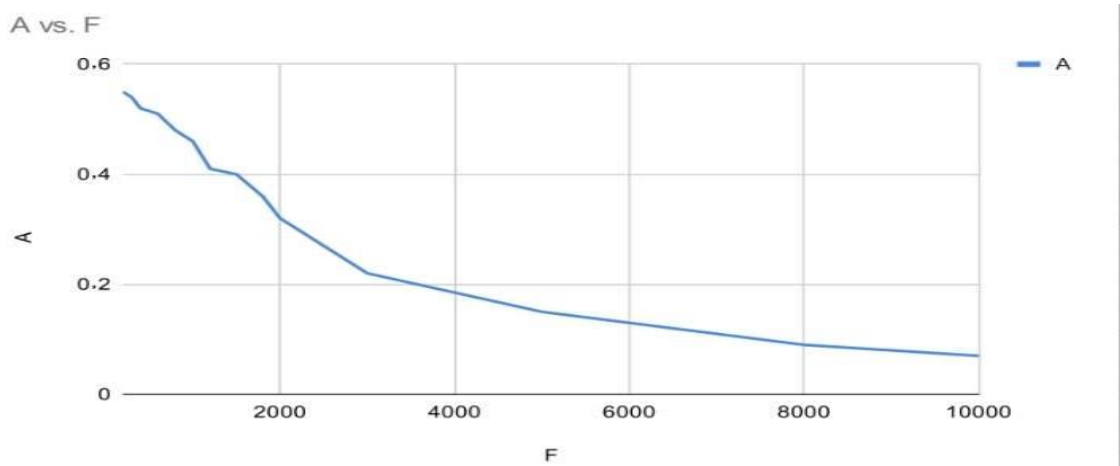

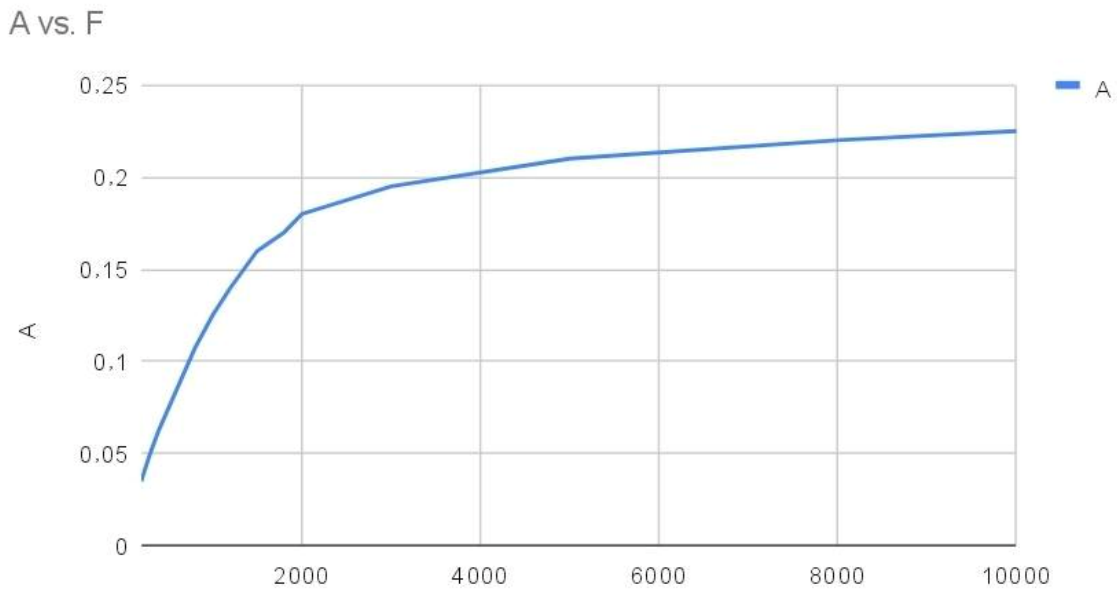Attenuation factor A as a function of frequency for Low-pass filter



Attenuation factor A as a function of frequency for High-pass filter

Results and Conclusion:

The difference between low-pass and high-pass filters and what their omega for the cut off frequency is, as well as how to find the integration and differentiation using the filter circuits: Low-pass filter and High-pass filter. To begin, the theoretical value of omega was found to equal to 10000 rad/sec which was relatively close to the experimental values found in the Attenuation vs. Omega graphs for both circuits.

As we can see from the results that we've got, the high-pass filter acts as a differentiator and the low-pass filter acts as an integrator.

The results we have experimentally is near the once we have Theoretically but there are some errors.

The experimental values of ω_{-3dB} for the high-pass and low-pass filters were both equal to 9420 rad/sec, meaning that a practical boundary between passed signals and highly attenuated ones were set to the half of their maximum power which proves the equation