
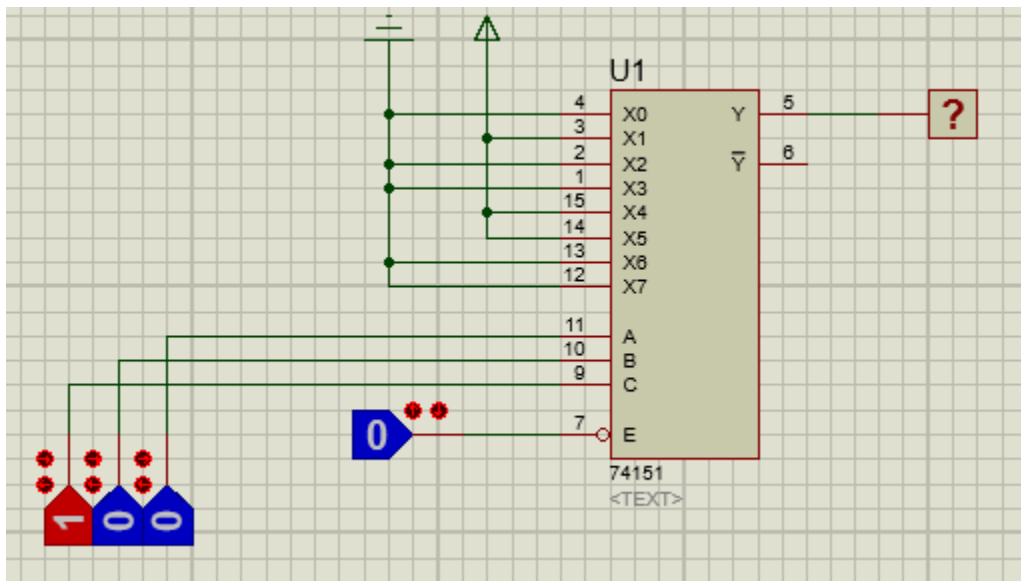


Q2 a-

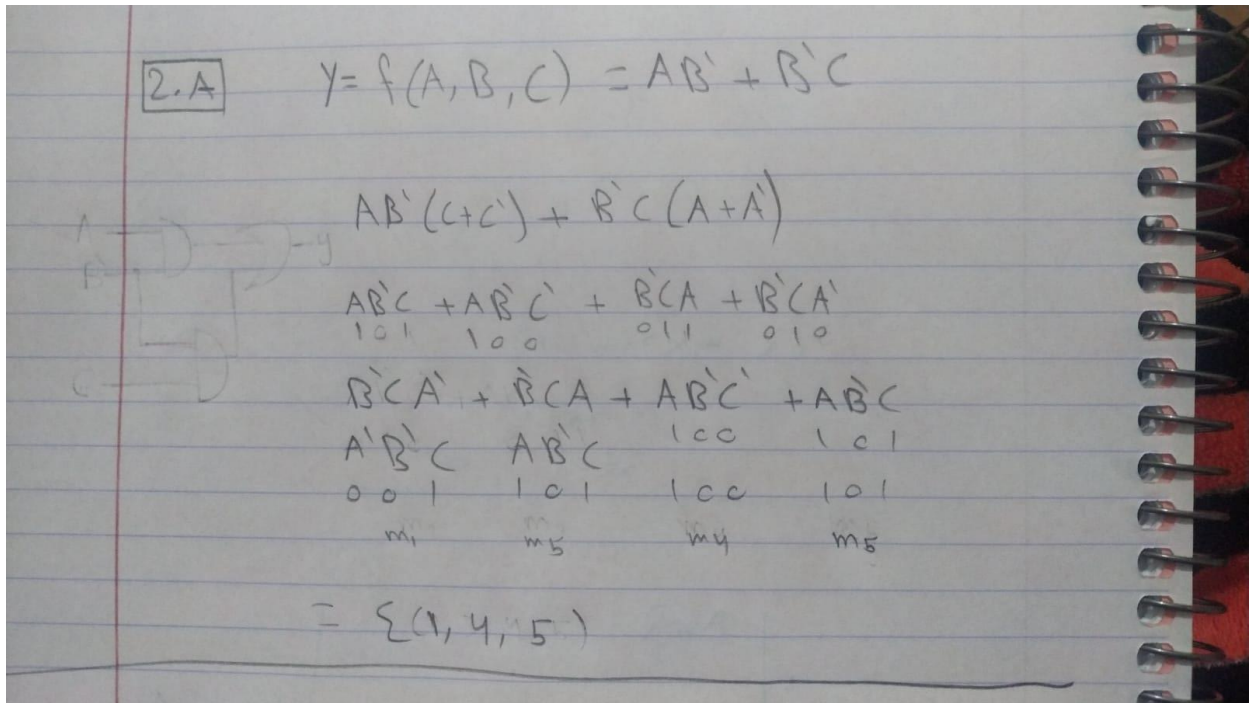

b-

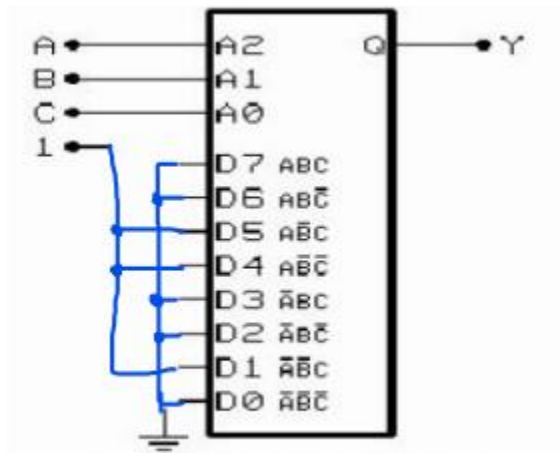


Figure 3.1:8-to-1 Multiplexer

Q3 a-

$$Y = A'BC + BC'$$

$$Y = A'BC + (A+A')BC'$$


$$Y = A'BC + ABC' + A'BC'$$

$$Y = 011 + 110 + 010$$

$$Y = \sum(2,3,6)$$


b-

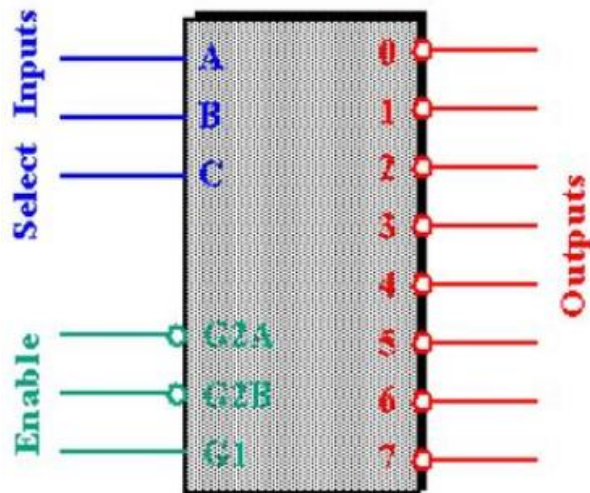this is the truth table of 3-8 multiplexer which shows how to connect the IC with inputs and outputs



Inputs						Output							
Enable			Select										
G2A	G2B	G1	C	B	A	0	1	2	3	4	5	6	7
1	X	X	X	X	X	1	1	1	1	1	1	1	1
X	1	X	X	X	X	1	1	1	1	1	1	1	1
X	X	0	X	X	X	1	1	1	1	1	1	1	1
0	0	1	0	0	0	0	1	1	1	1	1	1	1
0	0	1	0	0	1	1	0	1	1	1	1	1	1
0	0	1	0	1	0	1	1	0	1	1	1	1	1
0	0	1	0	1	1	1	1	1	0	1	1	1	1
0	0	1	1	0	0	1	1	1	1	0	1	1	1
0	0	1	1	0	1	1	1	1	1	1	0	1	1
0	0	1	1	1	0	1	1	1	1	1	1	0	1
0	0	1	1	1	1	1	1	1	1	1	1	1	0

Here is the circuit

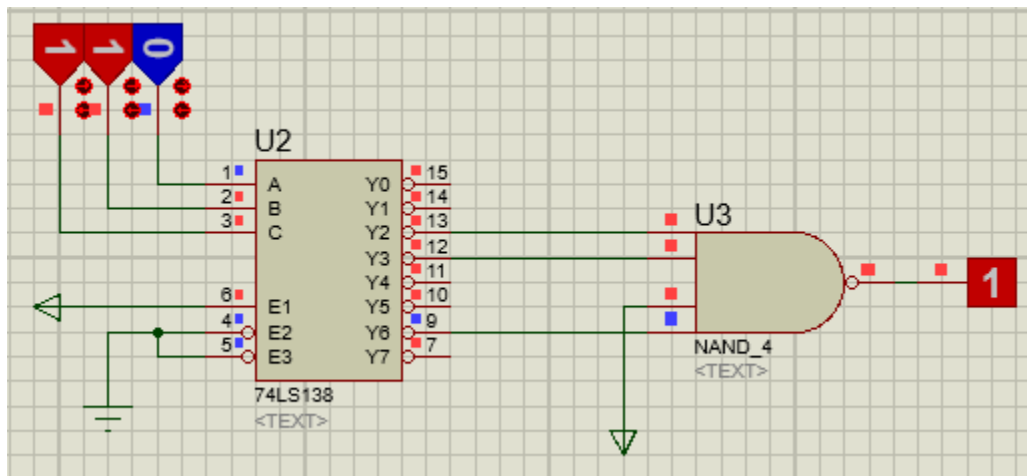

First we use the E1 enable only, then every input give one output and from the equation if the output was 2, 3 or 6 the output will give 1 (but it work onactive low so it give a qustion mark sign) and this work by using NAND gate.