

10/10



**ENCS 2110**  
**DIGITAL ELECTRONICS AND COMPUTER ORGANIZATION LABORATORY**

Quiz 1 - a

name & id: Roua H. Naji, 1201959

Q1. Given the logic system is shown in Fig. 1.17  
output of the system F is in "1" state in each of the following condition

- A, B are in the "1" state, C in "0" state.  $AB\bar{C}$
- A, B and D are in the "1" state  $ABD$
- C is in the "1" state A, B and D are in the "0" state.  $C\bar{A}\bar{B}\bar{D}$

**DO NOT USE TRUTH TABLE**

1. Write the boolean full equation as canonical sum.

 


Fig. 1.17 Block diagram

(4/4)

$$\begin{aligned}
 F &= AB\bar{C} + ABD + C\bar{A}\bar{B}\bar{D} \\
 &= AB\bar{C}D + AB\bar{C}\bar{D} + ABCD + ABC\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} \\
 &= m_{13} + m_{12} + m_{15} + m_{13} + m_2 \\
 &= \sum 2, 12, 13, 15
 \end{aligned}$$

0000  
 0001  
 0010  
 0011  
 0100  
 0101  
 0110  
 0111  
 1000  
 1001  
 1010  
 1011  
 1100  
 1101  
 1110  
 1111

**ENCS 2110**  
**DIGITAL ELECTRONICS AND COMPUTER ORGANIZATION LABORATORY**

Quiz 1 - a


name & id:

Q2. Complete the following diagram, to create a BCD adder that counts to 10 instead of 9

$10 \rightarrow (1010)$   
 $X_4 \cdot X_3 \cdot X_2 \cdot X_1$   
 $1000$   
 $1000$   
 $0000$

$X_4 \cdot X_3 = 1$   
 $X_4 \cdot X_2 = 1$   
 $X_4 \cdot X_1 \cdot X_2 = 1$

(4/4)

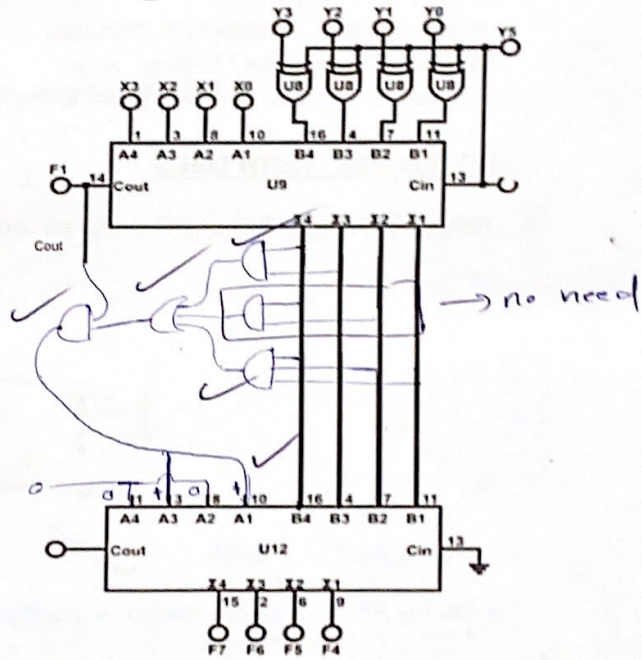

Q3. a circuit that converts  $n$  inputs to  $2^n$  outputs is called : (2/2)

- a. Decoder   
  b. Encoder   
  c. Multiplexer   
  d. Flip-Flop

✓



9/10

ENCS 2110  
DIGITAL ELECTRONICS AND COMPUTER ORGANIZATION LABORATORY


Quiz 3

name & id: Róa Nafi





1- Design a 2-bit Synchronous Counter Using J-K Flip Flops. Show all your work including truth tables, and boolean expressions used. In addition to the designed circuit diagram.



2-bit Synchronous Counter counts from 0 to 3 and return to count from 0 ;

P.S		N.S		$J_1 K_1$		$J_0 K_0$	
$Q_1$	$Q_0$	$Q_1$	$Q_0$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	1	0	X	1	X
0	1	1	0	1	X	X	1
1	0	1	1	X	0	1	X
1	1	0	0	X	1	X	1

 

$Q_1 Q_0$	J	K
00	0	X
01	1	X
10	X	1
11	X	0

    

  



ENCS 2110  
DIGITAL ELECTRONICS AND COMPUTER ORGANIZATION LABORATORY

Quiz 5

name & id: Roa Nafi 1201959

1- Write a verilog code to build a negative edge D Flip Flop

```
module DFlipFlop (D, Q);  
  input D;  
  output reg Q;  
  
  always @ (negedge clk)  
  begin  
    Q <= D;  
  end  
end module
```

