



**BIRZEIT UNIVERSITY**

Faculty of Engineering and Technology

Electrical and Computer Engineering Department

**ENCS234, Digital Systems**

Date: Thursday , 09/06/2016

Time: 11:00 - 13:30

Rooms: KNH625

**Total points: 100**

<b>Instructors:</b>	Khader Mohammad	M, W	14:00 - 15:20
	Mohammed Hussein	T, R	08:00 - 09:20
	Ahmad Alsadeh	S, M, W	10:00 - 10:50
		S, M, W	13:00 - 13:50

Name: \_\_\_\_\_

ID: \_\_\_\_\_

**Question 1:** Multiple choices are worth 2 points each. (30 points)

(ABET Outcome a: Ability to apply mathematics, science and engineering principles.)

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15

1) Converting  $(153)_{10}$  to base 8 yields which of the following results?

- a. 107
- b. 132
- c. 701
- d. 231**

2) 10100 is the two's complement representation of:


- a. +12
- b. -12**
- c. -20
- d. +20



3) Simplification of the Boolean expression  $AB + ABC + ABCD + ABCDE + ABCDEF$  yields which of the following results?

- a. ABCDEF
- b. AB**
- c.  $AB + CD + EF$
- d.  $A + B + C + D + E + F$

4) The shown circuit can be implemented using a minimum of :

 
- a. 3 NAND Gates
- b. 4 NAND Gates**
- c. 5 NAND Gates
- d. 4 NAND Gates and 1 NOR Gate


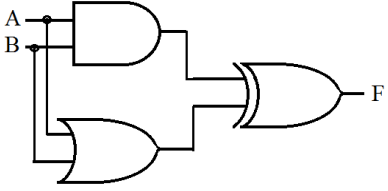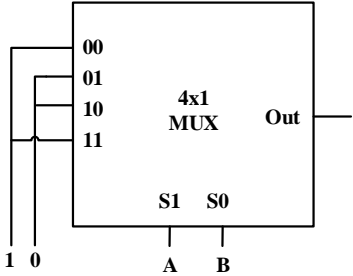
<p>5) What is the output of the following circuit?</p> <p>a. AB</p> <p>b. A+B</p> <p>c. A'B'+AB</p> <p>d. <b>A'B+AB'</b></p>																																		
<p>6) Identify the function which generates the K-map shown</p> <p>a. <math>F(A,B,C) = \sum (0,2,4,7)</math></p> <p>b. <b><math>F(A,B,C) = \sum (1,3,5,6)</math></b></p> <p>c. <math>F(A,B,C) = \sum (3,4,5,6)</math></p> <p>d. <math>F(A,B,C) = \prod (1,3,5,7)</math></p>	<table border="1" data-bbox="1019 373 1442 573"> <thead> <tr> <th colspan="2"></th> <th colspan="4">AB</th> </tr> <tr> <th colspan="2"></th> <th>00</th> <th>01</th> <th>11</th> <th>10</th> </tr> </thead> <tbody> <tr> <th rowspan="2">C</th> <th>0</th> <td>0</td> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <th>1</th> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> </tbody> </table>			AB						00	01	11	10	C	0	0	0	1	0	1	1	1	0	1										
		AB																																
		00	01	11	10																													
C	0	0	0	1	0																													
	1	1	1	0	1																													
<p>7) Identify the most simple Product of Sums (POS) expression which generates the K-map show</p> <p>a. <math>F(A, B, C) = (A + C')(A + B + C)</math></p> <p>b. <math>F(A, B, C) = (A + B)(B + C')</math></p> <p>c. <b><math>F(A, B, C) = (A' + B')(A' + C)(B' + C)</math></b></p> <p>d. <math>F(A, B, C) = (A' + C)(A' + B' + C)</math></p>	<table border="1" data-bbox="1019 711 1442 911"> <thead> <tr> <th colspan="2"></th> <th colspan="4">AB</th> </tr> <tr> <th colspan="2"></th> <th>00</th> <th>01</th> <th>11</th> <th>10</th> </tr> </thead> <tbody> <tr> <th rowspan="2">C</th> <th>0</th> <td>1</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <th>1</th> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> </tbody> </table>			AB						00	01	11	10	C	0	1	0	0	0	1	1	1	0	1										
		AB																																
		00	01	11	10																													
C	0	1	0	0	0																													
	1	1	1	0	1																													
<p>8) Identify the simplest expression from the K-map shown.</p> <p>a. <math>F(A, B, C, D) = BC' + BCD' + AC'D'</math></p> <p>b. <math>F(A, B, C, D) = BC' + BCD' + AB'C'D'</math></p> <p>c. <math>F(A, B, C, D) = AD + BCD' + CD</math></p> <p>d. <b><math>F(A, B, C, D) = BC' + BD' + AC'D'</math></b></p>	<table border="1" data-bbox="1060 1060 1474 1360"> <thead> <tr> <th colspan="2"></th> <th colspan="4">AB</th> </tr> <tr> <th colspan="2"></th> <th>00</th> <th>01</th> <th>11</th> <th>10</th> </tr> </thead> <tbody> <tr> <th rowspan="4">CD</th> <th>00</th> <td></td> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <th>01</th> <td></td> <td>1</td> <td>1</td> <td></td> </tr> <tr> <th>10</th> <td></td> <td></td> <td></td> <td></td> </tr> <tr> <th>11</th> <td></td> <td>1</td> <td>1</td> <td></td> </tr> </tbody> </table>			AB						00	01	11	10	CD	00		1	1	1	01		1	1		10					11		1	1	
		AB																																
		00	01	11	10																													
CD	00		1	1	1																													
	01		1	1																														
	10																																	
	11		1	1																														
<p>9) The circuit has the same functionality</p> <p>a. <b>XNOR</b></p> <p>b. XOR</p> <p>c. NAND</p> <p>d. NOR</p>																																		

10) For the shown multiplexer, the Boolean function:

 
- a.  $F = x' y + x' z + y z$
- b.  **$F = x y + x z + y z$**
- c.  $F = x y' + x z + y' z$
- d.  $F = x y + x z' + y z'$



11) In the shown circuit, given "X" is a 3-bit binary number


( $x_2x_1x_0$ ):

 - a.  $F = 1$  when "X" is less than 4
- b.  **$F = 1$  when "X" is greater than 4**
- c.  $F = 1$  when "X" is an even number
- d.  $F = 1$  when "X" is an odd number



12) In the shown circuit, given "X" is a 2-bit binary number ( $x_1x_0$ ):

 
- a. Sum = X
- b. Sum = 2 X
- c. **Sum = 2 X + 1**
- d. Sum = 2 X + 2



13) The sequential circuit below yields an output sequence of Z= 11011111 when you apply the input sequence X = 01101010.

What is the starting state of the JK Flip-Flop?

 - a.  $A, A' = 0, 0$
- b.  $A, A' = 0, 1$
- c.  **$A, A' = 1, 0$**
- d.  $A, A' = 1, 1$




14) A Universal Shift Register, USR, is connected as shown.  $S_1 =$

1,  $S_0 = 1$  select load operation. Initially  $Q_3Q_2Q_1Q_0 = 1010$ .

After 2 clock cycles:

 - a.  $Q_3Q_2Q_1Q_0 = 0000$
- b.  $Q_3Q_2Q_1Q_0 = 1111$
- c.  $Q_3Q_2Q_1Q_0 = 1001$
- d.  $Q_3Q_2Q_1Q_0 = 1010$



15) For the Given State Table:


- a. States A and B are equivalent
- b. **States A and D are equivalent**
- c. States C and D are equivalent
- d. States C and E are equivalent

Present State	Next State		Output	
	$x=0$	$x=1$	$x=0$	$x=1$
A	B	D	0	1
B	A	B	1	1
C	E	A	0	0
D	B	D	0	1
E	D	C	1	0


**Question 2 (15 points)**

A Mealy machine has one input X and one output Z. Given the following next-state table, use the **triangular table** provided below to minimize the number of states (use the implication chart method).

Present State	Next State		Output Z	
	X=0	X=1	X=0	X=1
S <sub>0</sub>	S <sub>4</sub>	S <sub>1</sub>	0	1
S <sub>1</sub>	S <sub>2</sub>	S <sub>3</sub>	1	0
S <sub>2</sub>	S <sub>5</sub>	S <sub>0</sub>	1	0
S <sub>3</sub>	S <sub>4</sub>	S <sub>5</sub>	0	1
S <sub>4</sub>	S <sub>2</sub>	S <sub>5</sub>	1	0
S <sub>5</sub>	S <sub>1</sub>	S <sub>3</sub>	1	0

 

Present state	Next state		Output Z	
	X=0	X=1	X=0	X=1
S <sub>0</sub>	S <sub>4</sub>	S <sub>1</sub>	0	1
S <sub>1</sub>	S <sub>2</sub>	S <sub>3</sub>	1	0
S <sub>2</sub>	S <sub>5</sub>	S <sub>0</sub>	1	0
S <sub>3</sub>	S <sub>4</sub>	S <sub>5</sub>	0	1
S <sub>4</sub>	S <sub>2</sub>	S <sub>5</sub>	1	0
S <sub>5</sub>	S <sub>1</sub>	S <sub>3</sub>	1	0

 

g0: {S0, S3}

g1: {S1, S2, S5}


g2: {S4}

g3:

Present state	Next state		Output Z	
	X=0	X=1	X=0	X=1
g0	g2	g1	0	1
g1	g1	g0	1	0
g2	g1	g1	1	0

 
**Question 3 (20 points)** (ABET Outcome c: Ability to design a system, component, or process to meet desired needs.)

Design the sequential circuit specified by the state diagram of Fig. Q2b using T flip-flops. (20 points)



Present State			Input	Next State			Flip-flop Inputs		
A	B	C	x	A	B	C	T <sub>A</sub>	T <sub>B</sub>	T <sub>C</sub>
0	0	0	0	0	0	1	0	0	1
0	0	0	1	0	1	0	0	1	0
0	0	1	0	0	1	0	0	1	1
0	0	1	1	0	1	1	0	1	0
0	1	0	0	0	1	1	0	0	1
0	1	0	1	1	0	0	1	1	0
0	1	1	0	1	0	0	1	1	1
0	1	1	1	1	0	1	1	1	0
1	0	0	0	1	0	1	0	0	1
1	0	0	1	1	1	0	0	1	0
1	0	1	0	1	1	0	0	1	1
1	0	1	1	1	1	1	0	1	0
1	1	0	0	1	1	1	0	0	1
1	1	0	1	0	0	0	1	1	0
1	1	1	0	0	0	0	1	1	1
1	1	1	1	0	0	1	1	1	0


$$T_C = x'$$

 

$$T_A = Bx + BC = B(x + C)$$

		Cx			
		00	01	11	10
AB	00	1	1	1	
	01	1	1	1	
	11	1	1	1	
	10	1	1	1	


$T_A = x + C$

 




**Question 4 (20 points)**

 
- a) Using the counter shown below and logic gates design a counter that counts in the sequence 3,4, 5, 6, 7, 8, 9, 10, 11, 12, 3, ... Connect all unused inputs. The counter may cycle through several unwanted states before settling into the final count sequence.  $Q_3$  is the most significant bit of the counter output. (10 points)



Function Table for the Counter				
<i>CLR</i>	<i>CLK</i>	<i>LD</i>	<i>Count</i>	Function
0	x	x	x	Clear to 0
1	↑	1	x	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

 

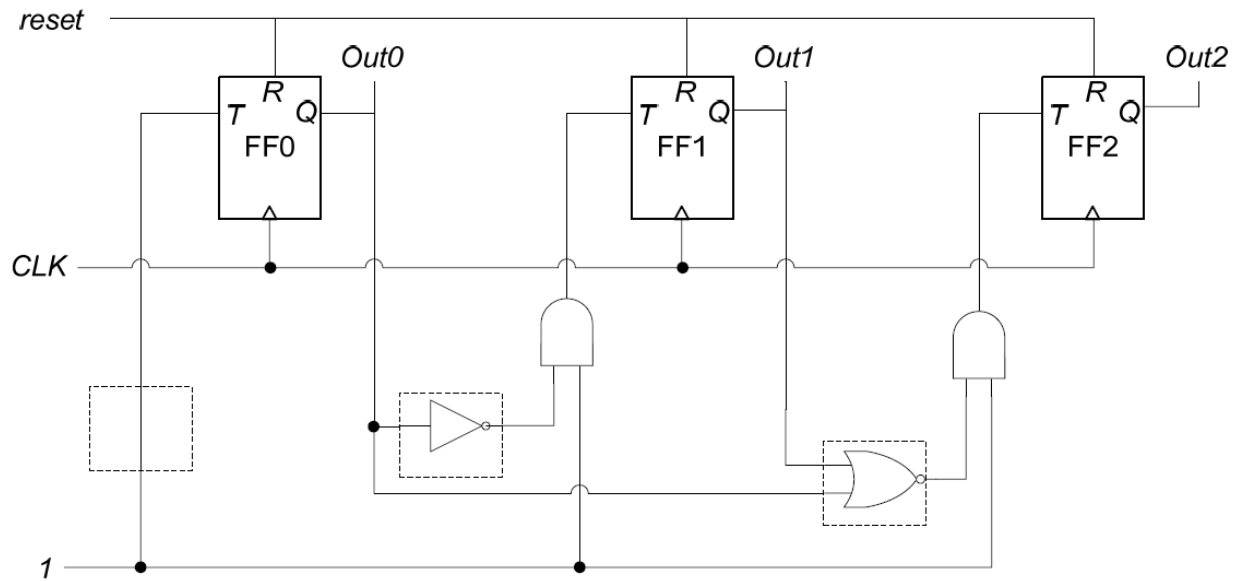- a) An incomplete schematic of a **down-counter** is shown below. This design uses **T flip-flops** as the internal storage. You are asked to finish up this design by filling in all the boxes. Each box can only contain a **direct wire** or exactly one gate which must belong to the cell library {**AND, OR, NAND, NOR, XOR, XNOR, inverter**}. (10 points)



**Question 5 (15 points)** (ABET Outcome e: Ability to identify, formulate and solve engineering problems.)

- a. Write a Verilog description for the MUX2x1 (5 points)
- b. Write a Verilog description for the DFF (5 points)
- c. Structurally build the Circuit in the figure (5 points)

