



Electrical and Computer Engineering Department

Summer Semester 2017

Digital Systems (ENCS234)

Final Exam

Allowed Time: 150 minutes

Date: 29/08/2017

Room: Masri109

Instructor: Dr. Abdellatif Abu-Issa

Dr. Ahmad Alsadeh

Student Name: _____ **Student ID:** _____

Question #	Full Mark	Student Mark
Q1	40	
Q2	14	
Q3	12	
Q4	12	
Q5	22	
TOTAL	100	

Note: write your solution on the space provided. If you need more space, write on the back of the sheet containing the question.

Q1] Select the correct answer (40 points, 2.5 points each):

1) In octal, the twelve-bit two's complement of the hexadecimal number $2AF_{16}$ is

- A. 6522_8
- B. 6251_8
- C. 5261_8
- D. 6521_8

2) Which of the following functions is the constant **1** function?

- A. $x' + xy$
- B. $xy + x' + xy'$
- C. $xy'(x' + y)$
- D. $(x' + y)(xy)$

3) Which of the following is equal to $F(x, y) = \sum(m_0, m_0)$

- A. $xy + x'y$
- B. $x.y' + x'.y$
- C. $(x + y')(x' + y)$
- D. $(x' + y')(x + y)$

4) How many 2-to-4 decoders with enable input should be used to make a 6-to-64 decoder?

- A. 19
- B. 18
- C. 20
- D. 21

5) The following function has ___ Essential prime implicants

- A. 2
- B. 4
- C. 5
- D. 8

	CD			
	00	01	11	10
AB	/			
00			1	
01	1	1	1	
11		1	1	1
10		1		


6) Which function is the best for implementing the following function with two level NOR-OR form

- A. $F = x'y'z' + xyz'$
- B. $F = x'y + xy' + z$
- C. $F = (x'y + xy' + z)'$
- D. $F = [(x + y + z)(x' + y' + z)]'$

x \ yz	00	01	11	10
0	1			
1				1


7) The following two circuits have the same functionality of

 - A. 2-input OR gate
- B. 2-input NOR gate
- C. 2-input XOR gate
- D. 2-input XNOR gate




8) Implementation of full adder with two half adders and an ___ gate

- A. OR
- B. NOR
- C. XOR
- D. XNOR

 

9) Implementation of a full adder with an active low decoder and two

 - A. OR gates
- B. NOR gates
- C. AND gates
- D. NAND gates



10) Two 'T' Flip-Flops, A and B, are used to implement a sequential circuit. To go from state "AB = 10" to "AB = 11" we need:

- A. $T_A = 0, T_B = 0$
- B. $T_A = 0, T_B = 1$
- C. $T_A = 1, T_B = 0$
- D. $T_A = 1, T_B = 1$


11) If the present state (ABC) is 110, and the input $x = 0$; what will be the next state if the flip flops input functions are:

$$J_A = B'x, K_A = 1; \quad J_B = A + C'x, K_B = xC' + Cx'; \quad J_C = Ax + A'B'x', K_C = x$$

- A. 111
- B. 001
- C. 010
- D. 011


12) If $S_1=1, S_0=0$ when the Clock is received, then $A_0(t + 1)$ and $A_1(t + 1)$ will be

 - A. $A_0(t + 1) = L \quad A_1(t + 1) = A_0$
- B. $A_0(t + 1) = A_1 \quad A_1(t + 1) = R$
- C. $A_0(t + 1) = I_0 \quad A_1(t + 1) = I_1$
- D. $A_0(t + 1) = A_0 \quad A_1(t + 1) = A_1$




13) Number of data bits that can be stored in the register shown below is _____ and number of clock cycles needed to store data is _____.

- A. 4, 1
- B. 4, 4
- C. 8, 1
- D. 8, 4

 

14) The sequence of counting in decimal for the counter shown below is


Clr	Clk	LD	Count	Operation
x	0	x	x	Clear to 0
1	↑	1	x	Load inputs
1	↑	0	1	Count up
1	↑	0	0	No change

 


- A. 6, 7, 8, 9, 10, 6 ...
- B. 12, 11, 10, 9, 8, 7, 6, 12, ...
- C. 6, 7, 8, 9, 10, 11, 12, 6, ...
- D. 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 0, ...

15) If *Load* input is zero, then the circuit will _____ when the clock is received.

 - A. Count up
- B. count down
- C. No change of the state
- D. Parallel load the inputs ($I_0 \dots I_3$)



 16) The serial transfer shown in Figure below consists of two 4-bit shift registers (*A* and *B*). Assume that the initial contents of registers *A* and *B* is 1011 and 0010 respectively. After 2 clock pulses, what would be the content of registers *A* and *B*.



- A. A = 1011 B = 1011
- B. A = 1101 B = 1001
- C. A = 1110 B = 1100
- D. A = 0111 B = 0110


Answering Sheet for Question 1

1)	
2)	
3)	
4)	
5)	
6)	
7)	
8)	
9)	
10)	
11)	
12)	
13)	
14)	
15)	
16)	

Q2] Given the state table below, minimize the number of states using implication chart method. Write down the equivalent states and the reduced table. **(14 points)**


Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
A	F	B	0	0
B	E	G	0	0
C	C	G	0	0
D	A	C	1	1
E	E	D	0	0
F	A	B	0	0
G	F	C	1	1

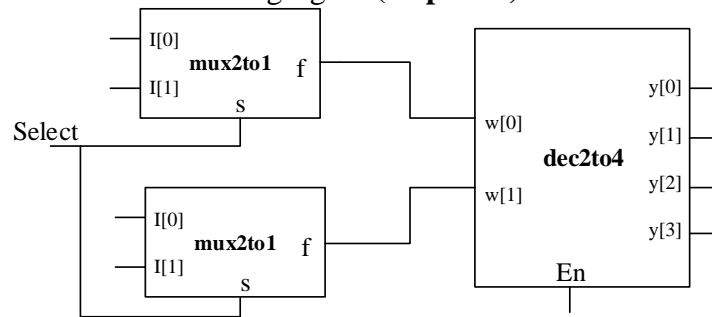Q3] For the system shown in the following figure **(12 points)**




- a) **(4 pts)** Write a Verilog behavioral description for the module `mux2to1`
- b) **(4 pts)** Write a Verilog behavioral description for the module `dec2to4`
- c) **(4 pts)** Write a Verilog code to describe the whole system structurally from its subsystems

 Q4] For the following circuit (12 points)



a) (2 pts) Is it ripple or synchronous and why?

 b) (6 pts) Draw the timing diagram Starting from ($Q_2Q_1Q_0=000$)



c) (4 pts) Draw the state diagram

Q5] Design a counter circuit that repeats five states in sequence; 000, 010, 011, 101, 110, 000 using D- Flip flops. The circuit is to be designed by treating the unused states as don't-care conditions. **(22 points)**

- a) **(2 pts)** Draw the state diagram of the circuit.
- b) **(6 pts)** Tabulate the state transition table.
- c) **(6 pts)** Derive the state equations for the flip-flops.
- d) **(4 pts)** Implement the counter using D- Flip flops and the needed gates
- e) **(4 pts)** Analyze the circuit obtained from the design to determine the effect of the unused states.
What will happen if a noise signal sends the circuit to one of the unused states?

