

Mohammed Hussem
key



Faculty of Engineering & Technology – Electrical & Computer Engineering Department

First Semester 2017-2018

Digital Systems (ENCS234)

Midterm Exam

Allowed Time: 90 minutes

Total Marks: 100

Date: 03/12/2017

Student ID : key (Only your ID without your name and your instructor name)

| ABET Outcome | Question # | Full Mark | Student Mark |
|--------------|--------------|------------|--------------|
| | Q#1 | 45 | |
| | Q#2 | 18 | |
| | Q#3 | 12 | |
| | Q#4 | 10 | |
| | Q#5 | 15 | |
| | TOTAL | 100 | |

Note: write your solution on the space provided. If you need more space, write on the back of the sheet containing the question.

Q1] Select the correct answer (45 points, 3 points each):

1) What is the number represented of the binary words 10010010, assuming the representation is in Two's complement

- A. -110
- B. 110
- C. -109
- D. -108
- E. None

2) The number $(161)_{10}$ is equivalent to:

- A. $(11)_{16}$
- B. $(1A)_{16}$
- C. $(A1)_{16}$
- D. $(AA)_{16}$
- E. None

3) The number $(55)_8$ is equivalent to:

- A. $(2D)_{16}$
- B. $(D2)_{16}$
- C. $(B1)_{16}$
- D. $(1B)_{16}$
- E. None

4) Using BCD code, when a computer adds $(01001001)_2 + (10000000)_2$ the result of this addition:

- A. is a correct BCD number.
- B. must be corrected by adding $(00000110)_2$.
- C. must be corrected by adding $(01100000)_2$.
- D. must be corrected by adding $(01100110)_2$.
- E. is wrong and can't be corrected.
- F. None

5) Even parity is:

- A. an extra bit added to make the total number of ones even to detect odd number of errors.
- B. an extra bit added to make the total number of ones even to detect even number of errors.



- C. an extra bit added to make the total number of ones odd to detect odd number of errors.
- D. an extra bit added to make the total number of ones odd to detect even number of errors.
- E. an extra bit added to make the total number of ones even to detect any number of errors.

6) Given $F(x, y, z) = \prod(0, 3, 4, 7)$, and G is the complement of F , then:

- A. $G(x, y, z) = \sum(0, 1, 2, 3, 5, 7)$
- B. $G(x, y, z) = \prod(0, 3, 4, 7)$
- C. $G(x, y, z) = \sum(1, 2, 5, 6)$
- D. $G(x, y, z) = \sum(0, 3, 4, 7)$
- E. None

7) The binary value of $S_4 S_3 S_2 S_1 S_0$ in the circuit beside is

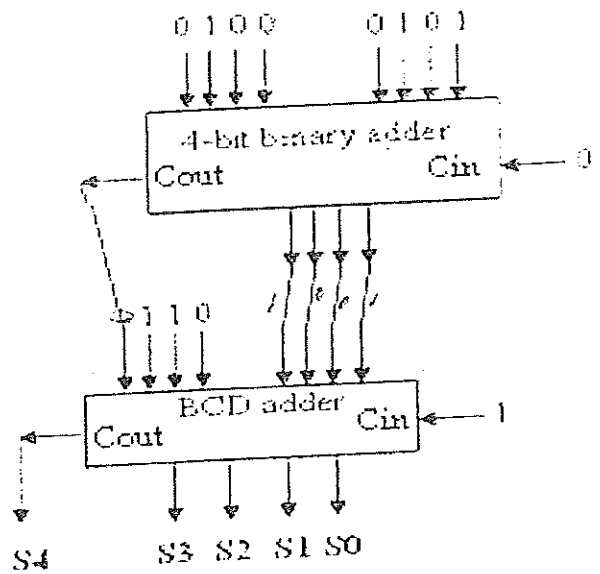 - A. 10001
- B. 10110
- C. 10000
- D. 01001
- E. None



8) What is the result of Boolean expression simplification for $(B \oplus C) + (AB)'(A' + C)'$

- A. $B \oplus C$
- B. $A \oplus C$
- C. $(B \oplus C)'$

$$\begin{aligned}
 &= B'C + BC' + [A'BC + ABC] \\
 &= B'C [1 + A] + BC' \\
 &= B \oplus C
 \end{aligned}$$

D. $(A \oplus B)'$

E. None

9) In the shown K-map, the essential prime implicant is

A. AC

B. CD

C. $A'D$

D. $A'C'$

E. None

| | | | | | |
|----|----|----|----|----|----|
| | | CD | | | |
| | AB | 00 | 01 | 11 | 10 |
| 00 | | 1 | X | 1 | X |
| 01 | | 1 | X | 1 | |
| 10 | | | | 1 | X |
| 11 | | | | X | X |

10) The output Y of the circuit computes


A. the sum bit of a full adder

B. the carry bit of a full adder

C. the complement of A


D. Complement of B

E. None

 


11. Which function F is implemented by using this 4X1 Multiplexer

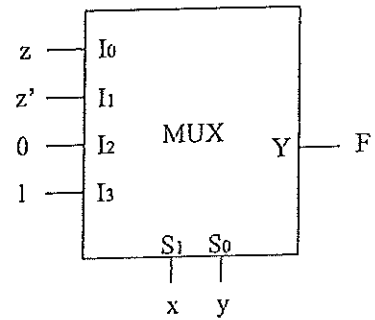- A. $F(x, y, z) = \sum(0, 3, 4, 5)$
- B. $F(x, y, z) = \sum(1, 3, 6, 7)$
- C. $F(x, y, z) = \sum(1, 2, 6, 7)$
- D. $F(x, y, z) = \sum(1, 2, 5, 7)$
- E. None



12. Implementation of full adder with two half adders and an ___ gate

 - A. OR
- B. NOR
- C. XOR
- D. XNOR
- E. None




13. For the function F , the minimum product of sums expression

- A. $F = w'x + w'y' + xy'z'$
- B. $F = x'y + wx' + wz + wy$
- C. $F = (x + y')(w' + x)(w' + z')(w' + y')$
- D. $F = (w + x')(w + y)(x' + y + z)$
- E. None

| | | | | | |
|------|----|------|----|----|----|
| | | wx | | | |
| | | 00 | 01 | 11 | 10 |
| yz | 00 | 1 | 1 | 1 | 0 |
| | 01 | 1 | 1 | 0 | 0 |
| | 11 | 0 | 1 | 0 | 0 |
| | 10 | 0 | 1 | 0 | 0 |


14. For the shown Demux, the Boolean function is

 - A. $F = x' y' z + x y z$
- B. $F = x' y z + x y z$
- C. $F = x y' z + x y z$
- D. $F = x y' z' + x y z$
- E. None



15. For the shown circuit the function F is

 - A. $F = X \text{ AND } Y$
- B. $F = X \text{ OR } Y$
- C. $F = X \text{ XOR } Y$
- D. $F = X \text{ XNOR } Y$
- E. None



| | | | | | | | | | |
|---|---|---|---|---|---|---|---|---|----|
| 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 |
| A | C | A | C | A | D | B | A | D | A |

| | | | | |
|----|----|----|----|----|
| 11 | 12 | 13 | 14 | 15 |
| C | A | C | C | C |

Q2] 18 points

Simplify using QM Tabulation method the following function

$F(A,B,C,D) = \sum m(0,1,2,3,5,7,8,10,14,15)$

1st 2

1st 1

| miniterm | A | B | C | D |
|----------|---|---|---|---|
| ✓ 0 | 0 | 0 | 0 | 0 |
| ✓ 1 | 0 | 0 | 0 | 1 |
| ✓ 2 | 0 | 0 | 1 | 0 |
| ✓ 8 | 1 | 0 | 0 | 0 |
| ✓ 3 | 0 | 0 | 1 | 1 |
| ✓ 5 | 0 | 1 | 0 | 1 |
| ✓ 10 | 1 | 0 | 1 | 0 |
| ✓ 7 | 0 | 1 | 1 | 1 |
| ✓ 14 | 1 | 1 | 1 | 0 |
| 15 | 1 | 1 | 1 | 1 |

| miniterm | A | B | C | D |
|----------|---|---|---|---|
| ✓ (011) | 0 | 0 | 0 | 1 |
| ✓ (012) | 0 | 0 | 1 | 0 |
| ✓ (013) | 0 | 0 | 1 | 1 |
| ✓ (113) | 1 | 0 | 0 | 1 |
| ✓ (115) | 1 | 0 | 1 | 1 |
| ✓ (213) | 0 | 1 | 0 | 1 |
| ✓ (215) | 0 | 1 | 1 | 1 |
| ✓ (8110) | 1 | 0 | 1 | 0 |
| ✓ (317) | 0 | 1 | 1 | 1 |
| ✓ (517) | 0 | 1 | 1 | 1 |
| (10114) | 1 | 0 | 1 | 0 |
| (7115) | 0 | 1 | 1 | 1 |
| (14115) | 1 | 1 | 1 | 1 |

1st 3


| miniterm | A | B | C | D |
|-----------|---|---|---|---|
| 011213) | 0 | 0 | - | - |
| 01218110) | - | 0 | - | 0 |
| 1131517) | 1 | 0 | - | - |
| 10114 | 1 | 0 | - | - |
| 7115 | 0 | 1 | - | - |
| 14115 | 1 | 1 | - | - |

| | 0 | 1 | 2 | 3 | 5 | 7 | 8 | 10 | 14 | 15 |
|----------|---|---|---|---|---|---|---|----|----|----|
| 011213 | ✓ | ✓ | ✓ | ✓ | | | | ✓ | | |
| 01218110 | ✓ | | ✓ | | ✓ | ✓ | | | | |
| 1131517 | | ✓ | | | | | | ✓ | ✓ | |
| 10114 | | | | | | ✓ | | | | ✓ |
| 7115 | | | | | | ✓ | | | ✓ | ✓ |
| 14115 | | | | | | | | | ✓ | ✓ |

$F = \bar{0}\bar{1}\bar{2}\bar{3} + \bar{0}\bar{1}2\bar{8}110 + 1131517 + 10114 + 7115 + 14115$
 $= \bar{R}\bar{D}' + A'D + ABC$

 Q3] 12 points

For the shown logic diagram, determine for each input combination of X, Y and Z the value of each output, Y7 through Y0.



| X | Y | Z | Y7 | Y6 | Y5 | Y4 | Y3 | Y2 | Y1 | Y0 |
|---|---|---|----|----|----|----|----|----|----|----|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |


Q4] 10 points

Many offices and buildings use combination locks to control entry. As the design engineer of the *Wonderful Door Security Company*, you are asked to implement a door security system by using a card reader. There are four inputs to the card reader: inputs X, Y, and Z are used to validate the correct door code, and input V is used to check if the card reader is still valid. After the card reader is being read by the system, there are three outputs to this system: alarm (A), door open (D), and Error (E). Door (D) will only open when the decimal value of the binary inputs (x, y, z) is odd (عدد فردي) AND the card reader is valid. The Error (E) signal goes on when the code on the card is correct (i.e. decimal value equal to odd) but the card is no longer valid. Finally, the alarm (A) will trigger when the code is incorrect (i.e. decimal value equal to even). Derive the truth table only

| X | Y | Z | V | A | D | E |
|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 1 | 0 |

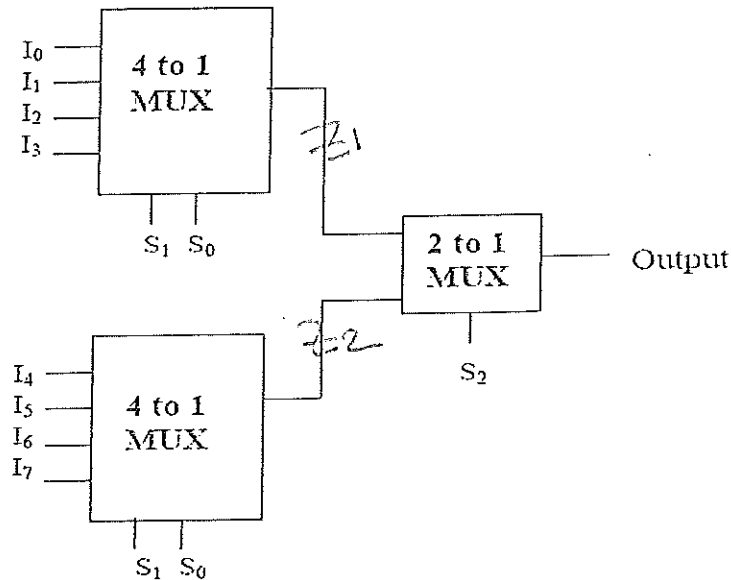Q5] 15 points

For the system shown in the following figure



1. (5 points) Write a Verilog HDL code to describe the module mux4x1
2. (4 points) Write a Verilog HDL code to describe the module mux2x1
3. (6 points) Write a Verilog HDL code to describe the whole system structurally from its subsystems

①

```

module mux4x1 ( A, B, C, D, X, Y, F );
  input  A, B, C, D, X, Y;
  output F;

  wire  w1, w2;
  wire  w3, w4, w5, w6;
  not   G1 (w1, X);
  not   G2 (w2, Y);
  and   G3 (w3, A, w1, w2);
  and   G4 (w4, B, w1, Y);
  and   G5 (w5, C, X, w2);
  and   G6 (w6, D, X, Y);
  or    G7 (F, w3, w4, w5, w6);

  // X Y selection
  // A B C D inputs

```

```

2 module mux21 (A, B, S, Y);
  output Y;
  input A, B, S;
  wire W1, W2, W3;
  not G1 (W1, S);
  and G2 (W2, A, W1);
  and G3 (W3, B, S);
  or G4 (Y, W2, W3);
end module

```

```

3 module wholesystem (I0, I1, I2, I3, I4, I5, I6, I7, S1, S2, S3, S4);
  output Output;
  input I0, I1, I2, I3, I4, I5, I6, I7, S1, S2, S3, S4;
  wire Z1, Z2;

  mux41 G1 (I0, I1, I2, I3, S1, S0, Z1);
  mux41 G2 (I4, I5, I6, I7, S1, S0, Z2);
  mux21 G3 (Z1, Z2, S2, Output);

end module

```