

Question 1: (60 points, 3 points each). Select the correct answer

1	2	3	4	5	6	7	8	9	10
B	D	A	D	A	<del>C</del>	B	D	B	C

11	12	13	14	15	16	17	18	19	20
B	C	D	B	C	D	D	A	C	A

1. Simplify the following expression  $\overline{ABCD}$

$$(\overline{AB(CD)}) = (A' + B') + C$$

- A.  $A'B'CD$
- B.  $A' + B' + CD$
- C.  $AB + C'D'$
- D.  $A' + B' + C + D$
- E. None

2. The code where all successive numbers differ from their preceding number by a single bit is

- A. Binary code
- B. BCD
- C. Excess - 3
- D. Gray
- E. None

3. (-8) is equal to a signed binary number

- A. 10001000
- B. 00001000
- C. 10000000
- D. 11000000
- E. None

4. How many AND gates are required to realize  $Y = CD + EF + G$

- A. 4
- B. 5
- C. 3
- D. 2
- E. None

5. Which of following are known as universal gates

- A. NAND & NOR
- B. AND & OR
- C. XOR & OR
- D. NAND & AND
- E. None

6. For the gate in the given figure, the output will be

- A. 0
- B. 1
- C. A
- D.  $A'$
- E. None



$$\overline{A \cdot 0} = \overline{0} = 1$$

A

7. A full adder can be made out of
- A. two half adders
  - B. two half adders and an OR gate
  - C. two half adders and a NOT gate
  - D. three half adders
  - E. None
8. An OR gate with schematic "bubbles" on its inputs performs the same functions as a \_\_\_\_\_ gate.
- A. NOR
  - B. OR
  - C. NOT
  - D. NAND
  - E. None
9. An adder-subtractor single unit can be designed using full adder and
- A. OR gates
  - B. XOR gates
  - C. NOR gates
  - D. NAND gates
  - E. None
10. The Boolean function  $F = A \oplus B \oplus C \oplus D = 1$  means:
- A. one or two or three of the inputs are ones
  - B. all inputs are zeros ( $A = 0, B = 0, C = 0, D = 0$ )
  - C. one or three of the inputs are ones.
  - D. all inputs are ones ( $A = 1, B = 1, C = 1, D = 1$ )
  - E. half of the inputs are zeros (for example:  $A = 0, B = 0, C = 1, D = 1$ )

11. The decimal number (64) in BCD requires \_\_\_\_\_ bits, and to represent the same decimal number in binary requires \_\_\_\_\_ bits.

- A. 3,2
- B. 8,7
- C. 7,7
- D. 6,5
- E. None

0110

2	64
0	32
0	16
0	8

12. The largest hexadecimal number which has 2 integer digits and 1 fraction digit is in hexadecimal \_\_\_\_\_, and it equals \_\_\_\_\_ in decimal.

- A.  $(FF.F)_{16}, (999.9)_{10}$
- B.  $(FF.0)_{16}, (999.9)_{10}$
- C.  $(FF.F)_{16}, (255.9375)_{10}$
- D.  $(FF.F)_{16}, (255.9753)_{10}$
- E. None

13. The number  $(B2.D)_{16}$  is equivalent to \_\_\_\_\_.

- A.  $(177.7125)_8$
- B.  $(262.64)_{10}$
- C.  $(262.64)_{12}$
- D.  $(178.8125)_{10}$
- E. None

0101101010

12 2 6 2

14. Let  $A = (69CE)_{16}$  and  $B = (6AFF)_{16}$  be hexadecimal numbers. The addition operation of  $A+B$  is \_\_\_\_\_ and the final carry bit (0 or 1) is \_\_\_\_\_.

- A. D4CD, 1
- B. D4CD, 0
- C. D5CD, 1
- D. D5CD, 0
- E. None

6	9	C	E	
6	A	F	F	
	9	D		

15. The 7-bit binary code for character "e" is 1100101. Using even parity, the sender inserts an extra parity bit equal to \_\_\_\_\_. The receiver receives an 8-bit binary code equal to 11100100, would the receiver detect an error (Yes/No)? \_\_\_\_\_.

- A. 0, Yes
- B. 1, Yes
- C. 0, No
- D. 1, No
- E. None

16. The 10's complement of  $(935)_{10}$  is \_\_\_\_\_.

- A. 286
- B. 074
- C. 174
- D. 175
- E. None

$$\begin{array}{r} 999 \\ 935 \\ \hline 064 \end{array}$$

17. What is the maximum number that we can count up to using 10 bits? \_\_\_\_\_.

- A. 1024
- B. 9999
- C. 1000
- D. 1023
- E. None

18. Convert  $(0055)$  hex value to decimal

- A. 85
- B. 15
- C. 146
- D. 2047
- E. None


19. Simplify the following Boolean expression  $x = ACD + A'BCD$

$$A \oplus C$$

- A. CD
- B. CDB
- C.  $ACD + BCD$
- D.  $CDA'$
- E. None

20. Write the Boolean expression for output x in the following figure

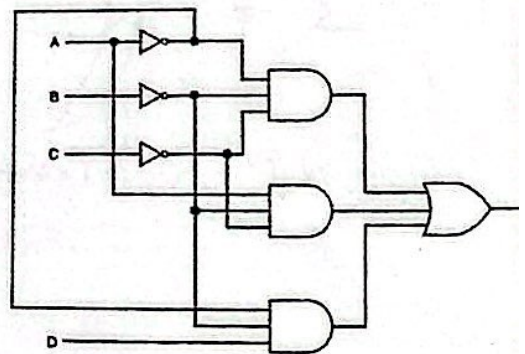- A.  $x = A'B'C' + AB'C' + A'B'D$
- B.  $x = A'B'C' + A'B'C' + A'B'D$
- C.  $x = A'B'C' + AB'C' + A'B'D'$
- D.  $x = A'B'C' + A'B'C' + A'B'D'$
- E. None



$$(A' B' C) + (A B' C) + (A' B' D)$$

Question#3: (14 points)

Design a logic circuit that has three inputs, A, B, and C, and whose output F will be HIGH only when a majority (two or more) of the inputs are HIGH.

1) (4 points) Find the truth table for the function F.

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$F = \Sigma (3, 5, 6, 7)$

2) (2 points) What is the canonical form for the function F given as SOM

$m_3 + m_5 + m_6 + m_7$

$F = \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$


3) (4 points) What is the minimized form for the function F given as SOP

AB	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$F = BC + AB + AC$

92

4)

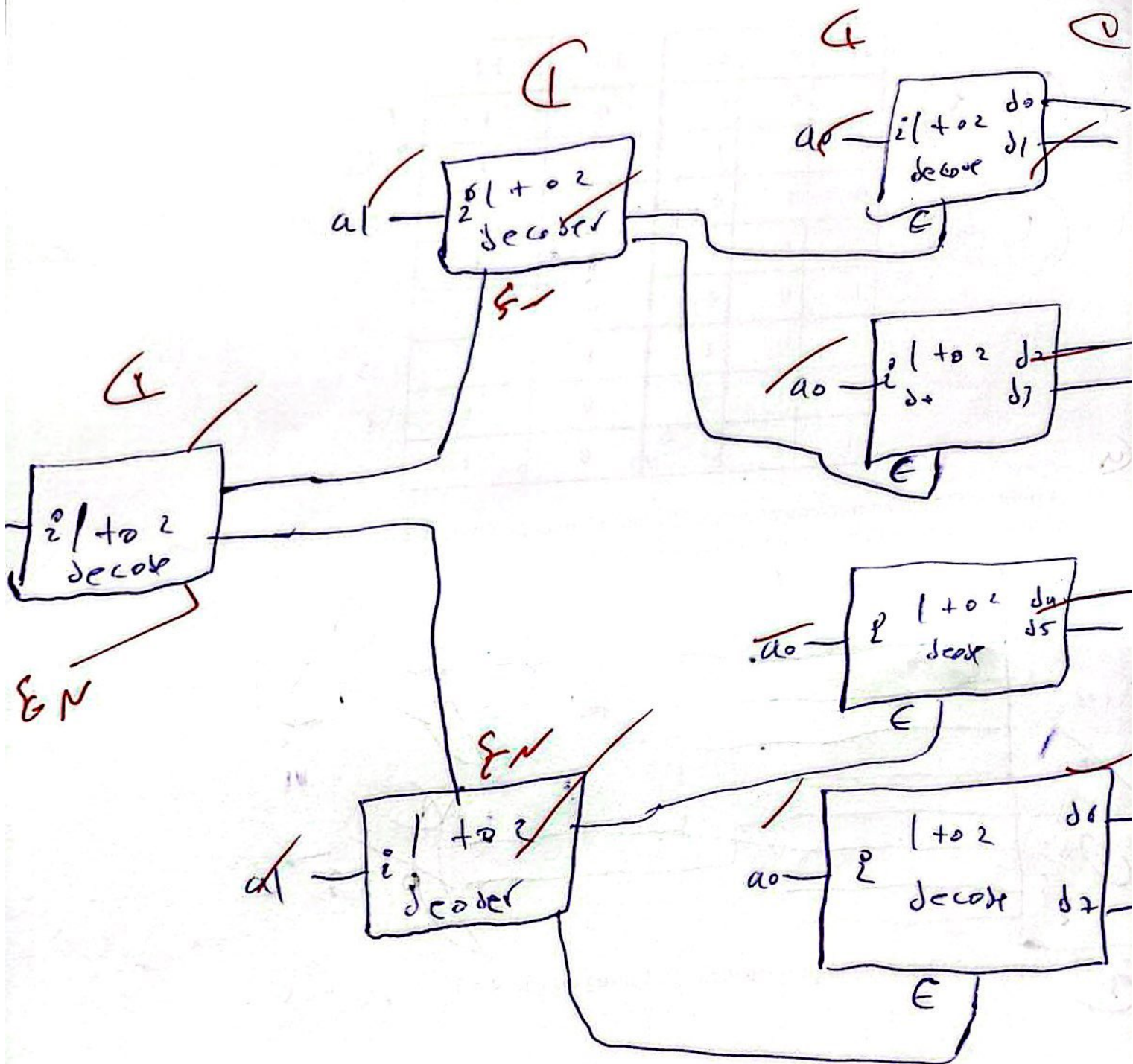

**Question#2: (16 points)**

Consider the functions  $F1(a_2, a_1, a_0)$  and  $F2(a_2, a_1, a_0)$ , whose truth table is shown below:


$a_2$	$a_1$	$a_0$	F1	F2
0	0	0	0	1
0	0	1	1	1
0	1	0	0	0
0	1	1	0	1
1	0	0	0	0
1	0	1	1	1
1	1	0	0	1
1	1	1	0	1

0  
1  
2  
3  
4  
5  
6  
7


$F1 = \{ (0, 1, 5) \}$

$F2 = \{ (1, 4) \}$

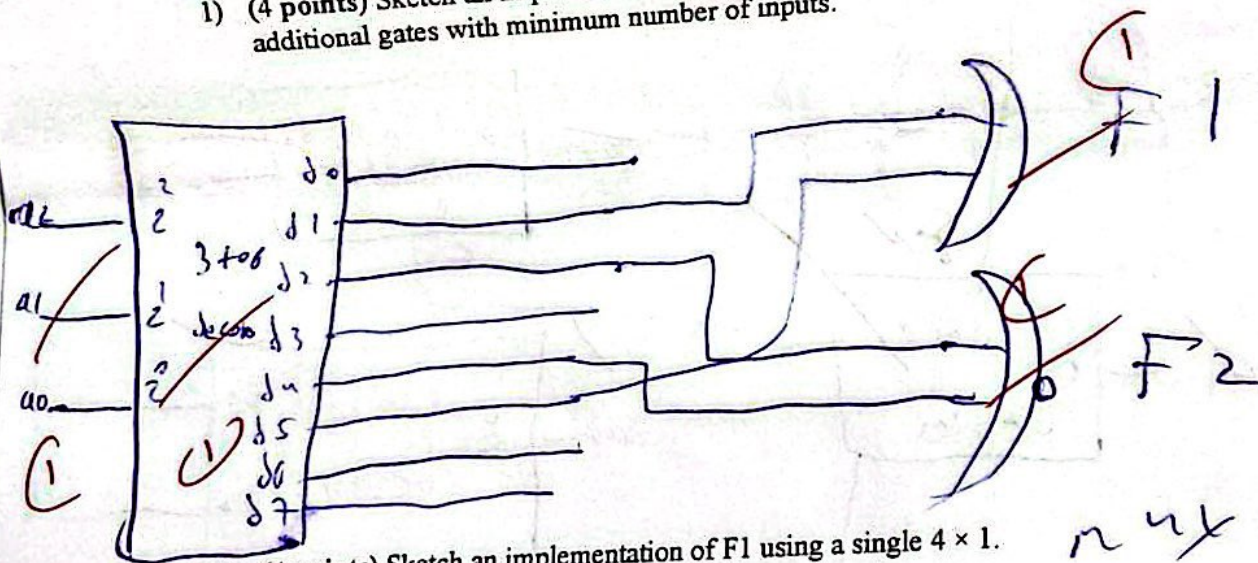- 1) (4 points) Sketch an implementation of F1 and F2 using a single 3-8 decoder and minimum additional gates with minimum number of inputs.






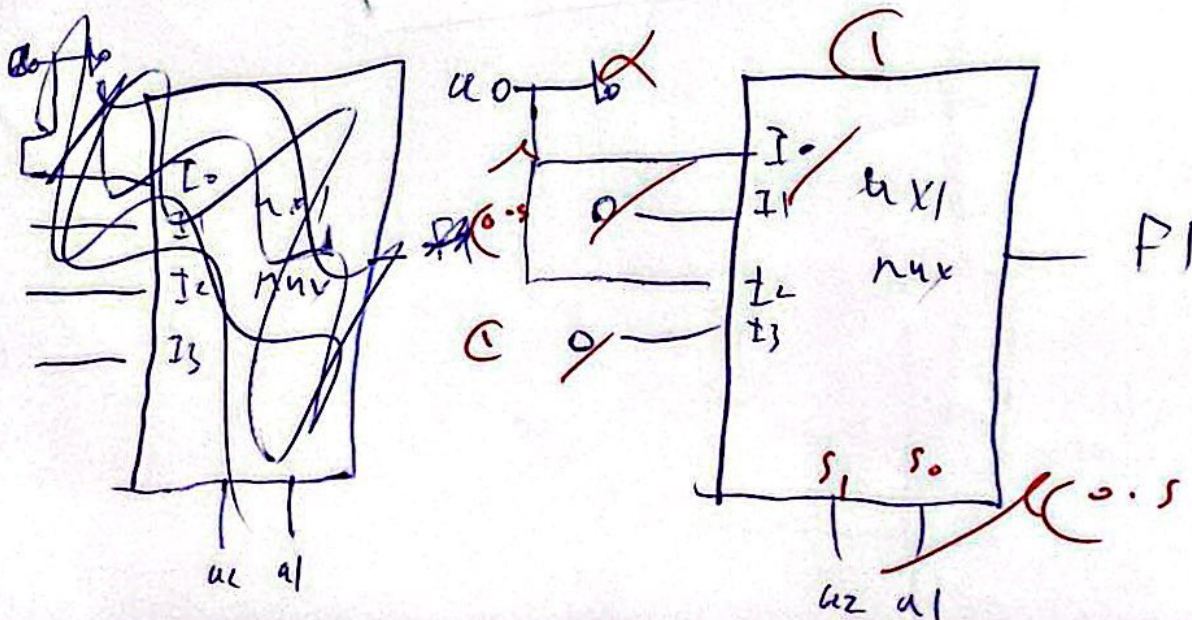- 2) (4 points) Sketch an implementation of F1 using a single  $4 \times 1$  mux.



0 0 1

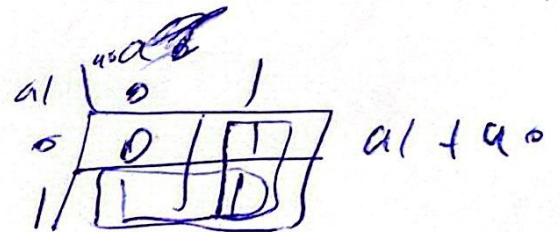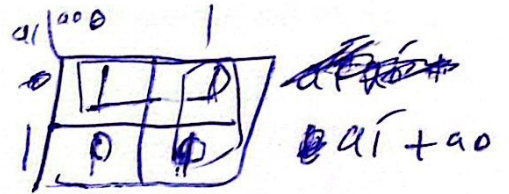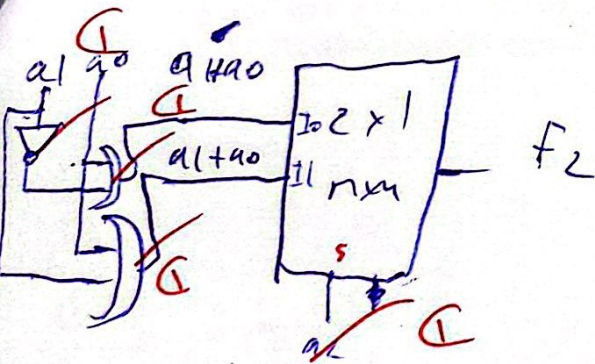
- 3) (4 points) Sketch an implementation of  $F_2$  using a single  $2 \times 1$  and minimum additional gates with minimum number of inputs.




- 4) (4 points) Show how you can construct a 3-8 decoder using minimum number of 1-2 decoders with enable inputs. In your implementation, mark which input corresponds to  $a_0, a_1,$  and  $a_2$ . Also, mark which output corresponds to  $d_0 \dots d_7$



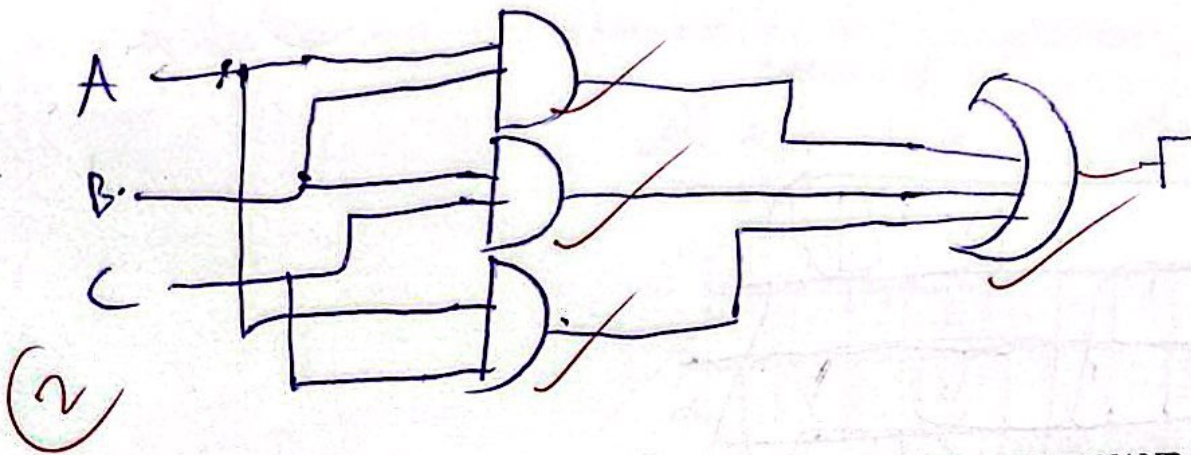4) (2 points) Implement the SOP form of the function  $F$  using AND-OR technology



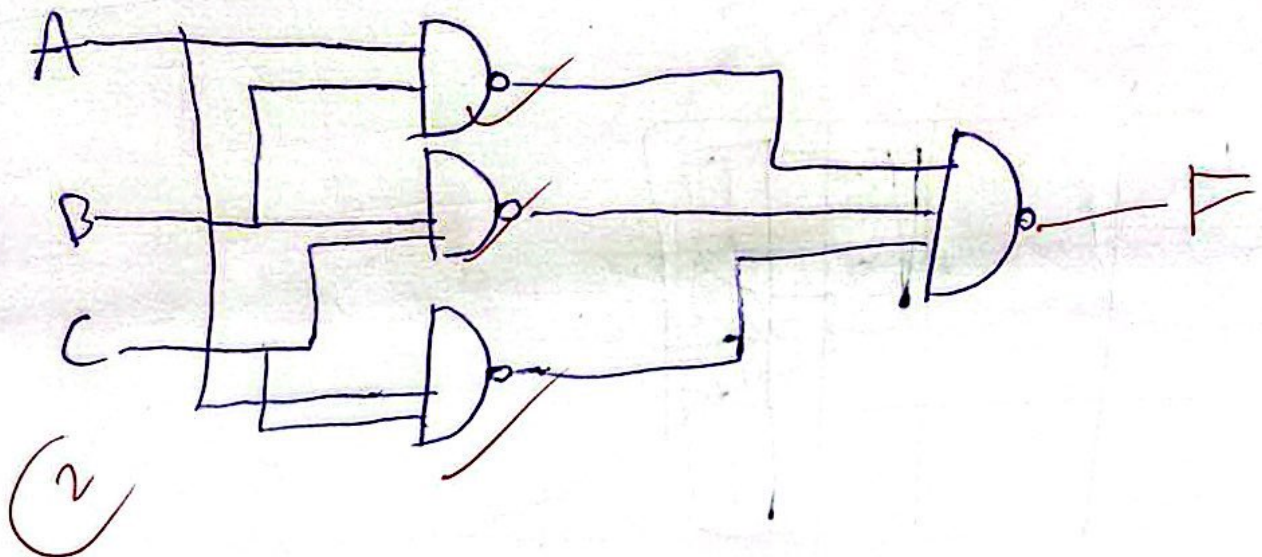5) (2 points) Implement the SOP form of the function  $F$  using NAND-NAND technology





Question#4: (10 points)

Given the following K-map of the function  $g(a, b, c, d)$ , where X is a don't-care:

**K-Map of  $g$**

		$cd$			
		00	01	11	10
$ab$	00	X		X	1
	01	X	1		
	11		1	X	X
	10	1		1	X

- 1) (4 points) Write the terms of all Prime Implicants (PIs) and all Essential Prime Implicants (EPIs) of  $g$ .

$$PIs = b\bar{c}, b\bar{c}d, ac, bc, \dots$$

$$EPIs = b\bar{c}, b\bar{c}d, 2, 5$$

- 2) (4 points) Find all minimum Sum-of-Products expressions of  $g$ .

$$f = b\bar{c} + ac + bcd$$

$$g = b\bar{c} + b\bar{c}d + bc$$

- 3) (2 points) Find all minimum Product-of-Sums expressions of  $g$ .

$$g = (b + d) \cdot (b + c + d) \cdot (b + c)$$