



Summer Semester 2020/2021

Time: 16:15 - 17:15 (75 minutes)

Digital Systems (ENCS2340)

Second...Exam

Date: 22/08/2022

**Instructors:**

- Dr. Aziz Mohammed Qaroush - section 1  
 Dr. Ayman Hroub - section 2

- Dr. Ayman Hroub  
 Dr. Bilal Karaki

- section 3  
- section 4

Student Name: Yazan AbuAlwan Student ID-: 1210115

Question #	Full Mark	Student's Mark
Q1	10	10
Q2	7	6.5
Q3	8	7.5
<b>TOTAL</b>	<b>25</b>	<b>24</b>

**Question 1:** (60 points, 3 points each). Select the correct answer

1	2	3	4	5	6	7	8	9	10
C	D	B	B	A	C	S	C	D	D

...

} 8  
2 11

1- We can construct a 5-to-32-line decoder using:


- A- Five 2-to-4-line decoders with enable.
- B- Two 4-to-16-line decoders without enable and NOT-gate. ✗
- C- Four 3-to-8-line decoders with enable and a 2-to-4-line decoder.
- D- Nine 2-to-4-line decoders with enable.

2- Consider a J-K flip-flop. Let the present state  $Q=0$ ,  $J=1$ , and  $K=1$ , what will be the next state  $Q$  after one clock?

- A. Open circuit (High Impedance)
- B.  $Q=2$
- C.  $Q=0$
- D.  $Q=1$
- E. None of the above.



3 - A digital circuit has two inputs X & Y each has a 2-bit unsigned number. Its output Z is the multiplication of the given inputs  $Z=X \cdot Y$ . The minimum number of bits required for the output number Z is ✗

- A- 3
- B- 4
- C- 5
- D- 6

 

4- The following circuit is an implementation for

  
- A.  $F(A, B, C) = \sum m(0, 1, 3, 4)$
- B.  $F(A, B, C) = \sum m(1, 5, 7)$
- C.  $F(A, B, C) = \sum m(0, 1, 5, 7)$
- D.  $F(A, B, C) = \sum m(0, 2, 3, 4, 7)$
- E. None



\*


5- The following circuit is an implementation of:

 - A- One bit comparator.  
 B- R-S Latch.  
 C- D-Flip-Flop.  
 D- D-Latch.  
 E- Non of the above.




6- What is the Boolean function  $F(x,y,z)$  that is implemented with a  $4 \times 1$  multiplexer as shown below.

 - C-  $F(x,y,z) = \sum (2, 3, 5, 6)$   
 D-  $F(x,y,z) = \sum (0, 1, 4, 7)$   
~~E~~ None of the above




7- The implementation of a full adder can be implemented using two half adders and

 - A- Priority encoder  
 B- NAND gate  
~~C~~ C- OR gate  
 D- NOR gate  
 E- AND gate



8- To construct a T-flip-flop using D-flip-flop as shown below, we need to use

 
- A- Not gate.  
 B- AND gate.  
~~C~~ C- XOR gate.  
 D- XNOR gate.  
 E- OR gate.



9- In the priority encoder shown with  $D_0$  having highest priority and  $D_7$  the lowest priority, if the status at inputs  $D_3 = 1$  and  $D_7 = 1$  and all other inputs are set to zero then the output of the encoder is

- A.  $Y_2 = 1, Y_1 = 1$ , and  $Y_0 = 0$ .
- B.  $Y_2 = 1, Y_1 = 1$ , and  $Y_0 = 1$ .
- C.  $Y_2 = 0, Y_1 = 0$ , and  $Y_0 = 1$ .
- D.  $Y_2 = 0, Y_1 = 1$ , and  $Y_0 = 1$ .
- E. None

0 1 1

 

d<sub>0</sub> d<sub>1</sub> d<sub>2</sub> d<sub>3</sub> d<sub>4</sub> d<sub>5</sub> d<sub>6</sub> d<sub>7</sub>

\* x x x x x x x x

10- Consider the following Verilog module:

```
module sec1234(A,B,C);
```

```
input A, B;
output C;
wire notA, notB, w1, w2;



not G1(notA, A);
not G2(notB, B);
and G3(w1, A, notB);
and G4(w2, B, notA);
or G5(C, w1, w2);

endmodule
```

This module can be used as an alternative to:

- A. Decoder
- B. MUX
- C. XNOR gate
- D. XOR gate
- E. None of the above


$$A \rightarrow \overline{A}$$

  


6

Q2) Implement the Boolean function  $F(A, B, C) = \sum m(0, 2, 3, 5)$

a) using one  $8 \times 1$  multiplexer

 

b) using one  $4 \times 1$  multiplexer

 

$A$	$B$	$C$	$F$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

$A$	$B$	$C$	$F$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

**7Q**  
 Q 3) Design a combinational logic circuit that receives a 3-bit unsigned number  $X$  and produces the floor of  $\frac{X}{2}$ , i.e.  $Z = \left\lfloor \frac{X}{2} \right\rfloor$ . (e.g. if  $X=5$  then  $Z=\left\lfloor \frac{5}{2} \right\rfloor=\left\lfloor 2.5 \right\rfloor=2$ ).

