



Faculty of Engineering & Technology – Electrical & Computer Engineering  
Department  
Digital Systems ENCS234 – **HW#3**

---

1. Simplify the following Boolean Functions, using k-map method:

a.  $F(x,y,z) = \Sigma (0,2,6,7)$

b.  $F(x,y,z) = \Sigma (3,5,6,7)$

c.  $F(A,B,C,D) = \Sigma (3,7,11,13,14,15)$

d.  $F(A,B,C,D) = \Sigma(1,3,5,7,9,15) + \Sigma d(4,6,12,13)$

e.  $F(A,B,C,D) = \prod(1,3,5,7,9,11,13,15)$

2. Simplify the following expressions in (1) sum of products and (2) products of sums:

a.  $x'z' + y'z' + yz' + xy$

b.  $AC' + B'D + A'CD + ABCD$

3. Implement the function  $F(A, B, C, D) = \Sigma(0, 1, 2, 3, 4, 8, 9, 12)$  with the following two-level forms:

- a. AND-OR
- b. NAND-NAND
- c. OR-AND
- d. NOR-OR.

4. In the following function determine the Essential prime implicant  
a.  $F(A,B,C,D) = \Sigma (0,2,5,7,6,8,9,10,11,13,14,15)$

Q5: Explain the concept of odd parity generator?