



BIRZEIT UNIVERSITY
Electrical and Computer Engineering
ENCS 234:
Chapter 3 Homework

1. Find the minterms for the following Boolean function by first plotting each function in the K-map

a. $F(A, B, C, D) = A'C' + BC + AB'$
b. $F(A, B, C) = B + C'$

2. Find all prime implicants and determine which are essential for:

a. $F(B, C, D) = \sum(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$
b. $F(W, X, Y, Z) = \sum(0, 2, 3, 5, 7, 8, 10, 11, 14, 15)$

3. Simplify the following Boolean functions, and implement them with two-level **NAND-NAND**:

a. $F(A, B, C, D) = ABC + A'BC + AB'C + A'B'C$
b. $F(A, B, C, D) = AB'D' + AB'D + A'D + A'D'$

4. Implement directly the following function with two-level **NOR-NOR** (without going first to plot the circuit using AND-OR)

$$F(A, B, C, D) = \sum(0, 1, 2, 3, 6, 7, 9, 14, 15)$$

5. Given the following function:

$$F(A, B, C, D) = \sum(0, 1, 2, 4, 5, 7, 8, 9, 10, 11, 15)$$

Implement this function using two-level:

- NAND-NAND
- NOR-NOR
- AND-NOR
- NAND-AND

6. Implement the following function with **two-input NOR** gates only:

$$w(x, y, z) = \sum(0, 1, 2, 5, 9, 10, 11, 13)$$

7. Simplify using QM Tabulation method the following function

$$F(A, B, C, D) = \sum(1, 3, 5, 7, 9, 15)$$

With don't-care conditions

$$d(A, B, C, D) = \sum(4, 6, 12, 13)$$