



**Digital Design HDL Homework**

**ENCS234**

**Dr : Mohammad Hussein**

**Section# : 1**

**Name : Maryam Shaheen**

**ID# : 1140427**


1 - Verilog HDL code to describe the module mux2x1 :

```
1  module Mux2x1 (A,B,select,out);
2  input A,B,select;
3  output out;
4  reg out;
5  always @(select)
6  if (select ==1)
7  out = A;
8  else
9  out = B;
10 endmodule
```

2 - Verilog HDL code to describe the module dcd2x4 :

```
1  module Decoder2x4 (en,A, B,out);
2  input A, B;
3  input en;
4  output[3:0] out ;
5  reg [3:0] out ;
6  initial
7  out = 4'b0000;
8  always
9  begin
10 if(en)
11 begin
12 if(A ==0 && B ==0)
13 out = 4'b1000;
14 else if( A ==0 && B==1)
15 out = 4'b0100;
16 else if( A==1 && B==0)
17 out = 4'b0010;
18 else
19 out = 4'b0001;
20 end
21 end
22 endmodule
```

### 3 - Block Diagram :

 

### Block diagram simulation :

	Name	Value at 19.43 ns	50.0 ns	60.0 ns	70.0 ns
0	A0	A 1			
1	A1	A 0			
2	B0	A 1			
3	B1	A 0			
4	enable	A 1			
5	out	A [2]		[2]	
10	selection	A 0			

4 - Verilog HDL code to describe the whole system structurally from its subsystems :

```

1  module HDLHW (A0, A1, B0, B1 , out , selection , enable);
2  input A0, A1, B0, B1, selection, enable;
3  output [3:0] out;
4  wire w1,w2,w3,w4,w5,w6;
5
6
7  assign w1=(A0&&B0);
8  assign w2=(A0||B0);
9  and G1(w3,A1,B1);
10 or G2(w4,A1,B1);
11 Mux2x1 m1(w1,w2,selection,w5);
12 Mux2x1 m2(w3,w4,selection, w6);
13 Decoder2x4 D1(enable, w5, w6, out);
14
15
16  endmodule

```

simulation :

