



BIRZEIT UNIVERSITY  
Electrical and Computer  
Engineering ENCS 234: Chapter 2  
Homework # 2

---

---

1. Simplify the following Boolean function to minimum number of literals

- $xy + xy'$
- $(A + B)' \cdot (A' + B')$
- $A'B'C'D' + A'B'C'D + A'BC'D' + A'BC'D$

2. Draw the logic diagrams for:

- $F = A'BC + A(B + C')$
- $F = (A + B)(B + C)(AB)$
- $F = AB + BC(D + A)$

3. For the following Boolean function, find the truth table and express it in Sum of Minterms and Product of Maxterms

$$F(W, X, Y, Z) = W + W'XY + W'XYZ$$

4. Convert the following Boolean function into Product of Sums

$$F = AB + AB'C$$

5. Given the following boolean function, implement it using AND, OR and NOT gates

$$F = A'B + B'C + B'C'$$

6. Given the following Boolean functions

$$F_1(A, B, C) = AB + C$$
$$F_2(A, B, C) = A + AB + ABC$$

- Show that the Boolean function  $F = F_1 + F_2$  contains the Sum of minterms of  $F_1$  and  $F_2$
- Show that the Boolean function  $F = F_1 \cdot F_2$  contains only the minterms that are common to  $F_1$  and  $F_2$