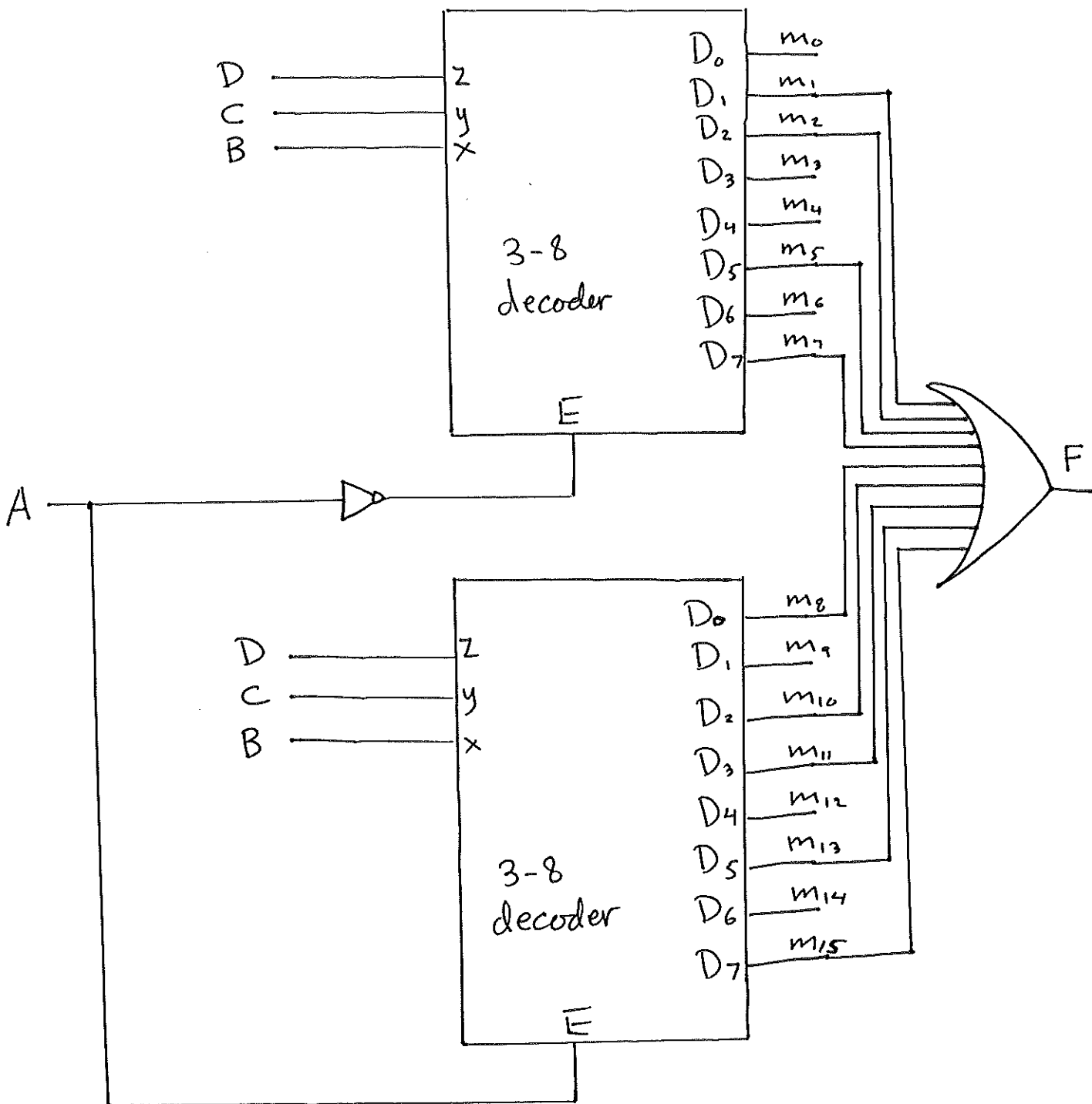


Problem 1 $F(A, B, C, D) = \sum (1, 2, 5, 7, 8, 10, 11, 13, 15)$


using two 3-8-line decoders with enable.



Problem 2: $F(A, B, C, D) = \sum(1, 2, 5, 7, 8, 10, 11, 13, 15)$

using a 8-1 MUX.


A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

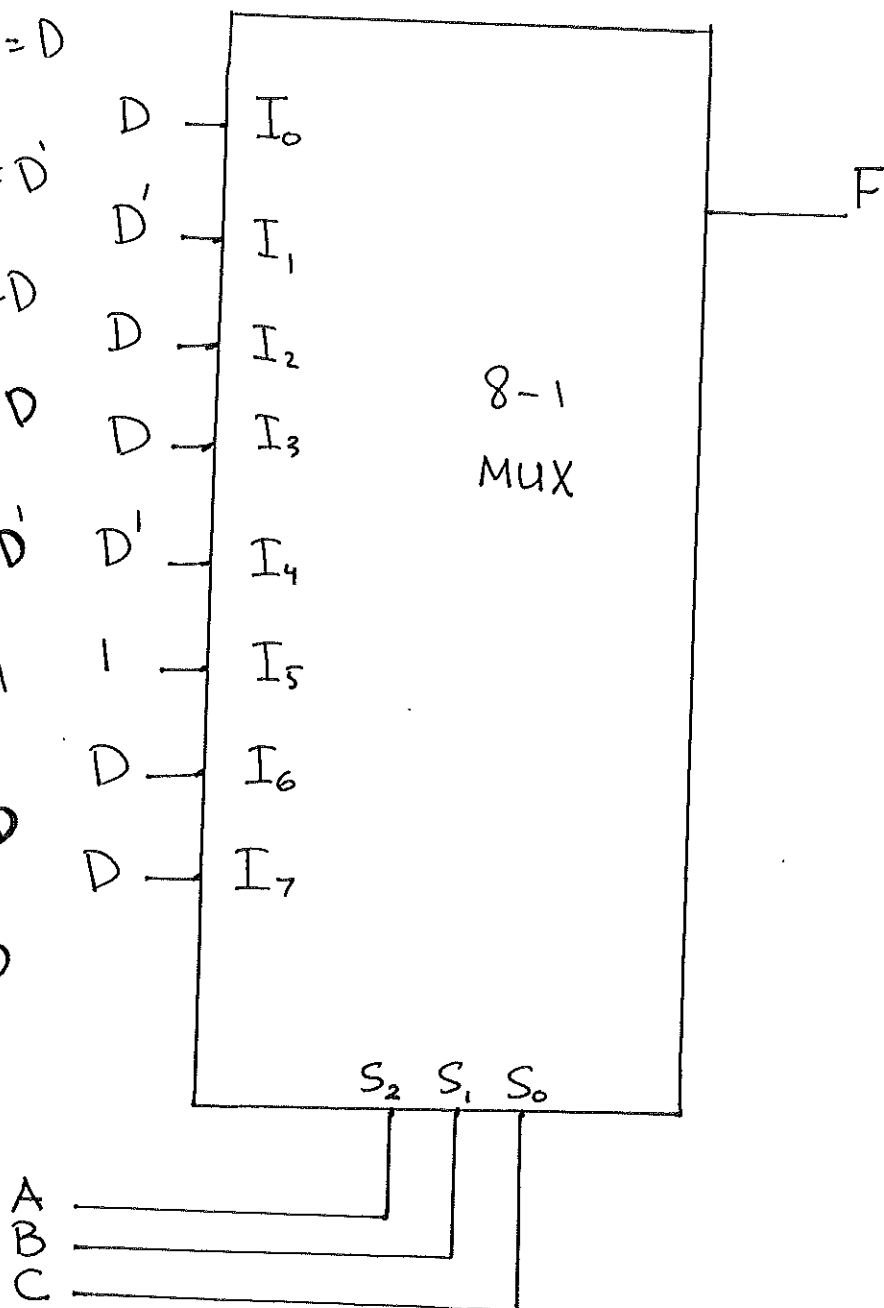

Problem 3: $F(A, B, C, D) = \sum(1, 2, 5, 7, 8, 10, 11, 13, 15)$

using two 4-1 MUXes with external gates.

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

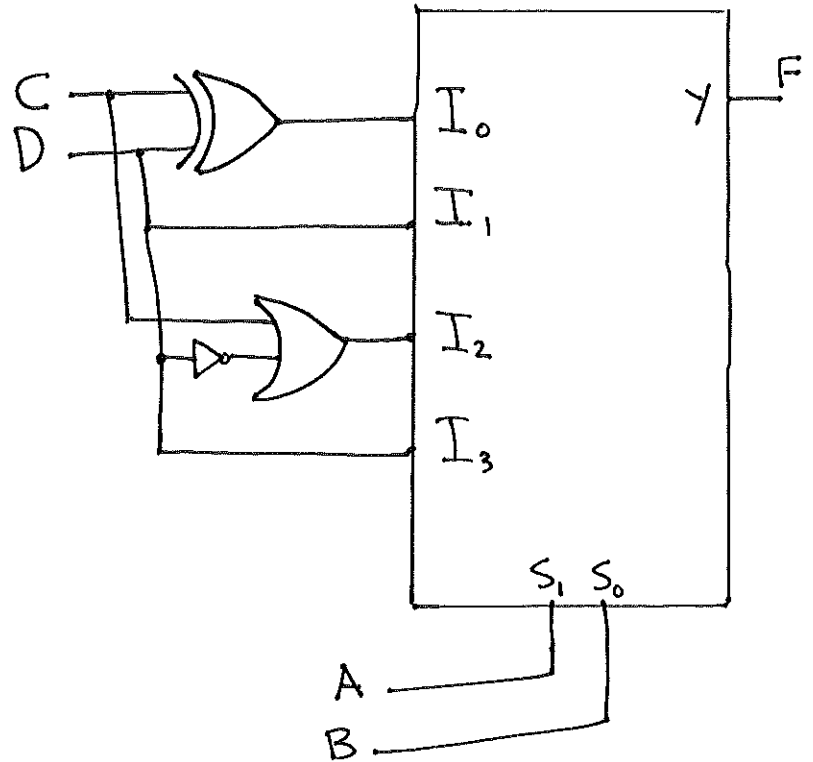


$$I_0 = C \oplus D$$

$$I_1 = I_3 = D$$

$$I_2 = C + D'$$

Problem 4: Using Six half adders to construct a six-bit incrementer. ($S = A + 1$)

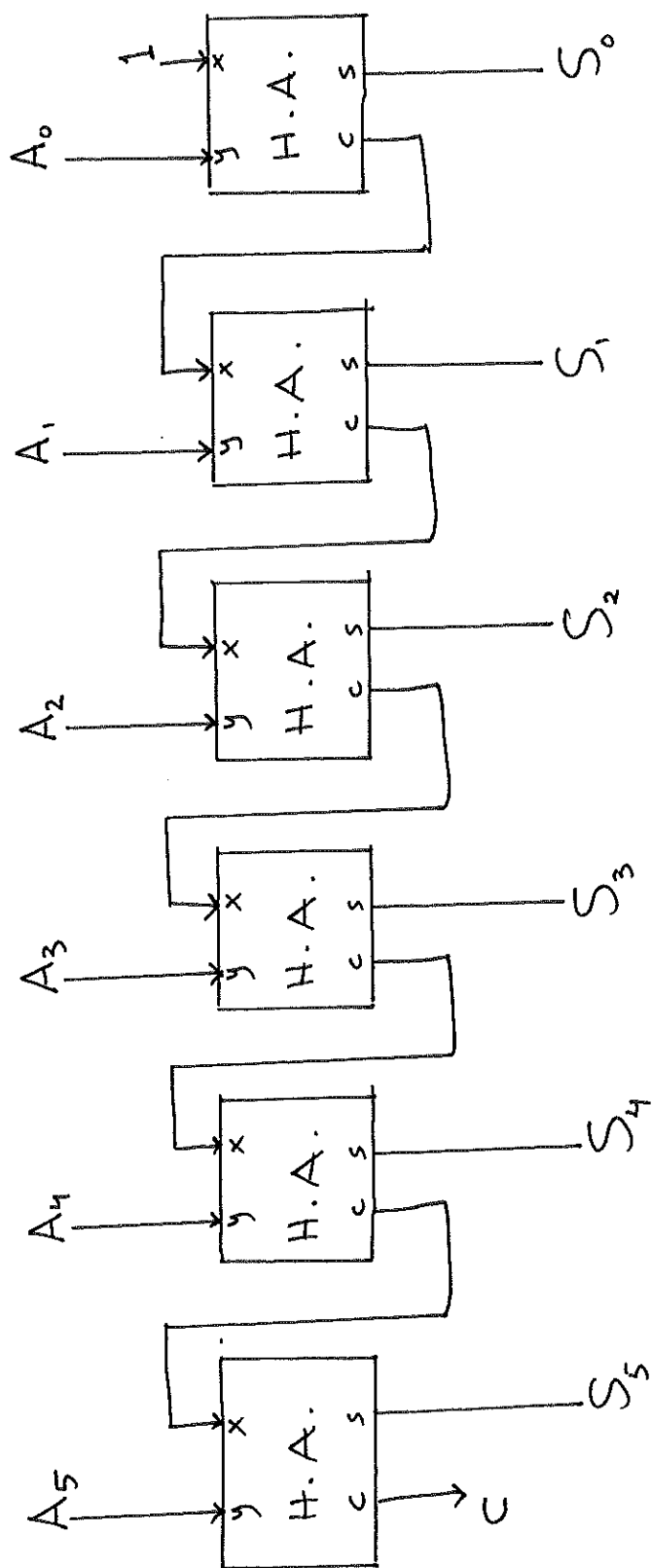

Problem 5:

$$A = 1011, B = 0110$$

(a) $M = 0 \Rightarrow$ addition

$$\begin{array}{r} c_3 \rightarrow 11 \\ 1011 \\ 0110 + \\ \hline 10001 \\ c_4 \rightarrow \end{array}$$

$$S = 0001, C = 1, V = 0$$

Interpretation of result:

$$A = -5, B = 6, A + B = +1$$

(b) $M = 1 \Rightarrow$ subtraction

2's complement of B is: 1010

$$\begin{array}{r} c_3 \rightarrow 01 \\ 1011 \\ 1010 + \\ \hline 10101 \\ c_4 \rightarrow \end{array}$$

$$S = 0101, C = 1, V = 1$$

Interpretation:

$A = -5, B = 6, A - B = -5 - 6 = -11$ which overflows the output register S. The result in S is invalid.