

# Homework Set 4 - Solutions -

## Problem 1 The PN Flip-Flop

(a) characteristic Table

P	N	Q(t+1)
0	0	0
0	1	Q(t)
1	0	Q'(t)
1	1	1

(b) characteristic equation

P	N	Q(t)	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

		NQ			
		00	01	11	10
P	0			1	
	1	1		1	1


$$Q(t+1) = PQ'(t) + NQ(t)$$

(c) Excitation Table

Q(t)	Q(t+1)	P	N
0	0	0	X
0	1	1	X
1	0	X	0
1	1	X	1

(d) convert the PN FF to a D FF.

By connecting P to N .  $D = P = N$

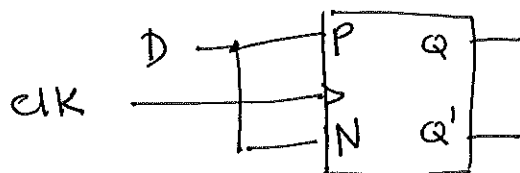

## Problem 2:

$$(a) Q(t+1) = JQ'(t) + K'Q(t)$$

$$A(t+1) = J_A A'(t) + K_A' A(t)$$

$$= x A'(t) + (x B(t))' A(t)$$

$$B(t+1) = J_B B'(t) + K_B' B(t)$$


$$= (x' + A(t)) B'(t) + (A'(t) + B(t))' B(t)$$

$$= x' B'(t) + A(t) B'(t) + \cancel{A'(t) B'(t) + B(t) B'(t)}$$

$$= x' B'(t) + A(t) B'(t)$$


(b) State Table

<u>Present State</u>		<u>Next State</u>	
<u>A</u>	<u>B</u>	<u>x=0</u>	<u>x=1</u>
		<u>A B</u>	<u>A B</u>
0	0	0 1	1 0
0	1	0 0	1 0
1	0	1 1	1 1
1	1	1 0	0 0

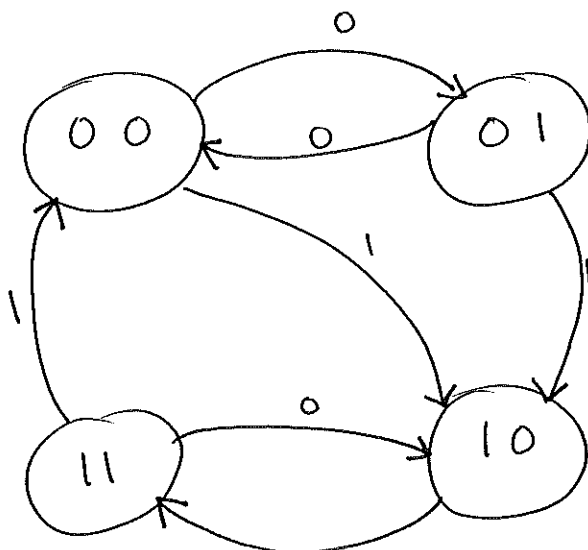

# Problem 3

(a) State Diagram.

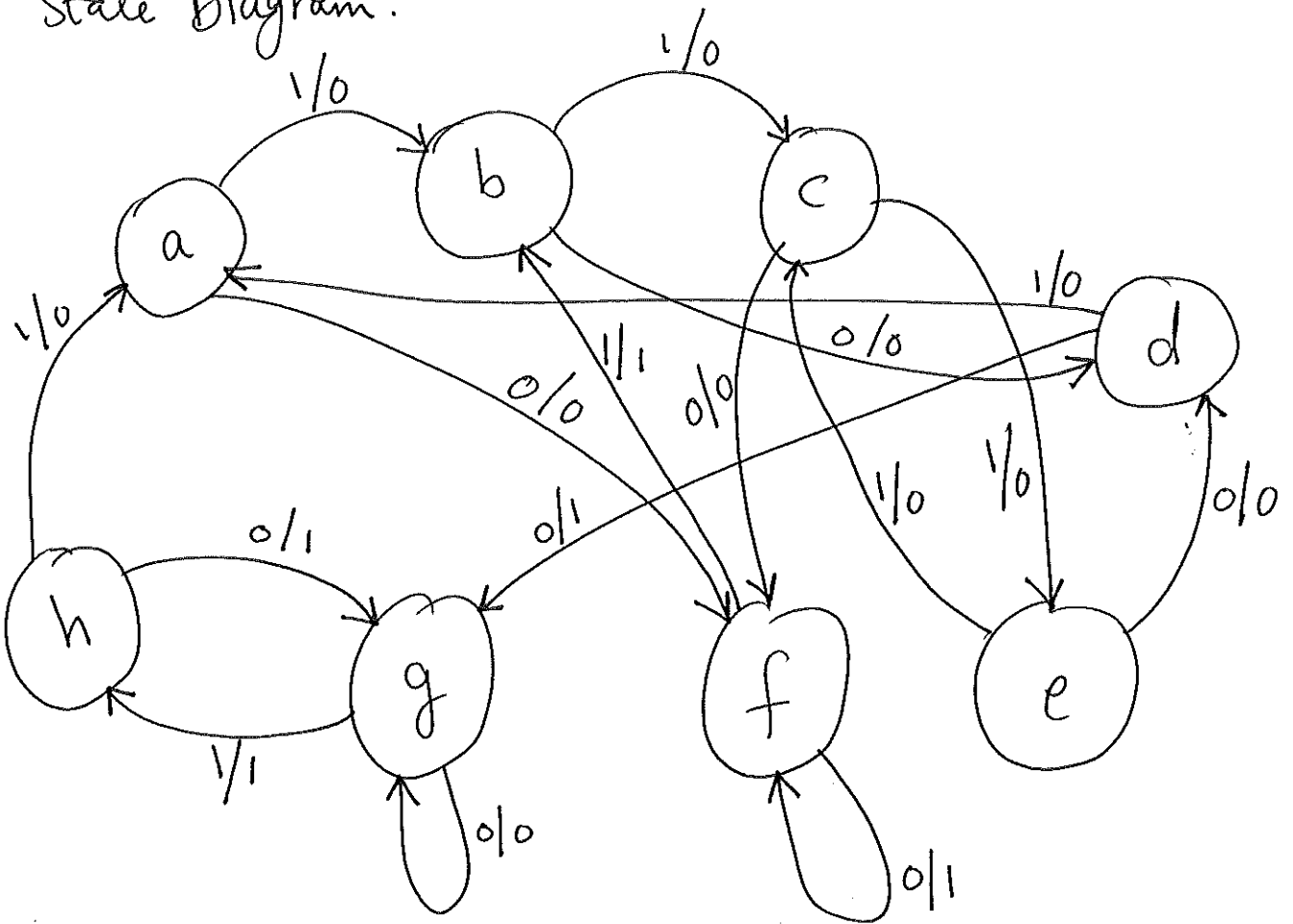

(b) Starting with state a:

State:	a	f	b	c	e	d	g	h	g	g	h	a
input:	0	1	1	1	0	0	1	0	0	1	1	
output:	0	1	0	0	0	1	1	1	0	1	0	

(c)

b	<del>f,d</del> c,e						
c	b,e	<del>f,d</del> e,e					
d	X	X	X				
e	<del>f,d</del> e,e	✓	<del>f,d</del> c,e	X			
f	X	X	X	X	X		
g	X	X	X	X	X	X	
h	X	X	X	✓	X	X	X
	a	b	c	d	e	f	g


$$h \equiv d, e \equiv b, c \equiv a$$

Thus we remove c, e, and h.

The reduced state table:

<u>Present State</u>	<u>Next State</u>		<u>Output</u>	
	<u>x=0</u>	<u>x=1</u>	<u>x=0</u>	<u>x=1</u>
a	f	b	0	0
b	d	a	0	0
d	g	a	0	0
f	f	b	1	1
g	g	d	0	1

(d) The reduced State diagram:

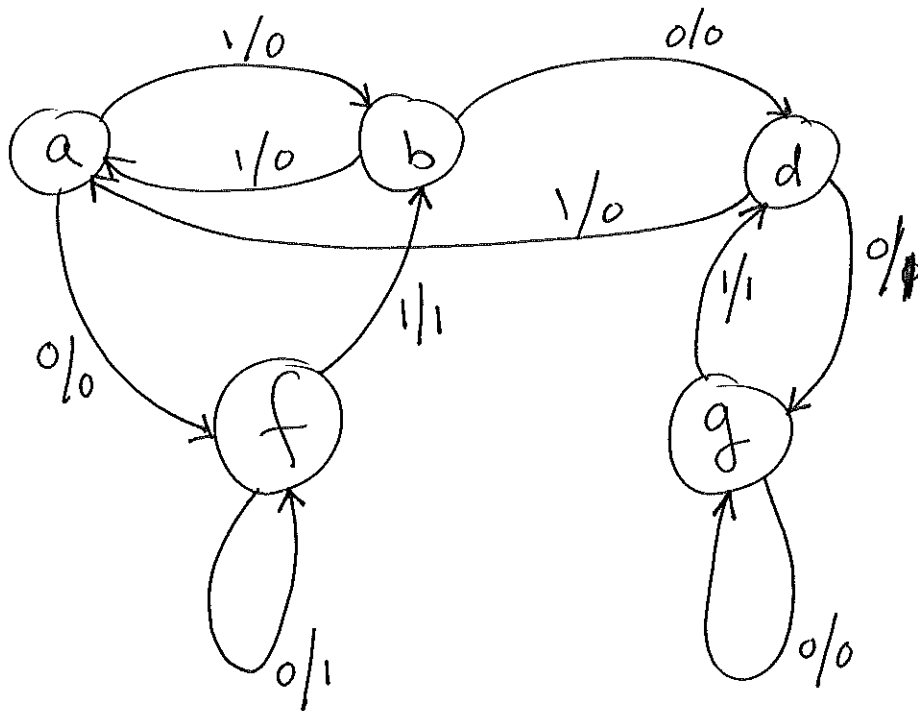

(e) Starting with state a

state:	a	f	b	a	b	d	g	d	g	g	d	a
input:	0	1	1	1	0	0	1	0	0	1	1	
output:	0	1	0	0	0	1	1	1	0	1	0	

(f) Assign  $a=000$ ,  $b=001$ ,  $d=010$ ,  $f=011$ ,  $g=100$

Three JK FFs are needed, call them A, B, C.

Excitation Table

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

<u>Present State</u>			<u>input</u>	<u>Next State</u>			<u>output</u>	<u>Flip-Flop inputs</u>					
<u>A</u>	<u>B</u>	<u>C</u>	<u>X</u>	<u>A</u>	<u>B</u>	<u>C</u>	<u>Y</u>	<u>J<sub>A</sub></u>	<u>K<sub>A</sub></u>	<u>J<sub>B</sub></u>	<u>K<sub>B</sub></u>	<u>J<sub>C</sub></u>	<u>K<sub>C</sub></u>
0	0	0	0	0	1	1	0	0	X	1	X	1	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X
0	0	1	0	0	1	0	0	0	X	1	X	X	1
0	0	1	1	0	0	0	0	0	X	0	X	X	1
0	1	0	0	1	0	0	1	1	X	X	1	0	X
0	1	0	1	0	0	0	0	0	X	X	1	0	X
0	1	1	0	0	1	1	1	0	X	X	0	X	0
0	1	1	1	0	0	1	1	0	X	X	1	X	0
1	0	0	0	1	0	0	0	X	0	0	X	0	X
1	0	0	1	0	1	0	1	X	0	1	X	0	X
1	0	1	0	X	X	X	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X	X	X

Note: unused states are being treated as Don't Care states.

$$y = Bx' + BC + AC'x$$

	Cx			
AB	00	01	11	10
00				
01	1		1	1
11	x	x	x	x
10		1	x	x

$$J_A = BC'x'$$

	Cx			
AB	00	01	11	10
00				
01	1			
11	x	x	x	x
10	x	x	x	x

$$K_A = B'x$$

	Cx			
AB	00	01	11	10
00	x	x	x	x
01	x	x	x	x
11	x	x	x	x
10		1	x	x

$$J_B = A'x' + Ax$$

	Cx			
AB	00	01	11	10
00	1			1
01	x	x	x	x
11	x	x	x	x
10		1	x	x

$$K_B = A'C' + A'x$$


	Cx			
AB	00	01	11	10
00	x	x	x	x
01	1	1	1	
11	x	x	x	x
10	x	x	x	x

$$J_C = A'B'$$

	Cx			
AB	00	01	11	10
00	1	1	x	x
01			x	x
11	x	x	x	x
10			x	x

$$K_C = B'C$$

	Cx			
AB	00	01	11	10
00	x	x	1	1
01	x	x		
11	x	x	x	x
10	x	x	x	x

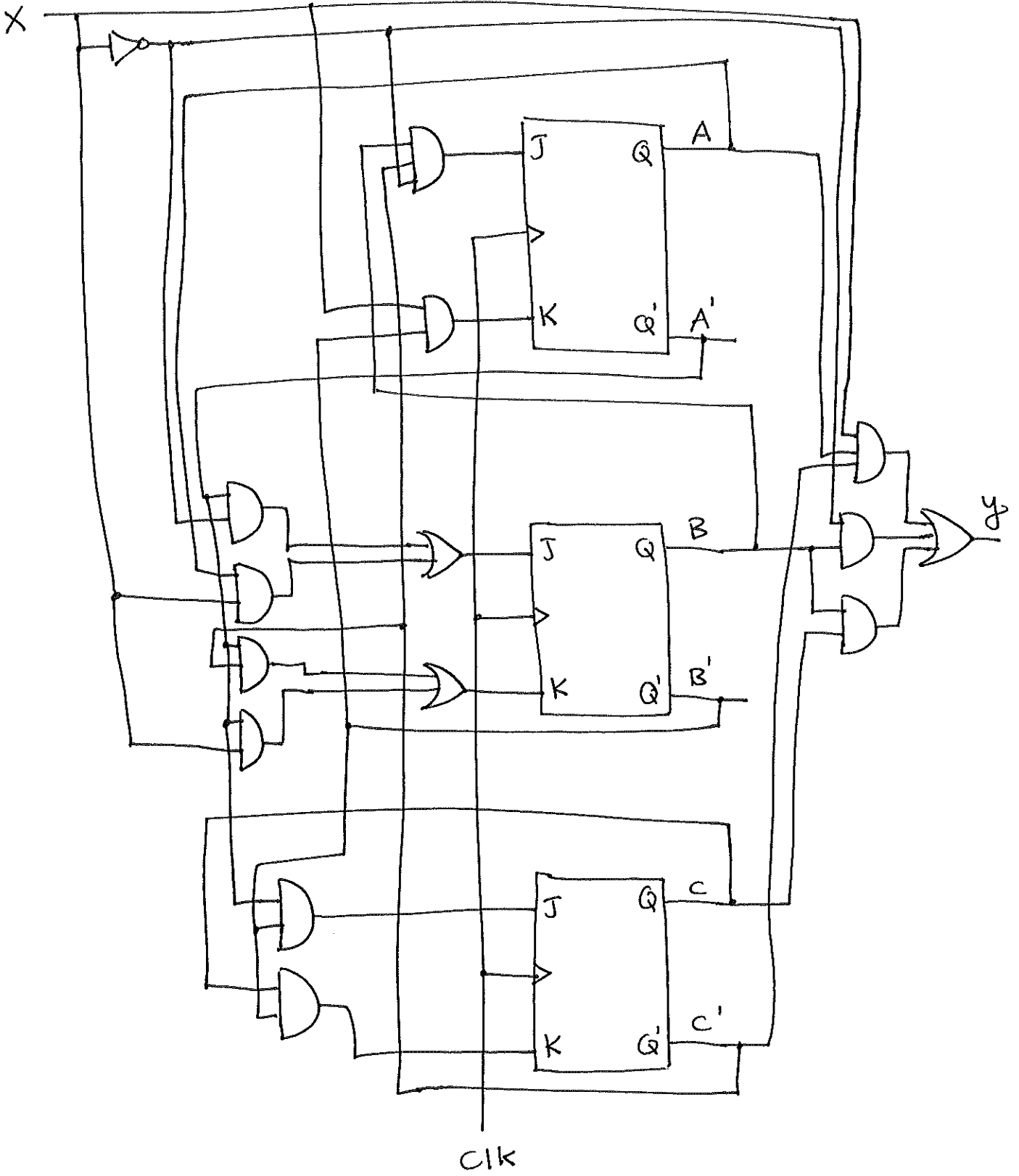




Problem 4 The serial 2's complementer begins in state 0, in which the output equals the input, and it moves to state 1 after it encounters the first 1. In state 1, the output is the complement of the input.

example:

input :	1 0 1 1 0 1 1 0 0
	↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓
output:	0 1 0 0 1 1 0 0
	state   state
	1   0

state diagram

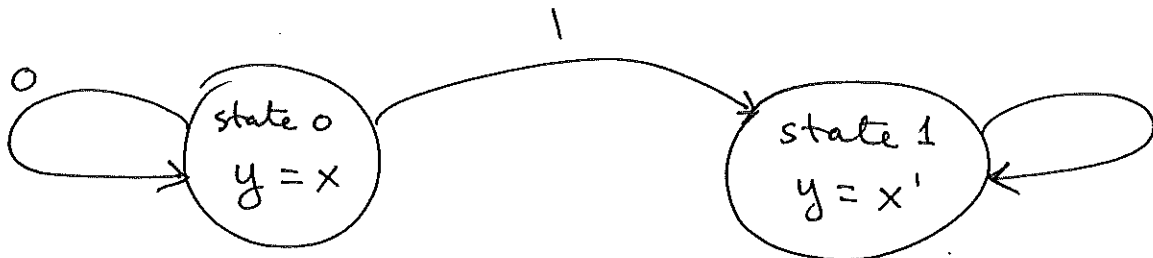

state table using one D Flip-Flop.

Present State	input x	Next State	output y	FF input D = Q(t+1)
0	0	0	0	0
0	1	1	1	1
1	0	1	1	1
1	1	1	0	1

$$\Rightarrow y = Q \oplus x, \quad D = Q + x$$

