



BIRZEIT UNIVERSITY

DIGITAL PROJECT

ENCS234

Name : Maryam Shaheen


ID# : 1140427

Section : 1

D.Abdel salam sayaad

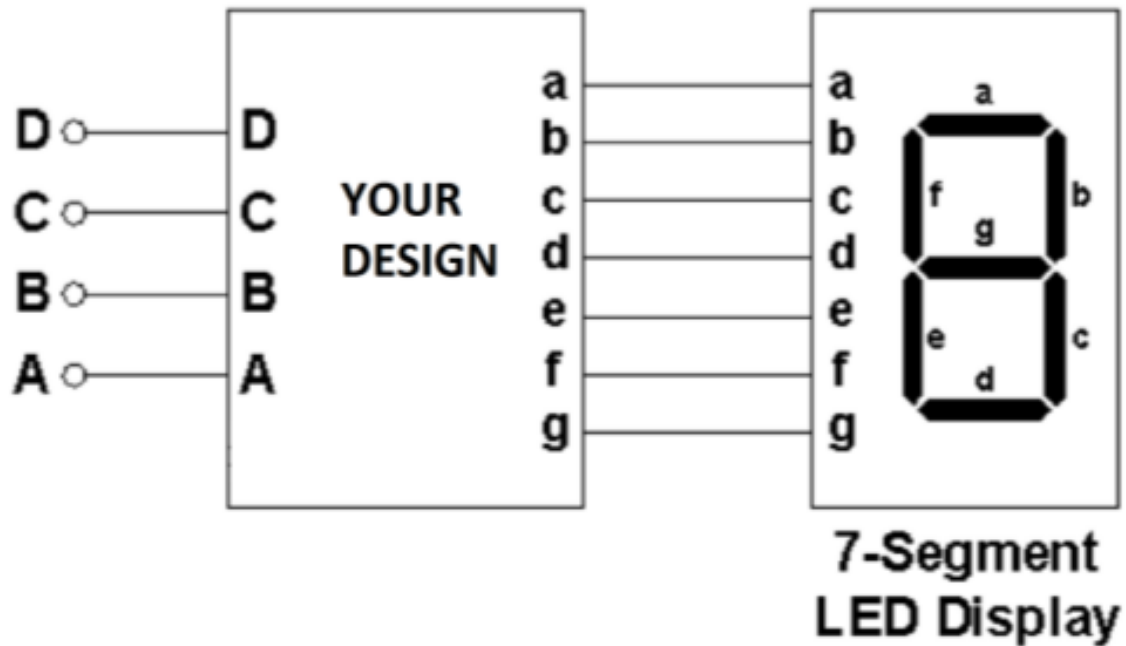1. Description :

Design a combinational circuit using Verilog to achieve the following functionality.



Your system will have 4 inputs (A, B, C, D) and 7 outputs (a through g) that drive a 7-segment display, whose inputs are active-high. The system shall behave according to the following table:


A	B	C	D	Display
0				The least significant decimal digit of your student ID
1				The second least significant decimal digit of your student ID
2				The third least significant decimal digit of your student ID
3				The fourth least significant decimal digit of your student ID
4				The fifth least significant decimal digit of your student ID
5				The sixth least significant decimal digit of your student ID
6				The most significant decimal digit of your student ID
7				The least significant decimal digit of your birth year
8				The second least significant decimal digit of your birth year
9				The third least significant decimal digit of your birth year
10				The most significant decimal digit of your birth year
11 - 15				Nothing

2. My Design





i. Truth Table

ID#	1140427
Birth Year	1996



	Inputs	Outputs
Input > Output	a b c d	A B C D E F G
0 > 7	0 0 0 0	1 1 1 0 0 0 0
1 > 2	0 0 0 1	1 1 0 1 1 0 1
2 > 4	0 0 1 0	0 1 1 0 0 1 1
3 > 0	0 0 1 1	1 1 1 1 1 1 0
4 > 4	0 1 0 0	0 1 1 0 0 1 1
5 > 1	0 1 0 1	0 1 1 0 0 0 0
6 > 1	0 1 1 0	0 1 1 0 0 0 0
7 > 6	0 1 1 1	1 0 1 1 1 1 1
8 > 9	1 0 0 0	1 1 1 0 0 1 1
9 > 9	1 0 0 1	1 1 1 0 0 1 1
10 > 1	1 0 1 0	0 1 1 0 0 0 0
11-15 > nothing	x x x x	0 0 0 0 0 0 0

 

ii. k-maps

    

  $G = a'bcd + a'bc'd' + a'b'cd' + ab'c' + b'c'd$



iii. Code :

```
module maryam_1140427(a,b,c,d,A,B,C,D,E,F,G);
input a,b,c,d; // inputs
output A,B,C,D,E,F,G; // outputs
/*
A,B,C,D,E,F,G are equations for obtaining the outputs :
*/
assign A= (!b && !c) || (!a && c && d); // the equation of A
assign B= (!a && !b) || (!b && !d) || (!a && !d) || (!a && !c) || (!b && !c); // the
equation of B
assign C= (!a && b) || (!a && c) || (!b && !d) || (a && !b && !c); // the equation of C
assign D= (!a && c && d) || (!a && !b && d); // the equation of D
assign E= (!a && c && d) || (!a && !b && d); // the equation of E
assign F= (!a && !b && c) || (!a && c && d) || (!a && !b && !c); // the equation of F
assign G= (!a && b && c && d) || (!a && b && !c && !d) || (!a && !b && c && !d) ||
(a && !b && !c) || (!b && !c && d); // the equation of G
endmodule
```

iv. Simulation:

