

Synchronous Sequential Logic

Aziz Qaroush


Combinational versus Sequential

❖ Two classes of digital circuits

- ❖ Combinational Circuits
- ❖ Sequential Circuits

❖ Combinational Circuit

 - ❖ $\text{Outputs} = F(\text{Inputs})$
- ❖ Function of Inputs only
- ❖ NO internal memory



❖ Sequential Circuit

- ❖ Outputs is a function of Inputs and internal Memory
- ❖ There is an internal memory that stores the state of the circuit
- ❖ Time is very important: memory changes with time

Introduction to Sequential Circuits

A Sequential circuit consists of:

1. Memory elements:

- ✧ **Latches or Flip-Flops**
- ✧ Store the **Present State**


2. Combinational Logic

- ✧ Computes the **Outputs** of the circuit

Outputs depend on Inputs and Current State

- ✧ Computes the **Next State** of the circuit

 Next State also depends on the Inputs and the Present State



Two Types of Sequential Circuits


1. **Synchronous** Sequential Circuit

- ✧ Uses a clock signal as an additional input
- ✧ Changes in the memory elements are controlled by the clock
- ✧ Changes happen at discrete instances of time

2. **Asynchronous** Sequential Circuit


- ✧ No clock signal
 - ✧ Changes in the memory elements can happen at any instance of time
- ❖ Our focus will be on Synchronous Sequential Circuits
- ✧ Easier to design and analyze than asynchronous sequential circuits

Synchronous Sequential Circuits

 


- ❖ Synchronous sequential circuits use a **clock signal**
- ❖ The clock signal is an input to the memory elements
- ❖ The clock determines **when** the memory should be updated
- ❖ The **present state** = output value of memory (stored)
- ❖ The **next state** = input value to memory (not stored yet)

The Clock

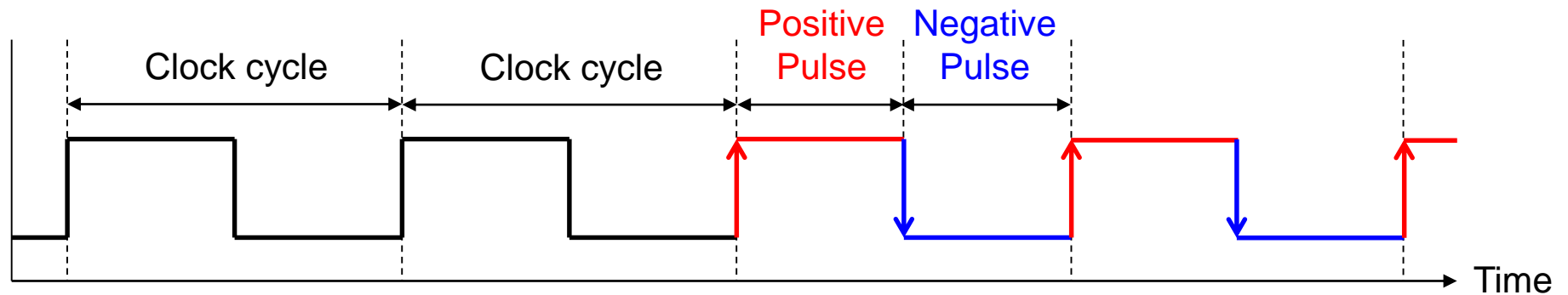

- ❖ Clock is a periodic signal = Train of pulses (1's and 0's)
- ❖ The same clock cycle repeats indefinitely over time
- ❖ **Positive Pulse**: when the **level** of the clock is **1**
- ❖ **Negative Pulse**: when the **level** of the clock is **0**
- ❖ **Rising Edge**: when the clock goes **from 0 to 1**
- ❖ **Falling Edge**: when the clock goes **from 1 down to 0**

Clock Cycle versus Clock Frequency

 

❖ Clock cycle (or period) is a time duration

✧ Measured in seconds, milli-, micro-, nano-, or pico-seconds

✧ $1 \text{ ms} = 10^{-3} \text{ sec}$, $1 \mu\text{s} = 10^{-6} \text{ sec}$, $1 \text{ ns} = 10^{-9} \text{ sec}$, $1 \text{ ps} = 10^{-12} \text{ sec}$

❖ Clock frequency = number of cycles per second (Hertz)

✧ $1 \text{ Hz} = 1 \text{ cycle/sec}$, $1 \text{ KHz} = 10^3 \text{ Hz}$, $1 \text{ MHz} = 10^6 \text{ Hz}$, $1 \text{ GHz} = 10^9 \text{ Hz}$

❖ Clock frequency = $1 / \text{Clock Cycle}$



✧ Example: Given the clock cycle = $0.5 \text{ ns} = 0.5 \times 10^{-9} \text{ sec}$

✧ Then, the clock frequency = $1/(0.5 \times 10^{-9}) = 2 \times 10^9 \text{ Hz} = 2 \text{ GHz}$

Memory Elements

- ❖ Memory can store and maintain binary state (0's or 1's)
 - ✧ Until directed by an input signal to change state
- ❖ Main difference between memory elements
 - ✧ Number of inputs they have
 - ✧ How the inputs affect the binary state
- ❖ Two main types:
 - ✧ Latches are level-sensitive (the level of the clock)
 - ✧ Flip-Flops are edge-sensitive (sensitive to the edge of the clock)
- ❖ Flip-Flops are used in synchronous sequential circuits
- ❖ Flip-Flops are built with latches


Memory Elements - Latches

  

- ❖ A basic memory element, as shown in Figure (a), is the **latch**.
- ❖ A latch is a circuit capable of storing one bit of information.
- ❖ The latch circuit consists of two inverters; with the output of one connected to the input of the other.
- ❖ The latch circuit has two outputs, one for the stored value (**Q**) and one for its complement (**Q'**).
- ❖ Figure (b) shows the same latch circuit re-drawn to illustrate the two complementary outputs.
- ❖ The problem with the latch formed by **NOT gates** is that **we can't change the** stored value. For example, if the output of inverter B has logic 1, then it will be latched forever; and there is no way to change this value.

SR Latch

 - ❖ An **SR Latch** can be built using two NOR gates
- ❖ Two inputs: S (Set) and R (Reset)
- ❖ Two outputs: Q and \bar{Q}



(a) Logic diagram


S	R	Q	\bar{Q}	
1	0	1	0	Set state
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined

(b) Function table

SR Latch Operation


- ❖ If $S = 1$ and $R = 0$ then **Set** ($Q = 1, \bar{Q} = 0$)
 - ❖ If $S = 0$ and $R = 1$ then **Reset** ($Q = 0, \bar{Q} = 1$)
 - ❖ When $S = R = 0$, Q and \bar{Q} are unchanged
 - ❖ The latch stores its outputs Q and \bar{Q} as long as $S = R = 0$
 - ❖ When $S = R = 1$, Q and \bar{Q} are undefined (should never be used)
-
- ❖ If $S = 1$ and $R = 0$ then **Set** ($Q = 1, \bar{Q} = 0$)
 - ❖ If $S = 0$ and $R = 1$ then **Reset** ($Q = 0, \bar{Q} = 1$)
 - ❖ When $S = R = 0$, Q and \bar{Q} are unchanged
 - ❖ The latch stores its outputs Q and \bar{Q} as long as $S = R = 0$
 - ❖ When $S = R = 1$, Q and \bar{Q} are undefined (should never be used)

SR Latch Timing Diagram

 


Characteristic Equation of the SR Latch

$Q(t)$	S	R	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	Indeterminate
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	Indeterminate

 

$$Q(t+1) = S + R'Q \quad SR = 0$$

\bar{S} \bar{R} Latch with NAND Gates

 

(a) Logic diagram


\bar{S}	\bar{R}	Q	\bar{Q}	
0	1	1	0	Set state
1	1	1	0	
1	0	0	1	Reset state
1	1	0	1	
0	0	1	1	Undefined

(b) Function table

Known as
the \bar{S} \bar{R} Latch

- ❖ If $\bar{S} = 0$ and $\bar{R} = 1$ then **Set** ($Q = 1$, $\bar{Q} = 0$)
- ❖ If $\bar{S} = 1$ and $\bar{R} = 0$ then **Reset** ($Q = 0$, $\bar{Q} = 1$)
- ❖ When $\bar{S} = \bar{R} = 1$, Q and \bar{Q} are unchanged (remain the same)
- ❖ The latch stores its outputs Q and \bar{Q} as long as $\bar{S} = \bar{R} = 1$
- ❖ When $\bar{S} = \bar{R} = 0$, Q and \bar{Q} are undefined (should never be used)


SR Latch with a Clock Input

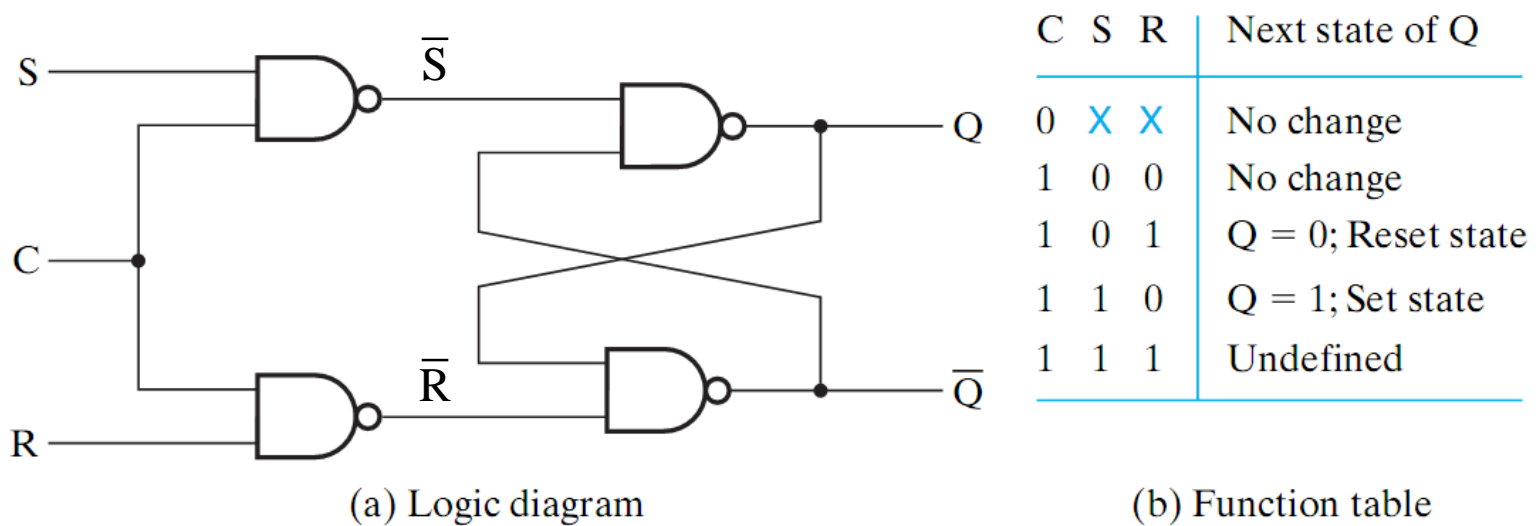

- ❖ An additional Clock input signal **C** is used
- ❖ Clock controls **when** the state of the latch can be changed
- ❖ When **C=0**, the S and R inputs have no effect on the latch
The latch will remain in the same state, regardless of S and R
- ❖ When **C=1**, then normal SR latch operation

SR Latch with a Clock Input


Logic Diagram

 


Function Table

C	S	R	Next State
0	X	X	No Change
1	0	0	No Change
1	0	1	Q=0; Reset
1	1	0	Q=1; Set
1	1	1	Indeterminate


No Change

 


No Change

 


Set

 


Reset

 

 SR Latch with a Clock Input Timing Diagram



D-Latch with a Clock Input

 

(a) Logic diagram

C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state


(b) Function table

❖ Elimination the undesirable condition of the indeterminate state in SR latch

- ❖ Only one data input D
- ❖ An inverter is added: $S = D$ and $R = \bar{D}$
- ❖ S and R can never be 11 simultaneously → No undefined state
- ❖ When $C = 0$, Q remains the same (No change in state)
- ❖ When $C = 1$, $Q = D$ and $\bar{Q} = \bar{D}$

D-Latch with a Clock Input


Logic Diagram

 


Function Table

<i>C</i>	<i>D</i>	Next State
0	X	No Change
1	0	$Q=0$; Reset
1	1	$Q=1$; Set

No Change

 


Set

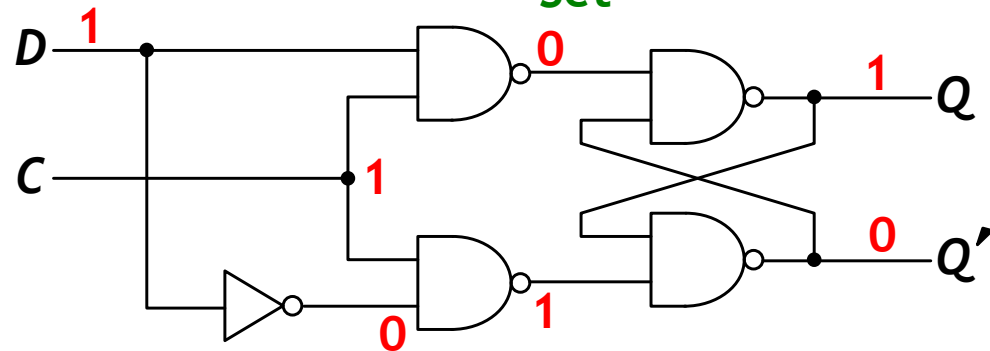

D-Latch with a Clock Input Timing Diagram


Regular D-latch response

 

*Outputs respond to input (D)
during these time periods*


Characteristic Equation of the D-Latch

$Q(t)$	D	$Q(t+1)$
0	0	0
0	1	1
1	0	0
1	1	1

 

$$Q(t+1) = D$$

Graphic Symbols for Latches

 

❖ A bubble appears at the complemented output \bar{Q}

Indicates that \bar{Q} is the complement of Q


❖ A bubble also appears at the inputs of an $\bar{S} \bar{R}$ latch

Indicates that **logic-0** is used (not logic-1) to set (or reset) the latch (as in the NAND latch implementation)

 Problem with Latches


- ❖ A latch is **level-sensitive** (sensitive to the level of the clock)
- ❖ As long as the clock signal is **high** ...
 - Any change in the value of input D appears in the output Q
- ❖ Output Q keeps changing its value during a clock cycle
- ❖ Final value of output Q is uncertain

Due to this uncertainty, latches are NOT used as memory elements in synchronous circuits



Flip-Flops

 - ❖ A **Flip-Flop** is a better memory element for synchronous circuits
- ❖ Solves the problem of latches in synchronous sequential circuits
- ❖ A **latch** is sensitive to the **level** of the clock
- ❖ However, a **flip-flop** is sensitive to the **edge** of the clock
- ❖ A flip-flop is called an **edge-triggered** memory element
- ❖ It changes its output value at the **edge** of the clock




Positive Edge-Triggered D Flip-Flop

- ❖ Built using two latches in a **master-slave** configuration
- ❖ A master latch (D-type) receives external inputs
- ❖ A slave latch (SR-type) receives inputs from the master latch
- ❖ Only one latch is enabled at any given time

When **C=0**, the master is enabled and the D input is latched (slave disabled)

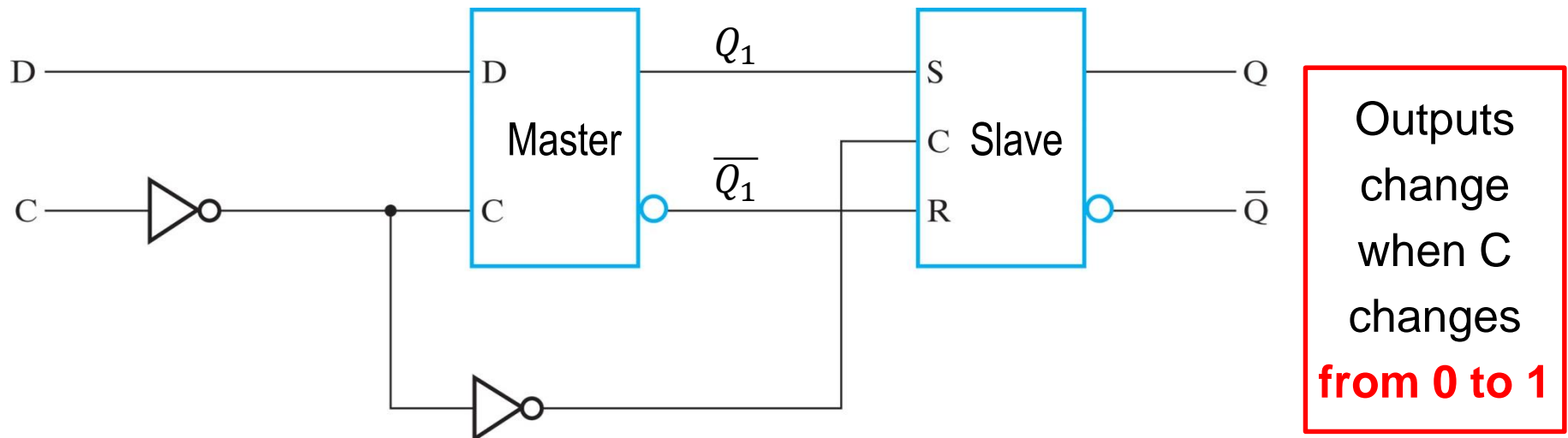When **C=1**, the slave is enabled to generate the outputs (master is disabled)




Negative Edge-Triggered D Flip-Flop

- ❖ Similar to positive edge-triggered flip-flop
- ❖ The first inverter at the Master C input is removed
- ❖ Only one latch is enabled at any given time


When **C=1**, the master is enabled and the D input is latched (slave disabled)

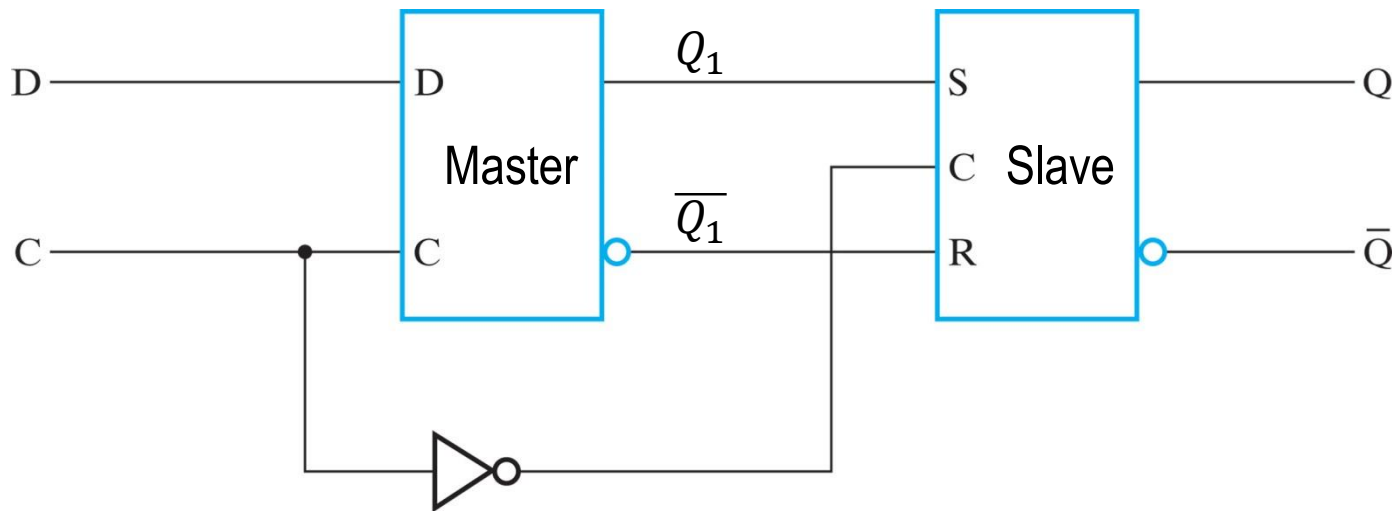When **C=0**, the slave is enabled to generate the outputs (master is disabled)



Outputs
change
when C
changes
from 1 to 0

Negative-Edge D Flip-Flop Timing Diagram




 


(a) Circuit





(b) Timing diagram

D-Latch vr. Edge-Triggered D Flip-Flop

    

Positive Edge-Triggered D Flip-Flop Another Construction

Positive Edge Trigger

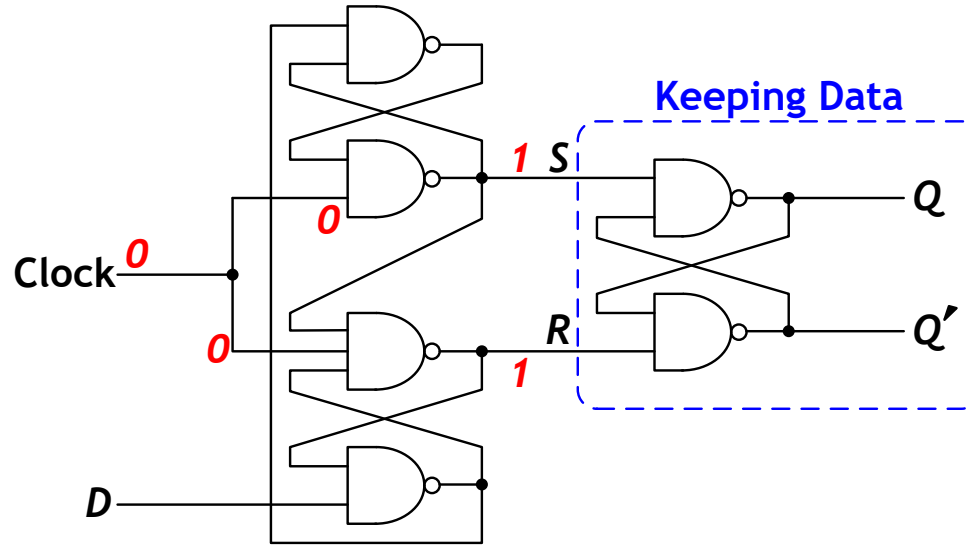 



Clock = 0 Clock = 0

Clock = 1



Set

Clock = 1

Reset

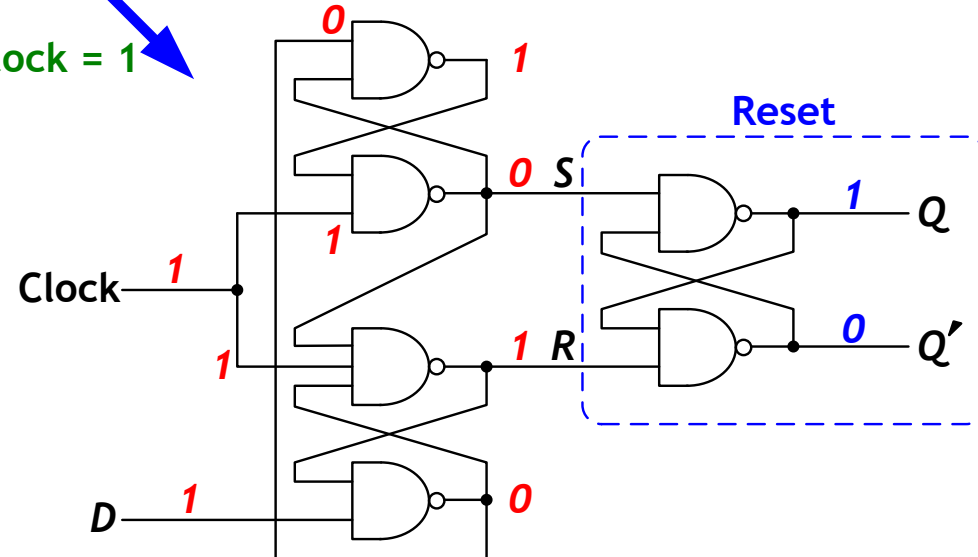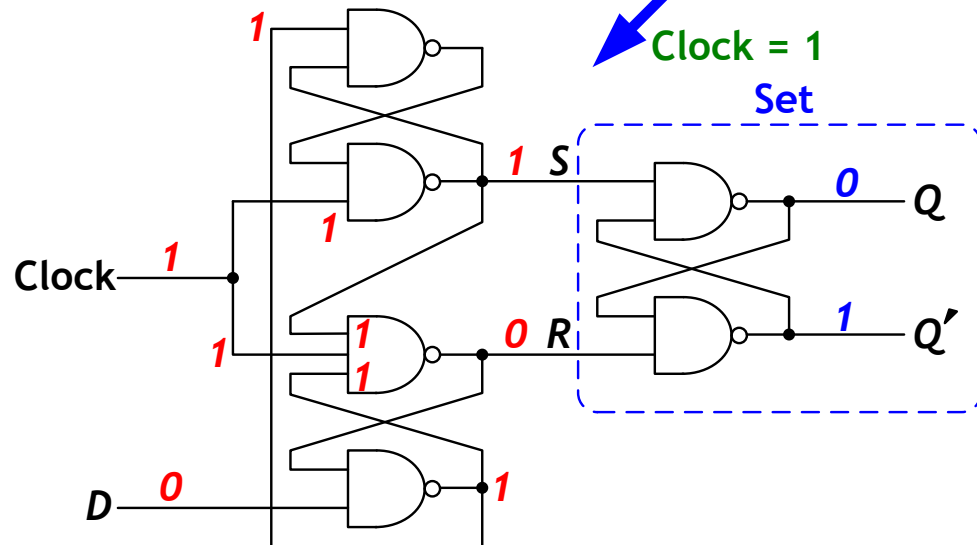


Graphic Symbols for Flip-Flops

  

- ❖ A Flip-Flop has a similar symbol to a Latch
- ❖ The difference is the arrowhead at the clock input C
- ❖ The arrowhead indicates sensitivity to the edge of the clock
- ❖ A bubble at the C input indicates negative edge-triggered FF

D Flip-Flop with Asynchronous Reset

 - ❖ When Flip-Flops are powered, their initial state is unknown
- ❖ Some flip-flops have an **Asynchronous Reset** input R
- ❖ Resets the state (to logic value **0**), independent of the clock
- ❖ This is required to initialize a circuit before operation
- ❖ If the R input is inverted (bubble) then $R = 0$ resets the flip-flop





Inputs			Outputs	
R	$Data$	Clk	Q	\bar{Q}
0	X	X	0	1
1	0	↑	0	1
1	1	↑	1	0


Function Table

D Flip-Flop with Asynchronous Reset

Circuit Diagram

  



Graphic Symbol

 

Function Table

R	C	D	Q	Q'
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0


D Flip-Flop with Asynchronous Reset

  


JK Flip-Flop

- ❖ The D Flip-Flop is the most commonly used type
- ❖ The JK is another type of Flip-Flop with inputs: J, K, and Clk
- ❖ When $JK = 10 \rightarrow$ Set, When $JK = 01 \rightarrow$ Reset
- ❖ When $JK = 00 \rightarrow$ No change, When $JK = 11 \rightarrow$ Invert outputs
- ❖ JK can be implemented using D FF

J	K	Q_{t+1}
0	0	Q_t
0	1	0
1	0	1
1	1	\overline{Q}_t

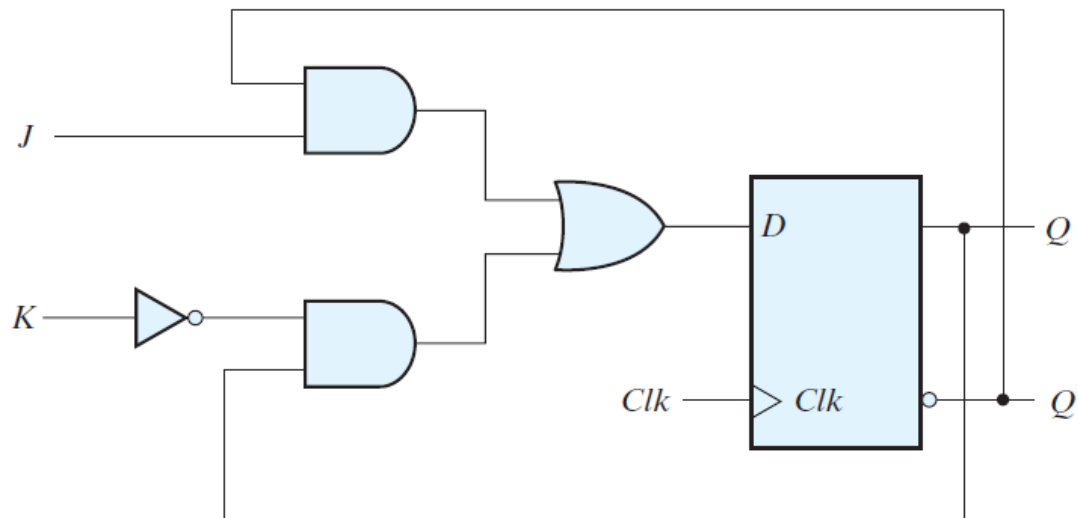


(a) Circuit diagram

 

(b) Graphic symbol


JK Flip-Flop Timing Diagram

 

T = toggle

Characteristic Equation of the JK Flip-Flop

$Q(t)$	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 


$$Q(t+1) = JQ' + K'Q$$


T Flip-Flop

- ❖ The T (Toggle) flip-flop has inputs: T and Clk
- ❖ When $T = 0 \rightarrow$ No change, When $T = 1 \rightarrow$ Invert outputs
- ❖ The T flip-flop can be implemented using a JK flip-flop
- ❖ It can also be implemented using a D flip-flop and a XOR gate


T	Q_{t+1}
0	Q_t
1	\overline{Q}_t

 

(a) From JK flip-flop

 


(b) From D flip-flop

 


(c) Graphic symbol

T Flip-Flop Timing Diagram

 

Characteristic Equation of the T- Flip Flop

$Q(t)$	T	$Q(t + 1)$
0	0	0
0	1	1
1	0	1
1	1	0

 

$$Q(t+1) = TQ' + T'Q$$

Flip-Flop Characteristic Table

- ❖ Defines the operation of a flip-flop in a tabular form
- ❖ Next state is defined in terms of the current state and the inputs

$Q(t)$ refers to current state **before** the clock edge arrives

$Q(t + 1)$ refers to next state **after** the clock edge arrives

D Flip-Flop		
D	$Q(t+1)$	
0	0	Reset
1	1	Set

JK Flip-Flop			
J	K	$Q(t+1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

T Flip-Flop		
T	$Q(t+1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

Flip-Flop Characteristic Equation

- ❖ The characteristic equation defines the operation of a flip-flop
- ❖ For D Flip-Flop: $Q(t + 1) = D$
- ❖ For JK Flip-Flop: $Q(t + 1) = J Q'(t) + K' Q(t)$
- ❖ For T Flip-Flop: $Q(t + 1) = T \oplus Q(t)$
- ❖ Clearly, the D Flip-Flop is the simplest among the three


D Flip-Flop	
D	$Q(t+1)$
0	0 Reset
1	1 Set

JK Flip-Flop	
J K	$Q(t+1)$
0 0	$Q(t)$ No change
0 1	0 Reset
1 0	1 Set
1 1	$Q'(t)$ Complement

T Flip-Flop	
T	$Q(t+1)$
0	$Q(t)$ No change
1	$Q'(t)$ Complement

Timing Considerations for Flip-Flops

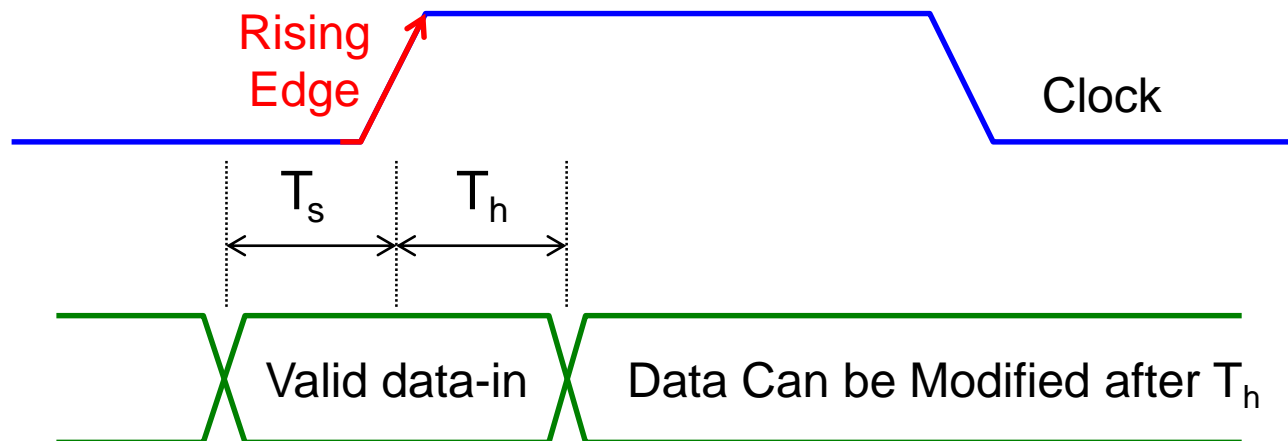- ❖ **Setup Time (T_s):** Time duration for which the data input must be valid and stable **before** the arrival of the clock edge.
- ❖ **Hold Time (T_h):** Time duration for which the data input must not be changed **after** the clock transition occurs.
- ❖ T_s and T_h must be ensured for the proper operation of flip-flops



Analysis of Clocked Sequential Circuits

- ❖ Analysis is describing what a given circuit will do
- ❖ The output of a clocked sequential circuit is determined by
 1. Inputs
 2. State of the Flip-Flops
- ❖ **Analysis Procedure:**
 1. Obtain the equations at the inputs of the Flip-Flops
 2. Obtain the output equations
 3. Fill the state table for all possible input and state values
 4. Draw the state diagram

Analysis Example

❖ Is this a clocked sequential circuit?

YES!

❖ What type of Memory?

D Flip-Flops

❖ How many state variables?


Two state variables: A and B

❖ What are the Inputs?

One Input: x

❖ What are the Outputs?

One Output: y

 

Flip-Flop Input Equations

- ❖ What are the equations on the D inputs of the flip-flops?

$$D_A = A x + B x$$

$$D_B = A' x$$


- ❖ A and B are the **current state**

$$A(t) = A, \quad B(t) = B$$

- ❖ D_A and D_B are the **next state**

$$A(t + 1) = D_A, \quad B(t + 1) = D_B$$

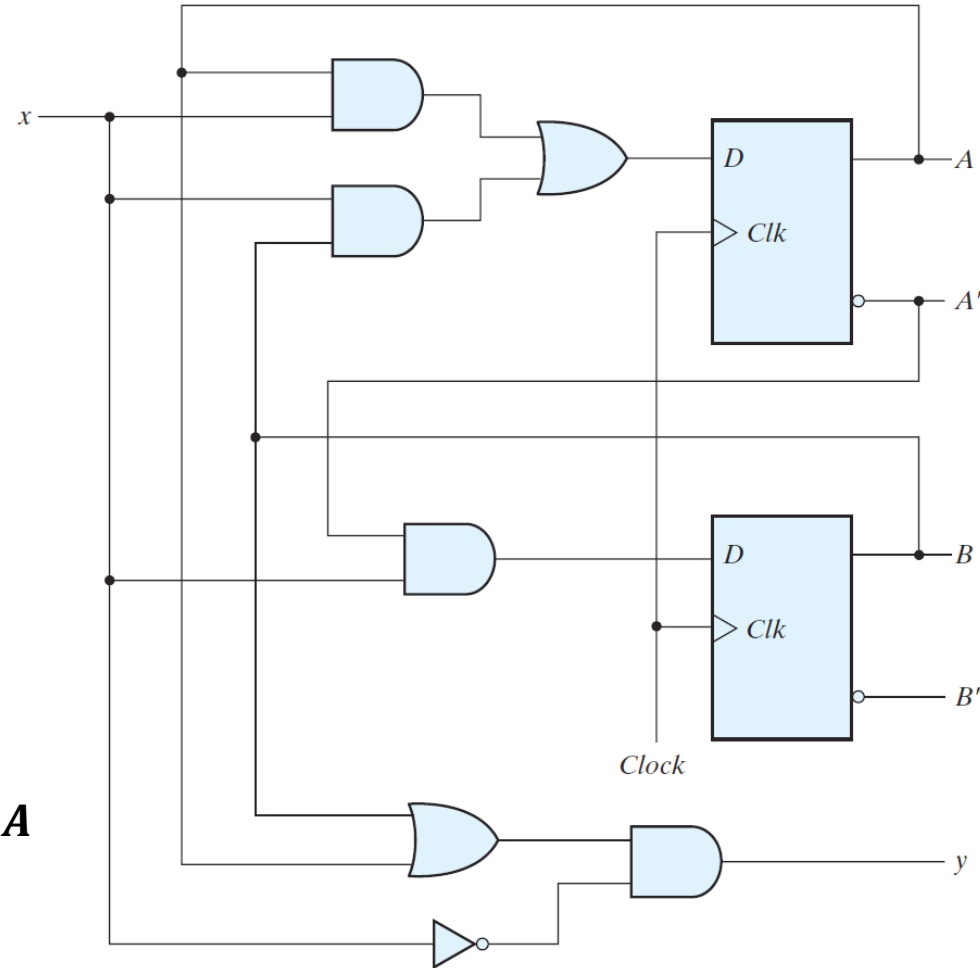- ❖ The values of A and B will be D_A and D_B at the next clock edge



Next State and Output Equations

- ❖ The next state equations define the **next state**

At the **inputs** of the Flip-Flops


- ❖ Next state equations?

$$A(t + 1) = D_A = A x + B x$$

$$B(t + 1) = D_B = A' x$$

- ❖ There is only one output y
- ❖ What is the output equation?

$$y = (A + B) x'$$

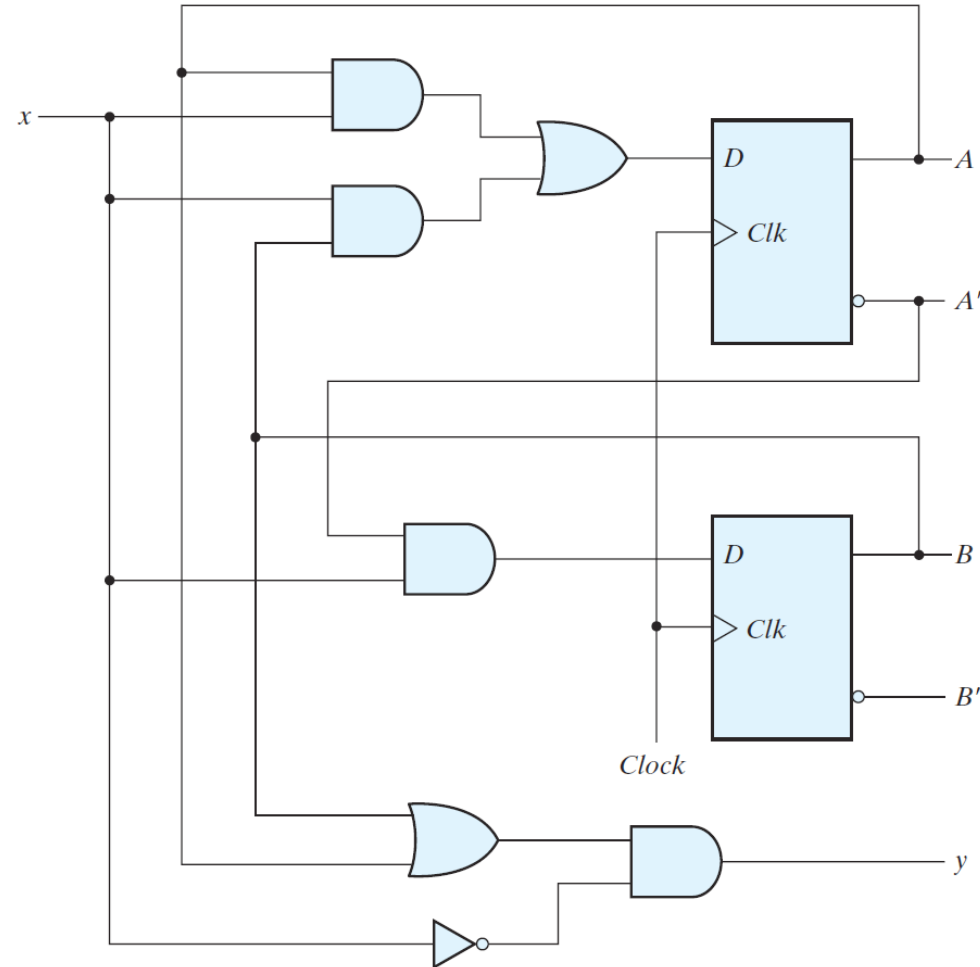

State Table

- ❖ State table shows the Next State and Output in a tabular form
- ❖ Next State Equations: $A(t + 1) = A x + B x$ and $B(t + 1) = A' x$
- ❖ Output Equation: $y = (A + B) x'$

Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Another form of the state table


Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

State Diagram

- ❖ State diagram is a graphical representation of a state table
- ❖ The circles are the states
- ❖ Two state variable \rightarrow Four states (ALL values of A and B)
- ❖ Arcs are the state transitions

Labeled with: Input x / Output y

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

 

Combinational versus Sequential Analysis

Analysis of Combinational Circuits

- ❖ Obtain the Boolean Equations
- ❖ Fill the Truth Table

Output is a function of input only

Analysis of Sequential Circuits


- ❖ Obtain the Next State Equations
- ❖ Obtain the Output Equations
- ❖ Fill the State Table
- ❖ Draw the State Diagram

Next state is a function of input and current state


Output is a function of input and current state

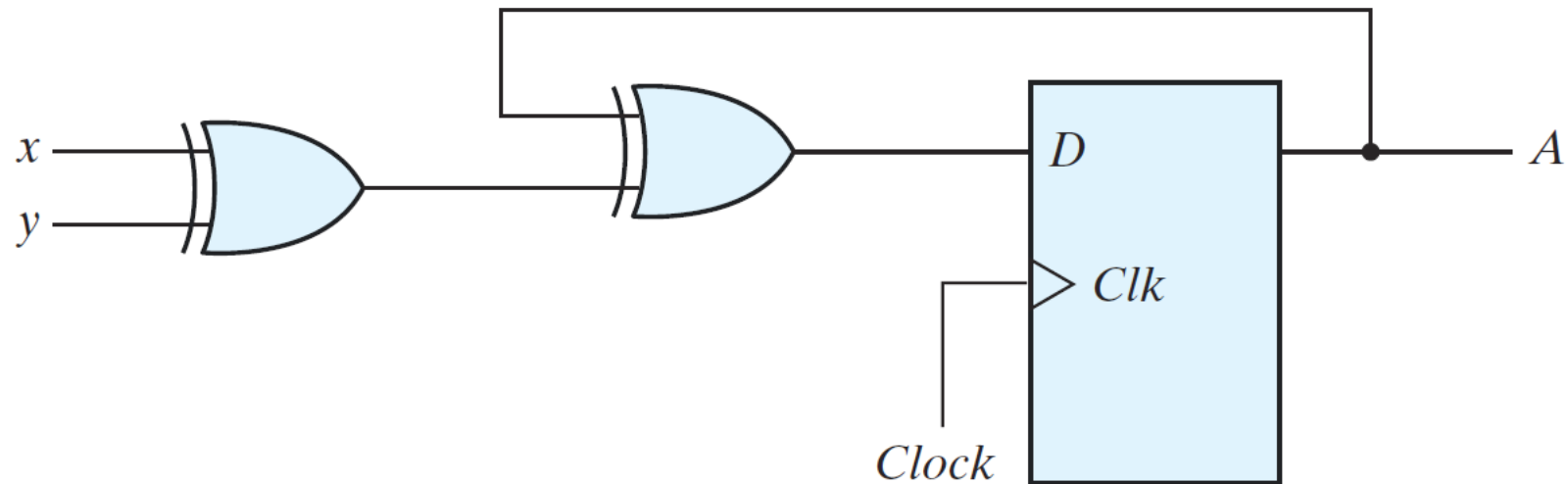Example with Output = Current State

- ❖ Analyze the sequential circuit shown below
- ❖ Two inputs: x and y
- ❖ One state variable A
- ❖ No separate output \rightarrow Output = current state A
- ❖ Obtain the next state equation, state table, and state diagram




Example with Output = Current State

 

❖ Flip-Flop Input Equation:


$$D_A = A \oplus x \oplus y$$

 ❖ Next State Equation: $A(t + 1) = A \oplus x \oplus y$



Present state	Inputs		Next state
<i>A</i>	<i>x</i>	<i>y</i>	<i>A</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Sequential Circuit with T Flip-Flops

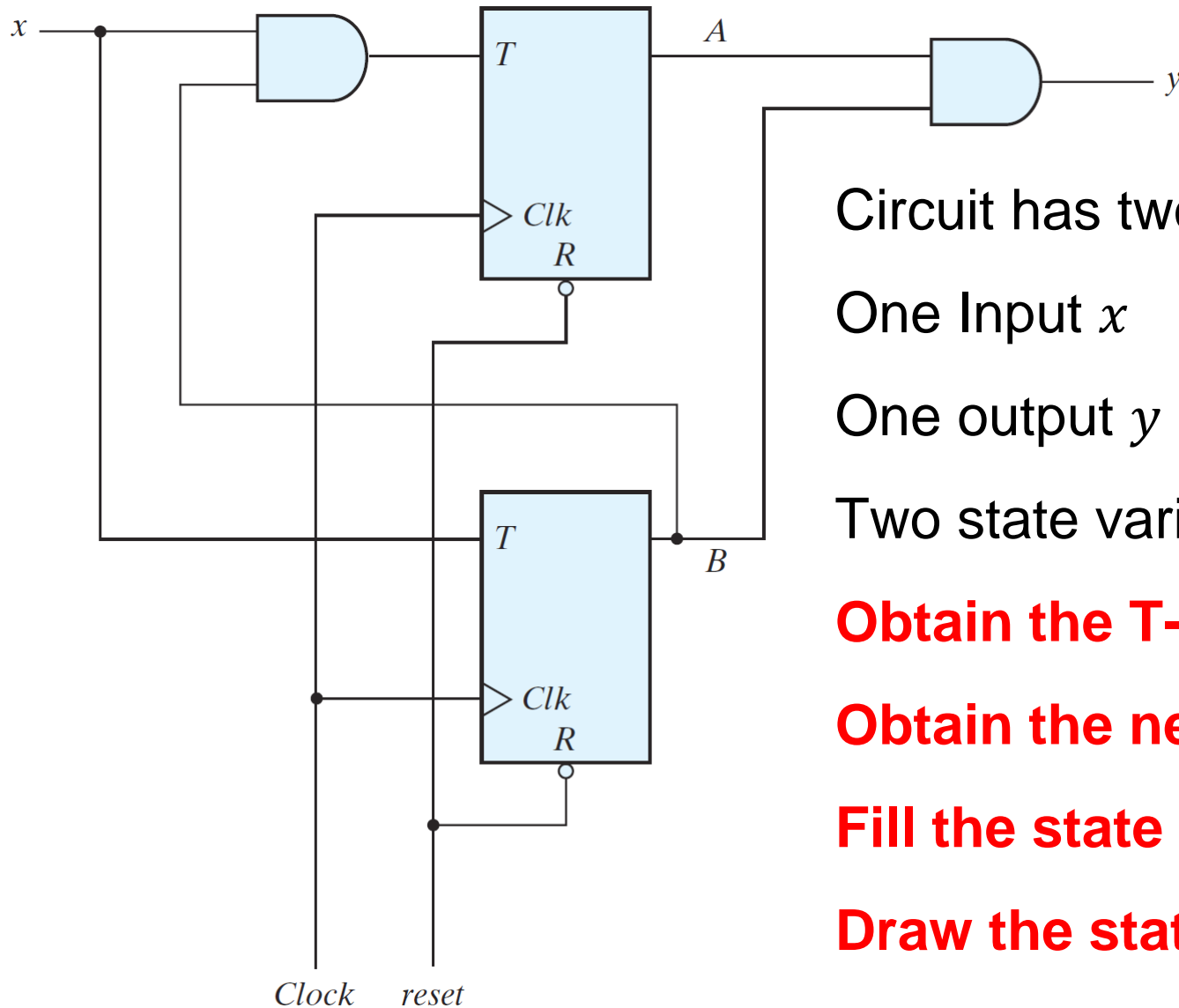

Circuit has two T Flip-Flops

One Input x

One output y

Two state variables: A and B

Obtain the T-FF input equations

Obtain the next state equations

Fill the state table

Draw the state diagram

Recall: Flip-Flop Characteristic Equation

❖ For D Flip-Flop: $Q(t + 1) = D$

❖ For T Flip-Flop: $Q(t + 1) = T \oplus Q(t)$

❖ For JK Flip-Flop: $Q(t + 1) = J Q'(t) + K' Q(t)$


These equations
define the Next State

D Flip-Flop	
D	$Q(t+1)$
0	0 Reset
1	1 Set

T Flip-Flop	
T	$Q(t+1)$
0	$Q(t)$ No change
1	$Q'(t)$ Complement

JK Flip-Flop	
J K	$Q(t+1)$
0 0	$Q(t)$ No change
0 1	0 Reset
1 0	1 Set
1 1	$Q'(t)$ Complement

Sequential Circuit with T Flip-Flops

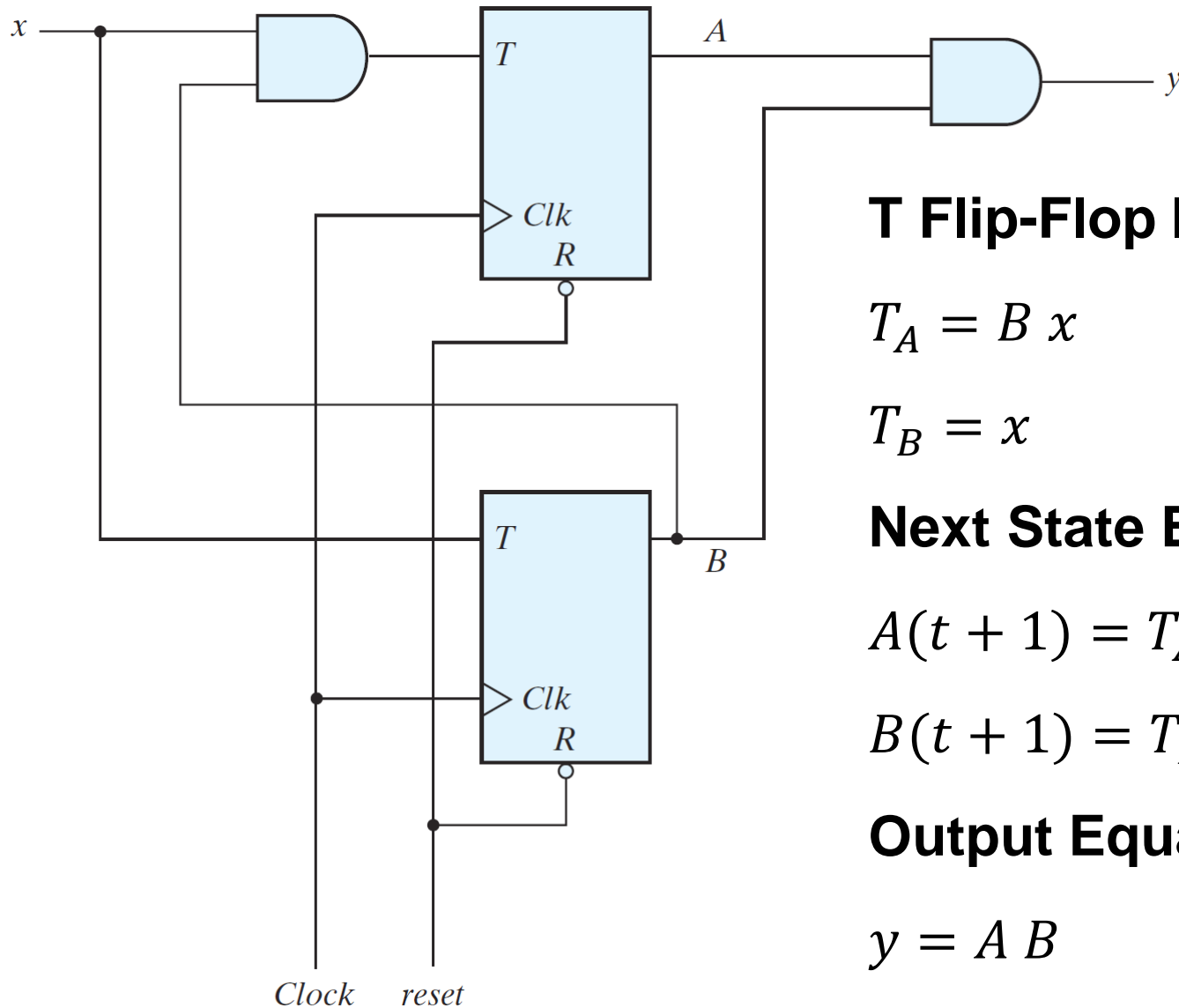

T Flip-Flop Input Equations:

$$T_A = B x$$

$$T_B = x$$

Next State Equations:

$$A(t + 1) = T_A \oplus A = (B x) \oplus A$$

$$B(t + 1) = T_B \oplus B = x \oplus B$$

Output Equation:

$$y = A B$$

From Next State Equations to State Table

T Flip-Flop Input Equations:

$$T_A = B x$$

$$T_B = x$$

Next State Equations:

$$A(t + 1) = (B x) \oplus A$$

$$B(t + 1) = x \oplus B$$

Output Equation:

$$y = A B$$


Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

Notice that the output is a function of the present state only.

It does **NOT** depend on the input x

From State Table to State Diagram

Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

 

- ❖ Four States: $AB = 00, 01, 10, 11$ (drawn as circles)
- ❖ Output Equation: $y = AB$ (does not depend on input x)
- ❖ Output y is shown inside the state circle (AB/y)

Sequential Circuit with a JK Flip-Flops

One Input x and two state variables: A and B (outputs of Flip-Flops)


No separate output \rightarrow Output = Current state $A B$

Obtain the JK input equations

Obtain the next state equations

Fill the state table

Draw the state diagram

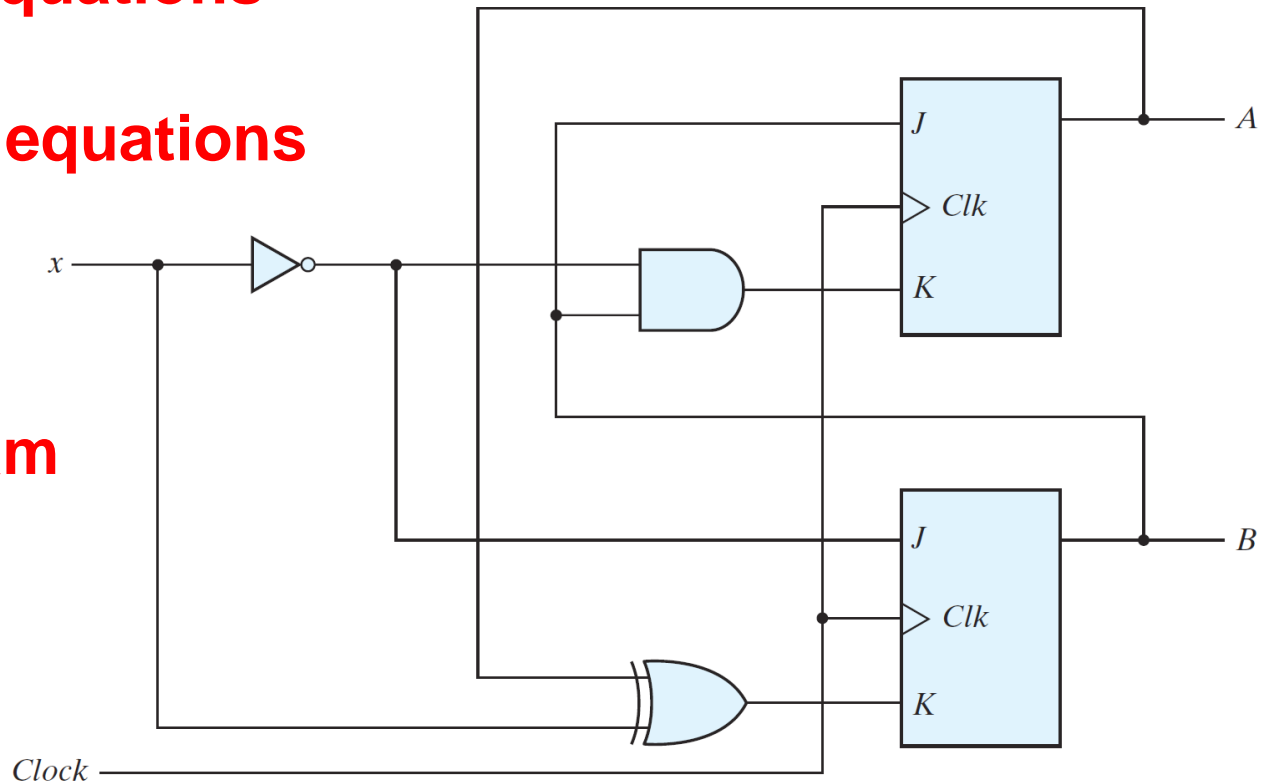

JK Input and Next State Equations

JK Flip-Flop Input Equations:

$$J_A = B \text{ and } K_A = B x'$$

$$J_B = x' \text{ and } K_B = A \oplus x$$

Next State Equations:


$$A(t + 1) = J_A A' + K_A' A$$

$$B(t + 1) = J_B B' + K_B' B$$

Substituting:

$$A(t + 1) = B A' + (B x')' A = A' B + A B' + A x$$
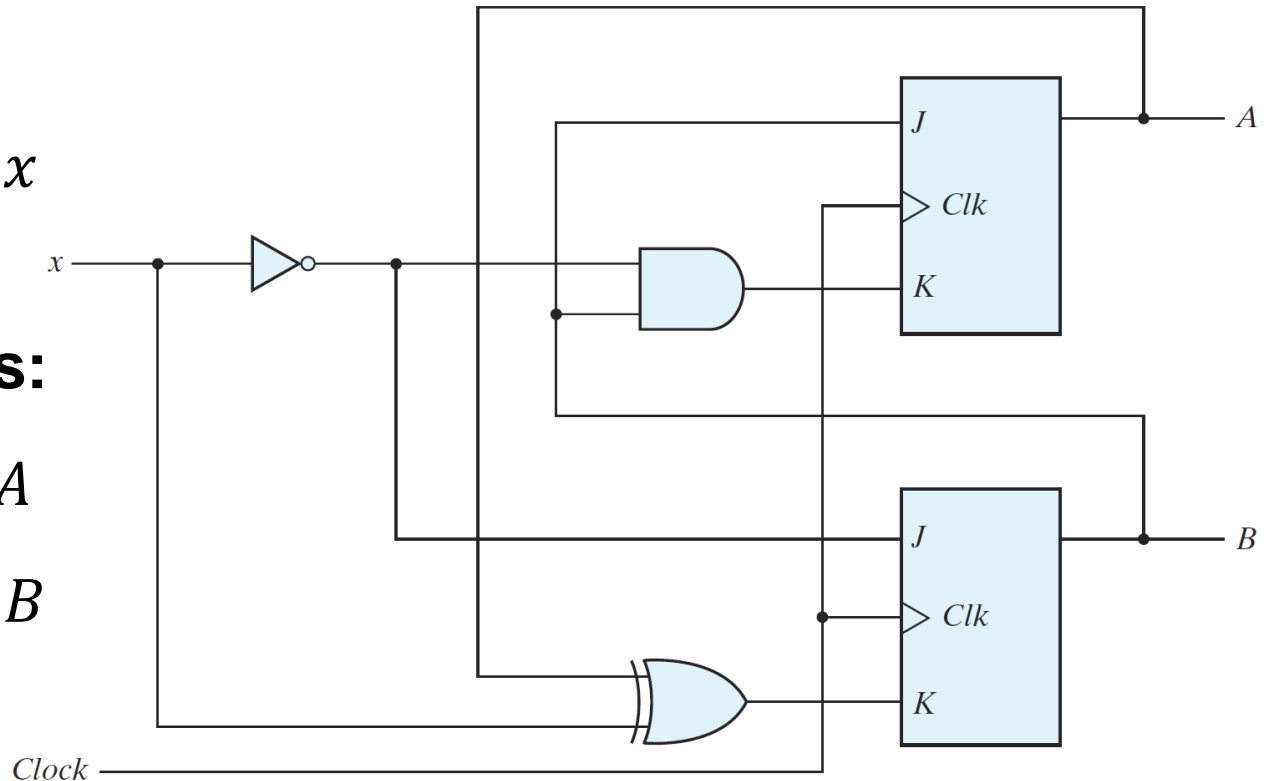
$$B(t + 1) = x' B' + (A \oplus x)' B = B' x' + A B x + A' B x'$$



From JK Input Equations to State Table

JK Input Equations: $J_A = B$, $K_A = B x'$, $J_B = x'$ and $K_B = A \oplus x$


Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

From State Table to State Diagram

Four states: $A B = 00, 01, 10, \text{ and } 11$ (drawn as circles)

Arcs show the input value x on the state transition



Present State		Input x	Next State	
A	B		A	B
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

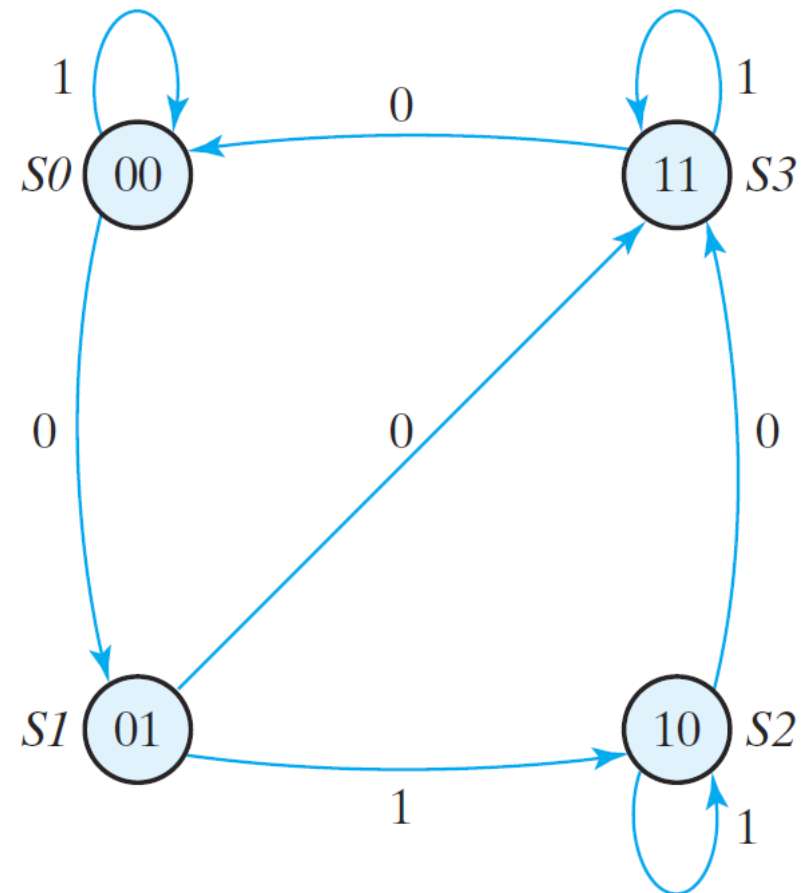

Mealy versus Moore Sequential Circuits

There are two ways to design a clocked sequential circuit:

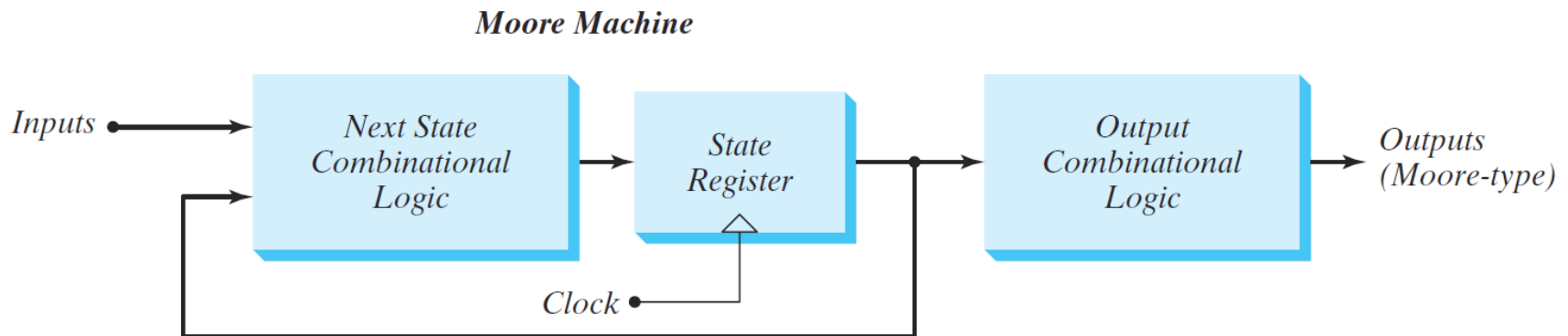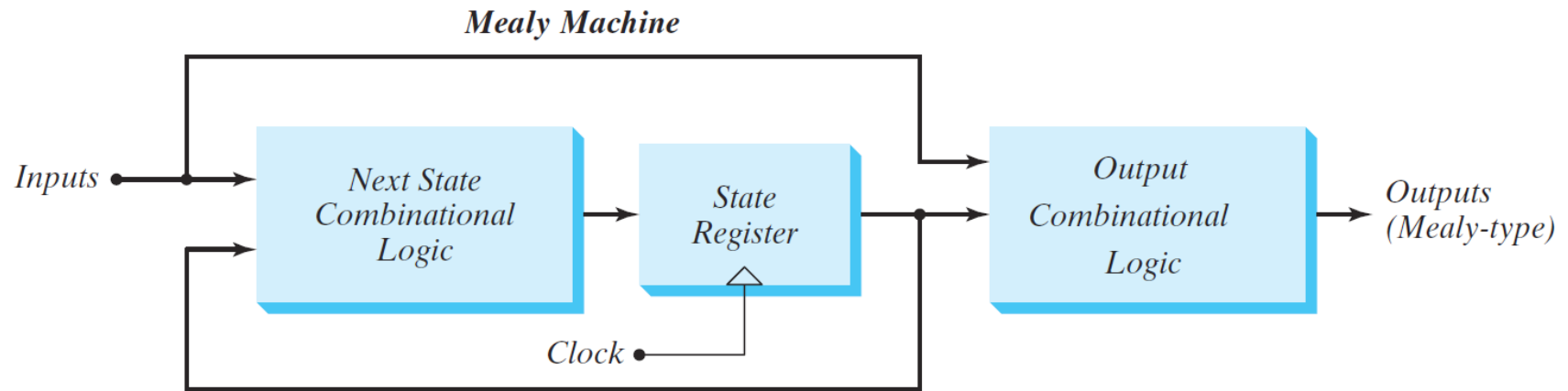
- 1. Mealy Machine:** Outputs depend on present state and inputs
- 2. Moore Machine:** Outputs depend on present state only



Mealy Machine


- ❖ The outputs are a function of the present state and Inputs
- ❖ The outputs are **NOT** synchronized with the clock
- ❖ The outputs may change if inputs change during the clock cycle
- ❖ The outputs may have momentary false values (called glitches)
- ❖ The correct outputs are present just before the edge of the clock

Mealy Machine

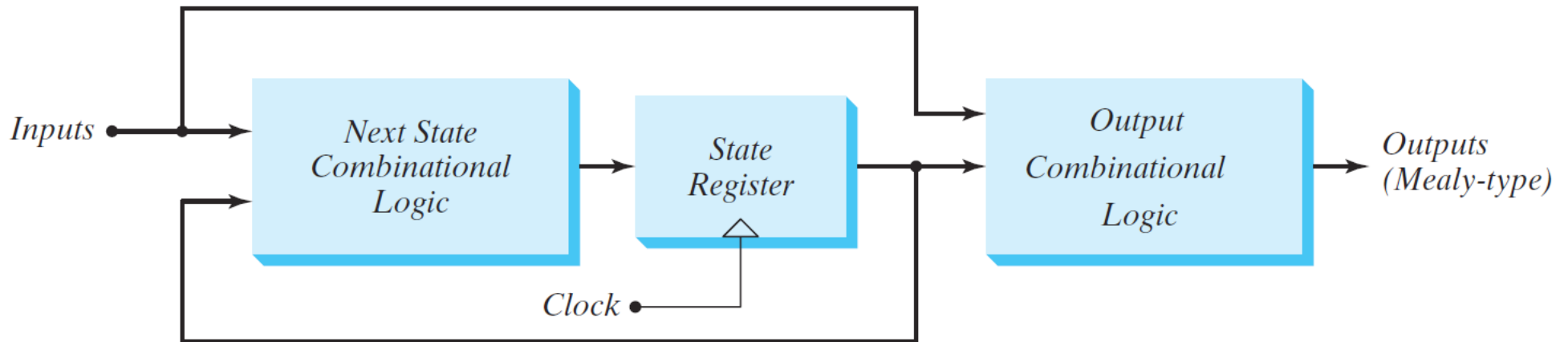


Mealy State Diagram

 - ❖ An example of a Mealy state diagram is shown on the right
- ❖ Each arc is labeled with:
Input / Output
- ❖ The output is shown on the arcs of the state diagram
- ❖ The output depends on the current state and input
- ❖ Notice that State 11 cannot be reached from the other states




Example of Mealy Model

 


Moore Machine

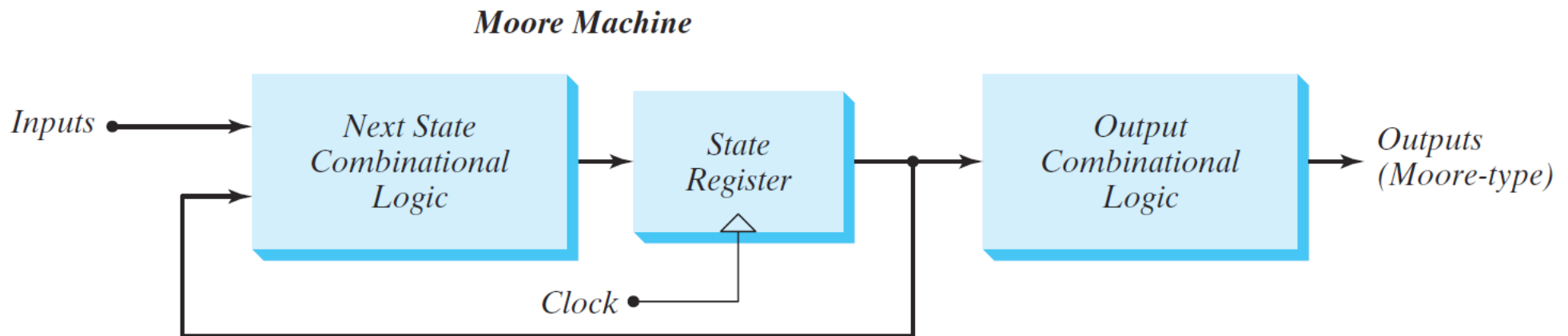- ❖ The outputs are a function of the Flip-Flop outputs only
- ❖ The outputs depend on the current state only
- ❖ The outputs are synchronized with the clock
- ❖ Glitches cannot appear in the outputs (even if inputs change)
- ❖ A given design might mix between Mealy and Moore




Moore State Diagram

 - ❖ An example of a Moore state diagram is shown on the right
- ❖ Arcs are labeled with input only
- ❖ The output is shown inside the state: (State / Output)
- ❖ The output depends on the current state only




Example of Moore Model

Sequential Circuit with JK Flip-Flop

 

State Reduction and Assignment

 
- ❖ Design starts with state table or diagram
- ❖ State reduction aims at exhibiting the same input-output behavior but with a **lower number** of internal states
- ❖ **State Reduction**
 - ✧ Reductions on the number of flip-flops and the number of gates.
 - ✧ A reduction in the number of states may result in a reduction in the **number of flip-flops**.
 - ✧ May lead to use more gates



State Reduction

State: a a b c d e f f g f g a
Input: 0 1 0 1 0 1 1 0 1 0 0
Output: 0 0 0 0 0 1 1 0 1 0 0

 - ✧ Only the input-output sequences are important.
- ✧ Two circuits are **equivalent**
 - Have identical outputs for all input sequences;
 - The number of states is not important.



Equivalent states

❖ Two states are said to be equivalent

❖ For each member of the set of inputs, they give exactly the same output and send the circuit to the same state or to an equivalent state.

❖ One of them can be removed.


Table 5.6
State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

$e = g$

Equivalent states

Remove state

 

Reducing the state table

- ❖ $e = g$ (remove g);
- ❖ $d = f$ (remove f);

Table 5.7
Reducing the State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

State Reduction

- ❖ The checking of each pair of states for possible equivalence can be done systematically
- ❖ The unused states are treated as **don't-care condition** \Rightarrow fewer combinational gates.

 


Table 5.8
Reduced State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1

State Assignment

- ❖ To minimize the cost of the combinational circuits.
- ❖ Three possible binary state assignments. (m states need n -bits, where $2^n > m$)

Table 5.9
Three Possible Binary State Assignments

State	Assignment 1, Binary	Assignment 2, Gray Code	Assignment 3, One-Hot
<i>a</i>	000	000	00001
<i>b</i>	001	001	00010
<i>c</i>	010	011	00100
<i>d</i>	011	010	01000
<i>e</i>	100	110	10000

What code assignment would you choose? Why?

State Assignment

- ❖ Any binary number assignment is satisfactory as long as each **state is assigned a unique number**.
- ❖ Use binary assignment 1.

Table 5.10

Reduced State Table with Binary Assignment 1

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
000	000	001	0	0
001	010	011	0	0
010	000	011	0	0
011	100	011	0	1
100	000	011	0	1


Implication Chart

- ❖ To check possible equivalent states in table with large number of states.
- ❖ Example

Present State	Next state		Output	
	X=0	X=1	X=0	X=1
a	d	b	0	0
b	e	a	0	0
c	g	f	0	1
d	a	d	1	0
e	a	d	1	0
f	c	b	0	0
g	a	e	1	0

Implication Chart

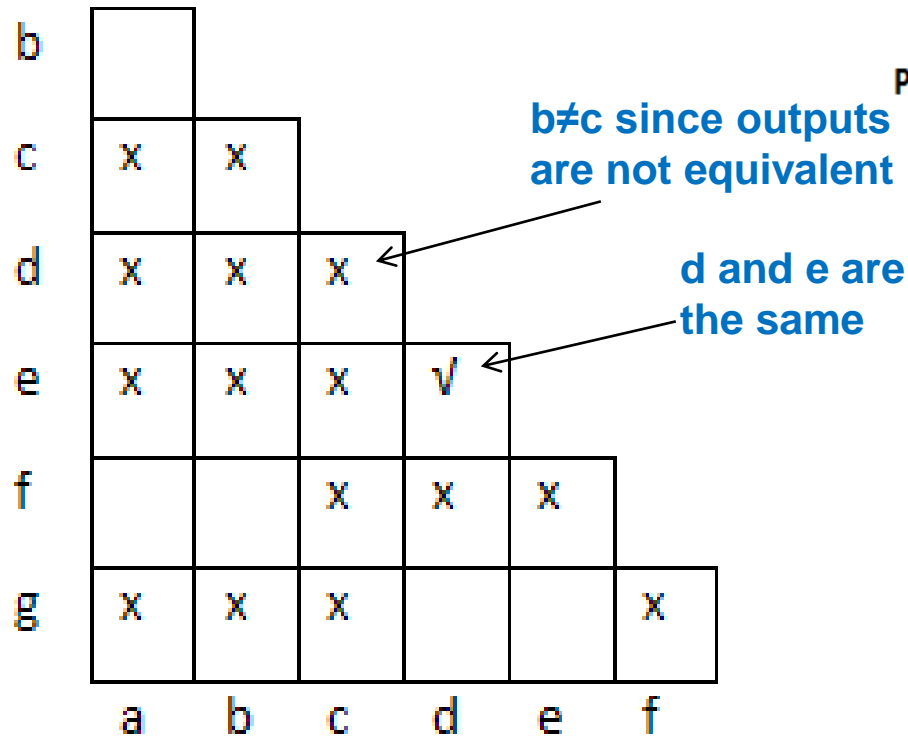- ❖ **Step1:** draw the implication chart and place (X) in any square of a pair of states whose outputs are not equivalent.
 - ✧ Place (\checkmark) for equivalent states (same outputs, same next state).



Present State	Next state		Output	
	X=0	X=1	X=0	X=1
a	d	b	0	0
b	e	a	0	0
c	g	f	0	1
d	a	d	1	0
e	a	d	1	0
f	c	b	0	0
g	a	e	1	0

Implication Chart

- ❖ **Step2:** for remaining squares, enter the implied states

$a \equiv b \text{ iff } d \equiv e$

b	a,b d,e					
c	X	x				
d	x	x	x			
e	x	x	x	✓		
f	c,d b,b	c,e a,b	x	x	x	
g	x	x	x	d,e	d,e	x
	a	b	c	d	e	f

Present State	Next state		Output	
	X=0	X=1	X=0	X=1
a	d	b	0	0
b	e	a	0	0
c	g	f	0	1
d	a	d	1	0
e	a	d	1	0
f	c	b	0	0
g	a	e	1	0

Implication Chart

- ❖ **Step3:** Place (\checkmark) for equivalent states and (X) for not equivalent states

b	a,b d,e				
c	X	x			
d	x	x	x		
e	x	x	x	\checkmark	
f	c,d b,b	c,e a,b	x	x	x
g	x	x	x	d,e	d,e
	a	b	c	d	e

Present State	Next state		Output	
	X=0	X=1	X=0	X=1
a	d	b	0	0
b	e	a	0	0
c	g	f	0	1
d	a	d	1	0
e	a	d	1	0
f	c	b	0	0
g	a	e	1	0

Implication Chart

- ❖ **Step4:** list equivalent states from squares with (\checkmark)

(a, b), (d, e), (d, g), (e, g)

$\underbrace{\hspace{1.5em}} \quad \underbrace{\hspace{1.5em}} \quad \underbrace{\hspace{1.5em}}$
 d d d

- ❖ **Step5:** combine pairs of states into large group

(a, b), (d, e, g)

b	a, b \checkmark d, e					
c	X	x				
d	x	x	x			
e	x	x	x	\checkmark		
f	\times c, d b, b	\times c, e a, b	x	x	x	
g	x	x	x	\checkmark d, e	\checkmark d, e	x
	a	b	c	d	e	f

Implication Chart

- ❖ **Step6:** the final states are the equivalent states and all remaining states in state table:

(a,b) \implies a

(c)

(d,e,g) \implies d

(f)

Implication Chart

❖ The table can be reduced from seven states into four states:

Present State	Next state		Output	
	X=0	X=1	X=0	X=1
a	d	b	0	0
b	e	a	0	0
c	g	f	0	1
d	a	d	1	0
e	a	d	1	0
f	c	b	0	0
g	a	e	1	0

Present State	Next state		Output	
	X=0	X=1	X=0	X=1
a	d	a	0	0
c	d	f	0	1
d	a	d	1	0
f	c	a	0	0

Design of Sequential Logic



❖ Design Procedure

1. From the word description and specifications of the desired operation, derive a state diagram for the circuit.
2. Reduce the number of states if necessary
3. Assign binary values to the states
4. Obtain the binary-coded state table
5. Choose the type of flip-flops to be used
6. Derive the simplified flip-flop input equations and output equations
7. Draw the logic diagram

Design of Clocked Sequential Circuits

❖ Example:

Detect 3 or more consecutive 1's

  


State	A	B
S_0	0	0
S_1	0	1
S_2	1	0
S_3	1	1


Design of Clocked Sequential Circuits

❖ Example:

Detect 3 or more consecutive 1's

 


Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

 

Design of Clocked Sequential Circuits

❖ Example:

Detect 3 or more consecutive 1's

 

Present State		Input	Next State		Output
<i>A</i>	<i>B</i>	<i>x</i>	<i>A</i>	<i>B</i>	<i>y</i>
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

Synthesis using *D* Flip-Flops

$$A(t+1) = D_A(A, B, x) \\ = \sum (3, 5, 7)$$

$$B(t+1) = D_B(A, B, x) \\ = \sum (1, 5, 7)$$

$$y(A, B, x) = \sum (6, 7)$$

Design of Clocked Sequential Circuits with D F.F.

❖ Example:





Detect 3 or more consecutive 1's

Synthesis using *D* Flip-Flops

$$D_A(A, B, x) = \sum (3, 5, 7) \\ = A x + B x$$

$$D_B(A, B, x) = \sum (1, 5, 7) \\ = A x + B' x$$


$$y(A, B, x) = \sum (6, 7) \\ = A B$$

    

Design of Clocked Sequential Circuits with D F.F.

❖ Example:

Detect 3 or more consecutive 1's

 


Synthesis using *D* Flip-Flops

$$D_A = A x + B x$$

$$D_B = A x + B' x$$

$$y = A B$$

 

Flip-Flop Excitation Tables

Present State	Next State	F.F. Input
$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

Present State	Next State	F.F. Input	
$Q(t)$	$Q(t+1)$	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

0 0 (No change)

0 1 (Reset)

1 0 (Set)

1 1 (Toggle)

0 1 (Reset)

1 1 (Toggle)

0 0 (No change)


1 0 (Set)

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

Design of Clocked Sequential Circuits with JK F.F.

❖ Example:

Detect 3 or more consecutive 1's

 

Present State		Input	Next State		Flip-Flop Inputs			
A	B	x	A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	0	x	0	x
0	0	1	0	1	0	x	1	x
0	1	0	0	0	0	x	x	1
0	1	1	1	0	1	x	x	1
1	0	0	0	0	x	1	0	x
1	0	1	1	1	x	0	1	x
1	1	0	0	0	x	1	x	1
1	1	1	1	1	x	0	x	0

Synthesis using JK F.F.

$$J_A(A, B, x) = \sum (3)$$

$$d_{JA}(A, B, x) = \sum (4, 5, 6, 7)$$

$$K_A(A, B, x) = \sum (4, 6)$$

$$d_{KA}(A, B, x) = \sum (0, 1, 2, 3)$$

$$J_B(A, B, x) = \sum (1, 5)$$

$$d_{JB}(A, B, x) = \sum (2, 3, 6, 7)$$

$$K_B(A, B, x) = \sum (2, 3, 6)$$

$$d_{KB}(A, B, x) = \sum (0, 1, 4, 5)$$

Design of Clocked Sequential Circuits with JK F.F.




❖ Example:

Detect 3 or more consecutive 1's

Synthesis using JK Flip-Flops

$$J_A = Bx \quad K_A = x'$$


$$J_B = x \quad K_B = A' + x'$$

   

Design of Clocked Sequential Circuits with T F.F.

❖ Example:

Detect 3 or more consecutive 1's

 

Present State		Input	Next State		F.F. Input	
A	B	x	A	B	T_A	T_B
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	0	0	1
0	1	1	1	0	1	1
1	0	0	0	0	1	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	1	1	1	0	0

Synthesis using T Flip-Flops


$$T_A(A, B, x) = \sum (3, 4, 6)$$

$$T_B(A, B, x) = \sum (1, 2, 3, 5, 6)$$

Design of Clocked Sequential Circuits with T F.F.

❖ Example:




Detect 3 or more consecutive 1's

 

Synthesis using *T* Flip-Flops

$$T_A = A x' + A' B x$$

$$T_B = A' B + B \oplus x$$

   

Design of a Binary Counter

Problem Specification:

- ❖ Design a circuit that counts up from 0 to 7 then back to 0


000 → 001 → 010 → 011 → 100 → 101 → 110 → 111 → 000

When reaching 7, the counter goes back to 0 then goes up again

- ❖ There is no input to the circuit
- ❖ The counter is incremented each cycle
- ❖ The output of the circuit is the present state (count value)
- ❖ The circuit should be designed using D-type Flip-Flops

Designing the State Diagram

 - ❖ Eight states are needed to store the count values 0 to 7
- ❖ No input, state transition happens at the edge of each cycle




Three Flip-Flops
are required for
the eight states

Each state is
assigned a unique
binary count value

State Table

Only two columns: Present State and Next State

State changes each cycle

 

Present State $Q_2 Q_1 Q_0$	Next State $D_2 D_1 D_0$
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	0 1 1
0 1 1	1 0 0
1 0 0	1 0 1
1 0 1	1 1 0
1 1 0	1 1 1
1 1 1	0 0 0

Deriving the Next State Equations

Present State			Next State		
Q_2	Q_1	Q_0	D_2	D_1	D_0
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

		D_2	
		Q_0	
Q_2Q_1	Q_0	0	1
00		0	0
01		0	1
11		1	0
10		1	1

		D_1	
		Q_0	
Q_2Q_1	Q_0	0	1
00		0	1
01		1	0
11		1	0
10		0	1

		D_0	
		Q_0	
Q_2Q_1	Q_0	0	1
00		1	0
01		1	0
11		1	0
10		1	0

$$D_2 = Q_2Q_1' + Q_2Q_0' + Q_2'Q_1Q_0$$

$$D_2 = Q_2(Q_1' + Q_0') + Q_2'Q_1Q_0$$

$$D_2 = Q_2(Q_1Q_0)' + Q_2'(Q_1Q_0) = Q_2 \oplus (Q_1Q_0)$$

$$D_1 = Q_1Q_0' + Q_1'Q_0 = Q_1 \oplus Q_0$$


$$D_0 = Q_0'$$

3-Bit Counter Circuit Diagram

$$D_2 = Q_2 \oplus (Q_1 Q_0)$$

$$D_1 = Q_1 \oplus Q_0$$

$$D_0 = Q'_0$$

 


Output = 3-bit Count Value

Design Example: 3-bit Binary Counter Using T FFs.

❖ State Diagram and State Table of 3-bit Binary Counter

State Diagram

 

Excitation Table

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0




State Table

Present State			Next State			Flip-Flop Inputs		
A_2	A_1	A_0	A_2	A_1	A_0	T_{A_2}	T_{A_1}	T_{A_0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

Refer to T-FF Excitation Table


Design Example: 3-bit Binary Counter Using T FFs.

   ❖ K-Map Logic Simplification for 3-bit Binary Counter



Design Example: 3-bit Binary Counter Using T FFs.

 ❖ Draw the 3-bit Binary Counter Circuits with T FFs




Up/Down Counter with Enable

- ❖ **Problem:** Design a synchronous up-down T flip-flop 2-bit binary counter with a select input line S and a count enable En input. When $S = 0$, the counter counts down; and when $S = 1$, the counter counts up. When $En = 1$, the counter is in normal up- or down- counting; and $En = 0$ for disabling both counts.
- ❖ **Solution:** Required mode of operation:

Inputs		Operation
En	S	
0	x	Hold status
1	0	Count Down
1	1	Count Up

 State Diagram/Table for 2-bit Up-Down Binary Counter



Arc Label: EnS

T Flip-Flop		
Q(t)	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0

Present State			Inputs		Next State			T flip-flops	
No	Q1	Q0	En	S	No	Q1	Q0	T _{Q1}	T _{Q0}
0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	0
0	0	0	1	0	3	1	1	1	1
0	0	0	1	1	1	0	1	0	1
1	0	1	0	0	1	0	1	0	0
1	0	1	0	1	1	0	1	0	0
1	0	1	1	0	0	0	0	0	1
1	0	1	1	1	2	1	0	1	1
2	1	0	0	0	2	1	0	0	0
2	1	0	0	1	2	1	0	0	0
2	1	0	1	0	1	0	1	1	1
2	1	0	1	1	3	1	1	0	1
3	1	1	0	0	3	1	1	0	0
3	1	1	0	1	3	1	1	0	0
3	1	1	1	0	2	1	0	0	1
3	1	1	1	1	0	0	0	1	1

Input Equations for 2-bit Up-Down Binary Counter

- The carry out signals:

- CO_{up} and CO_{down}

$CO_{up} = Q_0 Q_1 EnS \rightarrow$ counter reached 11 and it is counting up

$CO_{down} = Q_0' Q_1' EnS' \rightarrow$ counter reached 00 and it is counting down


EnS Q ₁ Q ₀	00	01	11	10
00	0	0	0	1
01	0	0	1	0
11	0	0	1	0
10	0	0	0	1

$$T_{Q_1} = Q_0 EnS + Q_0' EnS'$$

EnS Q ₁ Q ₀	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	0	1	1
10	0	0	1	1

$$T_{Q_0} = En$$

Circuit for 2-bit Up-Down Binary Counter

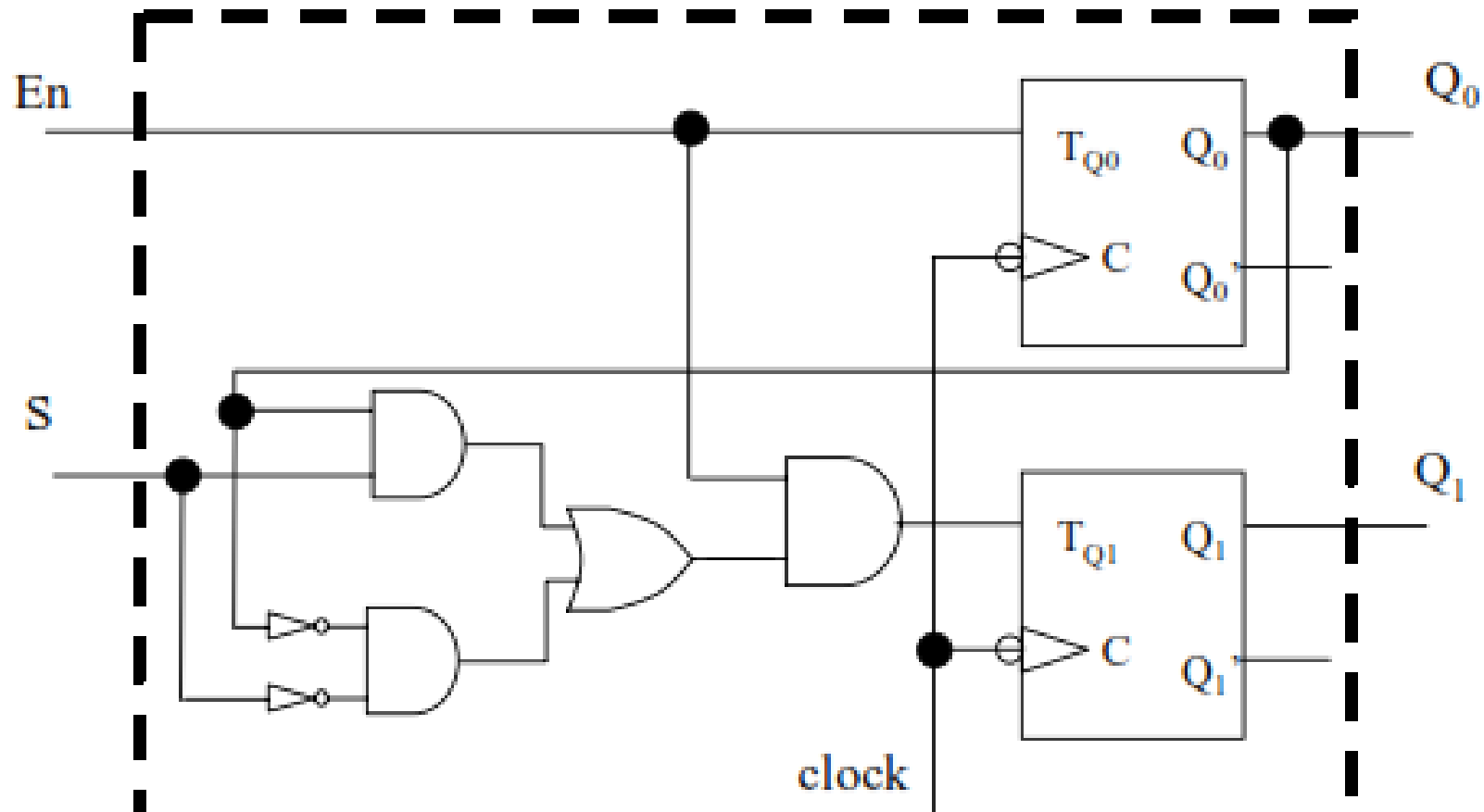

Dealing with Unused States

- ❖ An n -bit counter has 2^n states, but there are occasions when we wish to use less than the total number of states available.
- ❖ The unused states may be treated as “don’t care” conditions (or assigned to specific next states).
- ❖ Because outside interference may land the counter in these states, we must ensure that the counter can find its way back to a valid state.

Dealing with Unused States

❖ Self-correcting counter

- ✧ Ensure that when a counter enter one of its unused states, it eventually goes into one of the valid states after one or more clock pulses so it can resume normal operation.
- ✧ Analyze the counter to determine the next state from an unused state after it is designed
- ✧ If the unused states are assigned specific next states, this ensures that the circuit is self correcting by design
- ✧ An alternative design could use additional logic to direct every unused state to a specific next state.

❖ Design your counters to be self-starting

- ✧ Draw **all** states in the state diagram
- ✧ Fill in the **entire** state-transition table
- ✧ May limit your ability to exploit don't cares
 - Choose startup transitions that minimize the logic

Counters with unused states

State Table for Counter

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

K-Maps for JK Flip Flop Inputs

	BC	00	01	11	10	
A	0		1	X	X	$J_B = C$
	1		1	X	X	

	BC	00	01	11	10	
A	0	1	X	X		$J_C = B'$
	1	1	X	X		


	BC	00	01	11	10	
A	0	X	X	X	1	$K_B = 1$
	1	X	X	X	1	

	BC	00	01	11	10	
A	0	X	1	X	X	$K_C = 1$
	1	X	1	X	X	

	BC	00	01	11	10	
A	0	1	X	X		$J_C = B'$
	1	1	X	X		

	BC	00	01	11	10	
A	0	X	1	X	X	$K_C = 1$
	1	X	1	X	X	

Counter with unused states

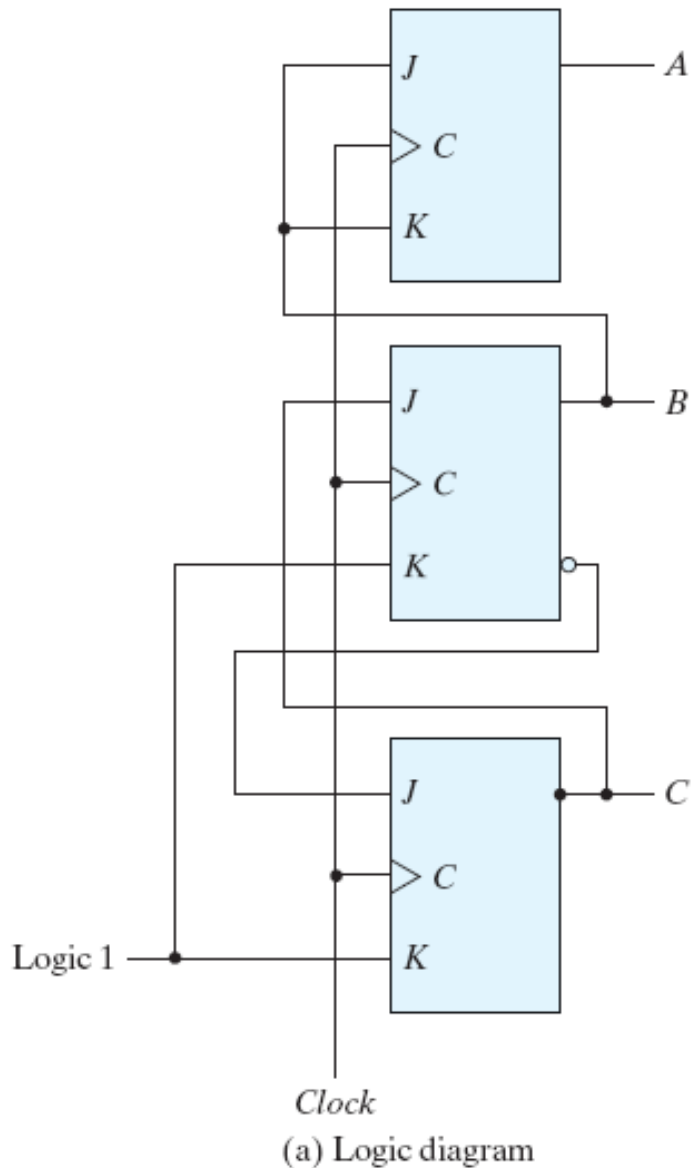


State Table for Counter

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

$$J_A = B \quad K_A = B$$

$$J_B = C \quad K_B = 1$$

$$J_C = B' \quad K_C = 1$$

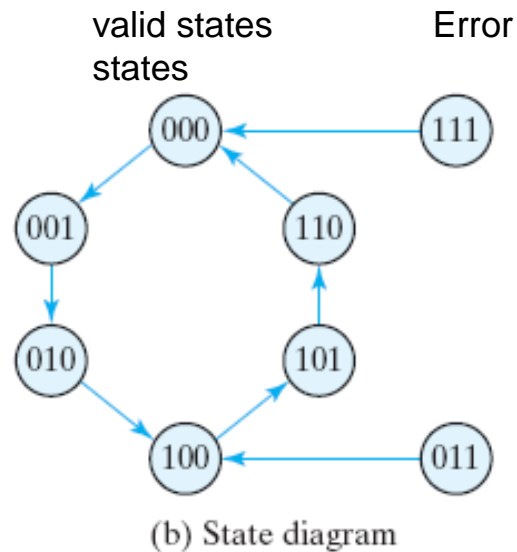


Example: 5-state counter

❖ Counter repeats 5 states in sequence

❖ Sequence is 000, 010, 011, 101, 110, 000

Step 1: State diagram

 

Step 2: State transition table

Assume D flip-flops

Present State		Next State			
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	X	X	X
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	X	X	X
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	X	X	X

Example: 5-state counter

Step 3: Encode next state functions

C+

		<u>C</u>			
	0	0		0	X
<u>A</u>	X	1		X	1
	<u>B</u>				

$$C+ = A$$

B+

		<u>C</u>			
	1	1		0	X
<u>A</u>	X	0		X	1
	<u>B</u>				

$$B+ = B' + A'C'$$


A+

		<u>C</u>			
	0	1		0	X
<u>A</u>	X	1		X	0
	<u>B</u>				

$$A+ = BC'$$

Example: 5-state counter


Step 4: Implement the design

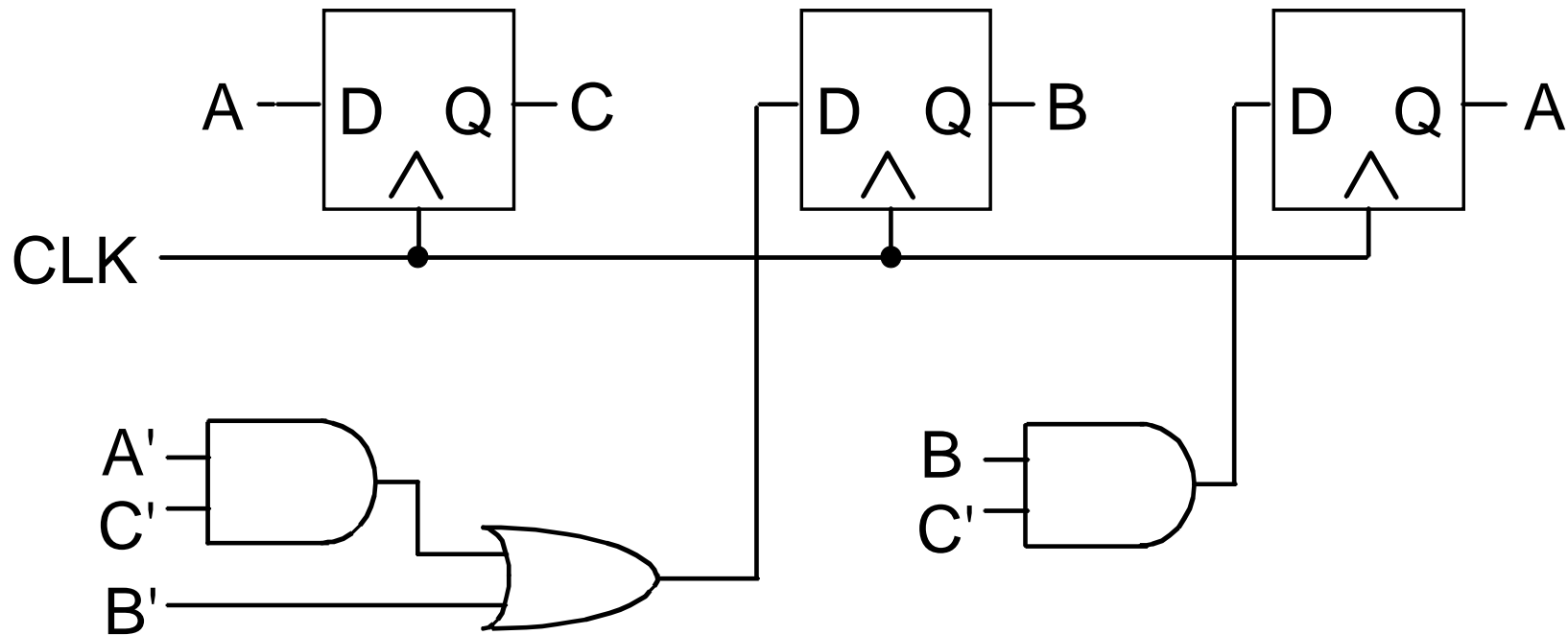

Recall that a D flip flop also produces Q' so A' , B' , and C' would all be available without any extra inverters

Is our design robust?

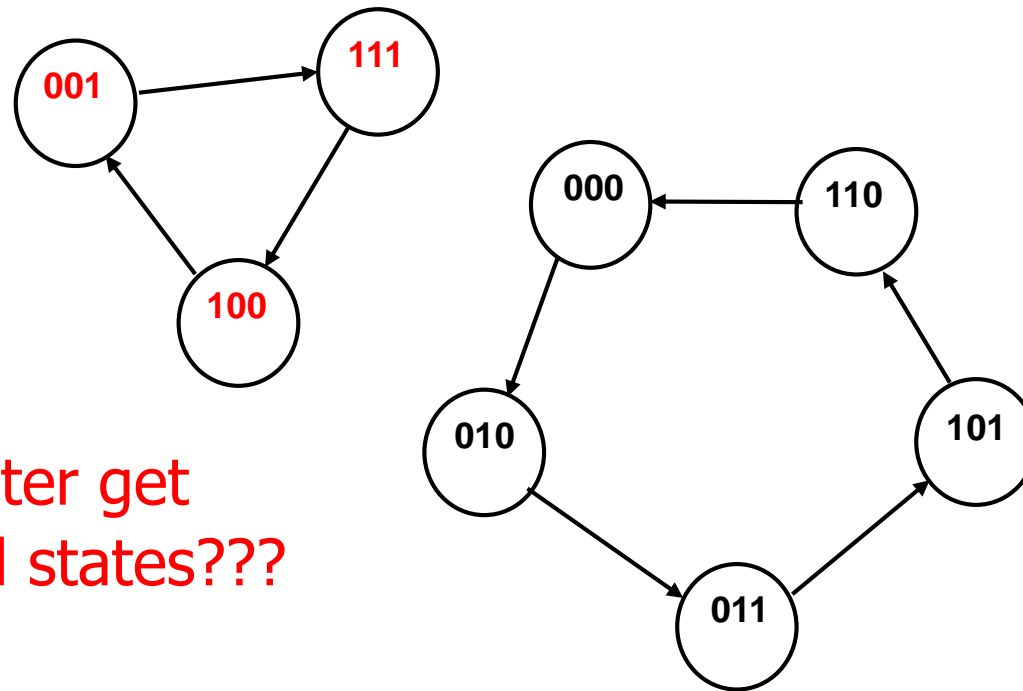- ❖ What if the counter starts in a 111 state?



Does our counter get stuck in invalid states???

5-state counter

- ❖ Back-annotate our design to check it

Fill in state transition table


Present State		Next State			
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0

$$A+ = BC'$$

$$B+ = B' + A'C'$$

$$C+ = A$$

Draw state diagram

 

The proper methodology is to **design** your counter to be self-starting