




ANSWER BOOKLET


Student: <u>Digital</u> Number <u>6</u>
Course: Department: _____ Number: _____
Division: _____ Instructor: _____
Date: _____
Day Month Year

For Instructor's Use

Question	Grade
1	
2	
3	
4	
5	
6	
7	
8	
9	
10	
11	
12	
Total	

 


Q Adder-subtractor is one circuit

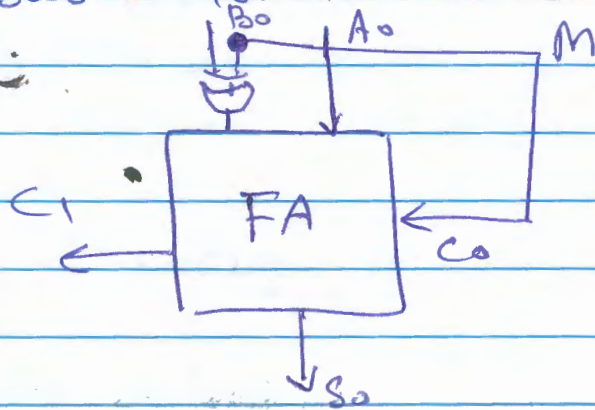

if $M = 0 \Rightarrow A_0 + B_0 + C_0$
 $= A_0 + B_0 + 0 = \text{normal addition}$

if $M = 1 \Rightarrow A_0 + \underbrace{B_0'} + 1$
 \downarrow 2's complement of B_0
i.e. $(A - B)$ \rightarrow subtraction

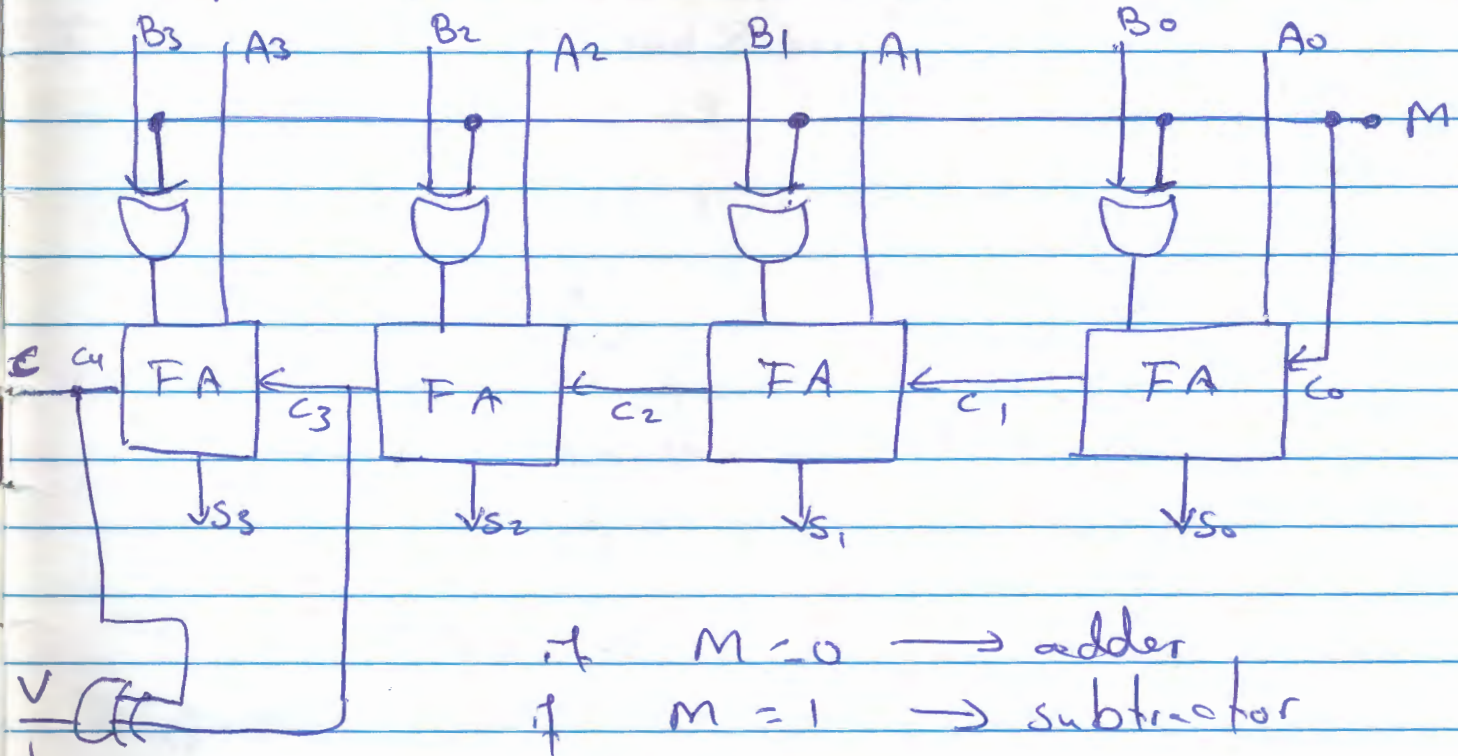\Rightarrow four bit adder-subtractor circuit



if $M = 0 \rightarrow$ adder
 if $M = 1 \rightarrow$ subtractor

overflow

⊗ Overflow

→ two numbers of n digits are added and the sum occupies $n+1$ digits, we say an overflow occurred.

- detection of overflow is important.

- for unsigned numbers: overflow is detected by the carry after the most significant bit

- in signed numbers, if one number is +ve and the second is -ve \Rightarrow no overflow.

- overflow may occur if ~~⊗~~ both numbers are +ve or -ve.

e.g. $70 + 80$ (in 8 bits register
(\leftarrow to -128 to $+127$))

sum = +150 (exceed 8 bits)

$$\begin{array}{r} 70 \quad \textcircled{0} \text{b} \\ 80 \\ \hline 150 \end{array} \quad \begin{array}{r} 01000110 \\ 01010000 \\ \hline 10010110 \end{array}$$

last 2 carries

$$\begin{array}{r} -70 \quad \textcircled{1} \text{b} \\ -80 \\ \hline \end{array} \quad \begin{array}{r} 1011010 \\ 10110000 \\ \hline 01101010 \end{array}$$

last 2 carries

⊗ note that the 9 bit answer will be correct (the last carry to be considered as the sign bit).

- an overflow condition can be detected by observing the carry into the sign bit position and the carry out of the sign bit position (if these are not equal, then an overflow

has occurred (use XOR gate for detection)

* Decimal Adder

- most ~~operant~~ arithmetic operations are in decimal.
→ numbers in binary coded form like BCD

- Decimal adder: requires a minimum of nine inputs and five outputs (since four bits are required to code each decimal digit and the circuit must have an input and output carry.).

* BCD Adder

→ $\underbrace{9}_{\text{first digit}} + \underbrace{9}_{\text{2nd digit}} + \underbrace{1}_{\text{carry of previous stage}} = 19$ (max number for the addition of 1 digit)

* Suppose we apply two BCD digits to a 4-bit binary adder (it is complex to make BCD adder because for 9 inputs we need 2^9 combinations!!).

⇒ The adder will form the sum in binary and produce a result that ranges from 0 through 19.


Decimal	Binary Sum					BCD Sum				
	K	Z ₈	Z ₄	Z ₂	Z ₁	c	S ₈	S ₄	S ₂	S ₁
0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	0	1
2	0	0	0	1	0	0	0	0	1	0
3	0	0	0	1	1	0	0	0	1	1
4	0	0	1	0	0	0	0	1	0	0
5	0	0	1	0	1	0	0	1	0	1
6	0	0	1	1	0	0	0	1	1	0
7	0	0	1	1	1	0	0	1	1	1
8	0	1	0	0	0	0	1	0	0	0
9	0	1	0	0	1	0	1	0	0	1
<hr/>										
10	0	1	0	1	0	1	0	0	0	0
11	0	1	0	1	1	1	0	0	0	1
12	0	1	1	0	0	1	0	0	1	0
13	0	1	1	0	1	1	0	0	1	1
14	0	1	1	1	0	1	0	0	0	0
15	0	1	1	1	1	1	0	1	0	1
16	1	0	0	0	0	1	0	1	1	0
17	1	0	0	0	1	1	0	1	1	1
18	1	0	0	1	0	1	1	0	0	0
19	1	0	0	1	1	1	1	0	0	1

⊛ Using K-map (with don't care conditions) we can find that

$$c = K + Z_8 Z_4 + Z_8 Z_2$$

⊛ we know that when $C = 1$ in BCD addition \Rightarrow we must add 6 (0110 in binary) (note: for subtraction we must subtract 6).

⊛ the final circuit

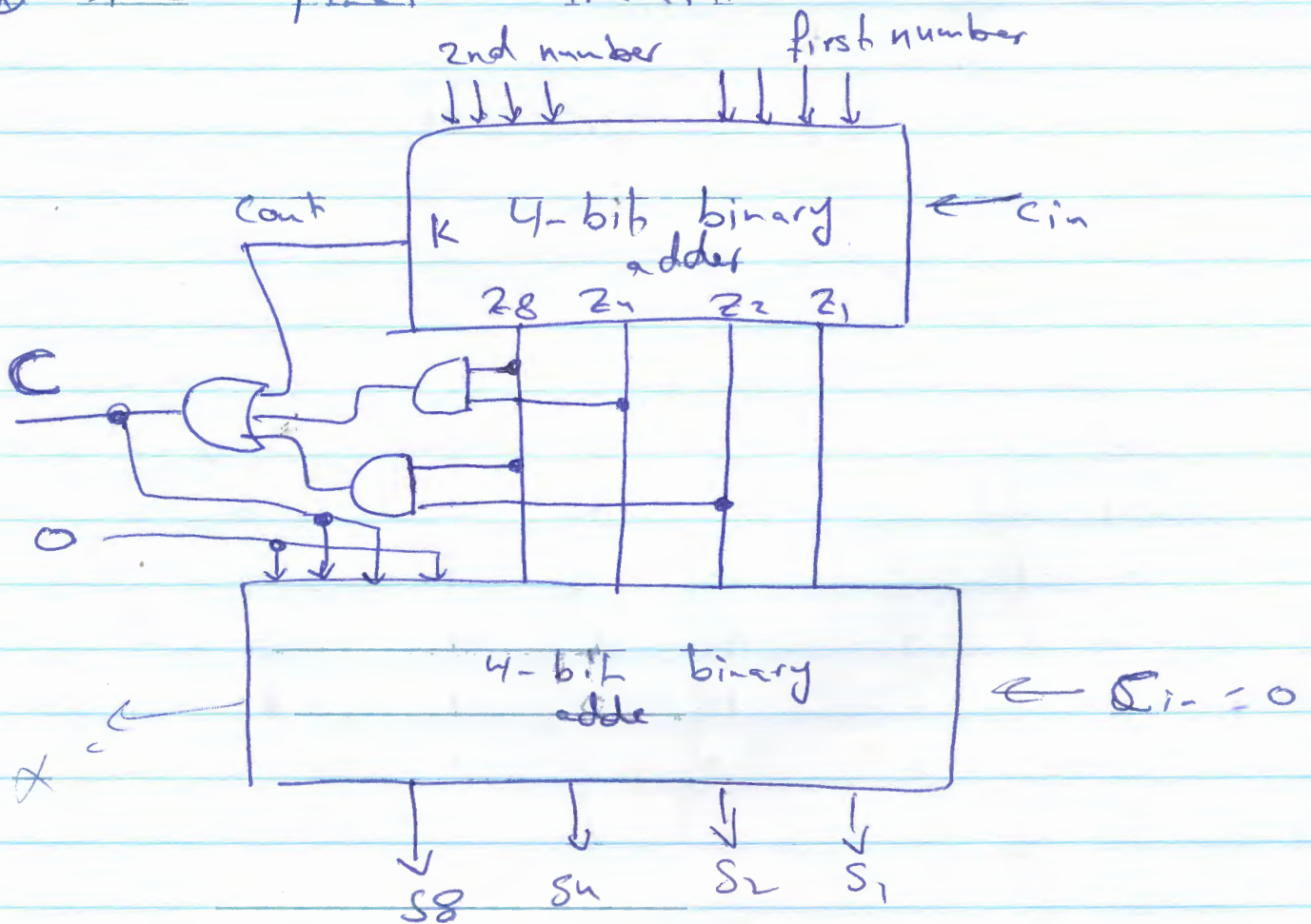


⊛ Binary Multiplier

- Example: multiplication of 2-bit numbers

A	B	result	
0	0	0	}
0	1	0	
1	0	0	
1	1	1	

⇒ and gate
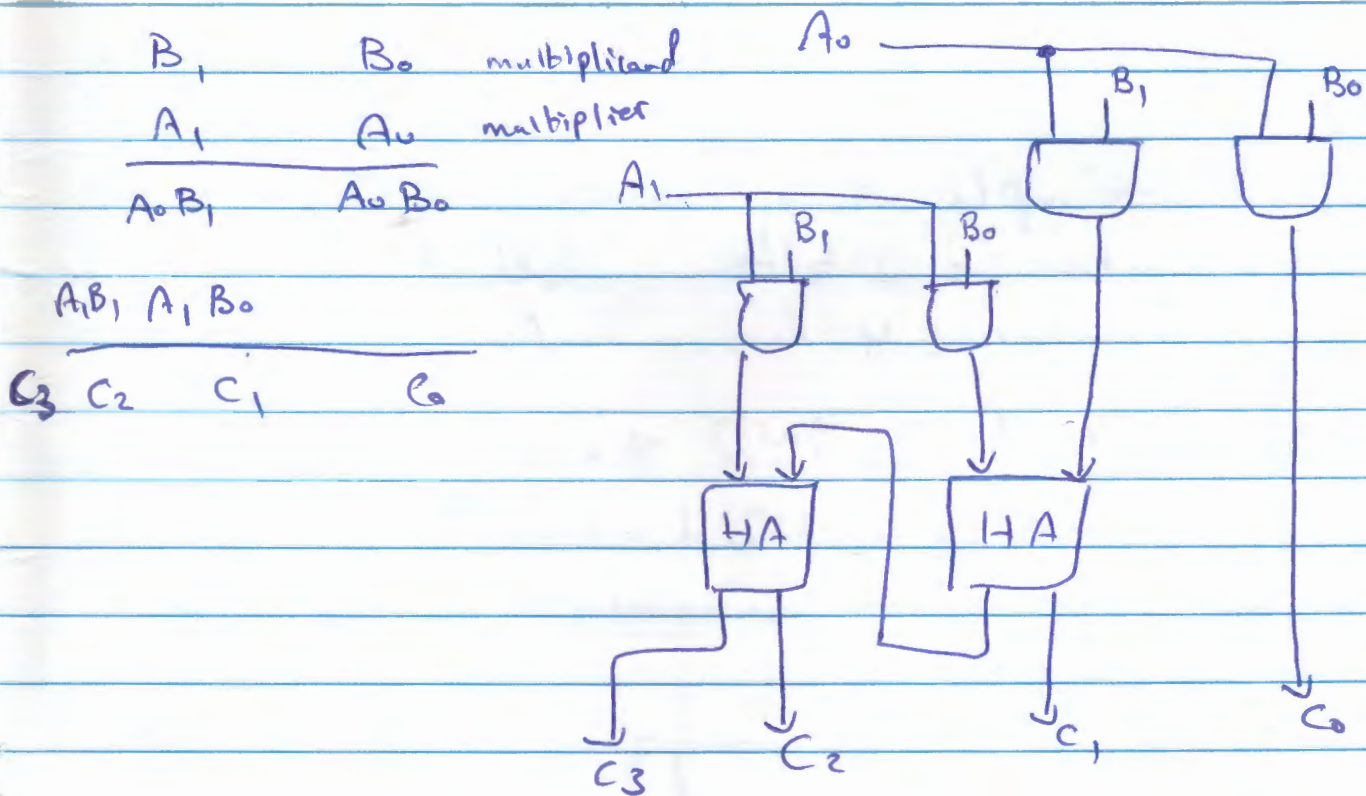
$$B_1 B_0 \times A_1 A_0 = C_3 C_2 C_1 C_0$$



- usually we need full adder instead of half adder (for more than 2-bits multiplications).

- In general, if $\left\{ \begin{array}{l} J \text{ multiplier} \\ k \text{ multiplicand} \end{array} \right.$ we want to multiply a number of J bits with another number of k bits \Rightarrow we need

- (1) $J \times k$ AND gates
- (2) $(J-1)$ k -bit adders (or $(k-1)$ J -bits)
- (3) the product will be $J+k$ bits

in the previous example (2-bit \times 2-bit)
 \Rightarrow 4 and gates, ~~2~~ 1 (2-bit adder),
the result is 4 digits

⊛ Another example

- first number = 3 bits ($J=3$)
- second number = 4 bits ($k=4$)

\Rightarrow we need 12 AND gates

2 (4-bit adder)

and we have an answer of up to 7 digits

(Figure 4-16 shows the circuit design).

④ Magnitude Comparator

~~3 outputs~~ (F_{A=B})

compare between 2 numbers A and B

on 3 outputs (A=B), (A>B), (A<B)

e.g. if A and B are 4-bit numbers

⇒ 8 inputs $2^8 = 256$ combinations of inputs !!!

use algorithmic procedure


$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

A ₃	B ₃	equal	
0	0	1	} XOR $x_i = A_i B_i + A_i' B_i'$
0	1	0	
1	0	0	
1	1	1	

A=B if all bits are equal
 
$$F_{A=B} = x_3 \cdot x_2 \cdot x_1 \cdot x_0$$



⊗ for $A \geq B$ or $B \geq A$

$$F(A \geq B) = A_3 B_3 + x_3 A_2 B_2'$$

$$+ x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$$

$$F(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1$$

$$+ x_3 x_2 x_1 A_0' B_0$$


(Figure 4-17 page 134 shows the circuit).

De
 ⑧ Encoders

- A decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines. If the n -bit coded information has unused combinations, the decoder may have fewer than 2^n outputs.

- decoder with n lines, m lines ($m \leq 2^n$) called n -to- m decoder

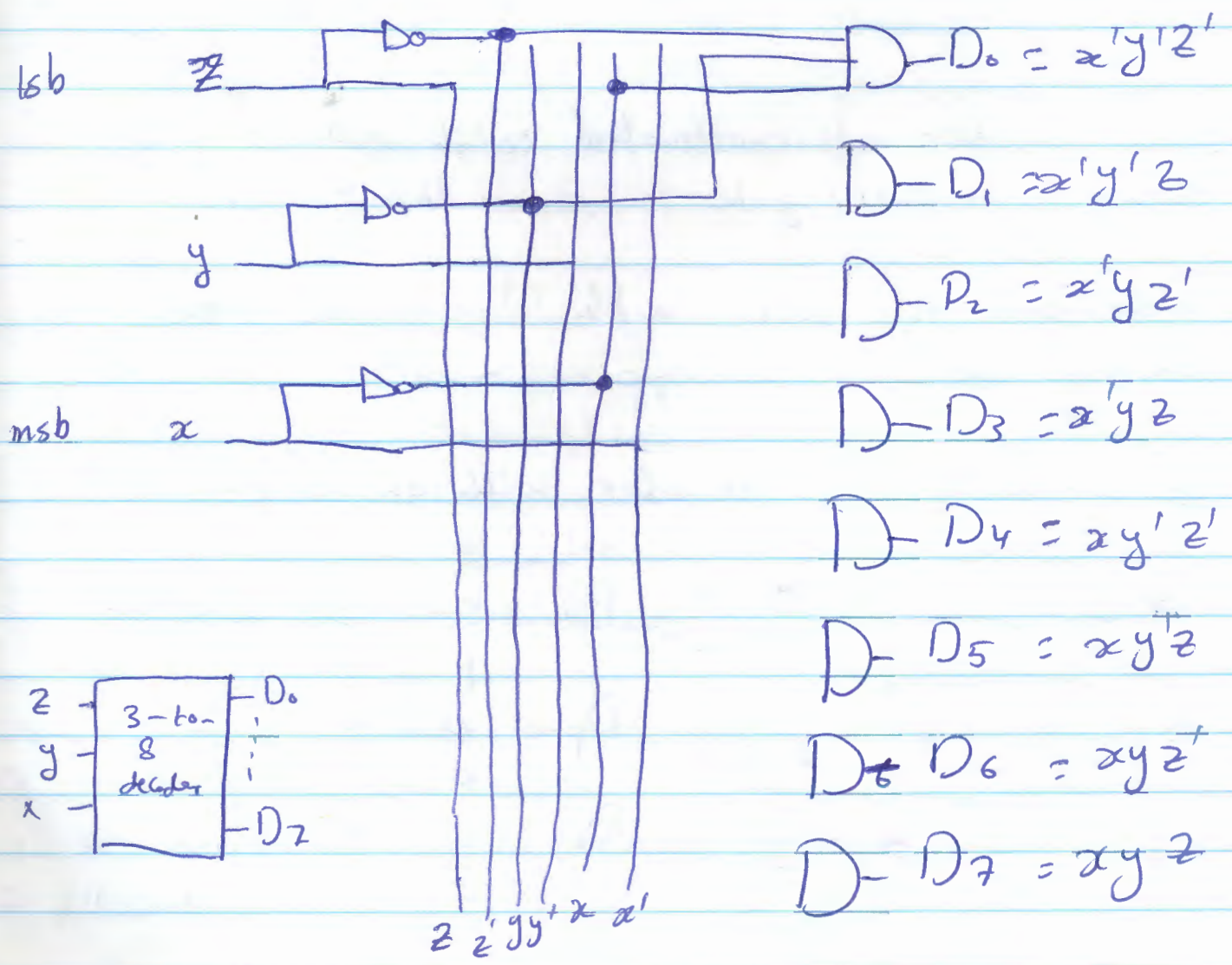e.g. 3-to-8 line decoder (application: binary to octal conversion)



(This decoder is implemented with "and" gates)


④ Truth table of the decoder (3-to-8)

inputs			outputs							
x	y	z	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

④ Some decoders are constructed with NAND gates, since a NAND gate is more commercial

- also one or more enable inputs are used to control the circuit operation

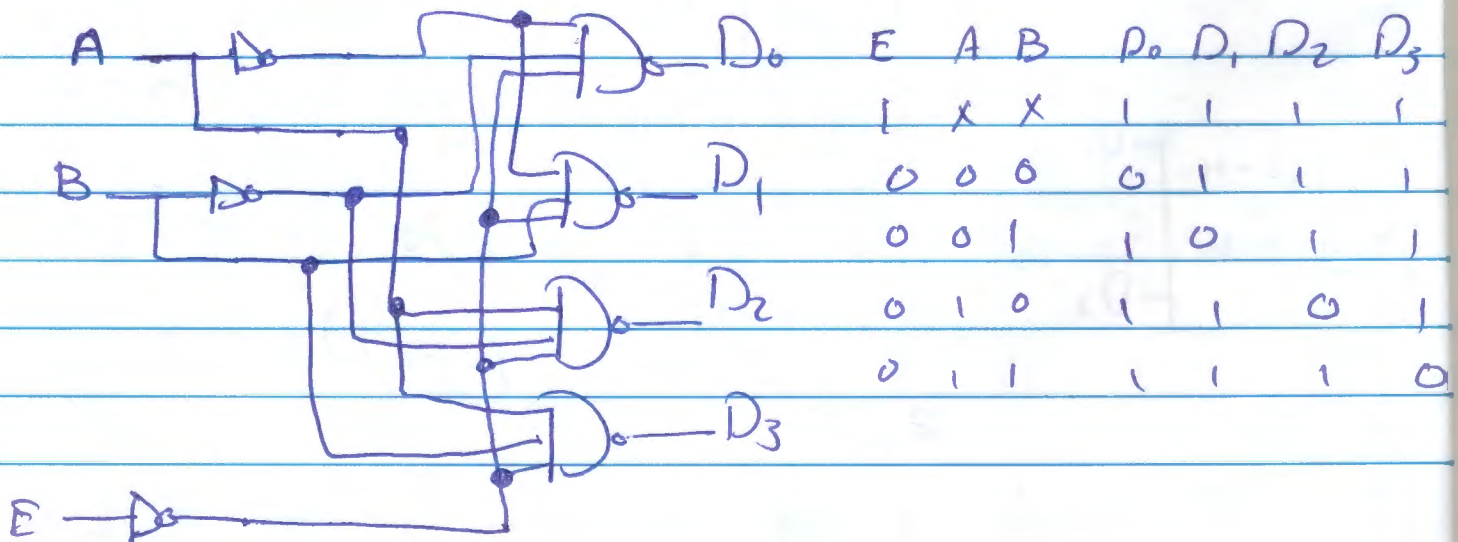
e.g. 2-to-4 line decoder with an enable input E



- may be more than 1 enable ~~to~~ used to control the decoder circuit.

- A decoder with enable input can function as a demultiplexer.

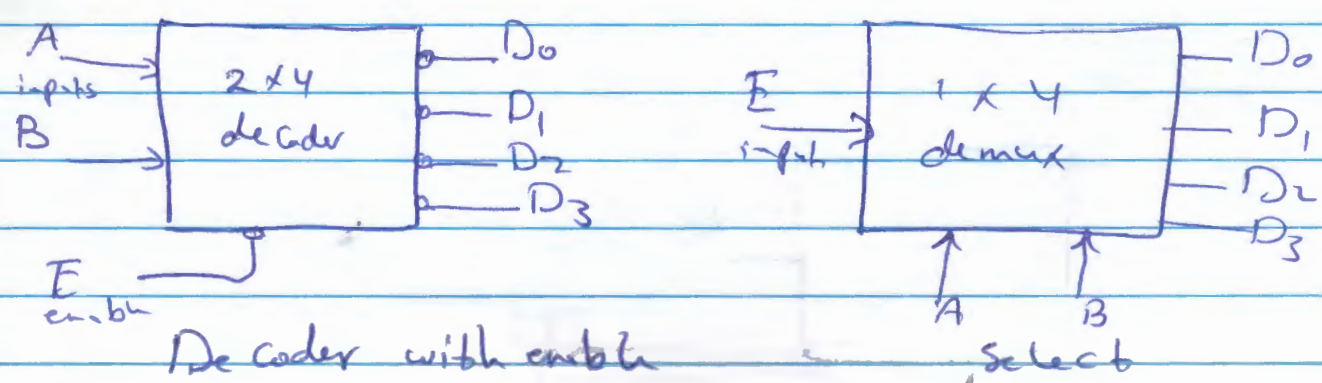- A demultiplexer is a circuit that receives information from a single line and directs it to one of 2^n possible output lines.




- E is taken as a data input line and A, B are taken as the selection inputs. \Rightarrow change from decoder to demultiplexer.

eg if $AB = 10 \rightarrow$ output D_2 will be same as the input E while all other outputs are maintained at 1.

- Because decoder and demultiplexer operations are obtained from the same circuit, a decoder with an enable input is referred to as a decoder/demultiplexer.

Decoder with enable inputs can be connected together to form a larger decoder circuit

 e.g. 3-to-8 line decoders (2 units) \Rightarrow
4-to-16 line decoder



if $w=0 \rightarrow$ top decoder is enabled, lower is disabled $w=0 \Rightarrow \underline{0000} - \underline{0111}$

when $w=1 \rightarrow$ lower decoder is enable
 $w=1 \Rightarrow 1000 - 1111$

④ Combinational Logic Implementation with decoder :-

- any combinational circuit with n -inputs and m outputs can be implemented with an n -to- 2^n line decoder and m OR gates


- Boolean function is expressed in sum of minterms (AND gates are internally implemented in decoder.)

Example full adder

$$S(x, y, z) = \sum (1, 2, 4, 7)$$

$$C(x, y, z) = \sum (3, 5, 6, 7)$$

 \Rightarrow we need to 3-to-8 line decoder because we have 3 inputs,



④ - if function has alot of minterms and F' has fewer number of minterms \rightarrow implement f' and use nor gate to get f

- if decoder is implemented with nand gates \Rightarrow use nand gates instead of OR.

⊕ Encoders

- inverse operation of a decoder.
- 2^n (or fewer) input lines and n output lines.
- example: octal-to-binary encoder :-

D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

problem:

- it is assumed that only one input has a value of 1 at any given time.

⊕ implementation directly from the truth table

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

⇒ the encoder can be implemented with 3 OR gates