

Yazan Yousef

Final Part 1

1170249

Q1:  $F(A, B, C, D) = BC'D' + A'C'D$

k map  $\Rightarrow$

AB \ CD	00	01	11	10
00	0	1	0	0
01	1	1	0	0
11	1	0	0	0
10	0	0	0	0

Hazard may occur when moving from:

$$\overline{ABCD} \Rightarrow 0100 \leftrightarrow 0101$$

The new added term:

$$\boxed{A'BC'}$$


New Function:

$$F(A, B, C, D) = \underbrace{A'BC'}_{\text{New}} + BC'D' + A'C'D$$

□



logic diagram:

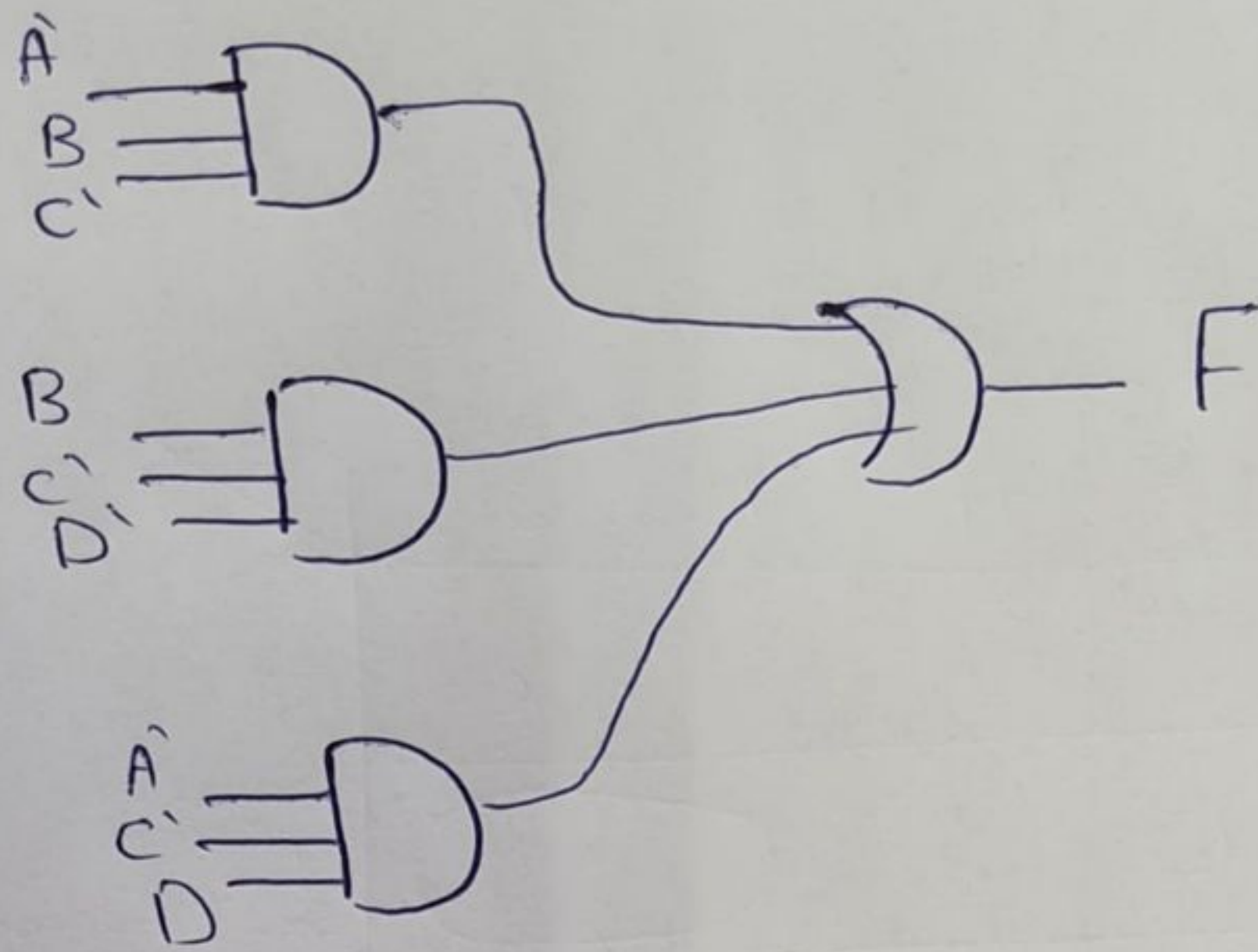




Q2:

Primitive Table:

	$x_1 x_2$			
	00	01	11	10
a	d, -	(a), 1	b, -	-1-
b	-1-	a, -	(b), 1	e, -
c	d, -	-1-	b, -	(c), 0
d	(d), 0	f, -	-1-	c, -
e	d, -	-1-	b, -	(e), 1
f	d, -	(f), 0	b, -	-1-


Implication Chart:

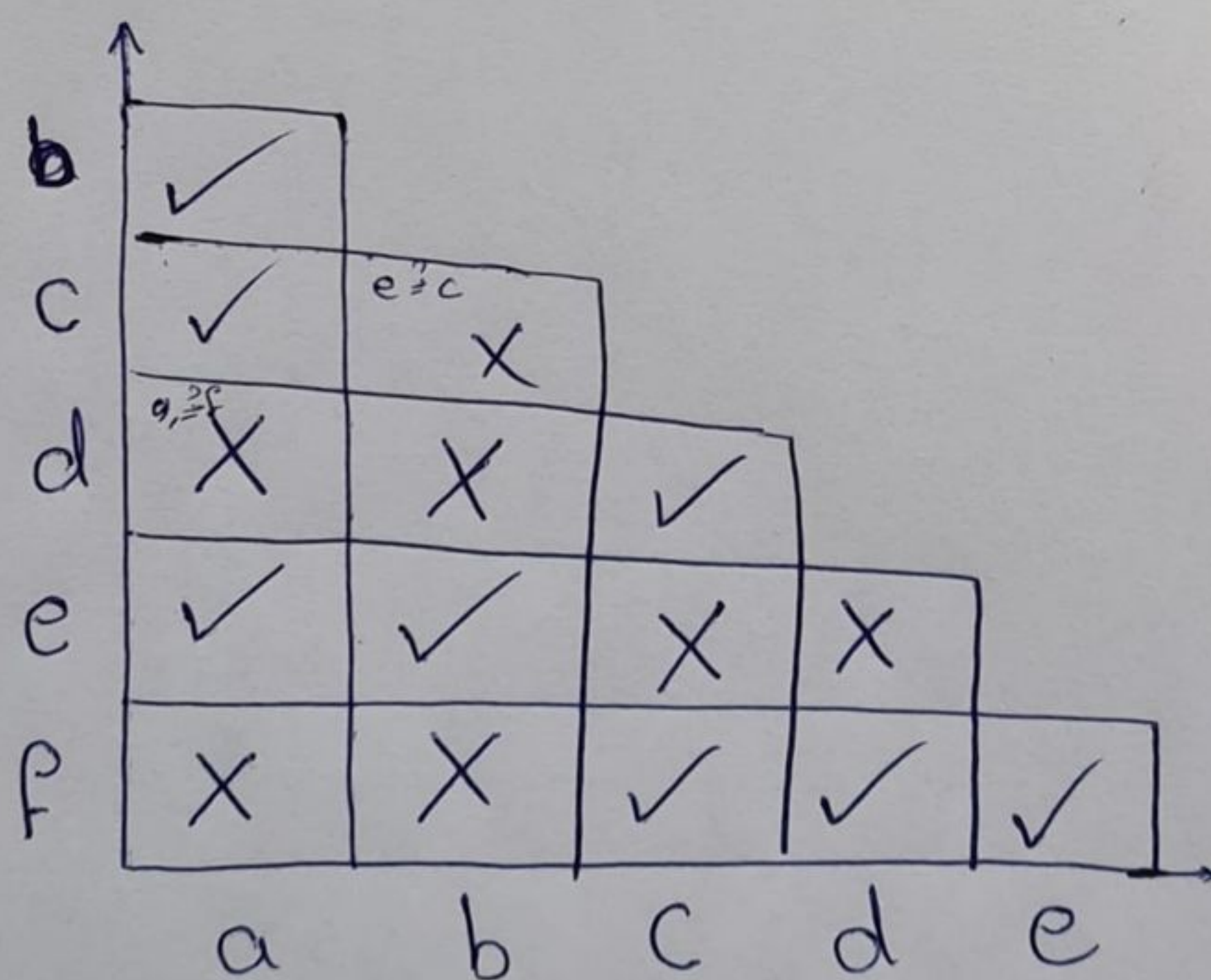

Compatible pairs:

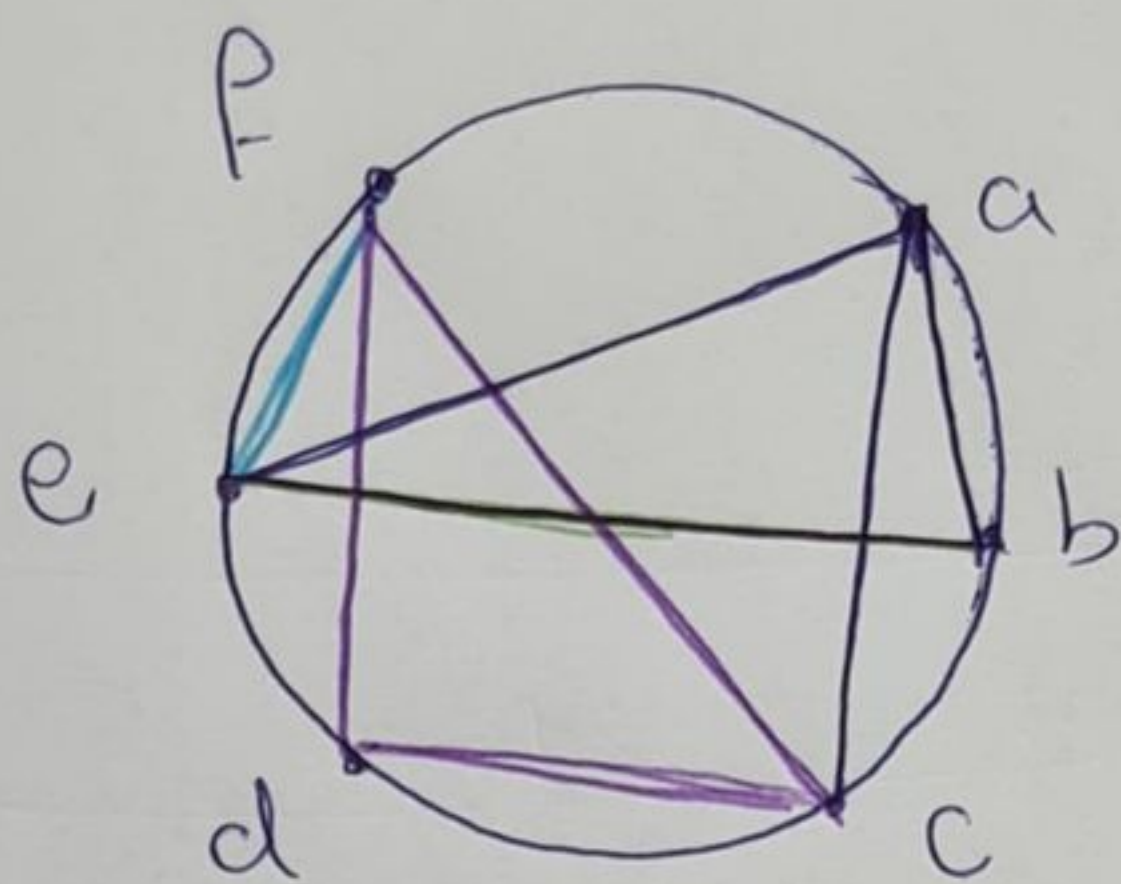- (a, b) (b, e) (c, d) (d, f) (e, f)  
 (a, c) (c, f)  
 (a, e)





① (a, b, e)

② (a, c) → included in ① & ③

③ (c, d, f)

④ (e, f) → included in ① & ③

$x_1 x_2$

		00	01	11	10
(a, b, e)	A	d, -	Ⓐ, 1	Ⓑ, 1	Ⓔ, 1
(c, d, f)	B	Ⓓ, 0	Ⓕ, 0	b, -	Ⓒ, 0

$x_1 x_2$

		00	01	11	10
A		B, -	Ⓐ, 1	Ⓐ, 1	Ⓐ, 1
B		Ⓑ, 0	Ⓕ, 0	A, -	Ⓒ, 0

The Final states = 2  
 state variables = 1 → y<sub>1</sub>

let A = 0 → B = 1

④



$x_1 \ x_2$

$y$		00	01	11	10
0		1, -	0, 1	0, 1	0, 1
1		1, 0	1, 0	0, -	1, 0

For output :

$y$		00	01	11	10
0		X	1	1	1
1		0	0	X	0

$$Q = y'$$

5

For  $Y$ :

$x_1, x_2$

$y$	00	01	11	10
0	1	0	0	0
1	1	1	0	1

$S$ :

$x_1, x_2$

$y$	00	01	11	10
0	1	0	0	0
1	X	X	0	X

$$S = x_1' x_2'$$

$R$

$x_1, x_2$

$y$	00	01	11	10
0	0	X	X	X
1	0	0	1	0

$$R = x_1 x_2$$



# SR-latch design

