 


Sajeda Mulla  
1160724  
sec:1

Final Exam  
Instructor: Dr. Abdellatif S. Abu-Issa

Q1) (21 points)

a) For the following state diagram:




- i) Is this Mealy or Moore Machine and Why? [2 points]
- ii) Write a VHDL behavioural code to describe the circuit presented by the state diagram. [12 points]

b) Show the detailed diagram for the 4-bit LUT for  $F = A'B + C'D + AD'$ . [7 points]

Q2) (21 points)

The following figure shows a Built-In Self-Test Circuit for a 2-bit magnitude comparator. The test vectors are generated using a 4-bit LFSR and the results are analysed using a 3-bit MISR as shown in the figure.

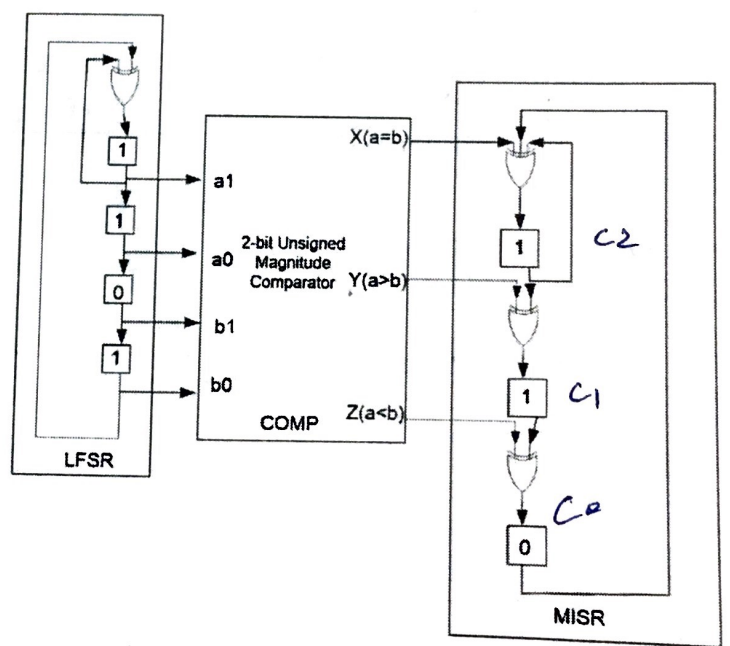- a) Show the first 8 test vectors generated by the LFSR. The first vector of the LFSR is "1101", you should show the next 7 test vectors. [6 points]
- b) What is the fault free signature of this system after we apply these test vectors? (Initial value of the MISR "110") [9 points]
- c) Assume that the output  $Z(a < b)$  is Sa0. What is the signature after we apply the same test vectors generated by the LFSR? (Initial value of MISR is "110") [6 points]



Q3) (38 points)

a) Assign output values to the don't care states in the following flow table in such a way as to avoid transient output pulses. [4 points]

	00	01	11	10
a	(a), 0	b, -	- , -	d, -
b	a, -	(b), 1	(b), 1	c, -
c	b, -	- , -	b, -	(c), 0
d	c, -	(d), 1	c, -	(d), 1

b) An asynchronous circuit with two inputs ( $x_1$  and  $x_2$ ) and one output ( $z$ ). When both inputs are zeros (i.e.  $x_1 = x_2 = 0$ ) then  $z = 0$ , and when both inputs are ones (i.e.  $x_1 = x_2 = 1$ ) then  $z = 1$ , otherwise the output will not change. Show the primitive follow table of this circuit.

[10 points]

c) Given the following primitive flow table, draw the reduced flow table after reducing the number of states. [12 points]

a	b	-	-	a	-
a	b	0	1	-	-
a	b	0	1	-	-
a	b	0	1	-	-
a	b	0	1	-	-
a	b	0	1	-	-

1, 2  
1, 6  
2, 3  
4, 5

1,2	a/0	a/0	b/0	c/0
2,3	a/0	b/0	b/0	d/1
1,6	a/0	b/0	d/1	c/0
4,5	a/1	b/1	d/1	d/1


		$x_1x_2$			
		00	01	11	10
1	①/0	2/0	-/-	6/0	
2	1/0	②/0	3/0	-/-	
3	-/-	2/0	③/0	4/-	
4	1/-	-/-	5/1	④/1	
5	-/-	2/-	⑤/1	4/1	
6	1/0	-/-	5/-	⑥/0	

d) i) Show the transition table for the following circuit. [3 points]

ii) Implement the same circuit using SR-latch. Use NAND gates only in your design. [9 points]

$S = (a'b)'$   
 $R = (a'b')'$

0	0	1	0
0	1	1	1

 

☺ Good Luck ☺