 



(3) PAL (Programmable Array Logic)



(*) FPGAs (Field Programmable Gate Array)


- FPGAs is usually based on a look-up table (LUT) approach.

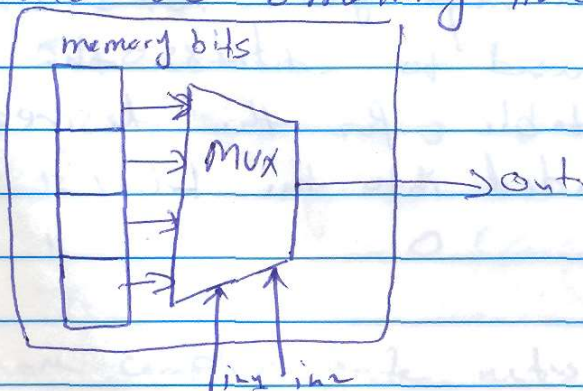For example a two input programmable logic gate would look something like this



In this example, the look up table (LUT) is a series of four memory bits. The two inputs (I_{in1} & I_{in2}) select one of the memory bits to be fed to the output.

 
For example if we want to implement an and gate using FPGA $c \leftarrow a \text{ AND } b$.



⊗ For example in ALTERA FLEX 10K, the gate ~~logic~~ logic is implemented using a (LUT). The LUT is a high speed 16×1 SRAM. \Rightarrow Four inputs are used to address the LUT memory. The truth table for the desired gate network is loaded into the LUT's SRAM during programming.

Ex:


$$F = A'B' + CD'$$

 

*

RAM Contents

Address				Data
A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

 

more complex gate networks can be feed to a D flip-flop and then to interconnections network