



ADVANCED DIGITAL SYSTEMS DESIGN

HW_1_

Prepared By:

*Anas Nimer

1180180

Instructor: Dr. Abdallatif Abuissa

Section: 1

Date: 25/9/2020

Table of Contents

Procedure:	3
1- Decoder 2x4 :	3
• Code.....	3
• Simulation:.....	3
2- Multiplexer 2x1:	4
• Code:.....	4
• Simulation:.....	4
3- All Circuit architecture:	5
• Code:.....	5
• Simulation:.....	5
4- All circuit behavioral:	6
• Code:.....	6
• Simulation:.....	6
Truth table , key_map and the equation :	7

❖ Procedure:


1- Decoder 2x4 :

- Code:

```
1 library ieee;
2 use ieee.std_logic_1164.all;
3
4 entity dec2x4 is
5     port(I:in std_logic_vector(1 downto 0);
6         En: in std_logic;
7         D:out std_logic_vector(3 downto 0));
8 end;
9
10 architecture Dec of dec2x4 is
11 begin
12     D(0)<= (not I(1) and not I(0)) and En ;
13     D(1)<= (not I(1) and I(0) ) and En ;
14     D(2)<= (I(1) and not I(0)) and En ;
15     D(3)<= (I(1) and I(0)) and En ;
16
17
18 end;
19
20
```

Fig_1_(code of decoder)

- Simulation:

 

Fig_2_(simulation of decoder)


2- Multiplexer 2x1:

- Code:

```
20
21 library ieee;
22 use ieee.std_logic_1164.all;
23 entity mux2x1 is
24     port(I: in std_logic_vector(0 to 1);
25         S: in std_logic;
26         Y: out std_logic);
27 end;
28
29 architecture mux of mux2x1 is
30 begin
31
32     Y<= (I(0) and not S)
33         or (I(1) and S) ;
34
35 end ;
36
```

Fig_3_(code of Multiplexer)

- Simulation:

 

Fig_4_(simulation of Multiplexer)


3- All Circuit architecture:

- Code:

```
36
37 library ieee;
38 use ieee.std_logic_1164.all;
39 entity allcircuit is
40     port(A,B,C,D: in std_logic;
41          F: out std_logic);
42 end;
43
44 architecture structural of allcircuit is
45     signal inputs: std_logic_vector(1 downto 0);
46     signal j: std_logic_vector (3 downto 0);
47     signal l: std_logic_vector( 0 to 1);
48
49     begin
50         inputs<= A & B ;
51         l(0)<= j(0) xor j(1);
52         l(1)<= j(2) xnor j(3);
53
54         dec: entity work.dec2x4(Dec) port map(inputs,C,j);
55         max: entity work.mux2x1(mux) port map(l,D,F);
56     end;
57
58
```

Fig_5_(code of all circuit architecture)

- Simulation:

 

Fig_5_(simulation of all circuit architecture)


4- All circuit behavioral:

- Code:

```
57  
58 architecture behavioral of allcircuit is  
59 begin  
60     F<= (not C and D) or (not A and C);  
61 end;  
62  
63  
64
```

Fig_6_(code of all circuit behavioral)

- Simulation:

 

Fig_6_(simulation of all circuit behavioral)

❖ Truth table , key map and the equation :

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

By the truth table i make key map:

Map				
	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A.B}$	0	1	1	1
$\overline{A}.B$	0	1	1	1
$A.\overline{B}$	0	1	0	0
$A.B$	0	1	0	0

And hence the equation that we want is : $F = C' . D + A' . C$