



ADVANCED DIGITAL SYSTEMS DESIGN

HW_2_

Prepared By:

*Anas Nimer

1180180

Instructor: Dr. Abdallatif Abuissa

Section: 1

Date: 10/10/2020

Table of Contents

❖ Procedure:	3
1- mux 4x1 :	3
• Code.....	3
• Simulation:.....	3
2- Full adder:	4
• Code:.....	4
• Simulation:.....	4
3- Comparator:	5
• Code:.....	5
• Simulation:.....	5
4- All circuit structural:	6
• Code:.....	6
• Simulation:.....	6
5- All circuit behavioral:	7
• Code:.....	7
• Simulation:.....	7
6- All circuit test:	8
• Code:.....	8
• Simulation:.....	8
❖ Truth table Y_S (output of mux 1) , key_map and the equation :	9
• Truth table:	9
• key_map:	10
• equation that we want is :	10
❖ Truth table Y_cout (output of mux 2) , key_map and the equation :	11
• Truth table:	11
• key_map:	12
• equation that we want is :	12

❖ Procedure:


1- mux 4x1 :

- Code:

```
1
2
3 library ieee;
4 use ieee.std_logic_1164.all;
5 entity mux4x1 is
6     port(D: in std_logic_vector(3 downto 0);
7          S: in std_logic_vector(0 to 1);
8          Y: out std_logic);
9 end;
10
11 |
12 architecture mux of mux4x1 is
13 begin
14
15     Y<= (D(0) and not S(0) and not S(1))
16     or (D(1) and S(0) and not S(1))
17     or (D(2) and not S(0) and S(1))
18     or (D(3) and S(0) and S(1)) ;
19
20 end ;
21
```

Fig_1_(code of mux)

- Simulation:

 

Fig_2_(simulation of decoder)


2- Full adder:

- Code:

```
24
25 library IEEE;
26 use IEEE.STD_LOGIC_1164.ALL;
27 entity full_adder is
28     Port ( A : in STD_LOGIC;
29             B : in STD_LOGIC;
30             Cin : in STD_LOGIC;
31             S : out STD_LOGIC;
32             Cout : out STD_LOGIC);
33 end full_adder;
34
35 architecture full of full_adder is
36 begin
37
38     S <= A XOR B XOR Cin ;
39     Cout <= (A AND B) OR (Cin AND A) OR (Cin AND B);
40 end;
41
42
```

Fig_3_(code of Full adder)

- Simulation:

 

Fig_4_(simulation of Full adder)


3- Comparator:

- Code:

```
72
43 library IEEE;
44 use IEEE.STD_LOGIC_1164.ALL;
45
46 entity comp is
47     port(A : in STD_LOGIC;
48          B : in STD_LOGIC;
49          Y : out STD_LOGIC);
50 end comp;
51
52 architecture compe of comp is
53 begin
54
55     Y<=(A and not B);
56
57 end;
```

Fig_5_(code of comparator)

- Simulation:

 

Fig_6_(simulation of comparator)


4- All circuit structural:

- Code:

```
60 library ieee;
61 use ieee.std_logic_1164.all;
62
63 entity allcircuit1 is
64     port(A,B: in std_logic;
65          S: in std_logic_vector(0 to 1);
66          Y_S: out std_logic;
67          Y_Cout: out std_logic);
68 end;
69
70 architecture structural1 of allcircuit1 is
71 signal D1: std_logic_vector(3 downto 0);
72 signal D2: std_logic_vector(3 downto 0);
73
74 begin
75
76     D1(2)<= A and B;
77     D1(3)<= A or B;
78     D1(1)<='0';
79     D2(2)<='0';
80     D2(3)<='0';
81
82     full: entity work.full_adder(full) port map(A,B,'0',D1(0),D2(0));
83     comp: entity work.comp(compe) port map(A,B,D2(1));
84     mux1: entity work.mux4x1(mux) port map(D1,S,Y_S);
85     mux2: entity work.mux4x1(mux) port map(D2,S,Y_Cout);
86 end;
87
```

Fig_7_(code of all circuit structural)

- Simulation:

 

Fig_8_(simulation of all circuit structural)


5- All circuit behavioral:

- Code:

```
90 architecture behavioral of allcircuit1 is
91 begin
92     Y_S<= (S(1) and A and B) or (S(0) and S(1) and B) or (S(0) and S(1) and A) or (not S(0) and not S(1) and not A and B) or
93     (not S(0) and not S(1) and A and not B);
94     Y_Cout<= (not S(0) and not S(1) and A and B) or (S(0) and not S(1) and A and not B);
95
96 end;
97
```

Fig_9_(code of all circuit behavioral)

- Simulation:

 

Fig_10_(simulation of all circuit behavioral)


6- All circuit test:

- Code:

```
99 library ieee;
100 use ieee.std_logic_1164.all;
101
102 entity allcircuit1_Test is
103 end;
104
105 architecture Test of allcircuit1_Test is
106 signal A,B: std_logic:='0';
107 signal S: std_logic_vector(0 to 1):= "00";
108 signal Y_S , Y_Cout: std_logic;
109
110 begin
111
112 Y_S<= (S(1) and A and B) or (S(0) and S(1) and B) or (S(0) and S(1) and A) or (not S(0) and not S(1) and not A and B) or
113 (not S(0) and not S(1) and A and not B);
114 |
115 Y_Cout<= (not S(0) and not S(1) and A and B) or (S(0) and not S(1) and A and not B);
116
117 S(0) <= not S(0) after 200 ns;
118 S(1) <= not S(1) after 100 ns;
119 A<= not A after 50 ns;
120 B<= not B after 25 ns;
121
122
123
124 end;
```

Fig_11_(code of all circuit test)

- Simulation:

 

Fig_12_(simulation of all circuit test)

❖ Truth table Y_S (output of mux 1) , key_map and the equation :

- Truth table:

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

- key_map:

Map					Map Layout				
	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	CD		$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	CD
$\bar{A}\bar{B}$	0	1	0	1		0	1	3	2
$\bar{A}B$	0	0	1	0		4	5	7	6
$A\bar{B}$	0	1	1	1		12	13	15	14
AB	0	0	0	0		8	9	11	10

- equation that we want is :

$$Y_S = (S(1) \cdot A \cdot B) + (S(0) \cdot S(1) \cdot B) + (S(0) \cdot S(1) \cdot A) + (S(0)' \cdot S(1)' \cdot A' \cdot B) + (S(0)' \cdot S(1)' \cdot A \cdot B')$$

❖ Truth table Y_cout (output of mux 2) , key_map and the equation :

- Truth table:

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

- key_map:

Map					Map Layout				
	$\overline{C}\overline{D}$	$\overline{C}D$	$C\overline{D}$	$C.D$		$\overline{C}\overline{D}$	$\overline{C}D$	$C\overline{D}$	$C.D$
$\overline{A}\overline{B}$	0	0	1	0		0	1	3	2
$\overline{A}.B$	0	0	0	0		4	5	7	6
$A.\overline{B}$	0	0	0	0		12	13	15	14
$A.B$	0	0	0	1		8	9	11	10

- equation that we want is :

$$Y_{Cout} = (S(0)' \cdot S(1)' \cdot A \cdot B) + (S(0) \cdot S(1)' \cdot A \cdot B')$$