

$$2F = \frac{5000}{1} = 5000$$

$$2 \pi LE = \frac{7}{3} \times 2 \times \frac{5}{3} \times \frac{4}{3} \times 1 \times 1 = \frac{280}{27} \Rightarrow 10.37$$

$$2 \pi FB = 3 \times 2 = 6$$

$$a \text{ - } \pi LE \pi FB \times F = \frac{280}{27} \times 6 \times 5000 = 311,111.111$$

$$b \text{ - } \sqrt[6]{311,111.11} = 8.23163$$

$$c \text{ - } \text{Stage } f: 8.23163 = \frac{4}{3} \times \frac{5000}{f} \Rightarrow f = 809.294 \text{ f}$$

$$2 \times b \text{ - } e: 8.23163 = 1. \frac{809.294}{e} \Rightarrow e = 98.315 \text{ f}$$


$$d: 8.23163 = \frac{5}{3} \times \frac{98.315}{d} \Rightarrow d = 19.891 \text{ f}$$

$$c: 8.23163 = 2 \times \frac{19.891}{c} \Rightarrow c = 4.833 \text{ f}$$

$$b: 8.23163 = \frac{7}{3} \times 2 \times \frac{4.833}{b} \Rightarrow 2.74 \text{ f}$$

$$a: 8.23163 = 1 \times 3 \times \frac{2.74}{a} \Rightarrow a = .998 \checkmark$$

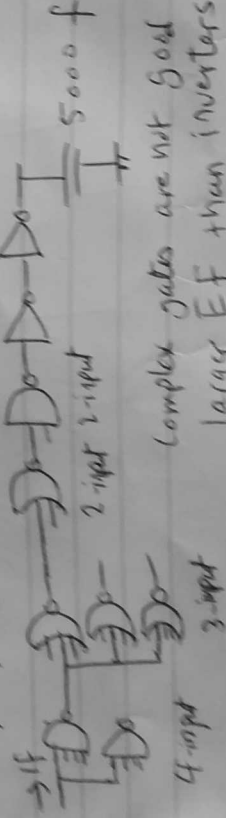yes, highest LE to the beginning of the chain




Complex gates are not good drivers, they need larger EF than inverters.

	N_{11}	N_{12}	N_{21}	N_{22}
1) N_{11}	4	2	3	2
2) N_{12}	5	3	4	2
3) N_{21}	3	4	5	3
4) N_{22}	2	3	4	5
TOTAL	14	12	15	12

Best Choice

30

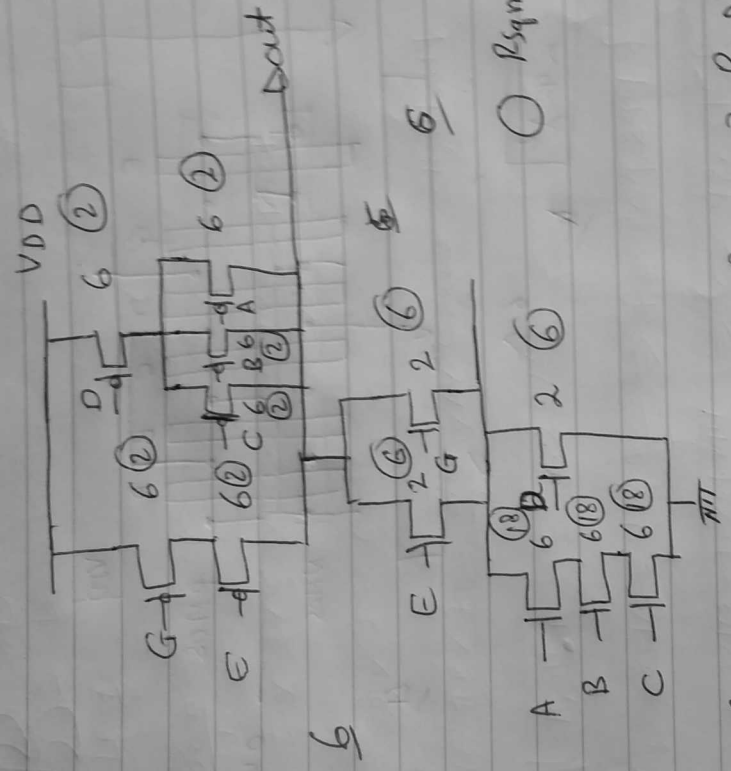Q2) $F = (A \cdot B \cdot C + D) \cdot (E + G)$



$R_{syn P} = 3 R_{syn}$


$R_{syn n} = 3 R_{syn}$

$LE_A = \frac{6+6}{4} = 3$
 $LE_B = \frac{6+6}{4} = 3$
 $LE_G = \frac{2+6}{4} = 2$


$LE_A = (18+2)/4 = 5$
 $LE_B = (18+2)/4 = 5$
 $LE_G = (16+2)/4 = 2$

Euler path: {E G D C B A S}

Euler bath { E G D C B A } 3

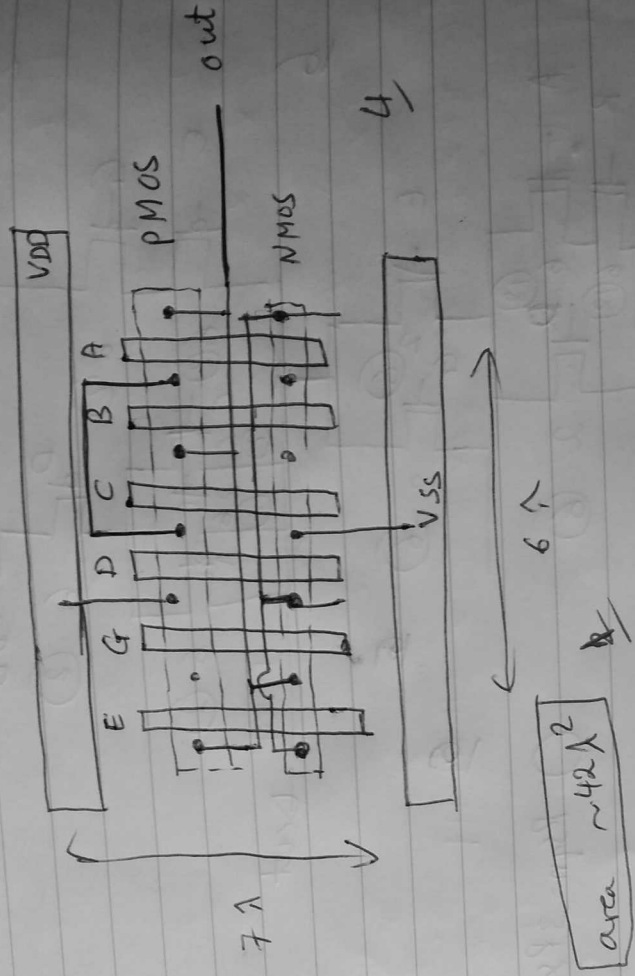

Q3) 25



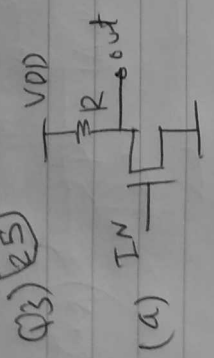


$R = 4 R_{NMOS}$


$V_{TN} = \frac{V_{DD}}{4}$

$0 < V_{in} < \frac{V_{DD}}{4} \rightarrow \text{out} = V_{DD}$

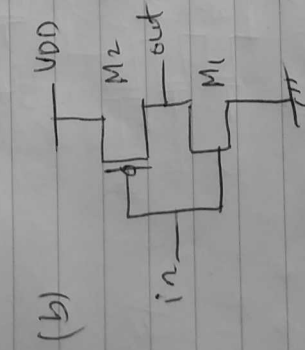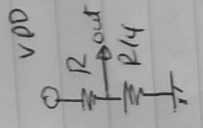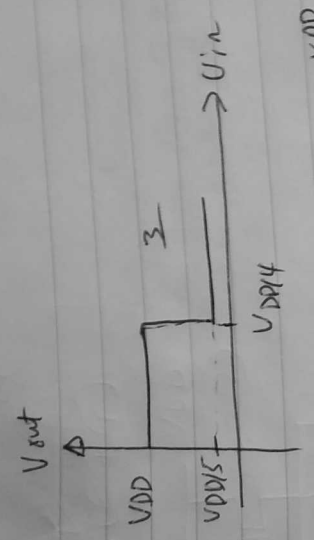$V_{in} > \frac{V_{DD}}{4} \rightarrow \text{out} = \frac{2/4 V_{DD}}{1+4} = \frac{V_{DD}}{5}$




$V_{TN} = \frac{V_{DD}}{4}$
 $|V_{TP}| = \frac{V_{DD}}{3}$
 $\beta_{PMOS} = 2\beta_{NMOS}$

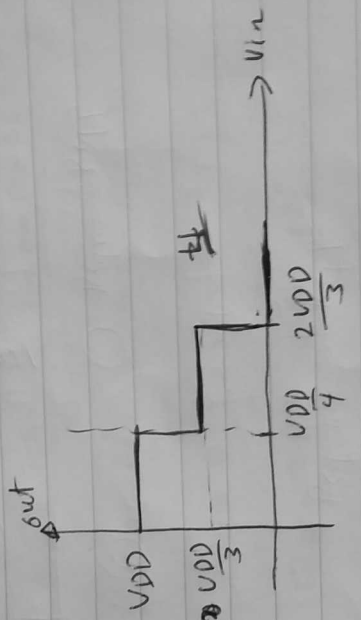

$V_{in} \leq \frac{V_{DD}}{4}$; M_1 is off; M_2 is on $\Rightarrow \text{out} = V_{DD}$


$\frac{V_{DD}}{4} < V_{in} < \frac{2V_{DD}}{3}$; M_1 is on; M_2 is on $\Rightarrow \text{out} = \frac{V_{DD}}{3}$

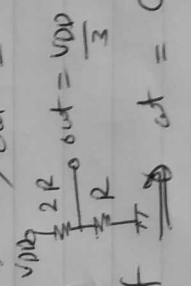$V_{in} > \frac{2V_{DD}}{3}$; M_1 is on; M_2 is off $\Rightarrow \text{out} = 0$



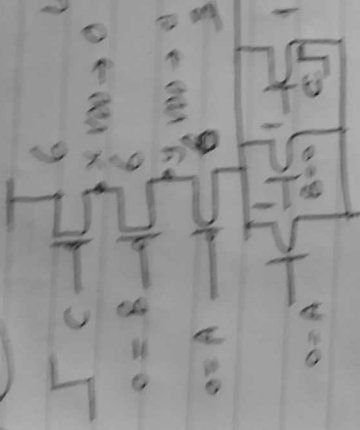Q4) (28)

What are delay when
 $A=B=0$ & goes from 0 to 1
 single NMOS has to drive all the stack 5




RC model:

$$R_p = \frac{30 \text{ k}\Omega}{\frac{D}{6 \mu\text{m}}} \times 100 \text{ nm} = 1.5 \text{ k}\Omega$$

$$R_n = \frac{15 \text{ k}\Omega}{\frac{D}{1 \mu\text{m}}} \times 100 \text{ nm} = 1.5 \text{ k}\Omega$$

$$C_{DP} = \frac{2 \text{ fF}}{\mu\text{m}} \times 6 \mu\text{m} = 12 \text{ fF}$$

$$C_{DN} = \frac{2 \text{ fF}}{\mu\text{m}} \times 1 \mu\text{m} = 2 \text{ fF}$$
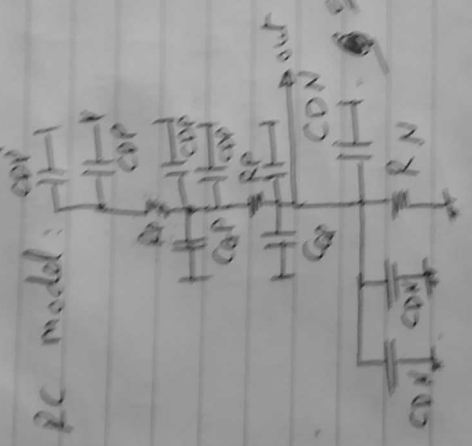
$$C_{CP} = \frac{2 \text{ fF}}{\mu\text{m}} \times 6 = 12 \text{ fF}$$


$$t_p = \ln(2) \cdot R_n (3C_{DN} + 5C_{CP} + 2C_{DP})$$

$$= \ln(2) \times 1.5 \text{ k}\Omega (3 \times 2 + 5 \times 12 + 2 \times 12)$$

$$= \ln(2) \times 1.5 \text{ k}\Omega \times 90 \text{ f} = 93.57 \text{ pf}$$

