 


The Wire




Schematic




Physical

Wire Models

 

All-inclusive model

 


Capacitance-only

Impact of Interconnect Parasitics

- Interconnect and its parasitics can affect all of the metrics we care about
 - Cost, reliability, performance, power consumption

- Parasitics associated with interconnect:
 - Capacitance
 - Resistance
 - Inductance


Interconnect Length Distribution

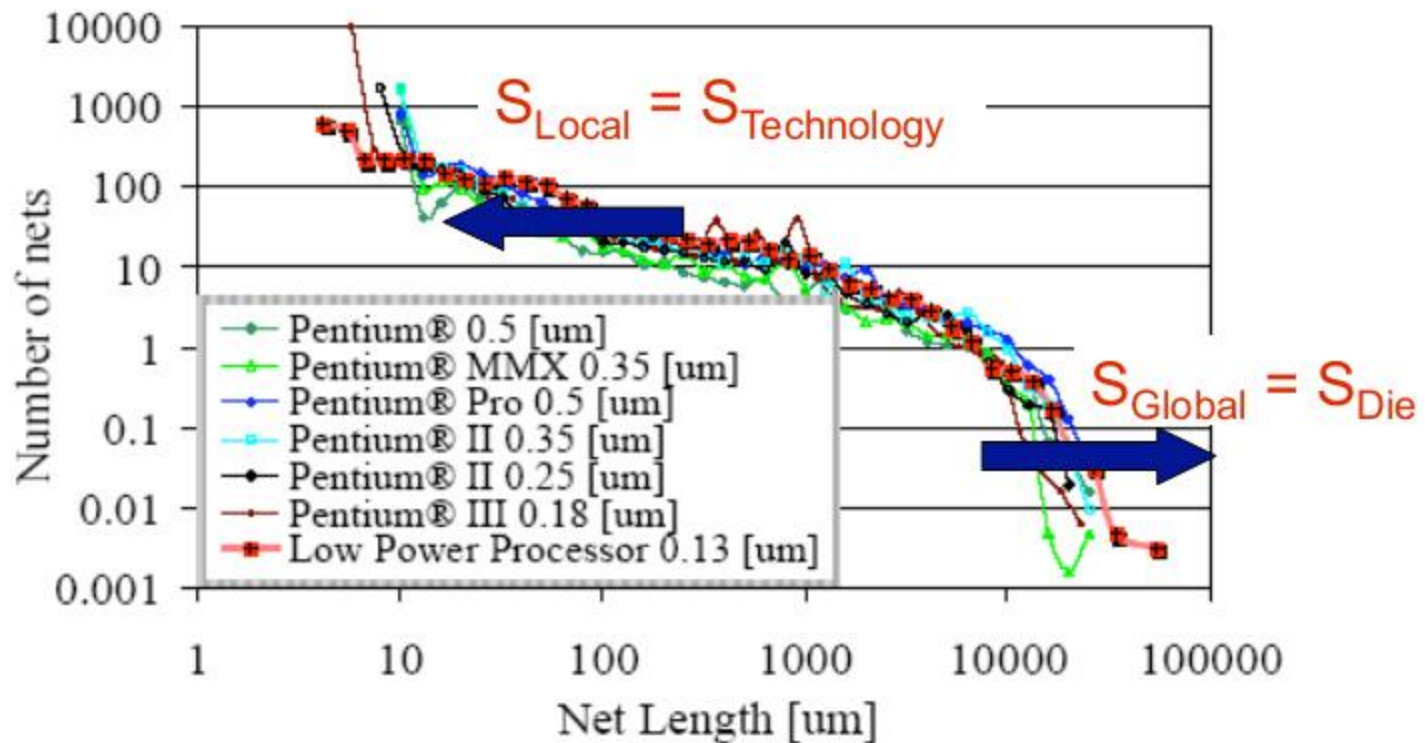

From Magen et al., "Interconnect Power Dissipation in a Microprocessor"

Buses, clock wire, global communication --- do not scale with technology

Capacitance: The Parallel Plate Model

 


$$C_{int} = \frac{\epsilon_{di}}{t_{di}} WL$$

Permittivity


Material	ϵ_r
Free space	1
Aerogels	~1.5
Polyimides (organic)	3-4
Silicon dioxide	3.9
Glass-epoxy (PC board)	5
Silicon Nitride (Si_3N_4)	7.5
Alumina (package)	9.5
Silicon	11.7

Fringing Capacitance
 
$$C_{\text{wire}} = C_{pp} + C_{\text{fringe}} = \frac{w\epsilon_{di}}{t_{di}} + \frac{2\pi\epsilon_{di}}{\log(t_{di}/H)}$$



(a)

 


(b)

$$C = C_{pp} \cdot W \cdot L + 2C_{\text{fringe}} L$$


Fringing versus Parallel Plate

Fringe is dominant



 


(from [Bakoglu89])


Interwire Capacitance

 

Coupling Capacitance and Delay

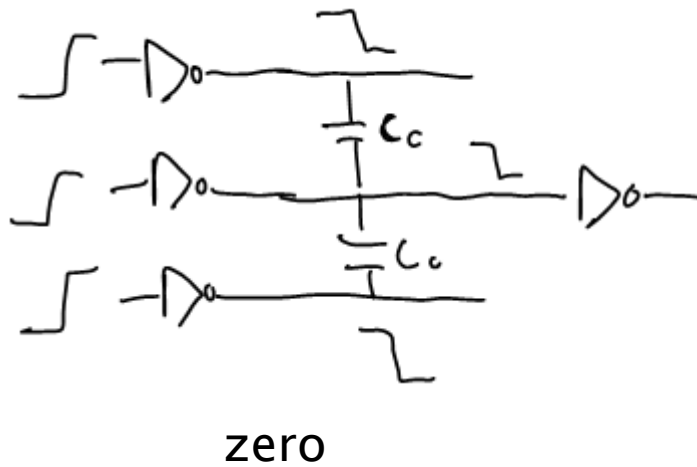  

Impact of Interwire Capacitance

 

(from [Bakoglu89])


Wiring Capacitances (0.25 μm CMOS)

Bottom plate

	Field	Active	Poly	Al1	Al2	Al3	Al4
Poly	88	$9\text{fF}/\mu\text{m}^2$					
	54	$9\text{fF}/\mu\text{m}$					
Al1	30	41	57				
	40	47	54				
Al2	13	15	17	36			
	25	27	29	45			
Al3	8.9	9.4	10	15	41		
	18	19	20	27	49		
Al4	6.5	6.8	7	8.9	15	35	
	14	15	15	18	27	45	
Al5	5.2	5.4	5.4	6.6	9.1	14	38
	12	12	12	14	19	27	52

Top plate

Wire Resistance

 


Interconnect Resistance

Material	ρ ($\Omega\text{-m}$)
Silver (Ag)	1.6×10^{-8}
Copper (Cu)	1.7×10^{-8}
Gold (Au)	2.2×10^{-8}
Aluminum (Al)	2.7×10^{-8}
Tungsten (W)	5.5×10^{-8}

Dealing with Resistance

- ❑ **Use Better Interconnect Materials**
 - e.g. copper, silicides
- ❑ **More Interconnect Layers**
 - reduce average wire-length
- ❑ **Selective Technology Scaling**

Polycide Gate MOSFET

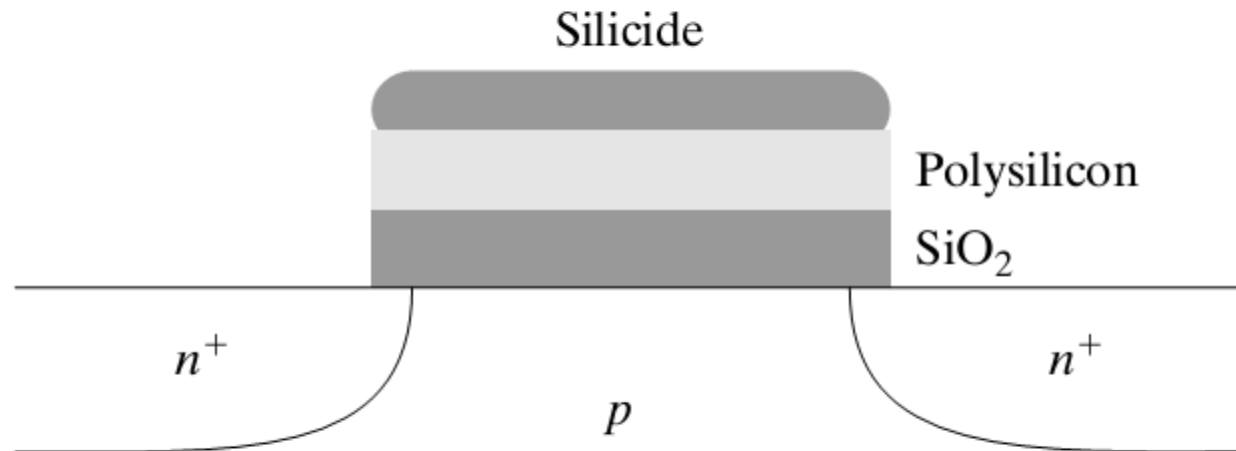



Silicides: WSi₂, TiSi₂, PtSi₂ and TaSi

Conductivity: 8-10 times better than Poly


Sheet Resistance

Material	Sheet Resistance (Ω/\square)
n- or p-well diffusion	1000 – 1500
n^+ , p^+ diffusion	50 – 150
n^+ , p^+ diffusion with silicide	3 – 5
n^+ , p^+ polysilicon	150 – 200
n^+ , p^+ polysilicon with silicide	4 – 5
Aluminum	0.05 – 0.1

The Lumped Model

  


The Distributed RC-line

 

- Analysis method:
 - Break the wire up into segments of length dx
 - Each segment has resistance ($r dx$) and capacitance ($c dx$)




The Distributed RC-line

 

$$I_c = c\Delta L \frac{\partial V}{\partial t} = \frac{(V_{i-1} - V_i) - (V_i - V_{i+1})}{r\Delta L} \longrightarrow \boxed{rc \frac{\partial V}{\partial t} = \frac{\partial^2 V}{\partial x^2}}$$

$$\boxed{\tau = \frac{L^2}{2} rc}$$

The Distributed RC Line

   


The diffusion equation


$$rc \frac{\partial V}{\partial t} = \frac{\partial^2 V}{\partial x^2}$$

$$\tau(V_{out}) = \frac{rc L^2}{2}$$

 Step-response of RC wire as a function of time and space




Simplified Model: Elmore Delay

 


- “Elmore delay”: approximation for delay of arbitrary (complex) RC circuits
- To find “Elmore time constant”:
 - For each capacitor, draw path of current from cap to input
 - Multiply C by sum of R 's on current path that are common with path from V_{in} to V_{out}
 - Add up RC products from all capacitors

Simplified Model: Elmore Delay

 

$$\tau_{Elmore} = R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3$$


Elmore Delay - Extended

 

$$R_{ik} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow i) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$$

Another Elmore Delay Example

 

$$\tau_{Elmore} =$$

Wire Model

Model the wire with N equal-length segments:

$$\tau_{DN} = \left(\frac{L}{N}\right)^2 (rc + 2rc + \dots + Nrc) = (rcL^2) \frac{N(N+1)}{2N^2} = RC \frac{N+1}{2N}$$


For large values of N:

$$\tau_{DN} = \frac{RC}{2} = \frac{rcL^2}{2}$$


RC-Models

Voltage Range	Lumped RC-network	Distributed RC-network
0→50% (t_p)	0.69 RC	0.38 RC
0→63% (τ)	RC	0.5 RC
10%→90% (t_r)	2.2 RC	0.9 RC

 Step Response of Lumped and Distributed RC Networks:
Points of Interest.



Driving an RC-line

 

$$\tau_D = R_s C_w + \frac{R_w C_w}{2} = R_s C_w + 0.5 r_w c_w L^2$$

$$t_p = 0.69 R_s C_w + 0.35 R_w C_w$$

The Global Wire Problem

$$T_d = 0.35 R_w C_w + 0.693(R_d C_{out} + R_d C_w + R_w C_{out})$$


Challenges

- No further improvements to be expected after the introduction of Copper (superconducting, optical?)
- Design solutions
 - Use of fat wires
 - Efficient chip floorplanning
 - Insert repeaters

Interconnect: # of Wiring Layers


of metal layers is steadily increasing due to:

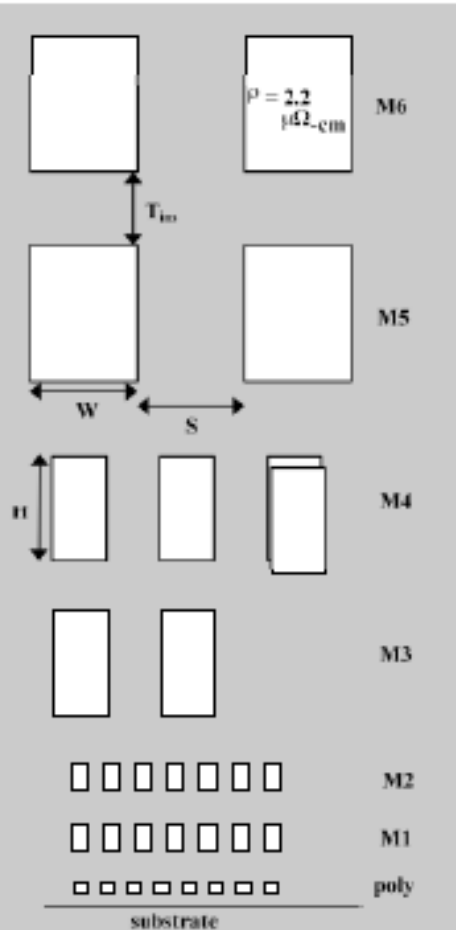- Increasing die size and device count: we need more wires and longer wires to connect everything
- Rising need for a hierarchical wiring network; local wires with high density and global wires with low RC




0.25 μm wiring stack


Minimum Widths (Relative)

 


Minimum Spacing (Relative)

 

Using Bypasses


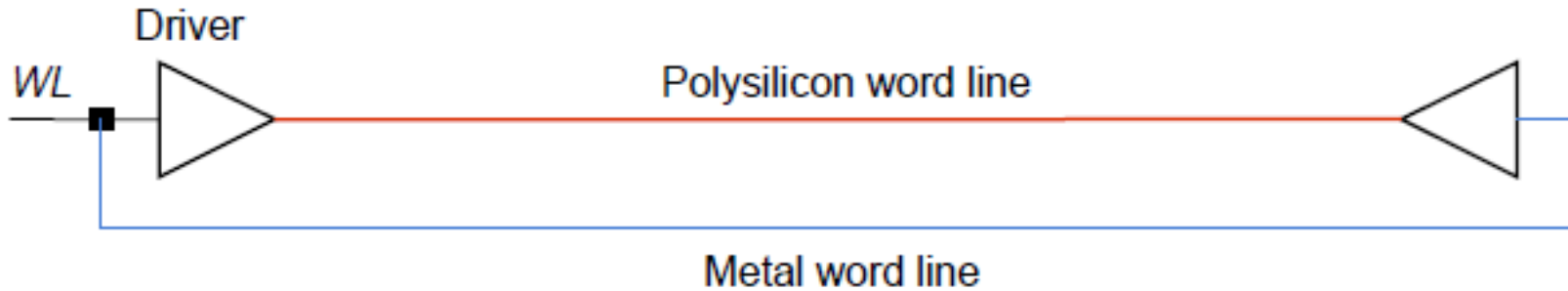


Driving a word line from both sides

 


Using a metal bypass

Diagonal Wiring

  


- 20+% Interconnect length reduction
- Clock speed
- Signal integrity
- Power integrity
- 15+% Smaller chips
plus 30+% via reduction

Reducing RC-delay Using Repeaters

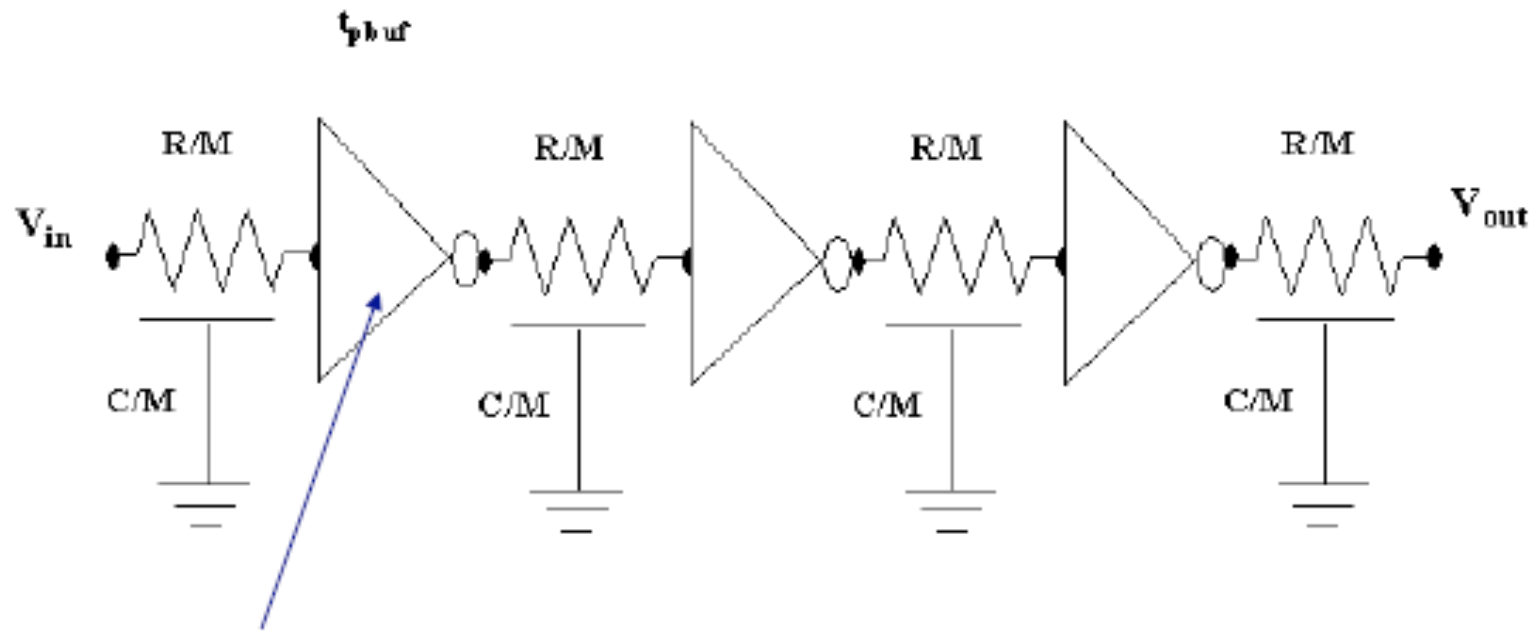

Repeater

Repeaters

 

$$t_p = m \left(0.69 \frac{R_d}{s} \left(s\gamma C_d + \frac{cL}{m} + sC_d \right) + 0.69 \left(\frac{rL}{m} \right) (sC_d) + 0.38rc \left(\frac{L}{m} \right)^2 \right)$$

$$m_{opt} = L \sqrt{\frac{0.38rc}{0.69R_d C_d (\gamma + 1)}} = \sqrt{\frac{t_{pwire(unbuffered)}}{t_{p1}}}$$
$$s_{opt} = \sqrt{\frac{R_d c}{r C_d}}$$

Repeater Insertion (Revisited)

Taking the repeater loading into account

$$m_{opt} = L \sqrt{\frac{0.38rc}{0.69R_dC_d(\gamma + 1)}} = \sqrt{\frac{t_{pwire(unbuffered)}}{t_{p1}}}$$


$$s_{opt} = \sqrt{\frac{R_dc}{rC_d}}$$

For a given technology and a given interconnect layer, there exists an optimal length of the wire segments between repeaters. The delay of these wire segments is **independent of the routing layer!**

$$L_{crit} = \frac{L}{m_{opt}} = \sqrt{\frac{t_{p1}}{0.38rc}} \quad t_{p,crit} = \frac{t_{p,min}}{m_{opt}} = 2 \left(1 + \sqrt{\frac{0.69}{0.38(1 + \gamma)}} \right) t_{p1}$$



Complex Gate Delay

- Use RC model to estimate delay:

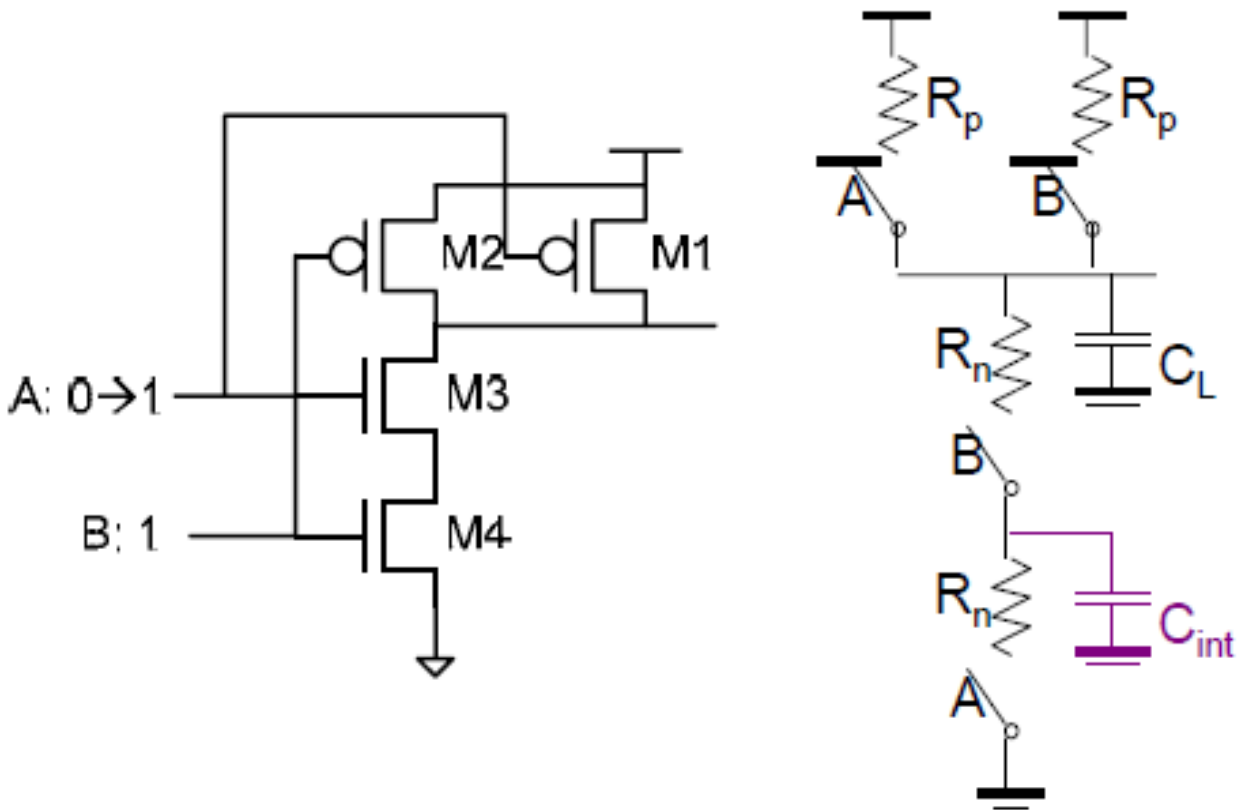

Complex Gate Delay (2)

□ What is the delay in this case?

  

PROBLEM.....

PROBLEM 2: Complex Gate Delay


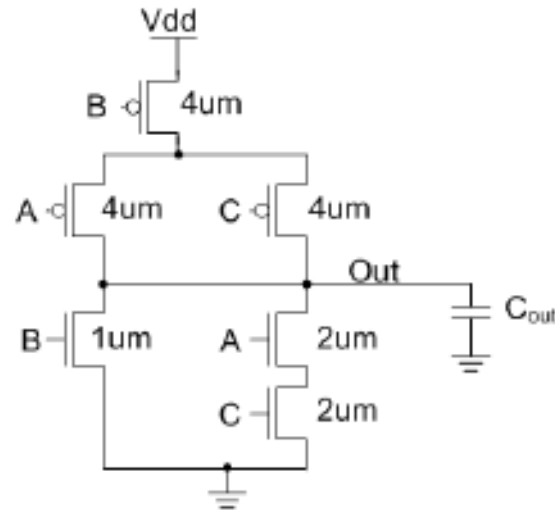


Figure 3.

For this problem you should assume that $L_{\text{min}} = 100\text{nm}$, $C_g = 2\text{ fF}/\mu\text{m}$, $C_d = 1.6\text{ fF}/\mu\text{m}$, $R_p = 20\text{ k}\Omega/\square$, and $R_n = 10\text{ k}\Omega/\square$, $C_{\text{out}} = 12\text{ fF}$.

- If $A = 1$ and $B = 0$, draw the switch model you would use to calculate the delay of the gate when C transitions from 1 to zero (i.e., the output going high).

 Using the switch model, the equivalent RC circuit we would use to calculate the delay when $A = 1$, $B = 0$, and C transitions from 1 to zero is shown below.



b) What is the delay of the gate in this case?

Solution:

Using Elmore delay, the time constant for this circuit is:

$$\tau_{LH} = 2R_P(5C_d + 6C_d + 2C_g + 4C_d + C_{out})$$


Where the resistance of each PMOS transistor is:

$$R_P = R_p \frac{L}{W} = 20k\Omega \frac{0.1\mu m}{4\mu m} = 500\Omega$$

Therefore, t_{pLH} for the gate will be:

$$t_{pLH} = \ln 2 \times \tau_{LH} = \ln 2 \times 2 \times 500\Omega \times (5 \times 1.6fF + 6 \times 1.6fF + 2 \times 2fF + 4 \times 1.6fF + 12fF) \approx 27.73ps$$

 Calculate Elmore delay from In to out1 and from In to out2?



Solution:

Elmore to out1 is $15RC$

Elmore to out2 is $16RC$