

Layout Rules


Design Rules

- ▶ Interface between the circuit designer and process engineer
- ▶ Guidelines for constructing process masks
- ▶ Unit dimension: minimum line width
 - scalable design rules: lambda parameter
 - absolute dimensions: **micron rules**
- ▶ Rules constructed to ensure that design works even when small fab errors (within some tolerance) occur
- ▶ A complete set includes
 - set of layers
 - intra-layer: relations between objects in the same layer
 - inter-layer: relations between objects on different layers

Why Have Design Rules?


- ▶ To be able to tolerate some level of fabrication errors such as

1. Mask misalignment

 

2. Dust

 3. Process parameters (e.g., lateral diffusion)




4. Rough surfaces

Design Rules

- Intra-layer
 - Widths, spacing, area
- Inter-layer
 - Enclosures, distances, extensions, overlaps
- Special rules (sub-0.25 μm)
 - Antenna rules, density rules, (area)


A Modern CMOS Process

 


Dual-Well Shallow-Trench-Isolated CMOS Process

Transistor Layout



 



 











Cross-Sectional View




Layout View




Layers in 0.25 μm CMOS process

Layer Description	Representation				
metal	 m1	 m2	 m3	 m4	 m5
well	 nw				
polysilicon	 poly				
contacts & vias	 ct	 v12, v23, v34, v45	 nwc	 pwc	
active area and FETs	 ndif	 pdif	 nfet	 pfet	
select (well contacts)	 nplus	 pplus	 prb		


Intra-Layer Design Rules

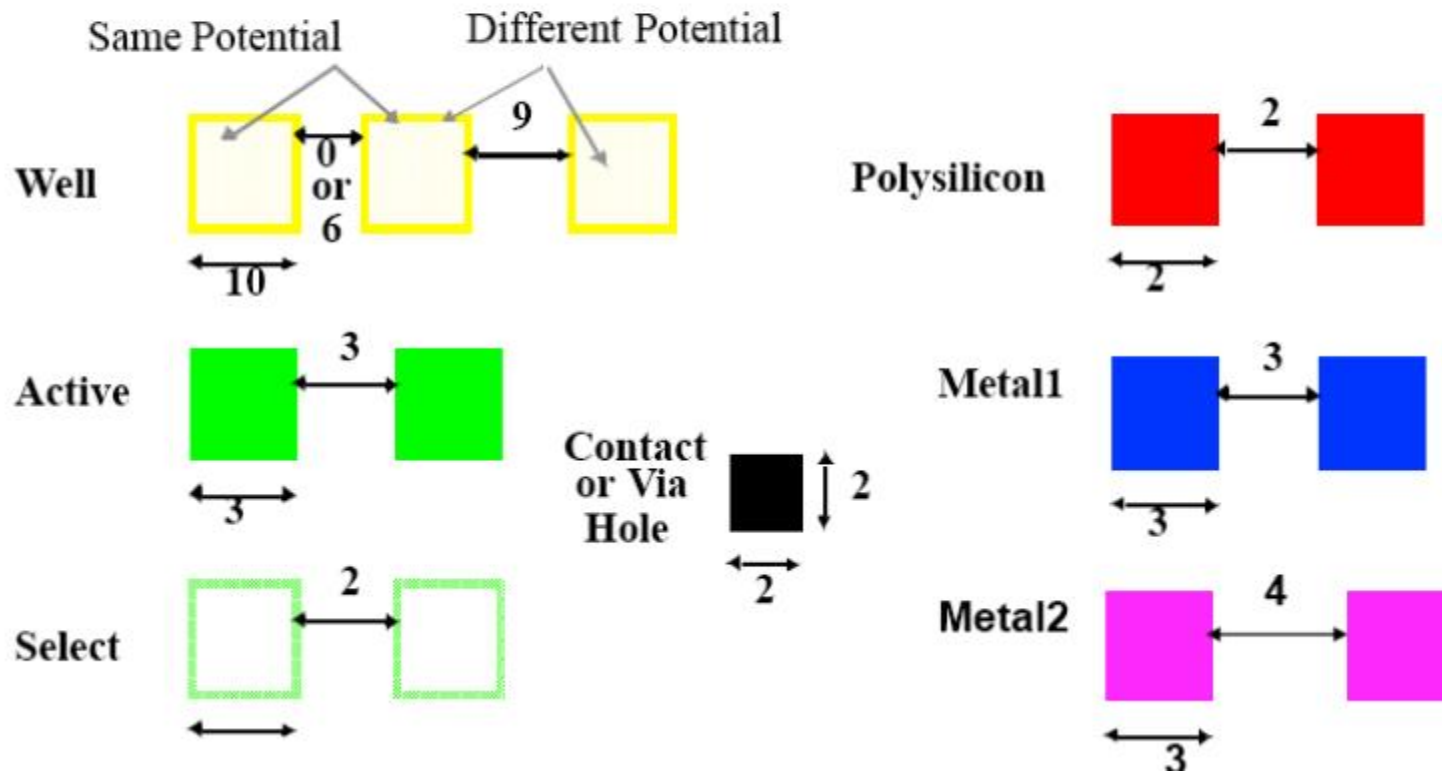

Layout Editor: *max* Design Frame

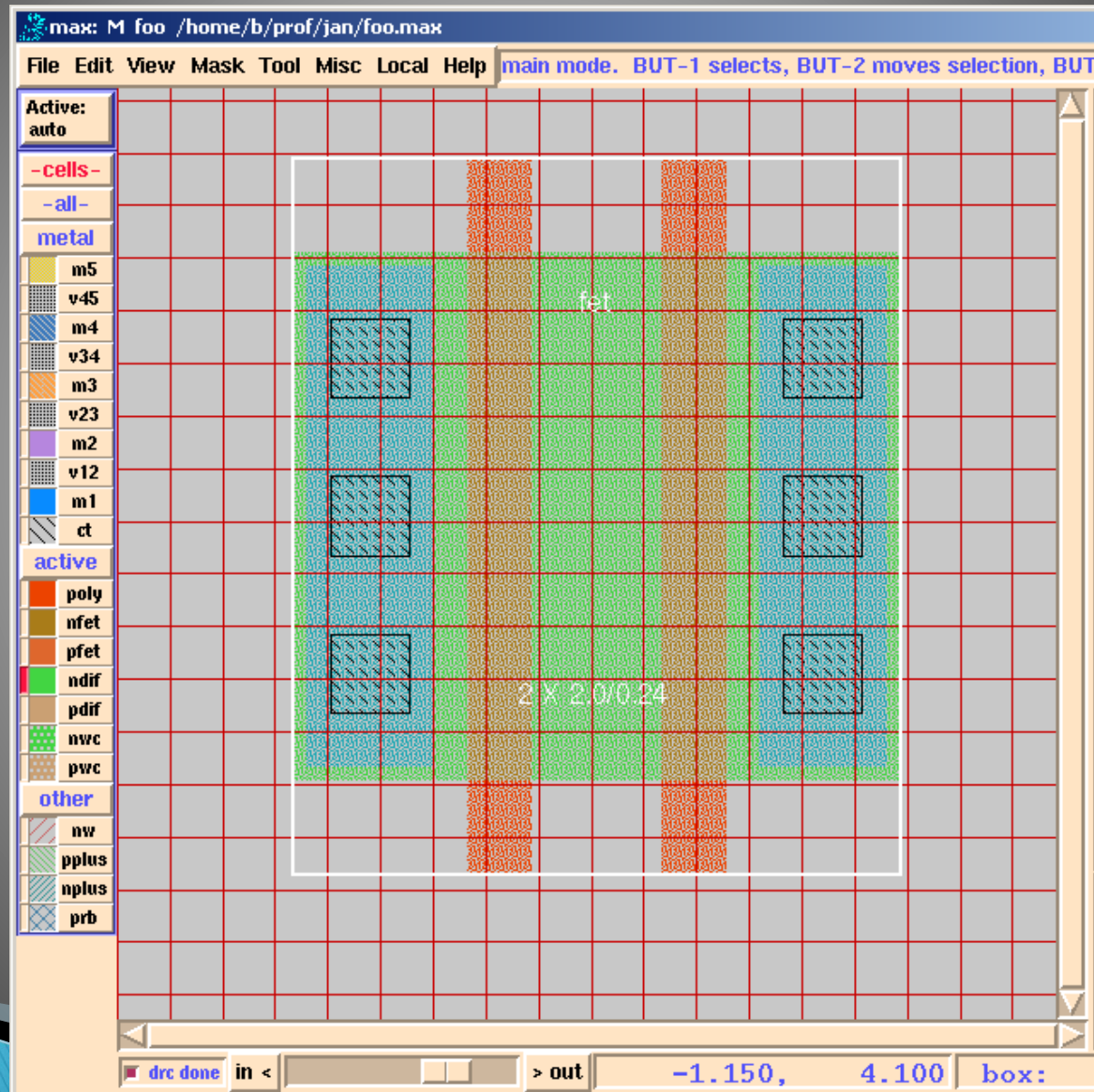


max Layer Representation

 


- ▶ Metals (five) and vias/contacts between the interconnect levels
 - Note that **m5** connects only to **m4**, **m4** only to **m3**, etc., and **m1** only to poly, ndif, and pdif
 - Some technologies support “stacked vias”
- Active – active areas on/in substrate (poly gates, transistor channels (**nfet**, **pfet**), source and drain diffusions (**ndif**, **pdif**), and well contacts (nwc, pwc))
- Wells (nw) and other select areas (pplus, nplus, prb)

CMOS Inverter *max* Layout

 

Intra-Layer Design Rule Origins

 
- ▶ Minimum dimensions (e.g., widths) of objects on each layer to maintain that object after fab
 - minimum line width is set by the resolution of the patterning process (photolithography)
- ▶ Minimum spaces between objects (that are *not* related) on the same layer to ensure they will not short after fab




Inter-Layer Design Rule Origins


1. Transistor rules – transistor formed by overlap of active and poly layers

Transistors

 


Unrelated Poly & Diffusion

 


 



Inter-Layer: Well and Substrate

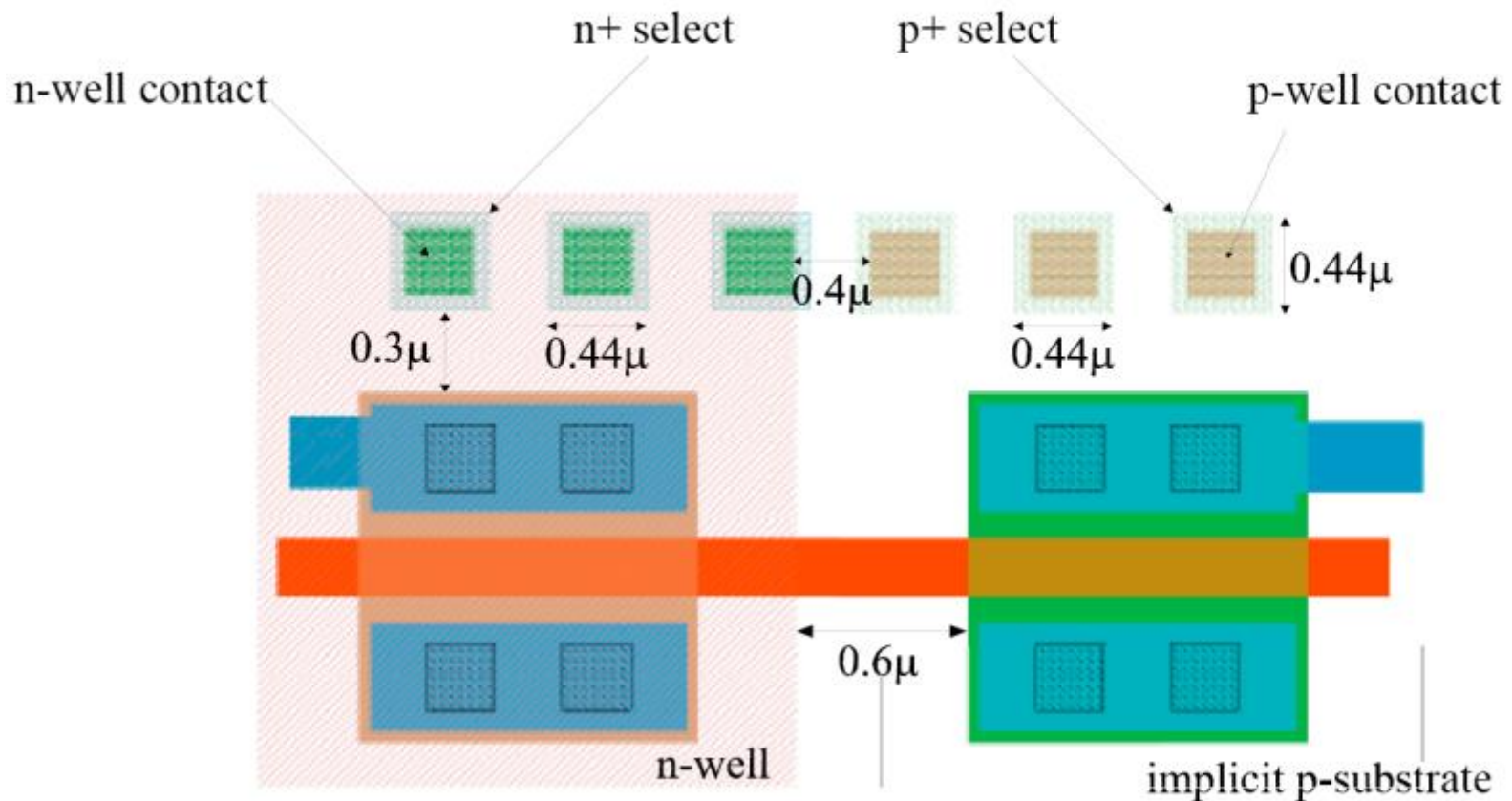

Circuit Under Design

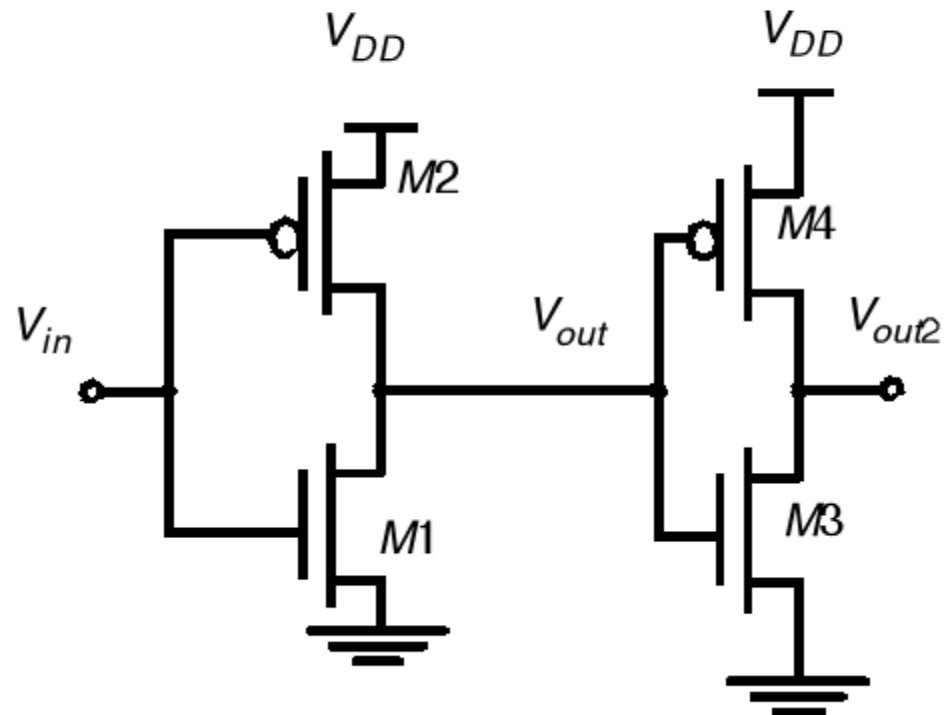



CMOS Inverter

  


Two Inverters

Share power and ground

Abut cells

  


CMOS Inverter Layout

 


Gate Layout

- Layout can be very time consuming
 - Design gates to fit together nicely
 - Build a library of standard cells
- Standard cell design methodology
 - V_{DD} and GND should abut (standard height)
 - Adjacent gates should satisfy design rules
 - nMOS at bottom and pMOS at top
 - All gates include well and substrate contacts

Example: Inverter

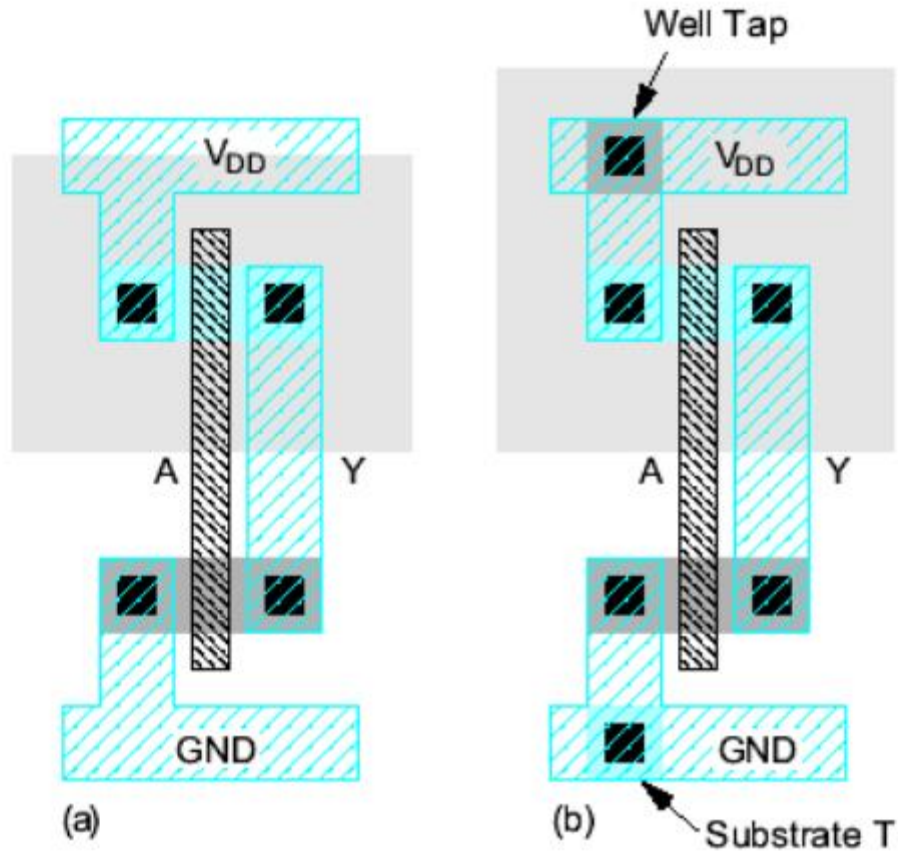

 Layout Design Rules *Conservative rules to get started!*



Design Rules Summary

- Metal and diffusion have minimum width and spacing of 4λ
- Contacts are $2\lambda \times 2\lambda$ and must be surrounded by 1λ on the layers above and below
- Polysilicon uses a width of 2λ
- Polysilicon overlaps diffusions by 2λ where a transistor is desired and has spacing of 1λ away where no transistor is desired
- Polysilicon and contacts have a spacing of 3λ from other polysilicon or contacts
- N-well surrounds pMOS transistors by 6λ and avoid nMOS transistors by 6λ

The power and ground lines are called supply rails

Inverter Layout

- Transistor dimensions specified as W / L ratio
- Minimum size is $4\lambda / 2\lambda$, sometimes called 1 unit



 
 
 
 


FIG 1.40 Inverter with dimensions labeled

Inverter Standard Cell Area (1/2)

 


3-input Standard Cell NAND

 


Wiring Tracks

 - A **wiring track** is the space required for a wire
 - 4λ width, 4λ spacing from neighbor = 8λ pitch
 - Transistors also consume one wiring track



Well Spacing

 - Wells must surround transistors by 6λ
 - Implies 12λ between opposite transistor flavors
 - Leaves room for one wire track




Area Estimation

Horizontal
 $4 \times 8 = 32$


Vertical
 $5 \times 8 = 40$

 - Estimate area by counting wiring tracks
 - Multiply by 8 to express in λ






Stick Diagrams

 - **Stick diagrams** help plan layout quickly
 - Need not be to scale
 - Draw with color pencils or dry-erase markers




CMOS Inverter Stick Diagrams

   - ▶ CMOS inverter described in other way.



Stick Diagram


$$F = (AB) + E + (CD)$$

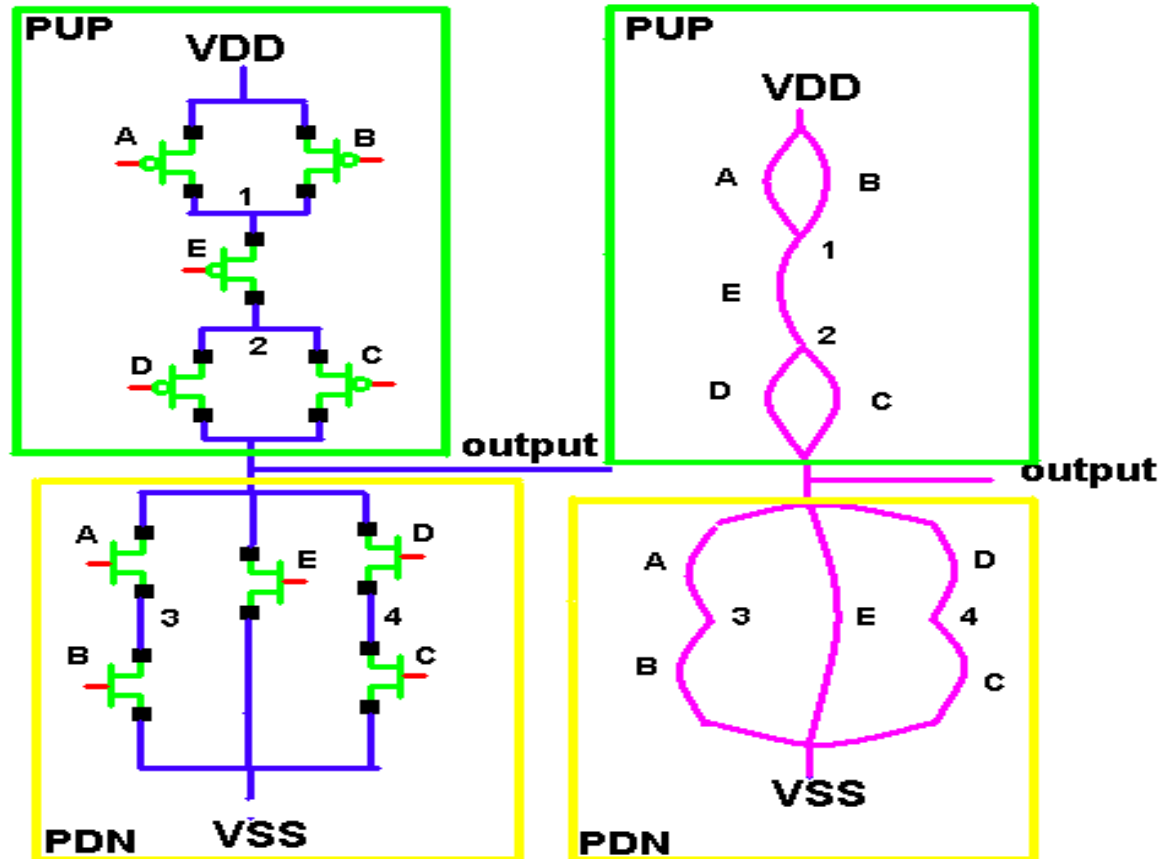

Identify each transistor and construct a logic graph
 connection to the transistor
 by a unique name

$$F = (AB)+E+(CD)$$

See the tutorial for further details.

 


EULER PATH = {A,B,E,D,C}

– construct one Euler path for both the Pull up and Pull down network

EULER PATH = {A,B,E,D,C}

— METAL 1
— POLY
— ACTIVE

 


- Trace two green lines horizontally to represent the NMOS and PMOS devices and surround them by n and p-wells
- Trace the number of inputs (5 in this example) vertically across each green strip and label them in order.
- Trace blue lines to represent VDD and VSS
- Place the connection labels upon the NMOS and PMOS devices

Layout

EULER PATH = {A,B,E,D,C}

METAL 1
POLY
ACTIVE

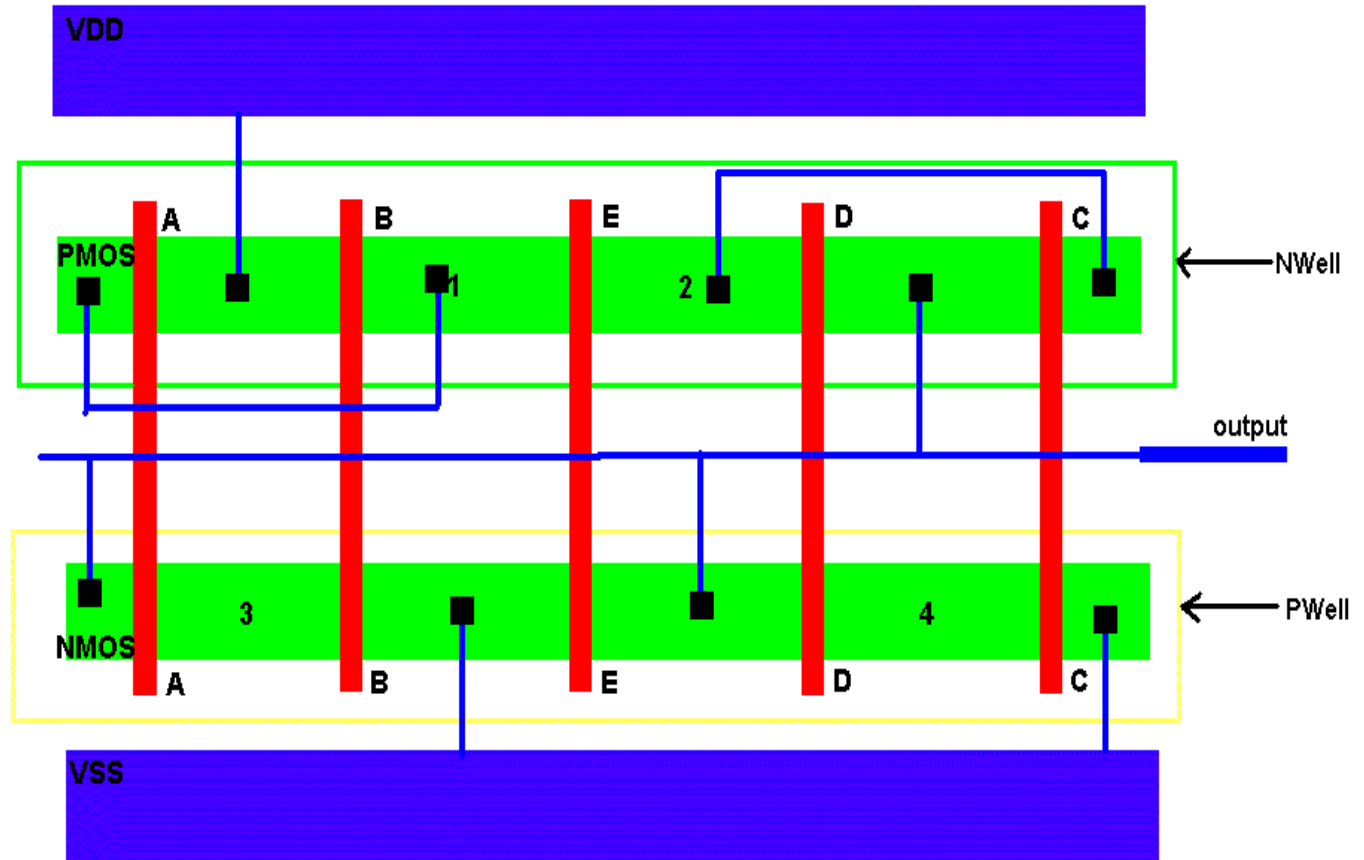

- Place the VDD, VSS and all output names upon the NMOS and PMOS devices
- interconnect the devices based on Euler path.