
 


Design Metrics


Textbook:

What is a Transistor?

 An MOS Transistor \leftrightarrow A Switch!



Switch Model of MOS Transistor

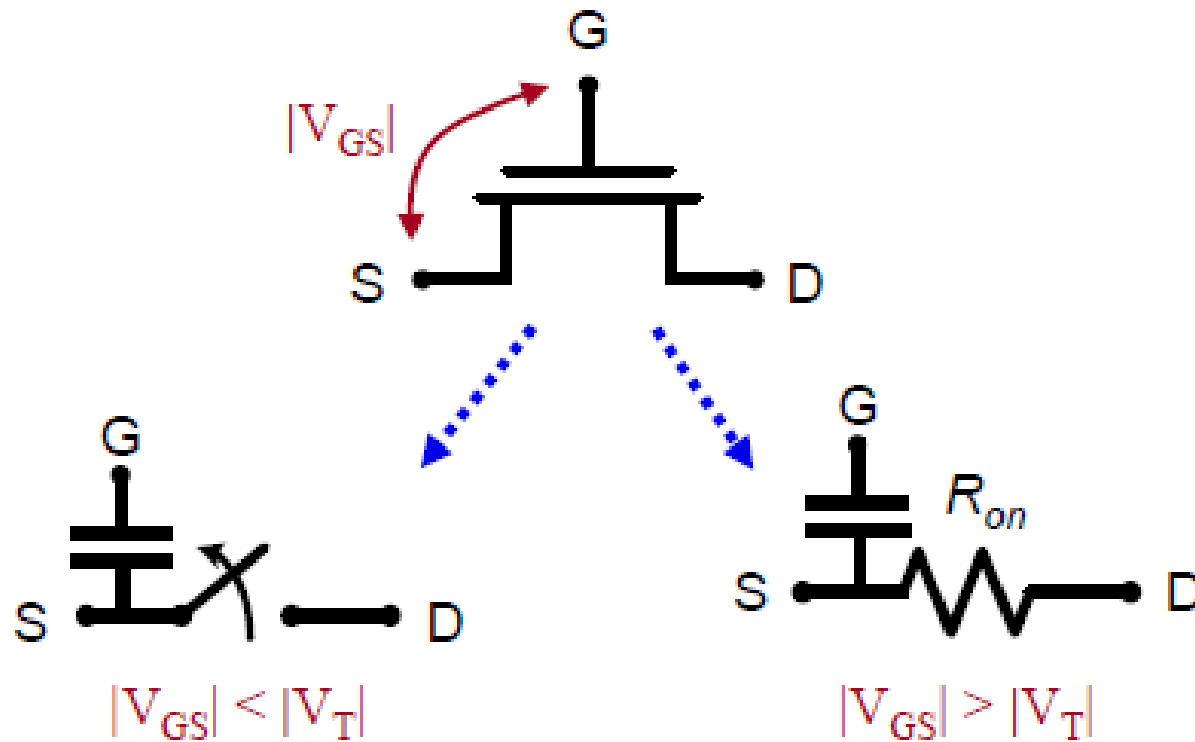


Design Metrics

- How to evaluate performance of a digital circuit (gate, block, ...)?
 - Cost
 - Reliability
 - Speed/Performance (delay, frequency)
 - Power


Introduction to IC CMOS Manufacturing

The MOS Transistor

 


Reliability

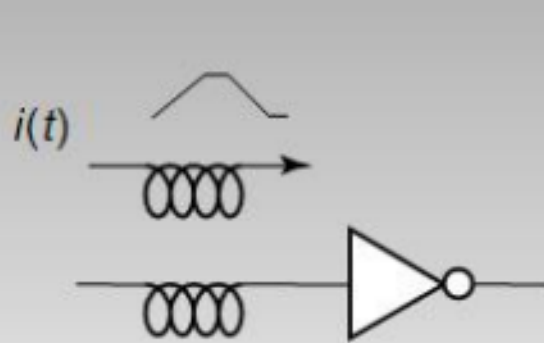
- The real world is analog
 - All physical quantities you deal with as a circuit designer are actually continuous
 - Thus, even a “digital” signal can be noisy:



Inductive coupling

 

Capacitive coupling

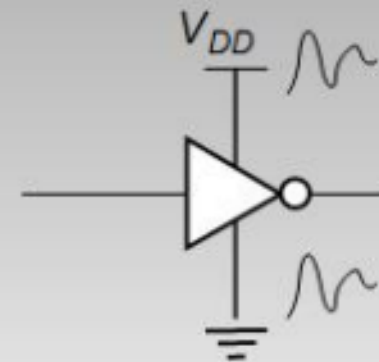

Power and ground noise


Noise and Digital Systems

- ❑ Circuit needs to work despite “analog” noise
 - Digital gates can reject noise
 - This is actually how digital systems are defined
- ❑ Digital system is one where:
 - Discrete values mapped to analog levels and back
 - All the elements (gates) can reject noise
 - For “small” amounts of noise, output noise is less than input noise
 - Thus, for sufficiently “small” noise, the system acts as if it was **noiseless**


Noise Rejection

- To see if a gate rejects noise
 - Look at its DC voltage transfer characteristic (VTC)
 - See what happens when input is not exactly 1 or 0

 - Ideal digital gate:
 - Noise needs to be larger than $V_{DD}/2$ to have any effect on gate output




More Realistic VTC

 


$$\begin{aligned}V_{OH} &= f(V_{OL}) \\V_{OL} &= f(V_{OH}) \\V_M &= f(V_M)\end{aligned}$$

Nominal Voltage Levels


Voltage Mapping

 


Definitions of Noise Margins

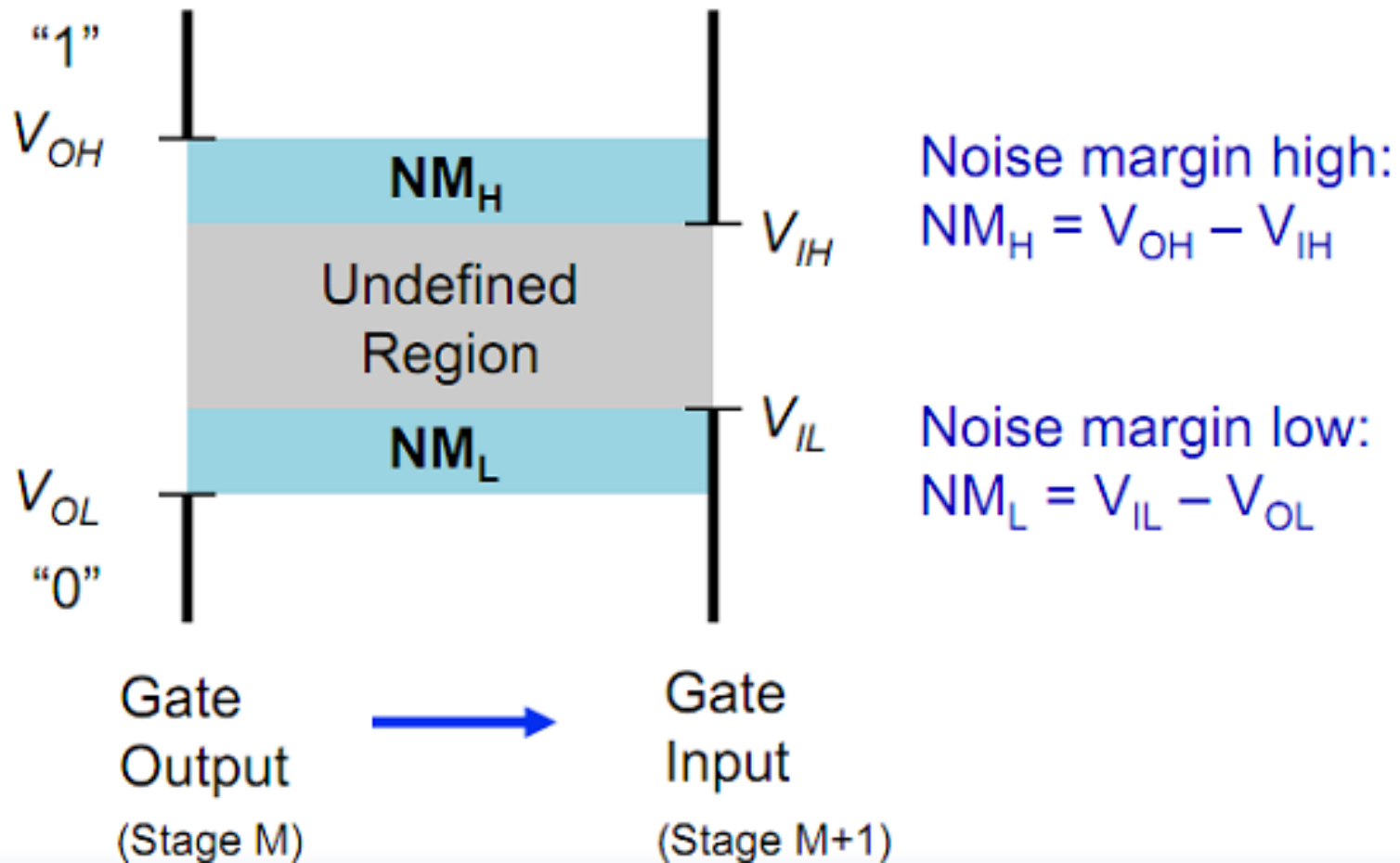

 Digital Noise Reduction: Regenerative Property




A chain of inverters

 


Simulated response


Regenerative Property

 


Regenerative

 

Non-Regenerative

 


Example NMOS Inverter of 1970

 

Example

- $V_{OH} = 3.6V$
- $V_{OL} = 0.4V$
- $V_{IL} = 0.6V$
- $V_{IH} = 2.3V$
- $NM_H = V_{OH} - V_{IH} = 1.3V$
- $NM_L = V_{IL} - V_{OL} = 0.2V$

CMOS Inverter VTC

 

Summary

- Understanding the design metrics that govern digital design is crucial
 - We discussed cost and reliability so far
- Key design messages so far:
 - Keep chip area as small as possible
 - Pick design styles and parameters so that noise margins are reasonable
- Summary of some key reliability metrics:
 - Noise transfer functions & margin (ideal: gain = ∞ , margin = $V_{dd}/2$)
 - Output impedance (ideal: $R_o = 0$)
 - Input impedance (ideal: $R_i = \infty$)


Static Logic Gates

At every point in time (except during the switching transients) each **gate output is connected to either V_{DD} or V_{SS}** via a low resistive path.

The outputs of the gates **assume at all times the value of the Boolean function** implemented by the circuit (ignoring, once again, the transient effects during switching periods).

(Will contrast this later to **dynamic circuit style**.)



Static Complementary CMOS

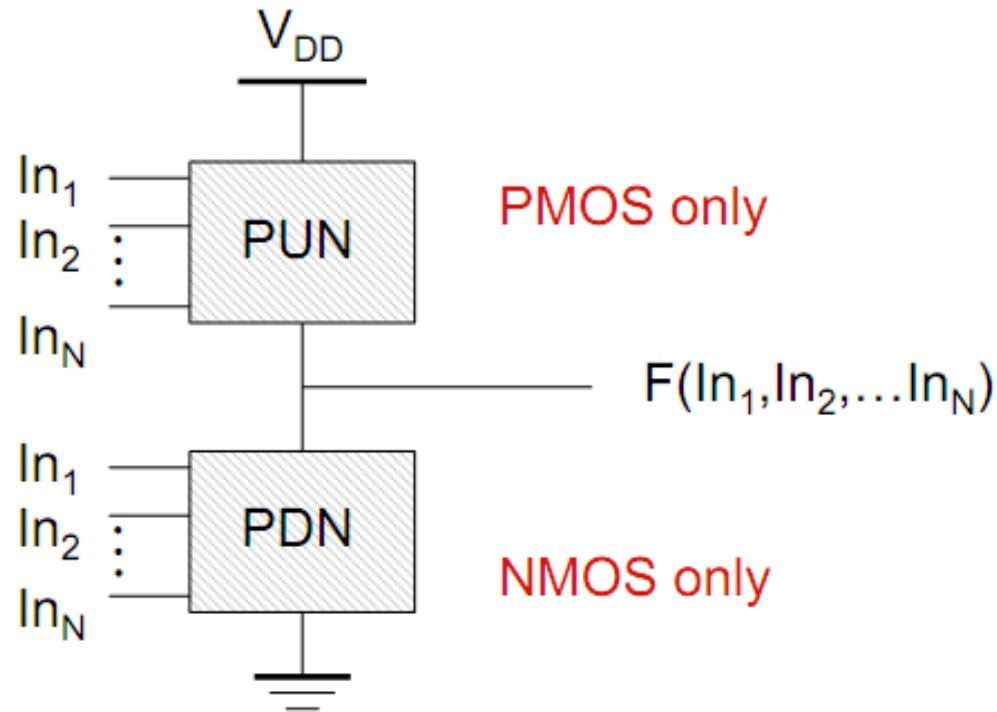



PUN and PDN are **dual** logic networks
PUN and PDN functions are **complementary**

REMEMBER

PUN

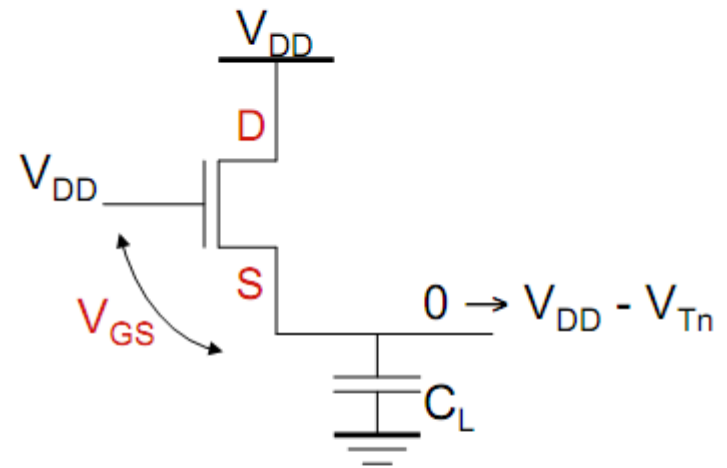
 


PDN

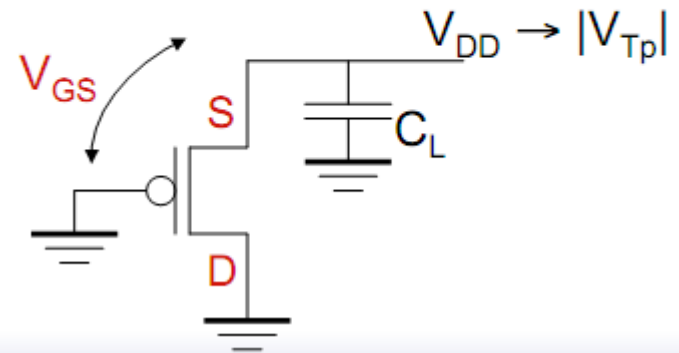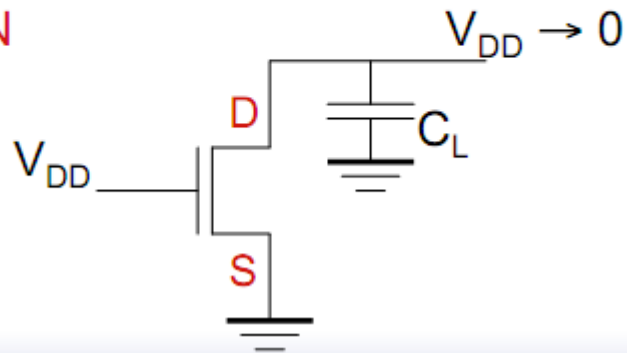

NMOS Transistors in Series/Parallel Connection

 
 
- Transistor \leftrightarrow switch controlled by its gate signal
 - NMOS switch closes when switch control input is high



- NMOS transistors pass a “strong” 0 but a “weak” 1

PMOS Transistors in Series/Parallel Connection

  - PMOS switch closes when switch control is low



- PMOS transistors pass a “strong” 1 but a “weak” 0


Complementary CMOS Logic Style

- PUP is the **dual** to PDN
(can be shown using DeMorgan's Theorems)

$$\overline{\overline{A + B}} = \overline{\overline{A} \overline{B}}$$

$$\overline{\overline{A} \overline{B}} = \overline{\overline{A}} + \overline{\overline{B}}$$

- Static CMOS gates are always inverting

 


AND = NAND + INV

Example Gate: NAND

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 


- PDN: $G = \underline{AB} \Rightarrow$ Conduction to GND
- PUN: $F = \overline{A} + \overline{B} = \overline{AB} \Rightarrow$ Conduction to V_{DD}
- $\overline{G(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)} \equiv F(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)$


Example Gate: NOR

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


Truth Table of a 2 input NOR gate

 


Complex CMOS Gate

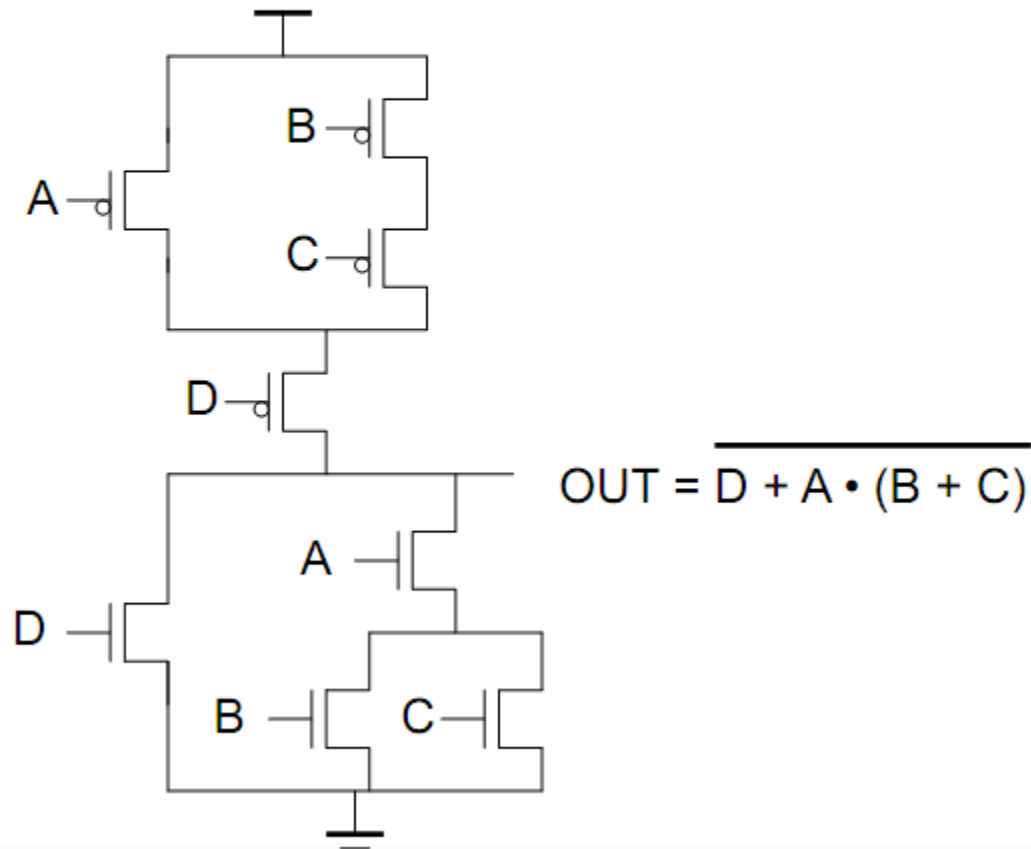

CMOS Properties

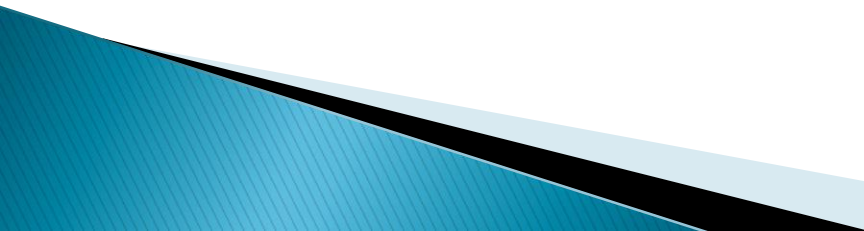
- ❑ Full rail-to-rail swing
 - ❑ Symmetrical VTC
 - ❑ Propagation delay function of load capacitance and resistance of transistors
 - ❑ No static power dissipation
 - ❑ Direct path current during switching
- 

Primary Performance Metric: Delay

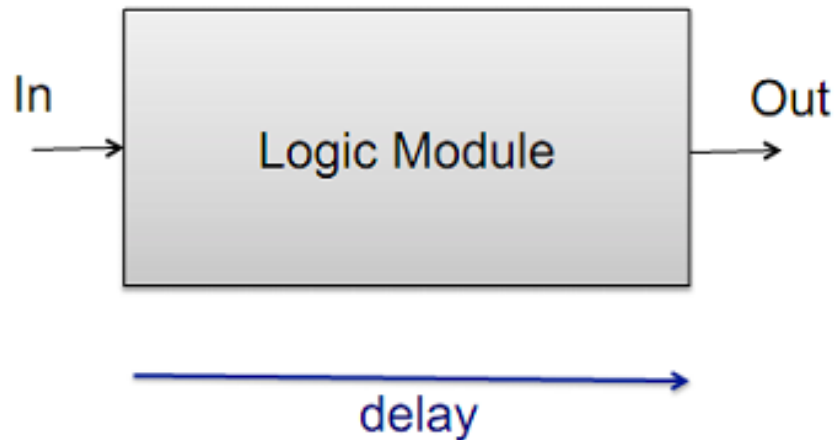


How to define delay in a universal way?

Delay Definitions

 

A First-Order RC Network

 

$$v_{out}(t) = (1 - e^{-t/\tau}) V$$



$$t_p = \ln(2) \tau = 0.69 RC$$

Important model – matches delay of an inverter

Power Dissipation

Instantaneous power:

$$p(t) = v(t)i(t) = V_{supply}i(t)$$

Peak power:

$$P_{peak} = V_{supply}i_{peak}$$

Average power:

$$P_{ave} = \frac{1}{T} \int_t^{t+T} p(t) dt = \frac{V_{supply}}{T} \int_t^{t+T} i_{supply}(t) dt$$


“Power-Delay” and Energy-Delay

- Want low power and low delay, so how about optimizing the product of the two?
 - So-called “Power-Delay Product”

- Power·Delay is by definition Energy
 - Optimizing this pushes you to go as slow as possible


- Alternative gate metric: Energy-Delay Product
 - $EDP = (P_{av} \cdot t_p) \cdot t_p = E \cdot t_p$

Energy in CMOS

 

- The voltage on C_L eventually settles to V_{DD}
- Thus, charge stored on the capacitor is $C_L V_{DD}$
 - This charge has to flow out of the power supply
- So, energy is just $Q \cdot V_{DD} = (C_L V_{DD}) \cdot V_{DD}$

Energy

 

$$E_{0 \rightarrow 1} = \int_0^T P_{DD}(t) dt = V_{DD} \int_0^T i_{DD}(t) dt = V_{DD} \int_0^{V_{DD}} C_L dv_{out} = C_L V_{DD}^2$$


$$E_C = \int_0^T P_C(t) dt = \int_0^T v_{out} i_L(t) dt = \int_0^{V_{DD}} C_L v_{out} dv_{out} = \frac{1}{2} C_L V_{DD}^2$$

Energy Thought Experiment (1)

- Why doesn't R matter?

Energy Thought Experiment (2)

- Where did the energy go?

 

$$E_{V_{in}} = C_L V_{in}^2$$

$$E_{C_L} = (1/2)C_L V_{in}^2$$